

PN-junction diode

Electrical resistivity ρ

Conductors $\rho \approx 10^{-8} \Omega\text{m}$

Semi-conductors $\rho \approx 1 \Omega\text{m}$

Non-conductors $\rho \approx 10^9 \Omega\text{m}$

Semiconductors e.g. silicon (Si)

n-type doping

P in Si

Donor Host
5 electrons 4 electrons

\Rightarrow 1 donor atom \Rightarrow 1 free electron

\Rightarrow n-type \Rightarrow negative sign

\Rightarrow electron

p-type doping

B in Si


3 electrons 4 electrons
Acceptor Host

\Rightarrow 1 acceptor atom \Rightarrow 1 free hole

\Rightarrow p-type \Rightarrow positive type


\Rightarrow hole (electron deficiency)

pn junction $V = 0$

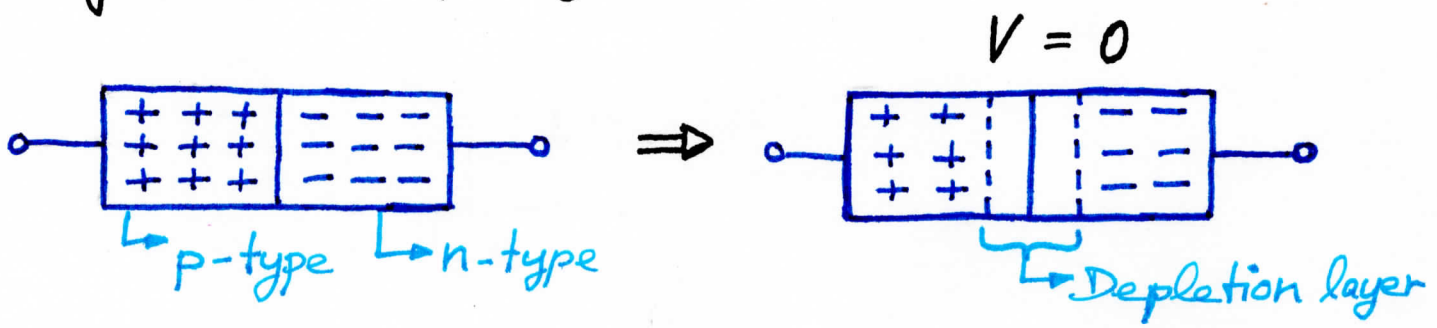


\Rightarrow Depletion layer \Rightarrow Diode is resistive at zero bias

Forward bias $V > 0$

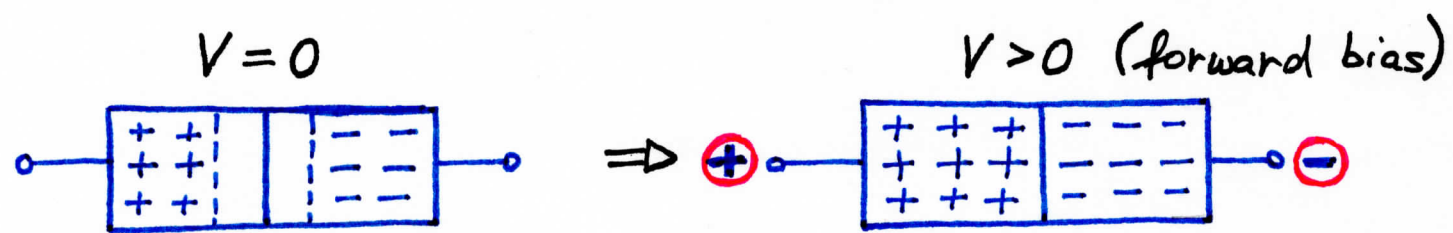

\Rightarrow Diode voltage $> 0 \Rightarrow$ Diode conducts
 \Rightarrow Threshold voltage required $\Rightarrow V_{th}$


Reverse bias $V < 0$

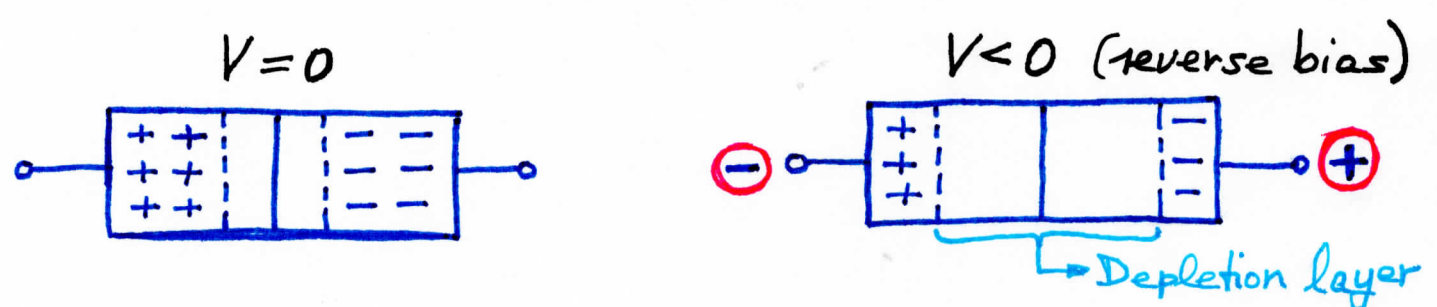



\Rightarrow Diode voltage $< 0 \Rightarrow$ Diode insulates

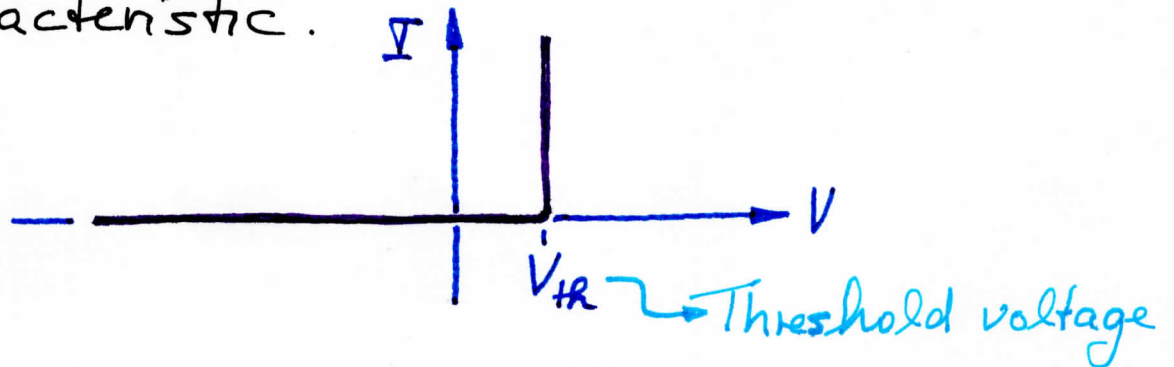(3)

Based on the qualitative understanding developed above, we construct the diode's I V characteristic.



Circuit symbol

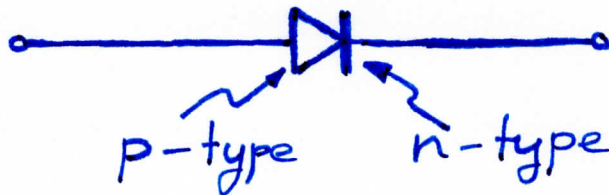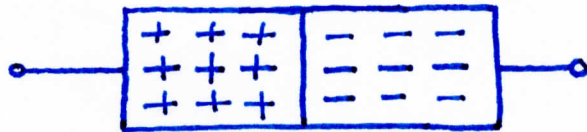

Theoretical IV characteristic

④

$$I = I_0 (e^{V/V_t} - 1)$$

V_t = Thermal voltage = $\frac{kT}{e} = 26 \text{ mV}$

k = Boltzmann constant = $1.38 \times 10^{-23} \text{ J/K}$

e = elementary charge = $1.602 \times 10^{-19} \text{ C}$

T = temperature = 300 K


I_0 = Reverse saturation current e.g. 10^{-10} A

Questions:

$$V=0 \Rightarrow I = ?$$

$$V=-10\text{V} \Rightarrow I = ?$$

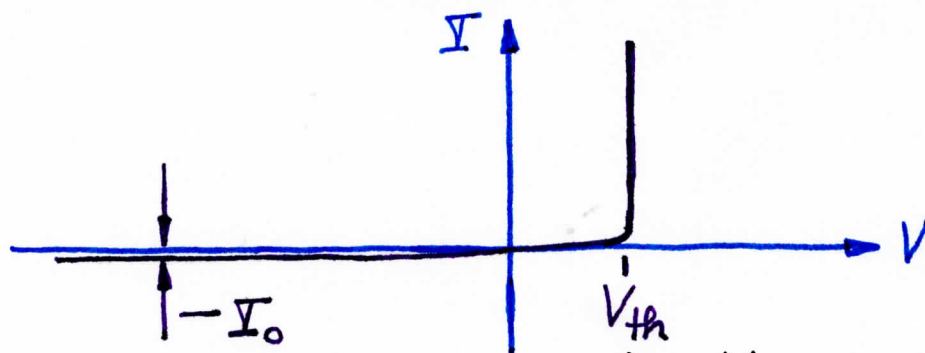$V > 0 \Rightarrow I$ grows exponentially



$\hookrightarrow V_{th} \approx 0.7 \text{ V}$ for Si

If we could freely choose parameters, what value would you choose for I_0 ? V_{th} ?

Approximate IV characteristic for forward bias

Recall: $I = I_0 (e^{V/V_t} - 1)$

For $V \gg V_t \Rightarrow V \gg 26 \text{ mV}$
 \Rightarrow e.g. $V = 200 \text{ mV}$

we realize $e^{V/V_t} \gg 1$

Therefore $I \approx I_0 e^{V/V_t}$

\hookrightarrow valid for $V \gg V_t$
 \hookrightarrow thermal voltage

(6)

Diode differential resistance

Recall: $I = I_0 e^{V/V_t}$ (forward voltage regime)

Diode differential resistance

$$\begin{aligned} r_{\text{Diode}} &= \frac{dV}{dI} = \left(\frac{dI}{dV} \right)^{-1} = \left(\frac{d}{dV} I_0 e^{V/V_t} \right)^{-1} \\ &= \left(\underbrace{I_0 e^{V/V_t}}_I \frac{1}{V_t} \right)^{-1} \\ &= \left(I \frac{1}{V_t} \right)^{-1} = \left(\frac{I}{V_t} \right)^{-1} = \frac{V_t}{I} \end{aligned}$$


$$\Rightarrow \boxed{r_{\text{Diode}} = V_t / I}$$

Example: $I = 1 \text{ A}$

$$\Rightarrow r_{\text{Diode}} = \frac{0.026 \text{ V}}{1 \text{ A}} = 0.026 \Omega$$

$\Rightarrow r_{\text{Diode}}$ is very small in the forward direction

Basic diode circuit

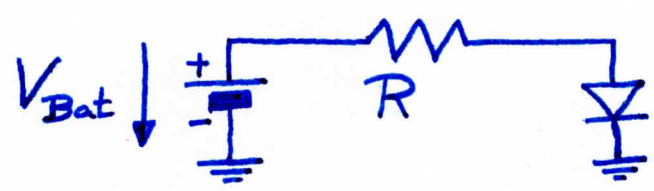

KVL $V_{Bat} = IR + V_{Diode}$

Recall: $I = I_{Diode} = I_0 e^{V/V_t}$

Insert in KVL: $V_{Bat} = \underbrace{I_0 e^{V_{Diode}/V_t}}_{I_R = I_{Diode}} R + V_{Diode}$


The equation has one unknown: V_{Diode} .

Solve for V_{Diode} ? Can eqn. be solved?

Mathematically, the eqn. has the following form

$A = e^x + x \Rightarrow \text{Cannot be solved.}$
 $\Rightarrow \text{Problem!}$

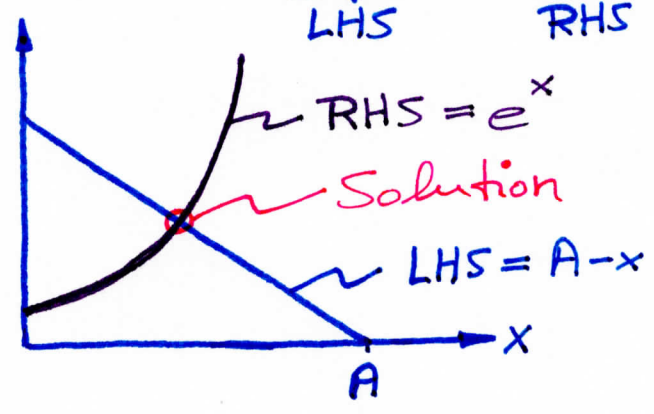
$\underbrace{A-x}_{LHS} = \underbrace{e^x}_{RHS}$



\Rightarrow Graphical solution is possible!

Graphical solution

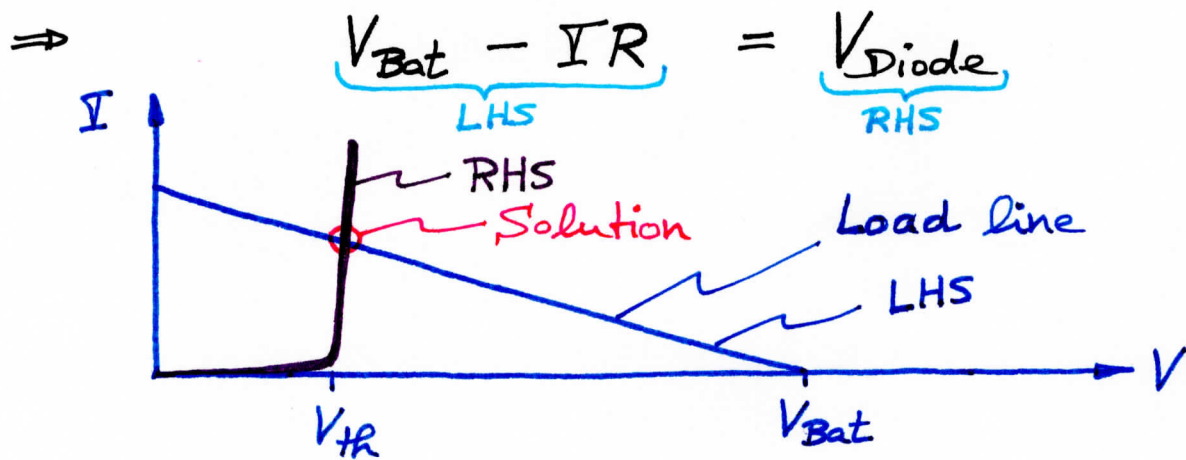We showed: $V_{\text{Bat}} = IR + V_{\text{Diode}}$



\Rightarrow Graphical solution is possible

Approximate analytic solution

Assume $V_{\text{Diode}} = V_{\text{th}} = 0.7\text{V}$ (forward direction)

$$\begin{aligned} \Rightarrow V_{\text{Bat}} &= IR + V_{\text{th}} \\ &= IR + 0.7\text{V} \end{aligned}$$

$$\Rightarrow I = (V_{\text{Bat}} - 0.7\text{V})/R$$

\Rightarrow Approximate analytic solution is possible!