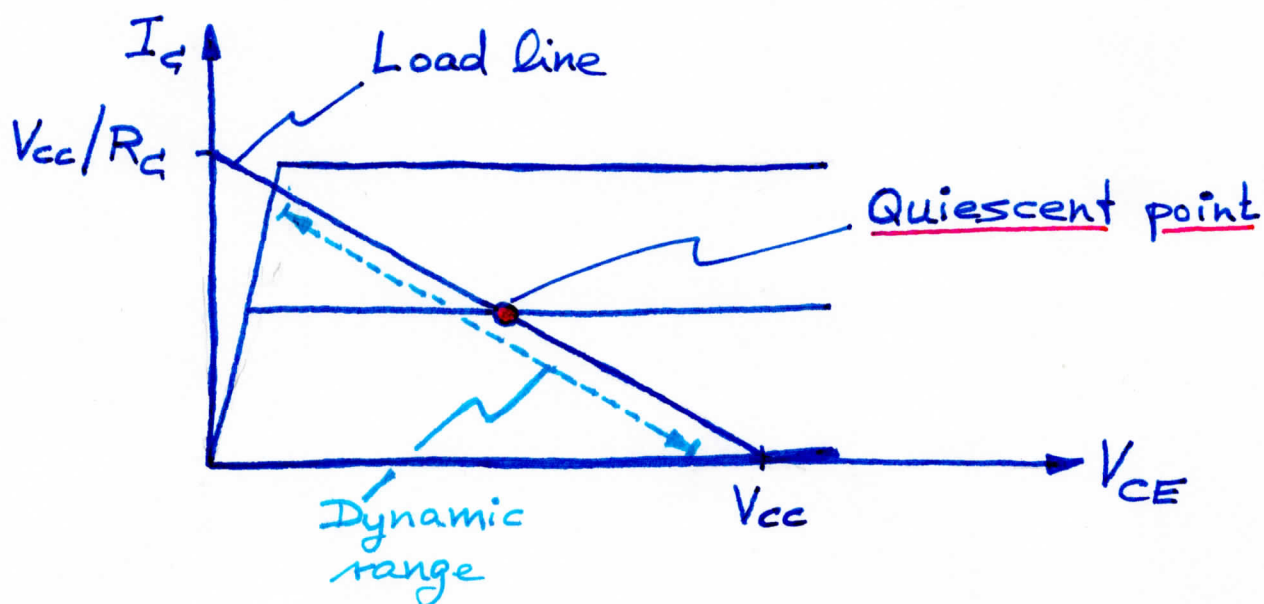


Quiescent point (Q-point)

Quiescent \Rightarrow Origin of word ? \Rightarrow Quiet \Rightarrow
static \Rightarrow no dynamic signal \Rightarrow DC

Quiescent point of BJT ? We choose the Q-point




Q: Where do we choose the Q-point to be located?

\Rightarrow Frequently in middle of load line.

\Rightarrow Bias network of transistor determines the quiescent point.

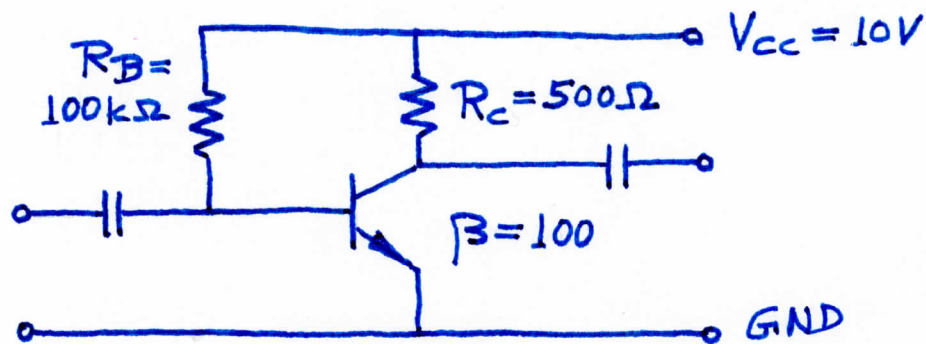1st exercise : Determine Q-point of the following circuit



Base current:
$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10V - 0.7V}{100k\Omega} = 93\mu A$$

$$\Rightarrow I_C = \beta I_B = 100 \times 93\mu A = \underline{9.3\text{ mA}} \quad (\text{Q-point})$$


$$\Rightarrow V_{CE} = V_{CC} - R_C I_C = 10V - 500\Omega \times 9.3\text{ mA} = 10V - 4.65V$$

$$= \underline{5.35V} \quad (\text{Q-point})$$

Q: Where is the Q-point located?

③

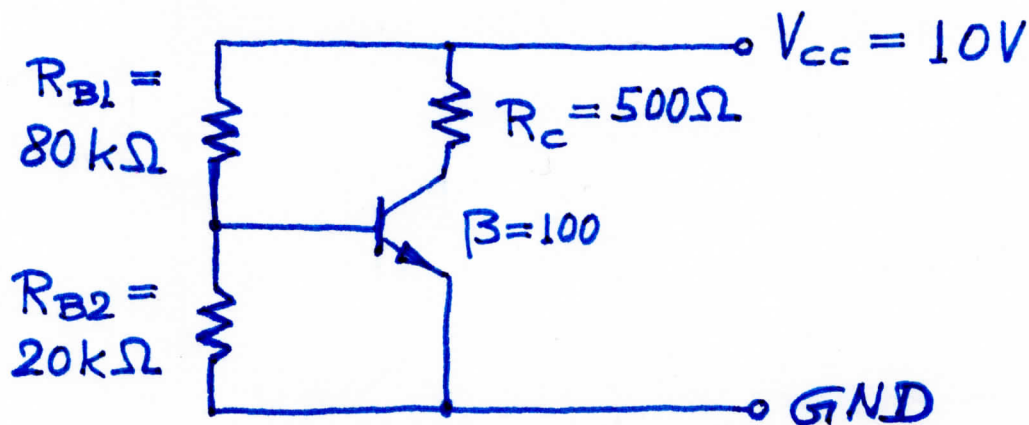2nd exercise: Determine Q-point of circuit below



Do R_{B1} & R_{B2} act as voltage divider?

\Rightarrow No \Rightarrow Why not? $\Rightarrow V_{BE} = 0.7V$

Calculate I_B .

$$I_{RB2} = \frac{V_{BE}}{R_{B2}} = \frac{0.7V}{20k\Omega} = 35\mu A$$

$$I_{RB1} = \frac{V_{CC} - V_{BE}}{R_{B1}} = \frac{9.3V}{80k\Omega} = 116\mu A$$

$$\Rightarrow I_B = I_{RB1} - I_{RB2} = 116\mu A - 35\mu A = 81\mu A$$


$$\Rightarrow I_C = \beta I_B = 100 \times 81\mu A = \underline{\underline{8.1\text{ mA}}}$$

$$\begin{aligned} \Rightarrow V_{BCE} &= V_{CC} - R_C I_C = 10V - 500\Omega \times 8.1\text{ mA} = \\ &= 10V - 4.05V = \underline{\underline{5.95V}} \end{aligned}$$

Q: Where is the Q-point located?

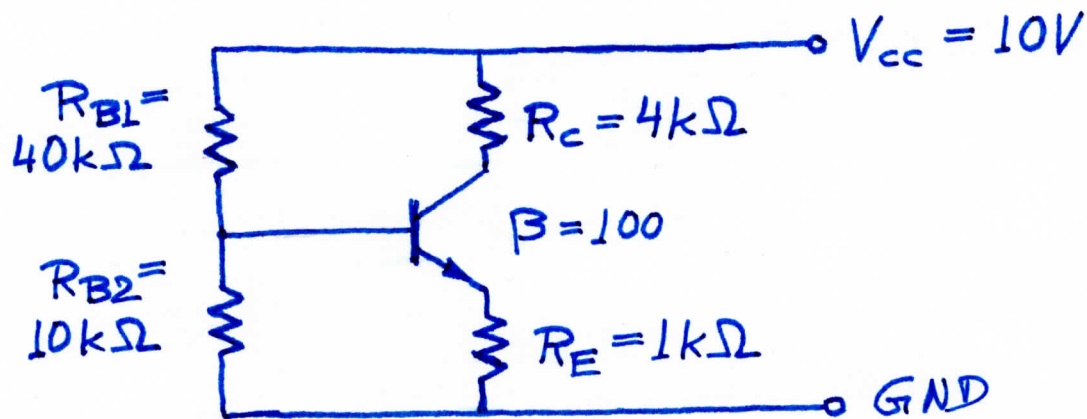(4)

3rd exercise: Determine Q-point of circuit below.



Q: Do R_{B1} & R_{B2} act as voltage divider?

We do not know. Let us assume that R_{B1} & R_{B2} act as voltage divider.

$$\Rightarrow V_{Base} = V_B = 10V \frac{R_{B2}}{R_{B1} + R_{B2}} = 10V \frac{10k\Omega}{50k\Omega} = 2.0V$$

$$\Rightarrow I_E = \frac{2V - 0.7V}{R_E} = \frac{1.3V}{1k\Omega} = 1.3mA$$

$$\Rightarrow I_B = \frac{I_E}{\beta + 1} \approx \frac{I_E}{\beta} = \frac{1.3mA}{100} = 13\mu A$$

Voltage divider carries about $200\mu A$ ($\frac{10V}{40k\Omega + 10k\Omega}$).

Load is $13\mu A$. $\Rightarrow R_{B1}$ & R_{B2} indeed act as voltage divider!

Next, we calculate I_C and V_{CE} of Q-point.

As calculated above $I_E = 1.3 \text{ mA}$

Collector current $\underline{I_C} = \alpha I_E \approx I_E = \underline{1.3 \text{ mA}}$

CE voltage: $\underline{V_{CE}} = V_{CC} - V_{RE} - V_{RC}$
 $= 10\text{V} - 1.3\text{mA} \cdot 1\text{k}\Omega - 1.3\text{mA} \cdot 4\text{k}\Omega$
 $= 10\text{V} - 1.3\text{V} - 5.2\text{V} = \underline{3.5\text{V}}$

Q: Where is the Q-point located on the load line? \Rightarrow Near the middle.

Q: Does the Q-point analysis provide us with I_E ? \Rightarrow Yes, of course.

Q: Which quantity can we calculate from I_E ? $\Rightarrow r_E = V_t / I_E$

Q: Why do we need r_E ? \Rightarrow Small-signal analysis