

Large-signal and small-signal analysis

Large-signal DC analysis

⇒ suitable for non-linear circuits

⇒ DC values I_B I_E I_C V_{BE} V_{CE}


Small-signal AC analysis

⇒ we can linearize any circuit and make it suitable for small-signal AC analysis.


⇒ Superposition principle applies

⇒ AC values i_B i_E i_C V_{BE} V_{CE}


Primitive common-E BJT circuit

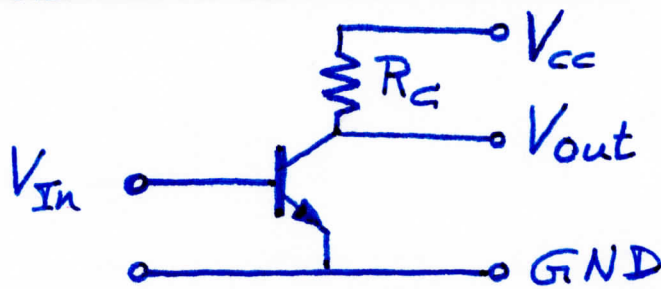

Equivalent circuit

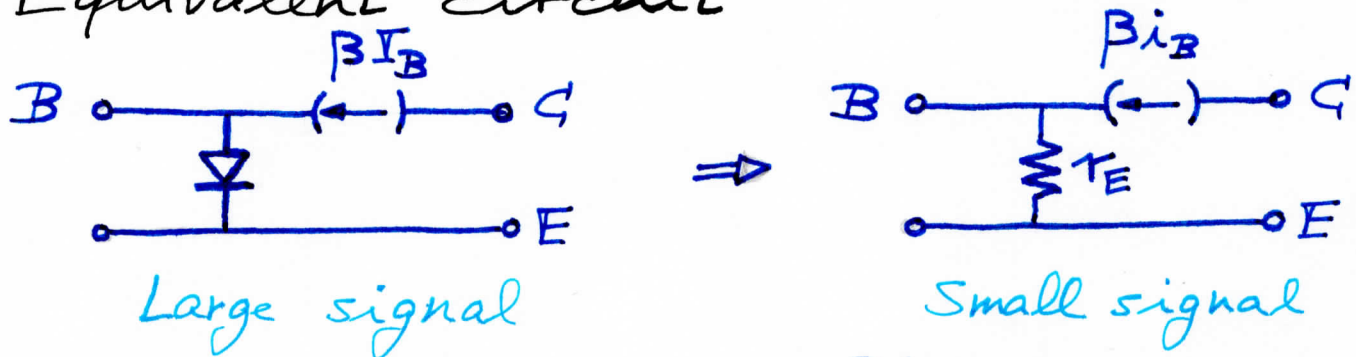

Include R_C

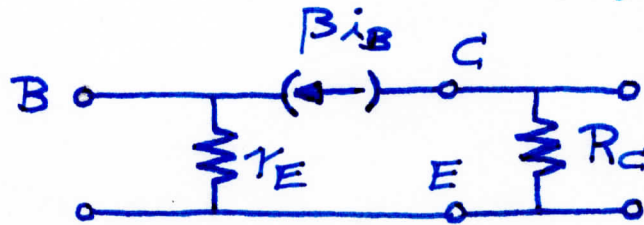

Voltage amplification

$$A_{VOC} = \frac{V_{out}}{V_{in}} = \frac{-\beta i_B R_C}{i_E r_E} = \frac{-\beta i_B R_C}{(\beta+1) i_B r_E}$$

$$\approx \underline{\underline{-R_C / r_E}}$$

Input impedance

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{r_E i_E}{i_B} = r_E \frac{(\beta+1) i_B}{i_B} \approx \underline{\underline{\beta r_E}}$$


Output impedance

$$Z_{out} = \frac{V_{out}}{i_{out}} = \frac{R_c i_c}{i_c} = \underline{R_c}$$

Q: What is a disadvantage of the primitive common-E circuit?

Q: Where is the quiescent point (Q-point) of the primitive common-E circuit?

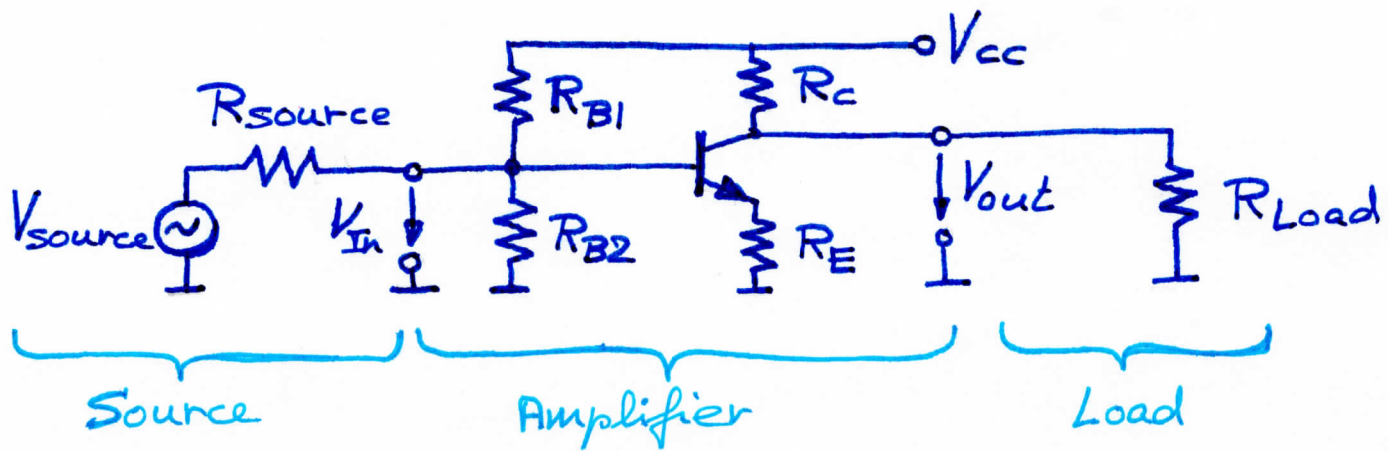Small-signal analysis of common-E amplifier



Strictly speaking, this is not a common-E amplifier.


But for $R_E = 0$, it would be a common-E amp.

Previously, we determined the Q-point. $\Rightarrow r_E = \frac{V_E}{I_E}$.

$V_{CC} \Rightarrow$ Ideal voltage source \Rightarrow Internal resistance?

\Rightarrow zero.

Small-signal equivalent circuit:

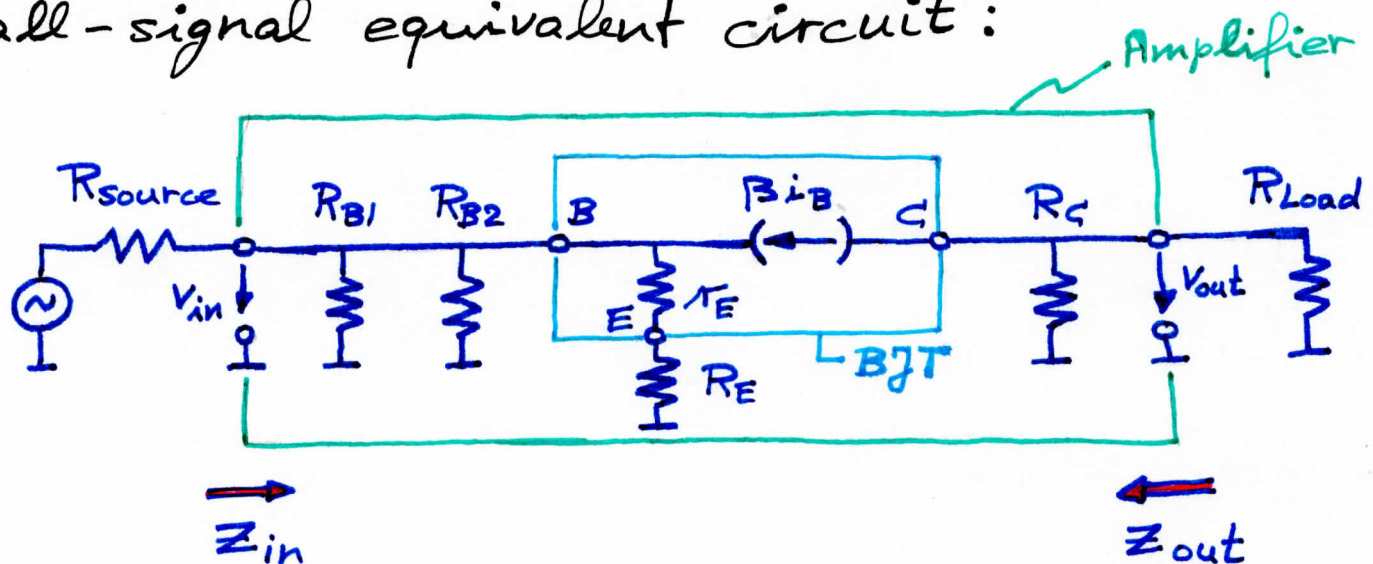

(5)

$$\underline{\underline{\text{Voltage amplification}}} = A_{VOC} = \frac{V_{out}}{V_{in}}$$

↳ VOC = open circuit voltage
⇒ No load

$$V_{in} = (i_B + \beta i_B)(r_E + R_E) = i_B (\beta + 1)(r_E + R_E) \\ \approx \beta i_B (r_E + R_E)$$

$$V_{out} = -\beta i_B R_C$$

$$\Rightarrow A_{VOC} = \frac{V_{out}}{V_{in}} = \frac{-\beta i_B R_C}{\beta i_B (r_E + R_E)} = \underline{\underline{\frac{-R_C}{r_E + R_E}}}$$

Input impedance

Input impedance without considering R_{B1} & R_{B2}

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{(r_E + R_E) i_E}{i_B} \quad \begin{matrix} \text{---} i_E = i_B(\beta + 1) \end{matrix} = (r_E + R_E)(\beta + 1) \\ \approx \underline{\underline{(r_E + R_E)\beta}}$$

Input impedance considering R_{B1} & R_{B2}

$$Z_{in} = \frac{V_{in}}{i_{in}} = (r_E + R_E)\beta \parallel \underbrace{(R_{B1} \parallel R_{B2})}_{R_B} \\ = \underline{\underline{\beta(r_E + R_E) \parallel R_B}}$$

⑥

Output impedance

Applying a voltage to the output terminals, which impedance would we "see"?

Recall: Resistance of $\circ \leftarrow \rightarrow \circ = \infty$

$$Z_{out} = \frac{V_{out}}{i_{out}} = \underline{\underline{R_C}}$$

$$\underline{\underline{\text{Current amplification}}} = A_{ISC} = \frac{i_{out}}{i_{in}}$$

$\rightarrow ISC = \text{Short circuit current}$

$$\Rightarrow R_L = 0$$

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{\beta i_B}{\underbrace{i_{RB} + i_B}} \approx \beta \frac{i_B}{i_{RB}}$$

$\rightarrow \text{Note: } i_{RB} \gg i_B. \text{ Why?}$

$$i_B = \frac{V_{in}}{(\tau_E + R_E) \beta}$$


$$i_{RB} = \frac{V_{in}}{R_B}$$

$$(R_B = R_{B1} \parallel R_{B2})$$

$$\Rightarrow A_{ISC} = \beta \frac{\underline{\underline{V_{in}}} R_B}{(\tau_E + R_E) \beta \underline{\underline{V_{in}}}} = \underline{\underline{\frac{R_B}{\tau_E + R_E}}}$$

Q: How to obtain a high current amplification?

Capacitive coupling in amplifiers

Recall:  $Z_C = \frac{1}{j\omega C}$

DC $\Rightarrow \omega = 0 \Rightarrow Z_C = \infty$


\Rightarrow For DC, the C is an OC

AC $\Rightarrow \omega = \text{finite, e.g. } 1 \text{ kHz}$

\Rightarrow Assume that C is large $\Rightarrow Z_C = 0$

\Rightarrow For AC, the C is a SC

Consider the following circuit:

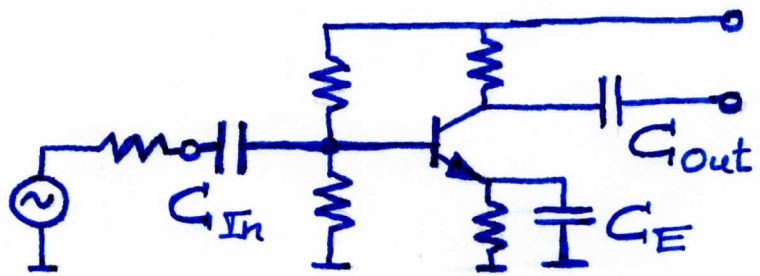

Q: What is purpose of C_{in} , C_{out} , and C_E ?

$\Rightarrow C_{in}$ decouples input from DC bias

$\Rightarrow C_{out}$ decouples output from DC bias

$\Rightarrow R_E$ provides operational stability but reduces A_{voc} . Bypassing R_E increases A_{voc} .