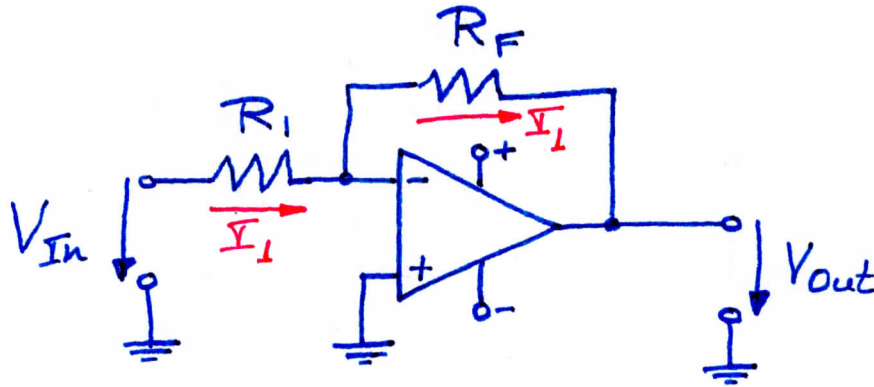


Basic differential amplifier circuit



⊕ Non-inverting input at GND

Ohm: $V_{In} = I_1 R_1$ $V_{out} = -I_1 R_F$

⇒ 2 eqns. ⇒ Eliminate I_1 ⇒ $\frac{V_{out}}{V_{In}} = \frac{-R_F}{R_1}$

⇒ $A = \frac{V_{out}}{V_{In}} = -\frac{R_F}{R_1}$

↳ Amplification or Gain


⇒ Amplification is largely controlled by the feedback resistor R_F

Feedback resistor R_F : Is feedback positive or negative? ⇒ Negative feedback. Why?

What would happen if we had positive feedback? ⇒ "Runaway"

For positive feedback ⇒ $V_{out} = +V_{cc}$

Summation circuit

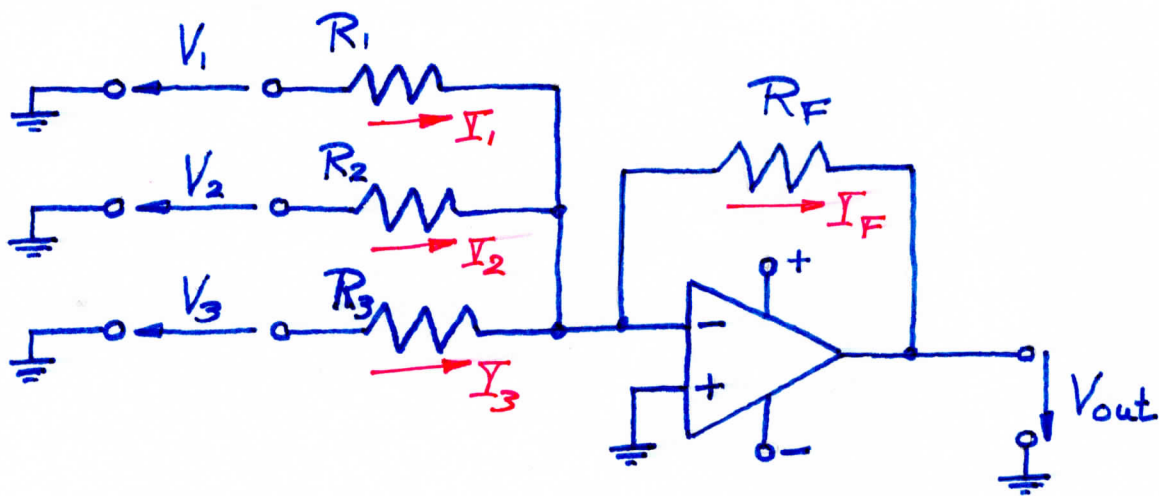

Non-inverting input \oplus connected to GND.
 Inverting input \ominus is "virtual GND". Why?

$$V_1 = I_1 R_1 \quad V_2 = I_2 R_2 \quad V_3 = I_3 R_3$$

$$I_F = I_1 + I_2 + I_3 \quad V_{out} = -I_F R_F$$

\hookrightarrow KCL \hookrightarrow KVL

$$\Rightarrow V_{out} = -R_F (I_1 + I_2 + I_3)$$

$$= -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

Consider the following case :

$$R_1 = R_2 = R_3 = R$$

$$\Rightarrow V_{out} = -\frac{R_F}{R} (V_1 + V_2 + V_3)$$

\Rightarrow Summation circuit

Consider the following case

$$R_1 = R_F$$


$$R_2 = \frac{1}{2} R_F$$

$$R_3 = 2 R_F$$

$$\begin{aligned} \Rightarrow V_{out} &= -R_F \left(\frac{V_1}{R_F} + \frac{V_2}{\frac{1}{2} R_F} + \frac{V_3}{2 R_F} \right) \\ &= - \left(V_1 + 2V_2 + \frac{1}{2} V_3 \right) \end{aligned}$$

\Rightarrow Weighted summation

Inverter circuit

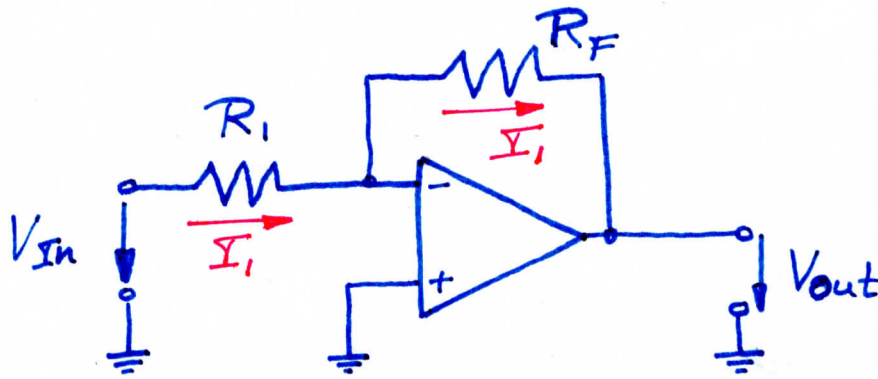

$$V_{In} = I_i R_i$$

$$V_{out} = -I_i R_F$$

Eliminate I_i from the two equations.

$$\Rightarrow V_{out} = -\frac{R_F}{R_i} V_{In}$$


Consider the following case:

$$R_F = R_i$$

$$\Rightarrow \boxed{V_{out} = -V_{In}}$$

\Rightarrow Inverter

Subtraction circuit

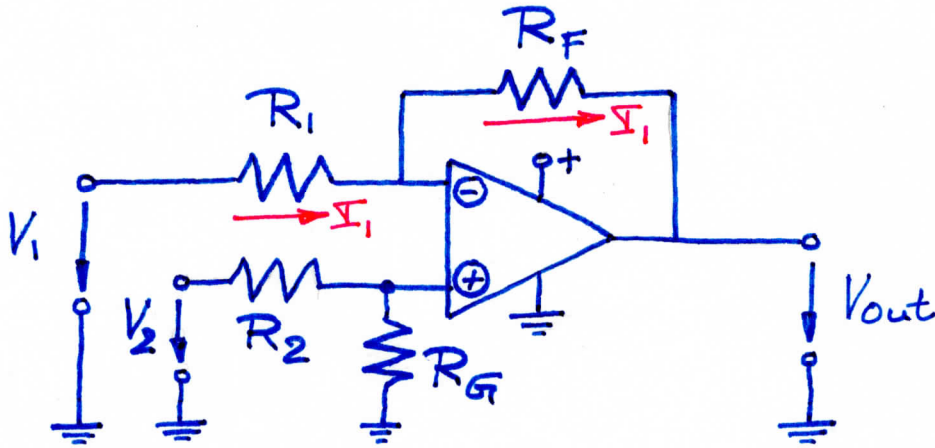

We can write: $V_{\oplus} = V_{\ominus}$ (Why?)

$$V_{\oplus} = V_2 \frac{R_G}{R_2 + R_G} = V_{\ominus} \quad (1) \text{ (voltage divider)}$$

$$V_1 = I_1 R_1 + V_{\ominus} \quad (2)$$

$$V_{out} = -I_1 R_F + V_{\ominus} \quad (3)$$

\Rightarrow 3 equations. 3 unknowns V_{out} , V_{\ominus} , I

* 1st step: eliminate I_1 from Eqns. (2) & (3)

$$\text{Eqn. (3): } I_1 = -\frac{V_{out} - V_{\ominus}}{R_F} \Rightarrow \text{Insert into Eqn. 2}$$

$$V_1 = \left(-\frac{V_{out} - V_{\ominus}}{R_F}\right) R_1 + V_{\ominus} \quad (4)$$

* 2nd step: eliminate V_{\ominus} from Eqns. (1) & (4)

$$\text{Eqn. (4): } V_1 = -\frac{R_1}{R_F} V_{out} + \frac{R_1}{R_F} V_2 \frac{R_G}{R_2 + R_G} + V_2 \frac{R_G}{R_2 + R_G}$$

⑥

$$-\frac{R_F}{R_1} V_1 = V_{out} - V_2 \frac{R_G}{R_2 + R_G} - V_2 \frac{R_F}{R_1} \frac{R_G}{R_2 + R_G}$$

$$V_{out} = -\frac{R_F}{R_1} V_1 + V_2 \left(\frac{R_G}{R_2 + R_G} + \frac{R_F}{R_1} \frac{R_G}{R_2 + R_G} \right)$$

$$= -V_1 \frac{R_F}{R_1} + V_2 \left(\frac{R_G}{R_2 + R_G} \right) \left(1 + \frac{R_F}{R_1} \right)$$

$$\Rightarrow V_{out} = -V_1 \frac{R_F}{R_1} + V_2 \left(\frac{R_G}{R_2 + R_G} \right) \left(\frac{R_1 + R_F}{R_1} \right)$$

Consider the following special case:

$$R_1 = R_2 = R_G = R_F$$

$$\Rightarrow V_{out} = -V_1 + V_2 = V_2 - V_1$$

\Rightarrow Voltage subtraction

Note: An alternative way to solve the present problem is to employ the superposition theorem.

V_1 and V_2 are inputs.

$$V_{out} = f(V_1) + f(V_2)$$

Consider the following special case:


$$R_1 = R_F \quad \text{and} \quad R_2 = 9R_G$$

$$\begin{aligned} \Rightarrow V_{out} &= -V_1 + V_2 \left(\frac{R_G}{9R_G + R_G} \right) \frac{2}{1} \\ &= -V_1 + V_2 \frac{1}{5} = \frac{1}{5} V_2 - V_1 \end{aligned}$$

\Rightarrow Weighted voltage subtraction

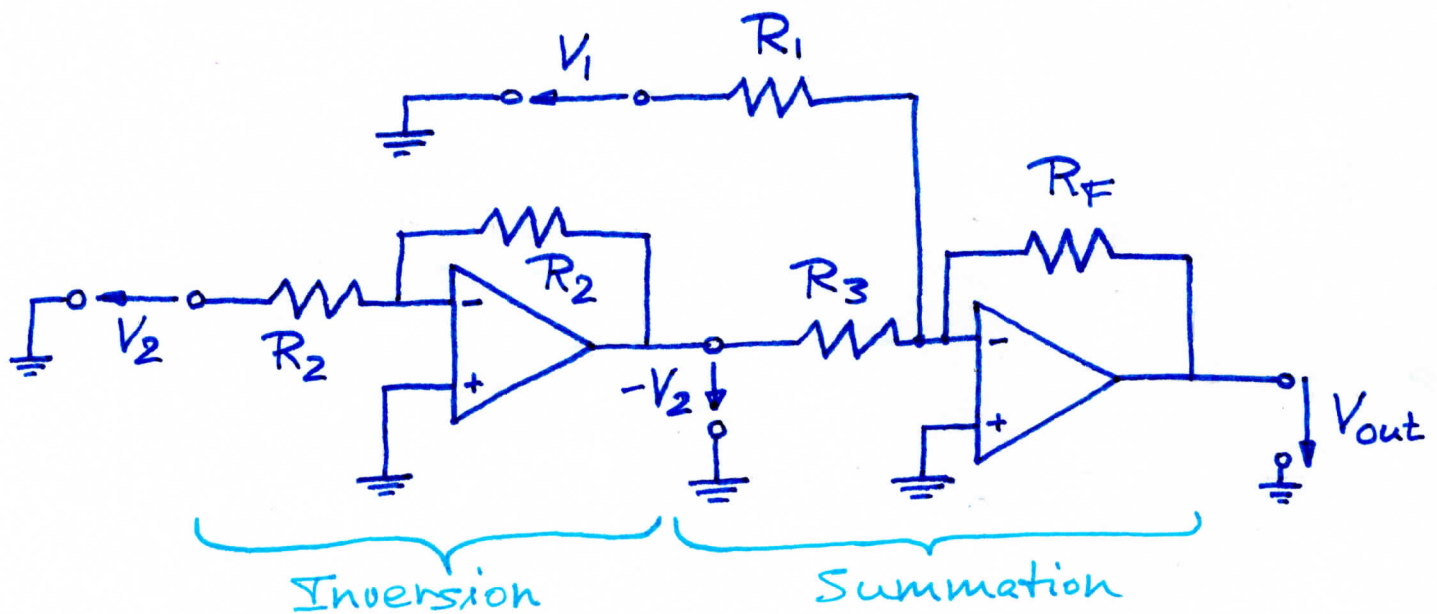(8)

Subtraction implemented by inversion - followed by - summation circuit



Output of inverting differential amplifier

$$V_{out, \text{inverter}} = -\frac{R_2}{R_2} V_2 = -V_2$$

Output of summation differential amplifier

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{-V_2}{R_3} \right) \quad (\text{shown previously})$$

$$= -\frac{R_F}{R_1} V_1 + \frac{R_F}{R_3} V_2$$


\Rightarrow Weighted subtraction

Consider the following special case:

$$R_1 = R_3 = R_F \Rightarrow V_{out} = V_2 - V_1$$

\Rightarrow Subtraction

Comparator circuit

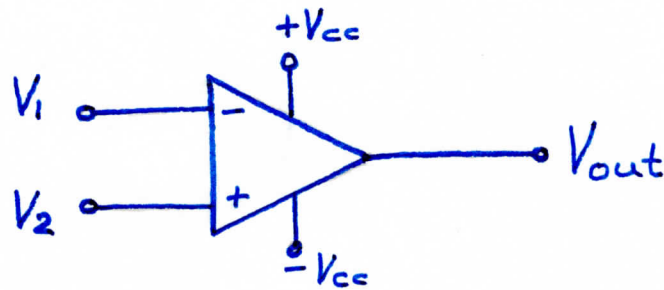


All voltages are with respect to GND

No feedback $\Rightarrow R_F = \infty \Rightarrow \text{Amplification} = \infty$

If $V_1 > V_2 \Rightarrow V_{out} = -V_{cc}$

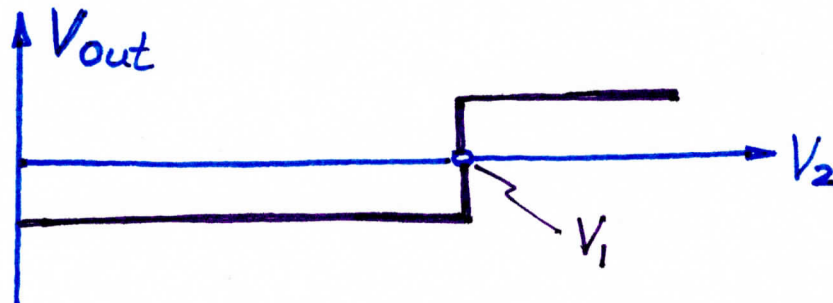If $V_1 < V_2 \Rightarrow V_{out} = +V_{cc}$



\Rightarrow Comparator functionality