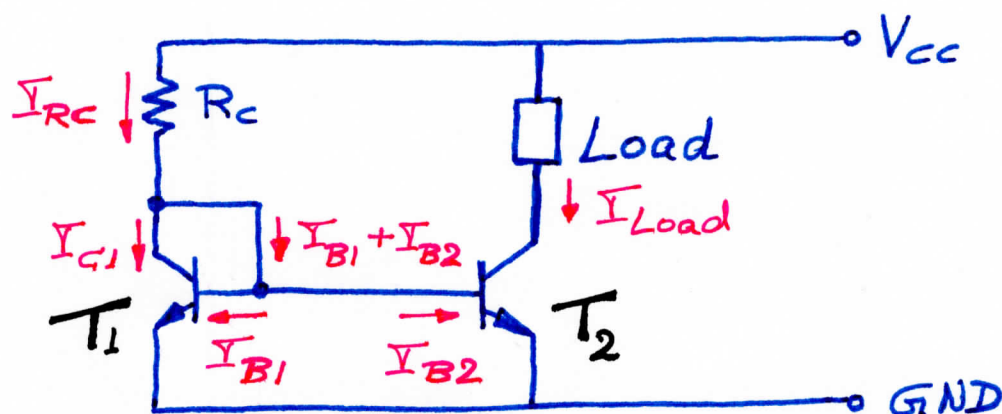


Iconic circuit: Current mirror

①



Assume T_1 & T_2 have the same properties: $\beta_1 = \beta_2 = \beta$

Function: The current through the LHS branch is mirrored (replicated) to the RHS branch

LHS = Left hand side RHS = Right hand side

Q: V_{BE} of T_1 & T_2 exactly the same?

Q: $I_{B1} = I_{B2}$?

Q: $V_{BE1} = ?$ $V_{BE2} = ?$

Q: What is V_{CE} of T_1 ?

Q: Is T_1 in saturation or forward active?

$$\Rightarrow I_{C1} = \beta I_{B1}$$

$$I_{C2} = \beta I_{B2}$$

(2)

Q: What is current through R_C ?

$$\begin{aligned} I_{RC} &= I_{C1} + I_{B1} + I_{B2} = \beta I_{B1} + 2 I_{B1} \\ &= I_{B1} (\beta + 2) \approx \underline{\underline{\beta I_{B1}}} \end{aligned}$$

Q: What is current through Load?

$$I_{Load} = I_{C2} = \beta I_{B2} = \underline{\underline{\beta I_{B1}}}$$

\Rightarrow

$$I_{Load} \approx I_{RC}$$