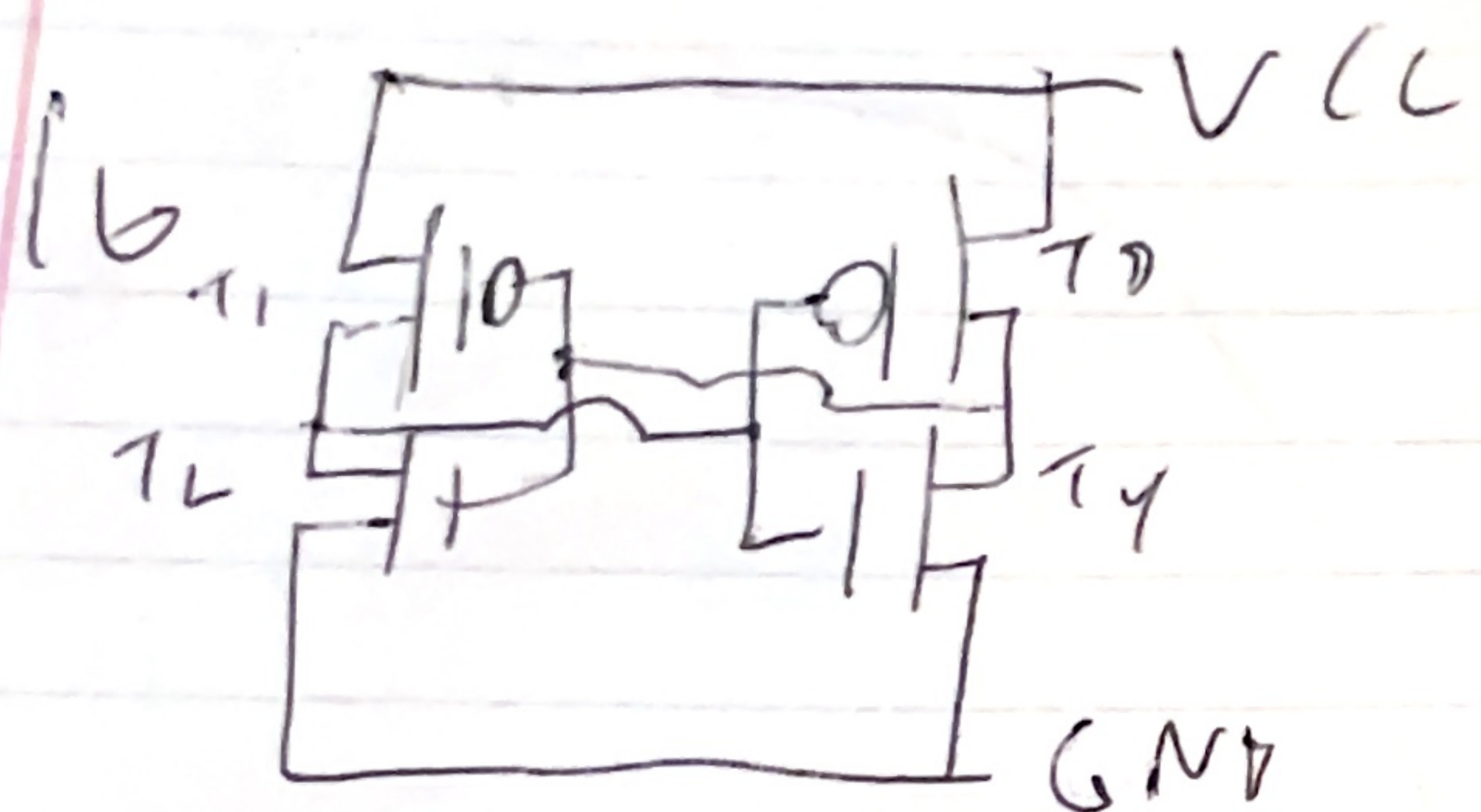



$$P \approx \frac{V_{CC}^2}{R_C} \quad \text{Since } R_C \gg R_D$$

$$V_{DC} \approx V_{CC}$$




Static power consumption

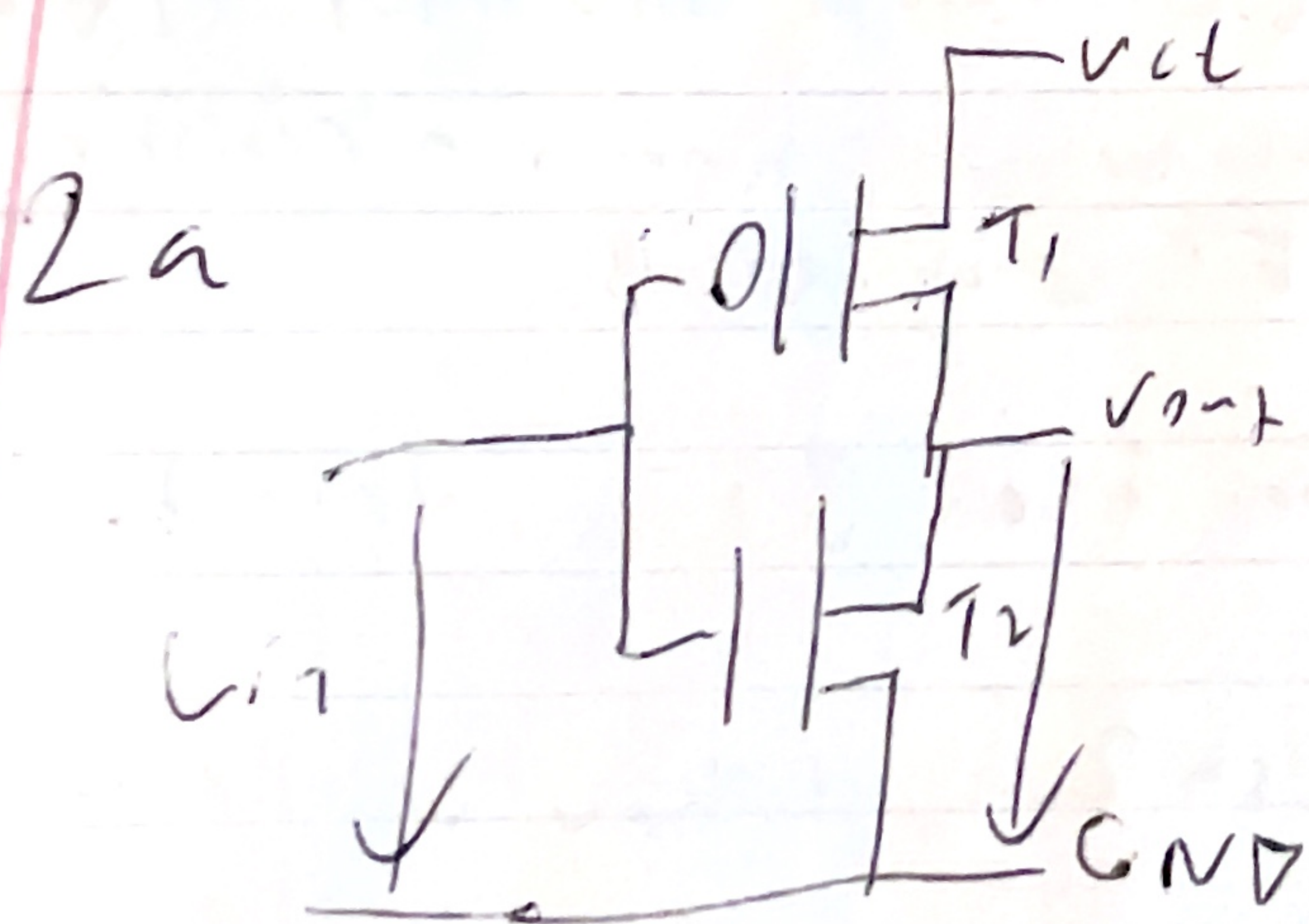(C) BJT based SRAM cells consume more power than their FET counterparts.



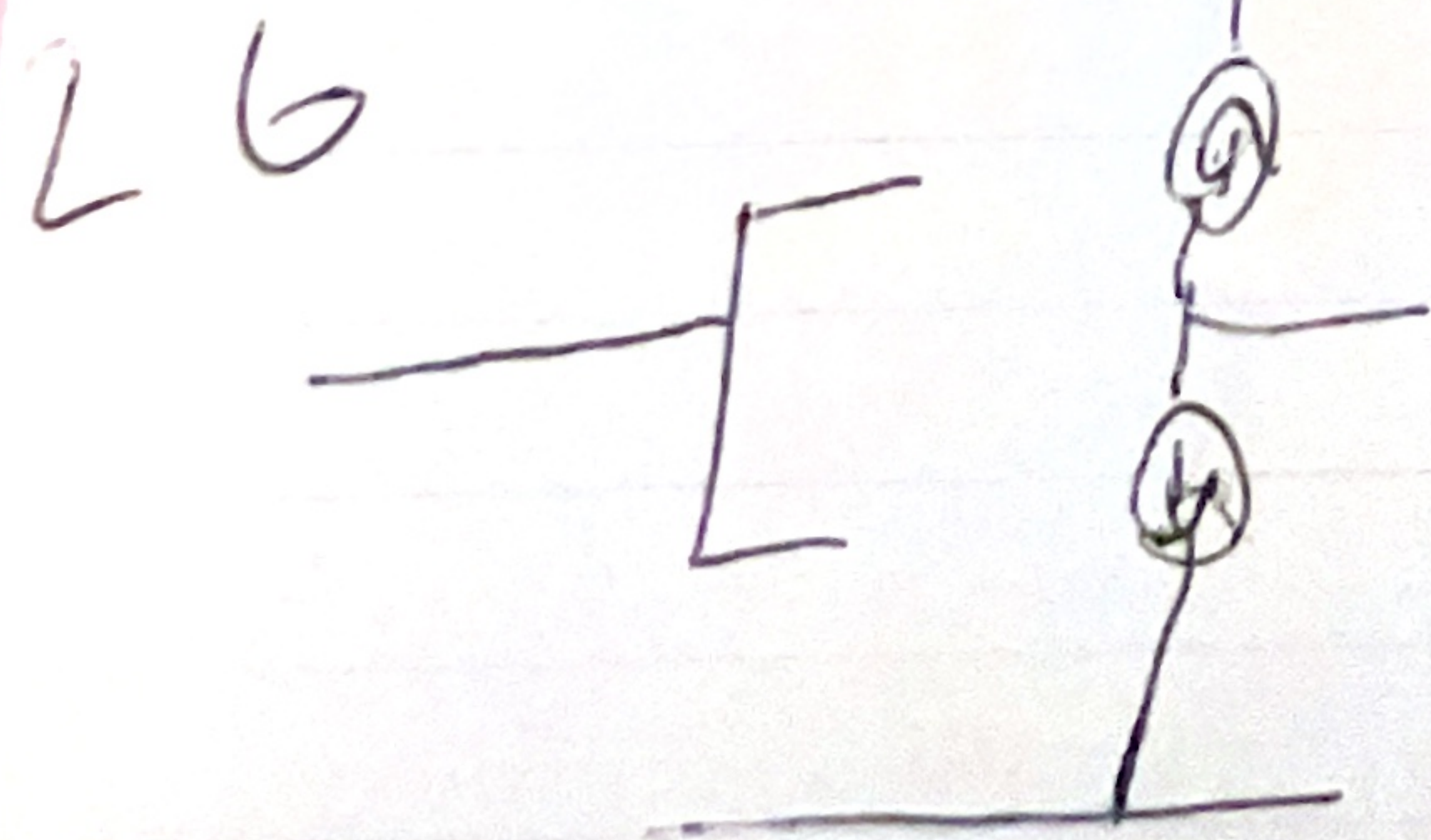If $V_{in} = 0$, T_1 is on and T_2 is off. This would make $V_{out} = V_{CC}$. If $V_{in} \approx V_{CC}$, then T_1 is off, making $V_{out} = GND$.




The small signal circuit has no interaction between V_{in} and V_{out} .

2c 0 static power consumption

2d They have 0 static power consumption, so they generate no heat.

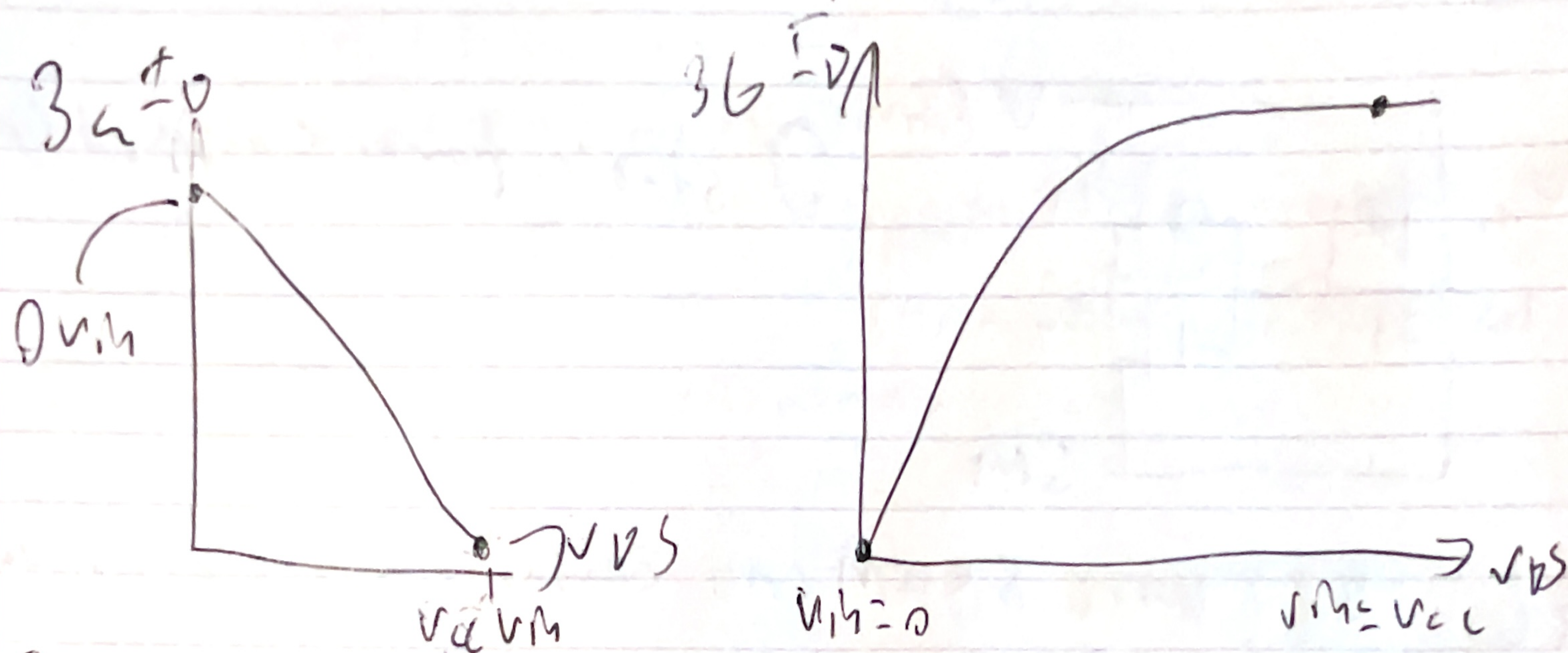2e They consume power, and thus produce heat.



3c They both invert V_{in} s but have different V_{out} vs V_{in} graphs. Due to the difference between having a resistor block access to V_{DD} or a pFET block access.

4a False. FETs are faster than BJTs in most instances.

4b True. With FETs high Z_{in} , they will draw little current from the signal, keeping it intact.