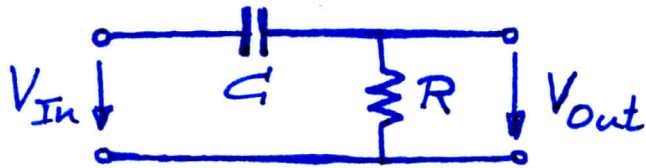


# High-frequency - pass filter



$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\omega \rightarrow 0 \Rightarrow |H(\omega)| \approx \omega RC \Rightarrow |H(\omega)| \rightarrow 0$$

$$\omega \rightarrow \infty \Rightarrow |H(\omega)| \approx 1 \Rightarrow |H(\omega)| \rightarrow 1$$


$$\omega = \frac{1}{RC} \Rightarrow |H(\omega)| = \frac{1}{\sqrt{2}} \Rightarrow 3\text{dB point}$$

$$\omega \ll \frac{1}{RC} \Rightarrow |H(\omega)| \approx \omega RC$$

$|H(\omega)| \propto \omega$

$$\Rightarrow \left. \begin{array}{l} 6\text{dB / octave} \\ 20\text{dB / decade} \end{array} \right\} \text{Voltage \& Power}$$



# Bode plot

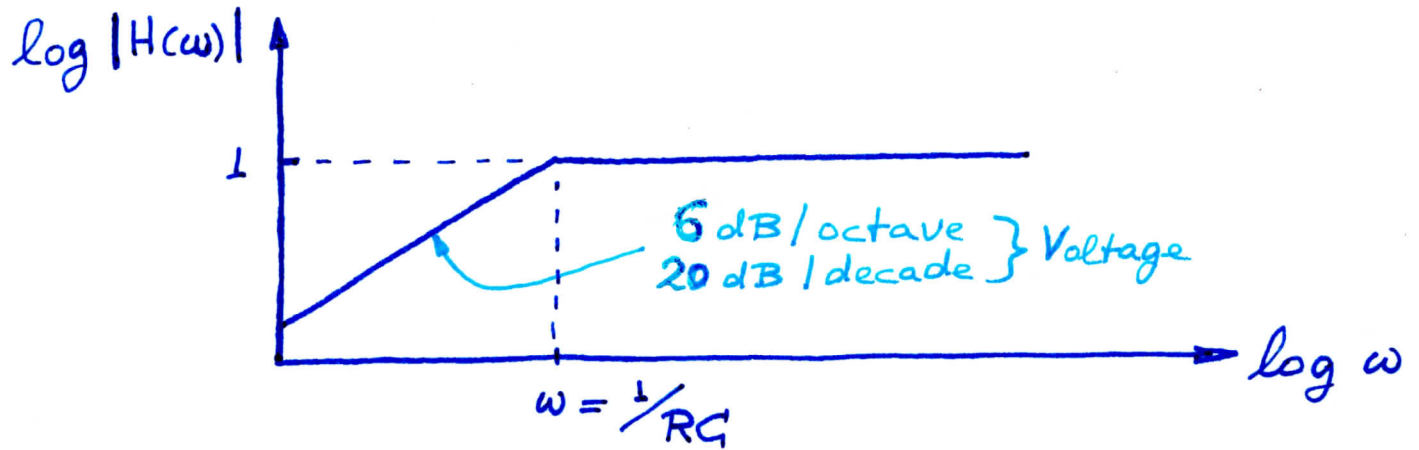



- ⇒ We find a qualitatively similar behavior (but opposite behavior) for low-pass filters and high-pass filters.
- ⇒ Common devices (Op Amps, BJTs, FETs...) share the characteristics discussed above because they are governed by RC circuits and associated RC time constants.

# Multi-stage filters



Recall:

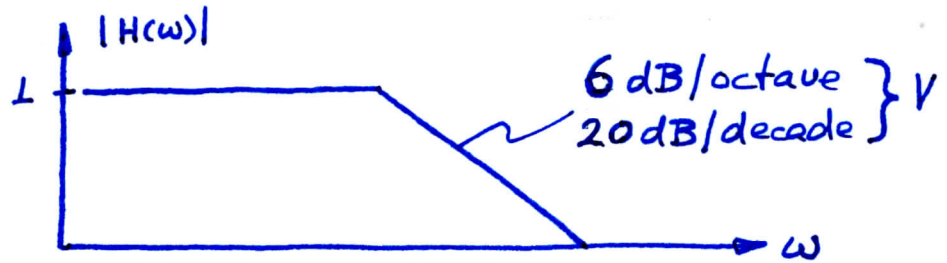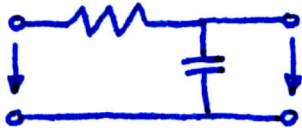

Consider two RC filters

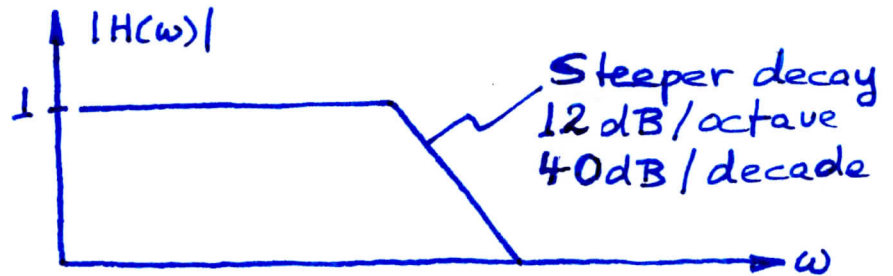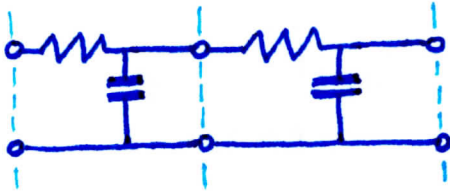


Consider  $N$  RC filters

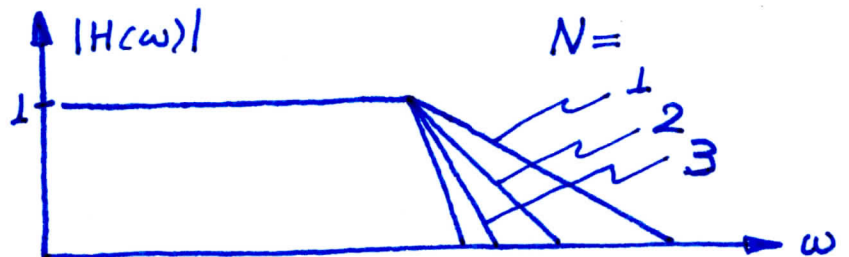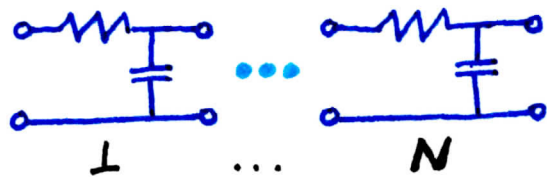

⇒ We can design the steepness of the cut-off region of the filter.

## DC - blocking capacitors

Consider the following circuit

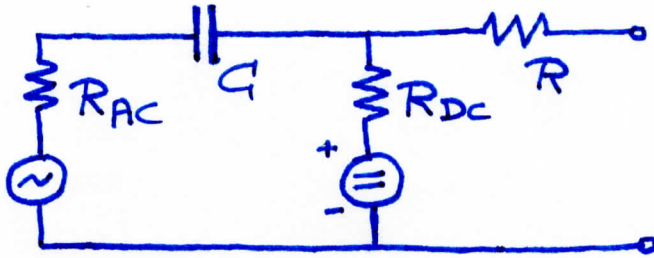

Q: What kind of filter is this ?

⇒ High-frequency-pass filter

Q: What about DC ?

⇒ For DC ⇒  $f = 0$

⇒ DC is blocked

Q: Implications for circuit ?

⇒ DC is blocked at C

⇒ AC source is decoupled from DC source

⇒ AC source is protected from DC source

⇒ We can use a C to let AC & DC propagate on different paths.

⇒ If C is sufficiently large, it lets AC go through yet blocks DC.