


Bipolar junction transistor (BJT)

- * Two pn-junctions, e.g. pnp, with the middle n-type layer being very thin
- * Base thickness \ll Diffusion length of carriers
- * Three electrodes: Emitter (E), Base (B) and Collector (C)

Emitter \Rightarrow Emits charge carriers


Base \Rightarrow Middle electrode; Control electrode

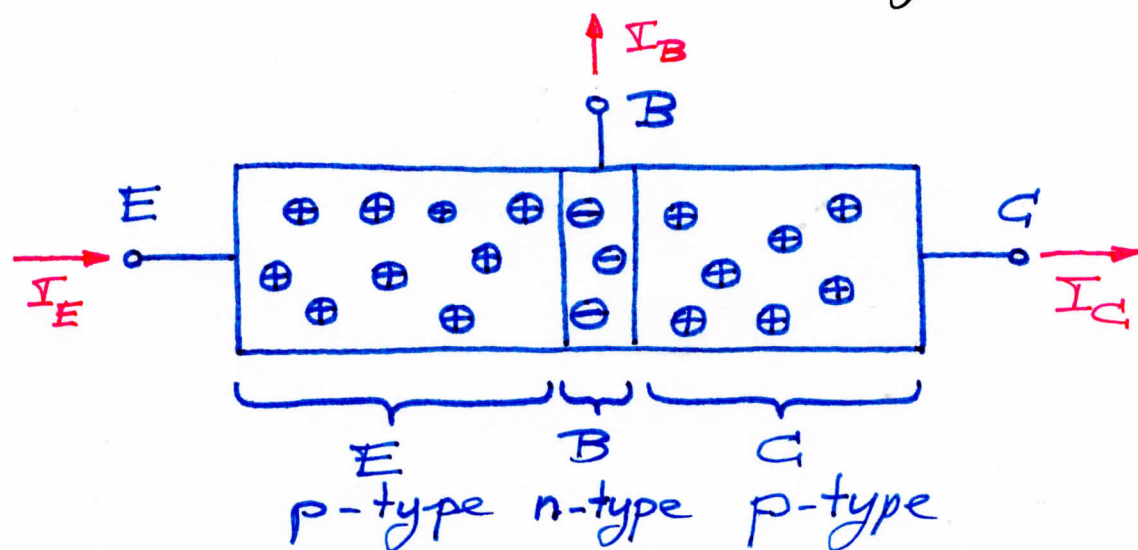Collector \Rightarrow Collects charge carriers




②

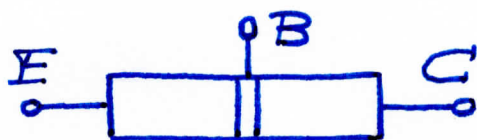
* BE diode \Rightarrow Forward bias $\Rightarrow V_{BE} \approx 0.7V$
 $\Rightarrow I_E$ is controlled by $V_{BE} \Rightarrow$ Base (B)
is very thin \Rightarrow Most carriers injected
from Emitter (E) into Base (B) reach
the Collector (C).



Current

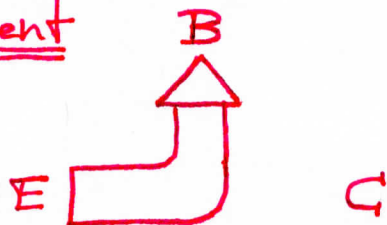

No! False!

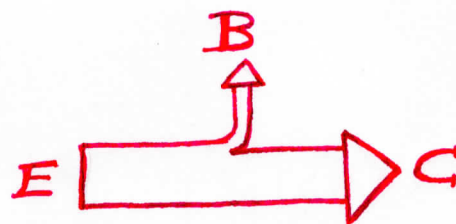


$$I_C = \alpha I_E$$

$\begin{cases} \rightarrow \approx 1.0 \\ \rightarrow 0.99 \end{cases}$

KCL

$$I_E = I_B + I_C$$


Flow of charge carriers

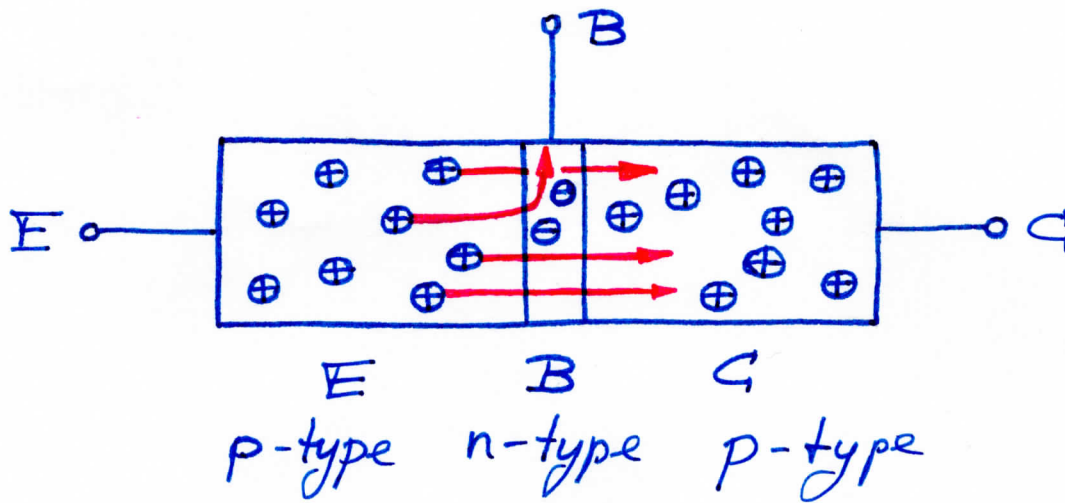

- \Rightarrow Most holes (\oplus) injected from E into B reach the C.
- \Rightarrow C is negatively biased with respect to B, thereby attracting holes and make them go from **E** to **C**.

BJT circuit symbols

pnP transistor

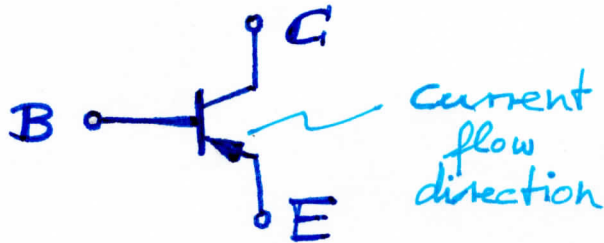


$C \Rightarrow$ p-type

$B \Rightarrow$ n-type

$E \Rightarrow$ p-type

$V_{BE} < 0$ (negative) in active regime

npn transistor

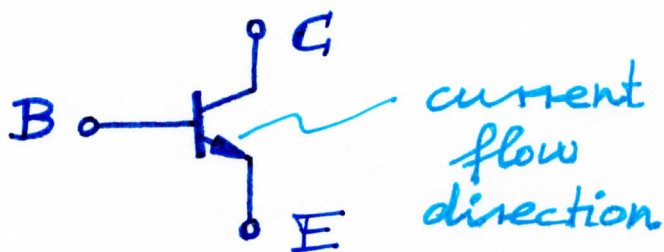

$C \Rightarrow$ n-type


$B \Rightarrow$ p-type

$E \Rightarrow$ n-type

$V_{BE} > 0$ (positive) in active regime

Current amplification

Common-base (B) circuit

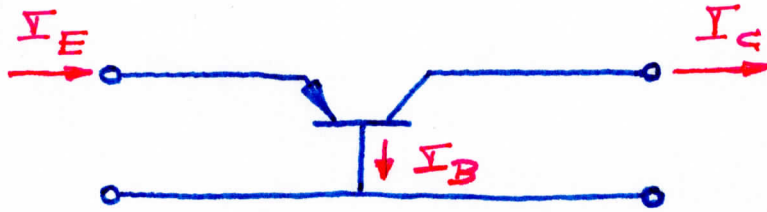


Recall: $I_C = \alpha I_E$ $\rightarrow \approx 1.0$ e.g. 0.99

KCL: $I_B = I_E - I_C$

Current amplification = $\frac{I_{out}}{I_{in}} = \frac{I_C}{I_E} = \alpha$

\Rightarrow $I_C = \alpha I_E$

Common-emitter (E) circuit

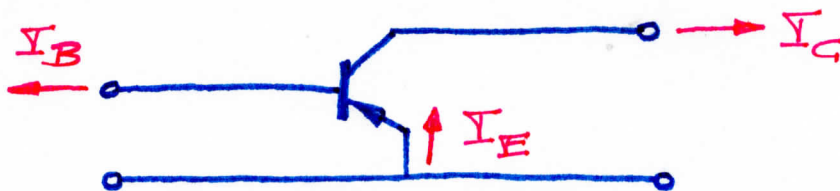

Recall: $I_C = \alpha I_E$

KCL: $I_B = I_E - I_C$


Current amplification = $\frac{I_{out}}{I_{in}} = \frac{I_C}{I_B} = \frac{I_C}{I_E - I_C} =$
 $= \left(\frac{I_E - I_C}{I_C} \right)^{-1} = \left(\frac{I_E}{\alpha I_E} - 1 \right)^{-1} = \left(\frac{1}{\alpha} - 1 \right)^{-1} = \frac{1}{\frac{1}{\alpha} - 1}$

⑥

$$= \frac{\alpha}{1-\alpha} = \beta \quad \text{with } \beta \gg 1 \quad \text{e.g. } \beta = 100$$

$$\Rightarrow \boxed{I_C = \beta I_B} \quad \boxed{\beta = \alpha / (1-\alpha)}$$

Common - collector (C) circuit

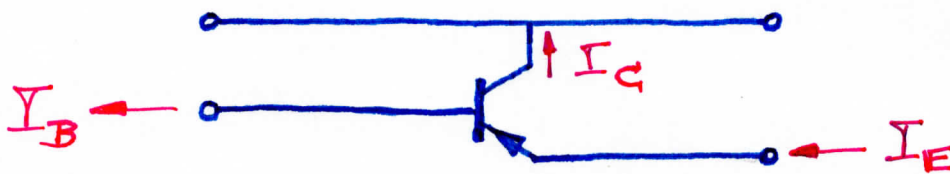

Recall: $I_C = \alpha I_E$

KCL: $I_B = I_E - I_C$

$$\begin{aligned} \text{Current amplification} &= \frac{I_{out}}{I_{in}} = \frac{I_E}{I_B} = \frac{I_E}{I_E - I_C} = \\ &= \left(\frac{I_E - I_C}{I_E} \right)^{-1} = \left(1 - \frac{I_C}{I_E} \right)^{-1} = (1 - \alpha)^{-1} = \frac{1}{1 - \alpha} = \end{aligned}$$

$$= \beta + 1 \quad \Rightarrow \quad \boxed{I_E = (\beta + 1) I_B}$$

Note: $\frac{\alpha}{1-\alpha} = \beta$

$$\frac{\alpha}{1-\alpha} + 1 = \beta + 1$$

$$\frac{\alpha + 1 - \alpha}{1 - \alpha} = \beta + 1$$

$$\boxed{\frac{1}{1-\alpha} = \beta + 1} \dots \text{what was to be shown}$$