
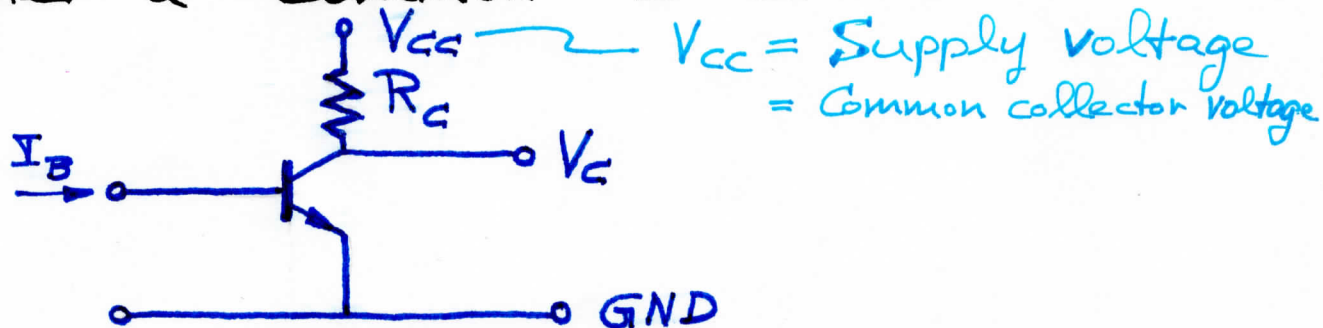


BJT output characteristic

Consider a common - E circuit

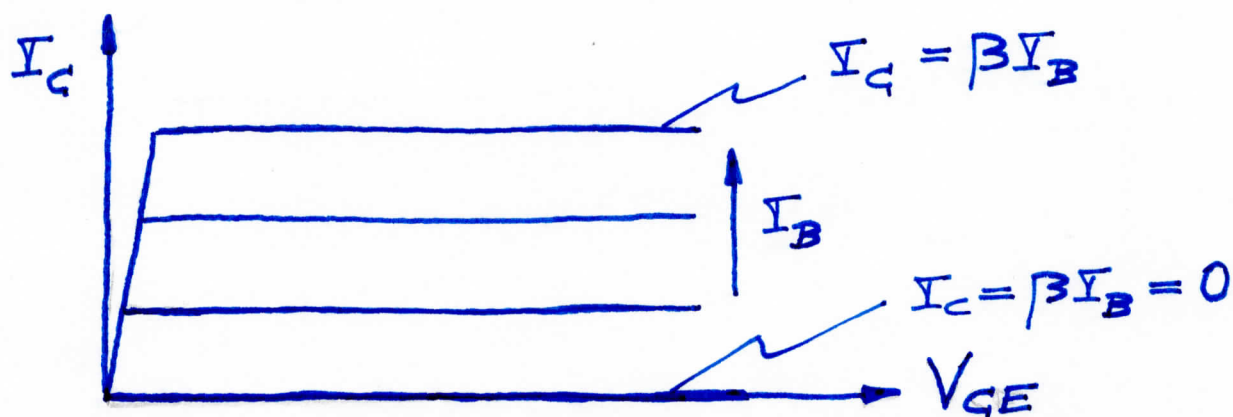

Transistor output characteristic




KVL $V_{CC} = I_C R_C + V_{CE}$ Load line

Solve for $I_C \Rightarrow$ $I_C = -\frac{1}{R_C} V_{CE} + \frac{V_{CC}}{R_C}$

Slope Variable Constant

Recall: Straight line $y = mx + c$

\Rightarrow Load line

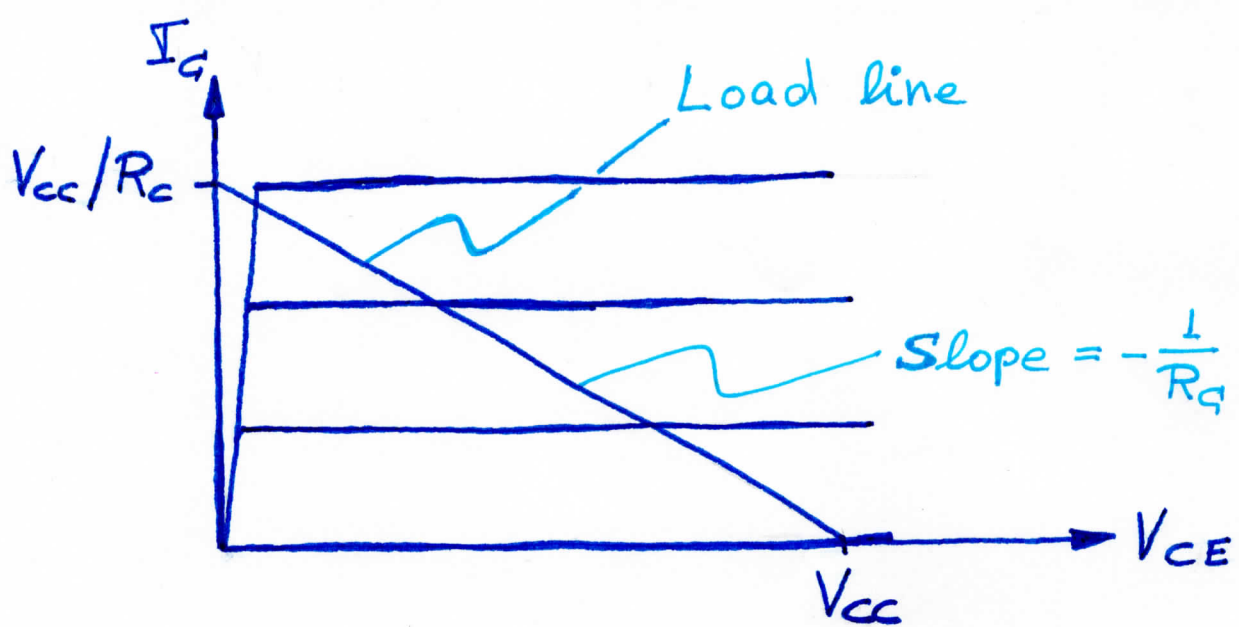

Q: What is output resistance of transistor?


Q: What is output resistance of the transistor circuit?

Q: Is a transistor a voltage source or current source?

Q: Can you write $V_C = f(I_B)$?

$$\begin{aligned} \Rightarrow V_C &= V_{CC} - I_C R_C \\ &= V_{CC} - \beta I_B R_C \end{aligned}$$

Operating regimes of BJT

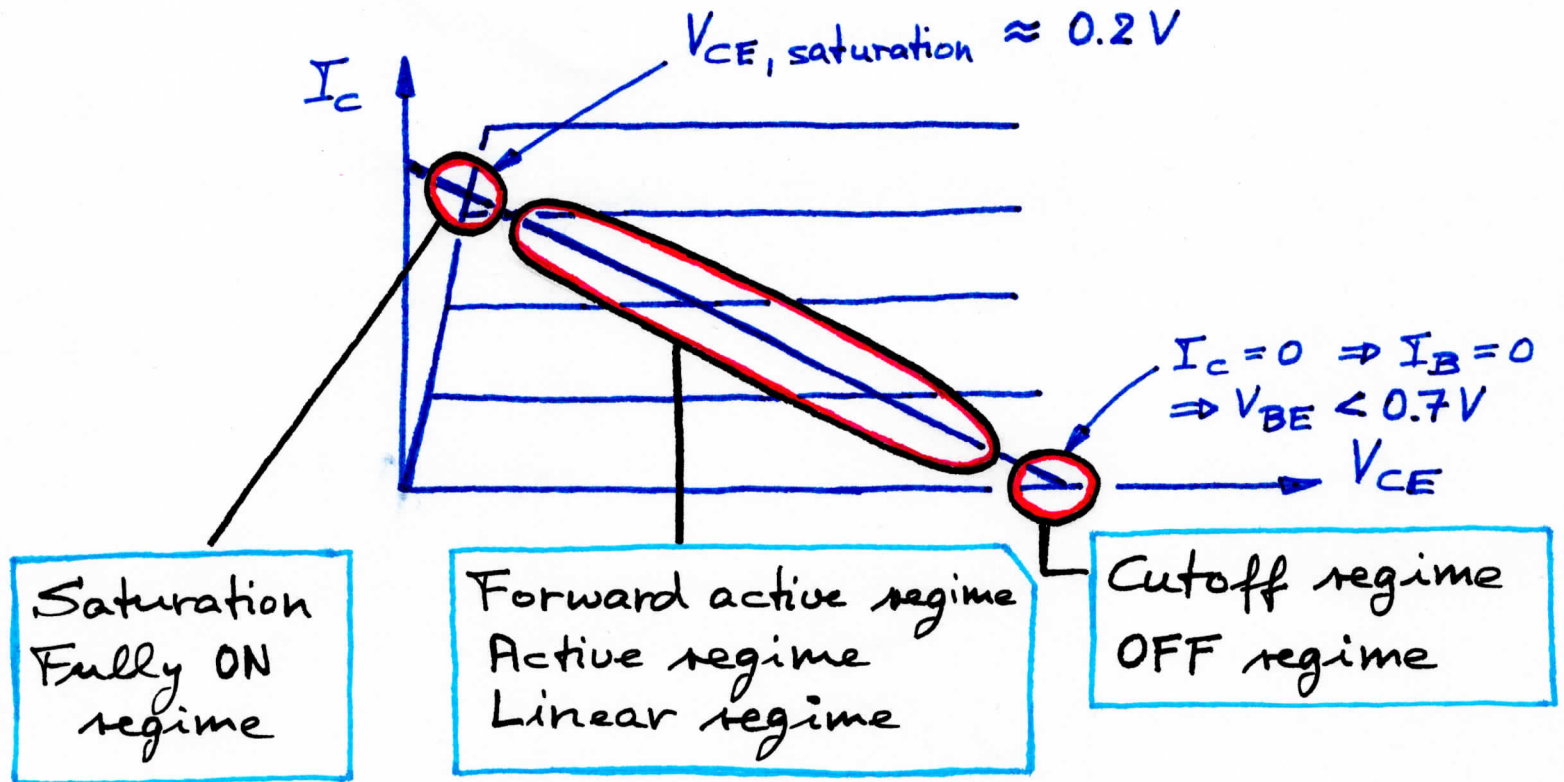

Cutoff: $V_{BE} < 0.7V \Rightarrow I_B = I_C = 0 \Rightarrow \text{OFF}$

CE "resistance" = $\infty \Rightarrow$ Transistor blocks

Forward active: $I_C = \beta I_B \Rightarrow$ Linear regime

$V_{BE} = 0.7V \Rightarrow$ Linear operating regime

\Rightarrow Used in amplifiers

Saturation: Transistor is fully **ON**

$V_{CE} \approx 0.1 \sim 0.2V$