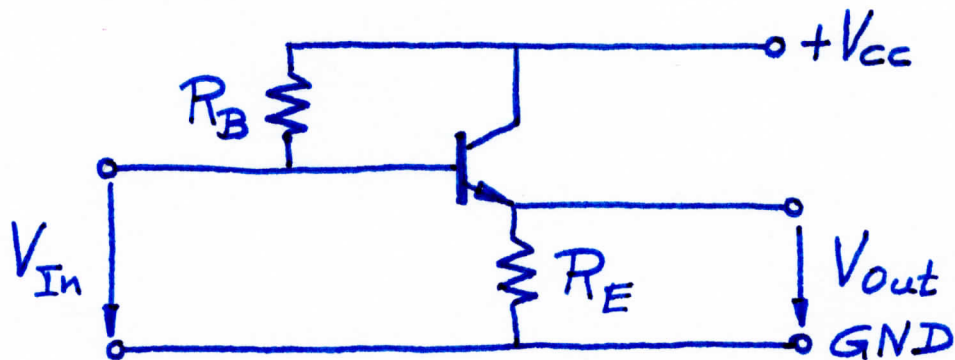


①

Common - collector circuit


⇒ Emitter follower



$$V_{out} = V_{In} - V_{BE} = V_{In} - 0.7V$$


⇒ V_{out} follows V_{In} but is $0.7V$ smaller than V_{In} ⇒ Emitter follower

Connect source and load

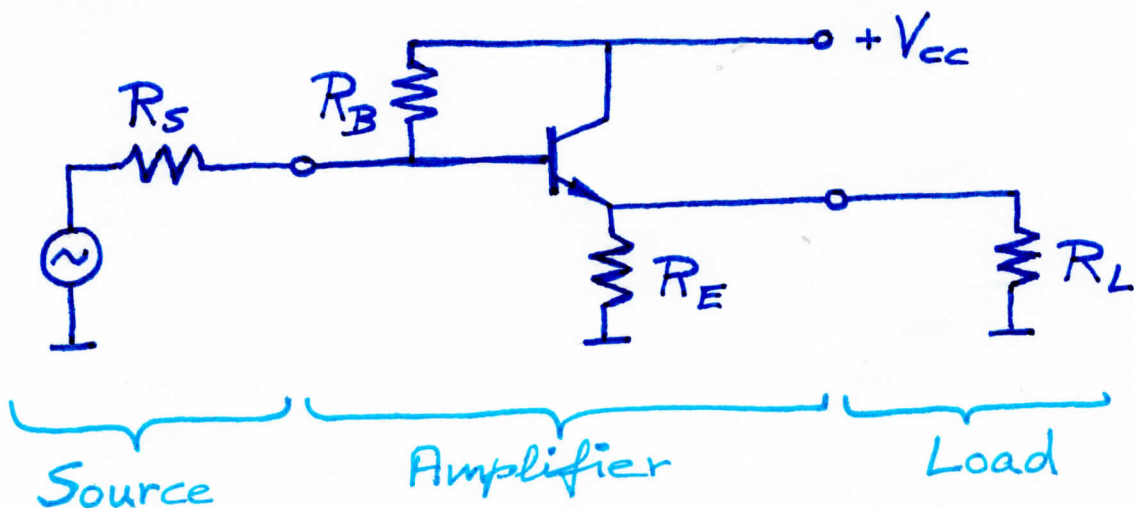

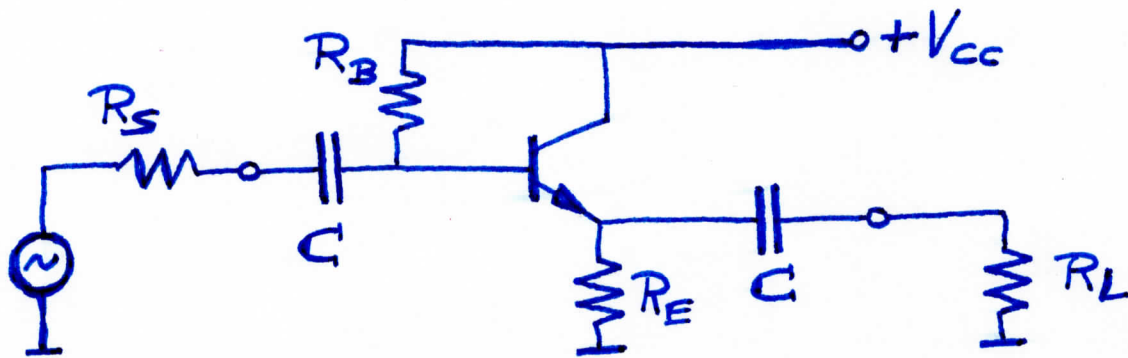(2)

AC coupling capacitors (to decouple source and load from DC bias of transistor)



DC analysis \Rightarrow Quiescent point (Q-point)

$$\text{KVL} \quad I_B R_B + \underbrace{V_{BE}}_{0.7V} + \underbrace{I_E R_E}_{(\beta+1)I_B} = V_{CC}$$

\Rightarrow One eqn. with one unknown (I_B)

\Rightarrow Solve for I_B

$$\Rightarrow I_B = \frac{V_{CC} - 0.7V}{R_B + (\beta+1)R_E}$$

$$\Rightarrow I_E = (\beta+1)I_B \quad I_C = \beta I_B$$


$$V_E = I_E R_E = (\beta+1)I_B R_E$$

$$V_{CE} = V_{CC} - V_E$$

\Rightarrow This completes Q-point calculation

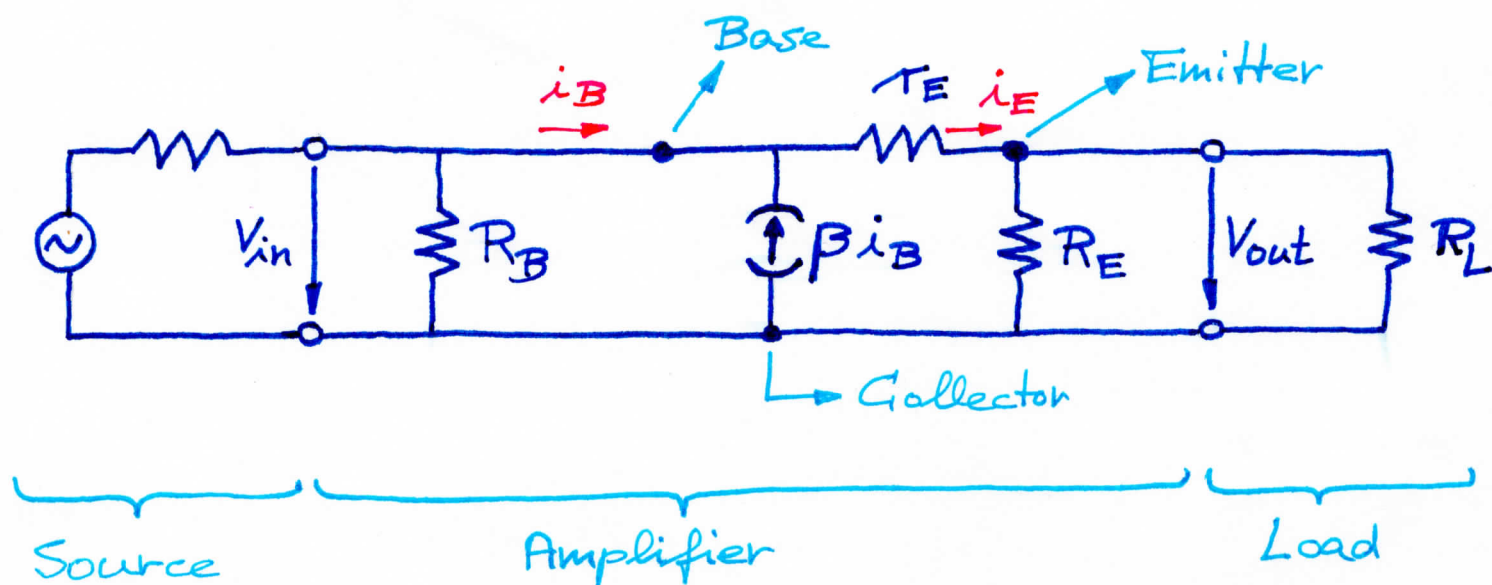(3)

AC analysis \Rightarrow AC equivalent circuit



OC voltage gain A_{voc}

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{i_E R_E}{i_E r_E + i_E R_E} = \frac{R_E}{r_E + R_E}$$

$$\Rightarrow A_{voc} < 1$$

$$\text{Recall: } r_E \ll R_E \Rightarrow A_{voc} \approx \frac{R_E}{R_E} \approx 1$$

$$\Rightarrow \boxed{A_{voc} \lesssim 1} \Rightarrow V_{out} \approx V_{in}$$

Input impedance Z_{in}

$$\begin{aligned}
 Z_{in} &= \frac{V_{in}}{i_{in}} = \frac{V_{in}}{i_{RB} + i_B} = \left(\frac{i_{RB} + i_B}{V_{in}} \right)^{-1} \\
 &= \left(\frac{1}{R_B} + \frac{i_B}{V_{in}} \right)^{-1} = R_B \parallel \frac{V_{in}}{i_B} \\
 &= R_B \parallel \frac{i_E (\tau_E + R_E)}{i_B} = R_B \parallel (\beta + 1)(\tau_E + R_E) \\
 &\approx R_B \parallel \beta(\tau_E + R_E)
 \end{aligned}$$


Note: Base bias network generally more resistive than R_E . Also: $\tau_E \ll R_E$

$$\Rightarrow \underline{Z_{in} \approx \beta R_E}$$

\Rightarrow Emitter follower has high input impedance.

Output impedance z_{out}
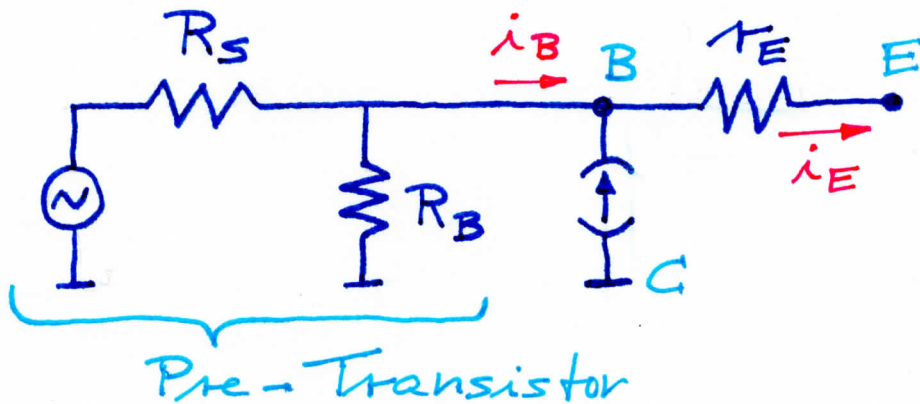
$$z_{out} = \frac{V_{out}}{i_{out}} = R_E \parallel (\tau_E + \underbrace{z_{pre-T}}_{z_{pre-Transistor}})$$



$$z_{pre-T} = \frac{V_{pre-T}}{i_E} = \frac{i_B (R_S \parallel R_B)}{i_E} = \frac{i_B (R_S \parallel R_B)}{(\beta + 1) i_B}$$

$$= \frac{R_S \parallel R_B}{\beta + 1}$$

$$\Rightarrow z_{out} = R_E \parallel \left(\tau_E + \frac{R_S \parallel R_B}{\beta + 1} \right)$$

$$\Rightarrow \underline{\underline{z_{out} \leq R_E}}$$

$\Rightarrow z_{out}$ is much smaller than z_{in}

\Rightarrow Difference is a factor of β

SC current gain

A_{ISC}

⑥

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{(\beta+1) i_B}{i_B + i_{RB}} = \frac{\beta+1}{1 + \frac{i_{RB}}{i_B}}$$

$$\text{Assume } i_{RB} \approx i_B \Rightarrow A_{ISC} = \beta/2$$

$$\text{Assume } i_{RB} \ll i_B \Rightarrow A_{ISC} = \beta$$

$$\Rightarrow \underline{\underline{A_{ISC} \leq \beta}}$$

Summary of emitter follower


$$Z_{in} \approx \beta R_E \quad (\text{high})$$

$$Z_{out} \approx R_E \quad (\text{low})$$

$$A_{voc} \approx 1 \quad (\text{low})$$

$$A_{ISC} \leq \beta \quad (\text{high})$$

Note on resistance transformation

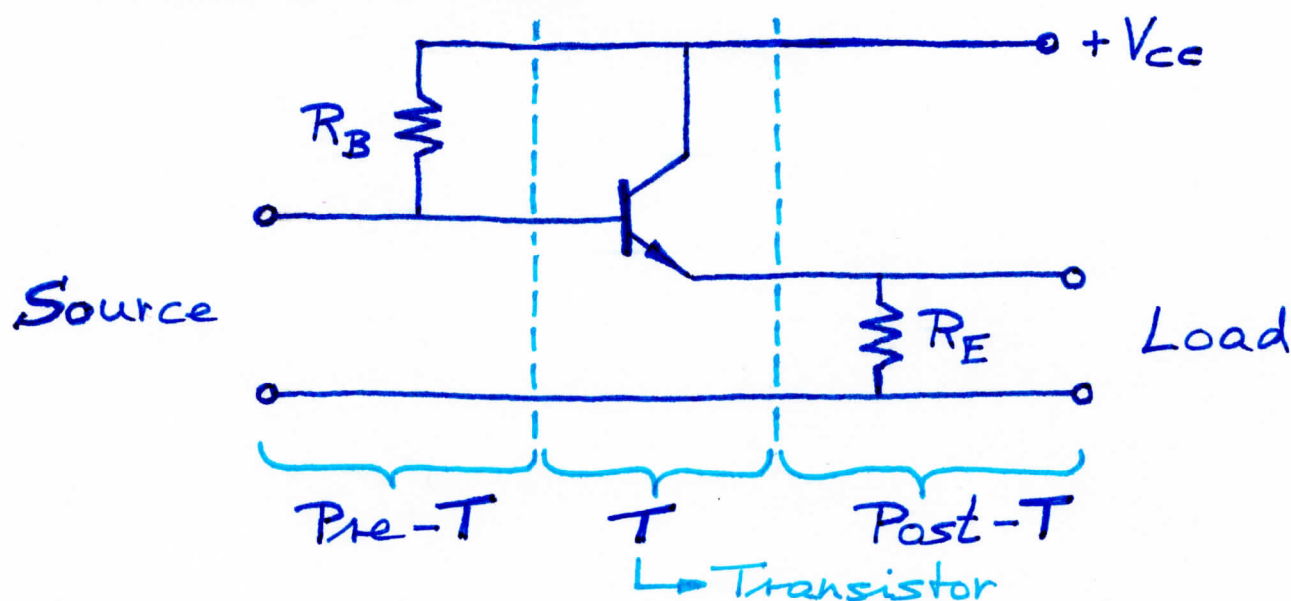

Note: When applying a signal i_B to the input side, the current through R_E is $(\beta+1)i_B$. Accordingly, the voltage drop across R_E is $i_B(\beta+1)R_E$, so that the resistance appears to be $(\beta+1)R_E$

Note: When applying a signal i_E to the output side, the current through R_B is $\frac{i_E}{\beta+1}$. Accordingly, the voltage drop across R_B is $i_E \frac{1}{\beta+1} R_B$, so that the resistance appears to be $R_B/(\beta+1)$.