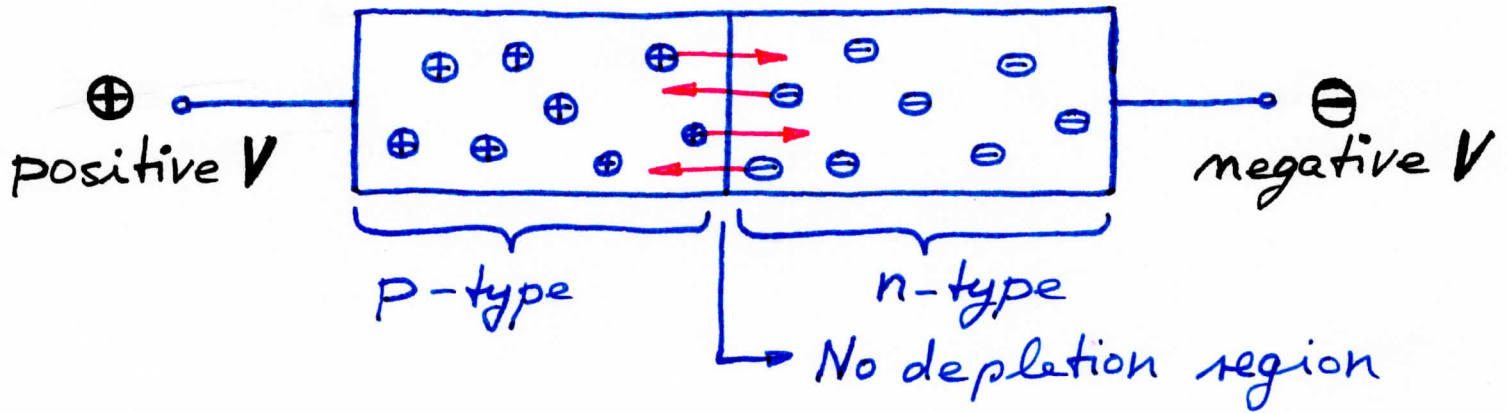



①

Zener diode

Recall: Diode forward direction



Recall: Diode reverse direction

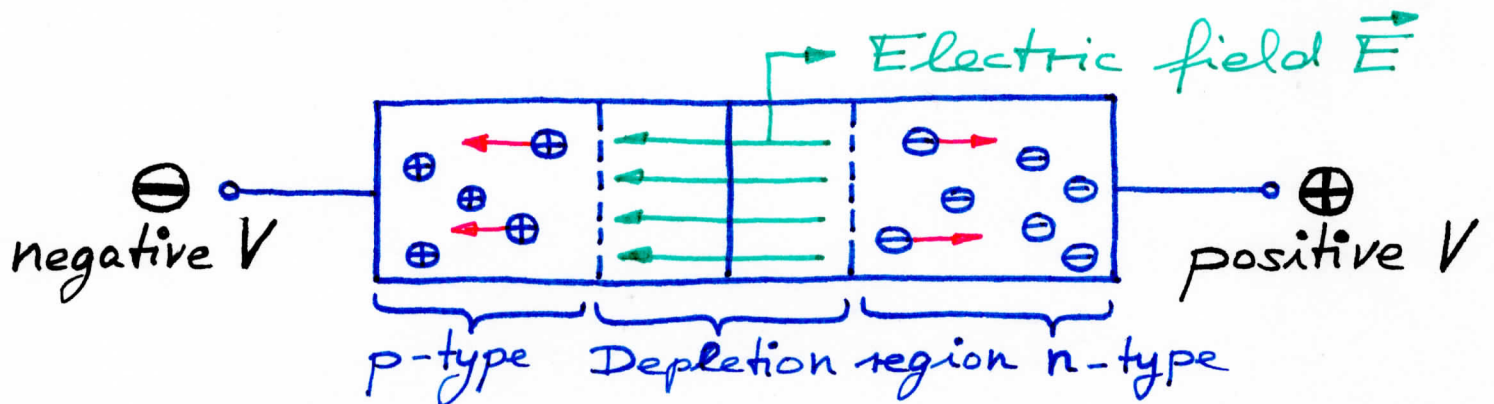


If $V_{\text{Diode}} = -10V$, where does the voltage drop across? \Rightarrow Depletion region \Rightarrow Why?

Every material has a breakdown electric field. For Si $\vec{E}_{\text{breakdown}} = 3 \times 10^5 \text{ V/cm}$
 $= 30 \text{ V}/\mu\text{m}$

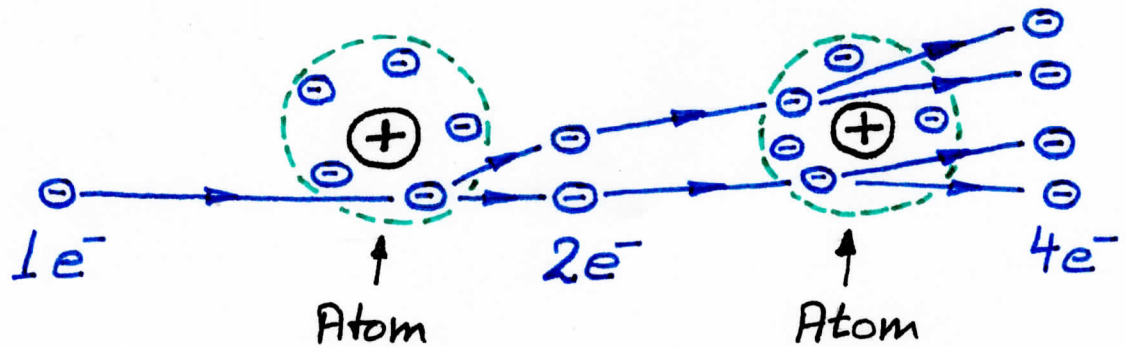(2)

What happens if $\vec{E} \geq \vec{E}_{\text{breakdown}}$?

\Rightarrow Impact ionization \Rightarrow Avalanche multiplication



\Rightarrow Current increases strongly for $\vec{E} \geq \vec{E}_{\text{breakdown}}$

\Rightarrow Is silicon material destroyed during breakdown?

\Rightarrow No! Only electronic processes, no structural changes.

Other technical field: Electrical breakdown in air. What happens? Have you seen such phenomenon?


Zener diode: The width of the depletion region can be tuned by doping:

$$W_D = \sqrt{\frac{2\epsilon}{e} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) V_{bi}}$$


\rightarrow Equation from Microelectronics course.

③
⇒ We can tune W_D , so that breakdown occurs at a desired voltage $V = V_{\text{breakdown}} = V_{\text{Zener}} = V_Z$

IV characteristic:

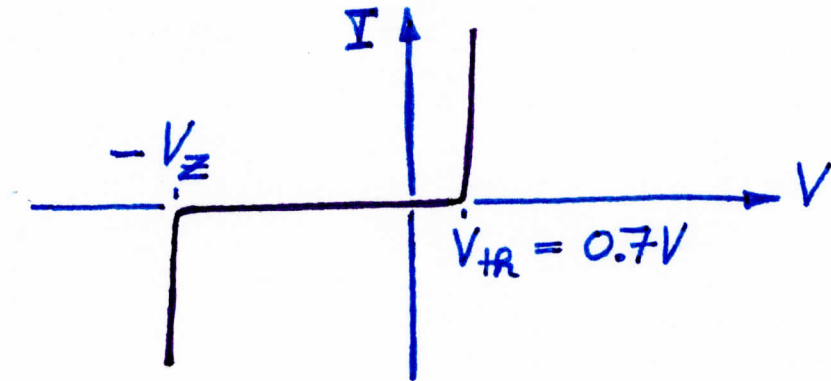

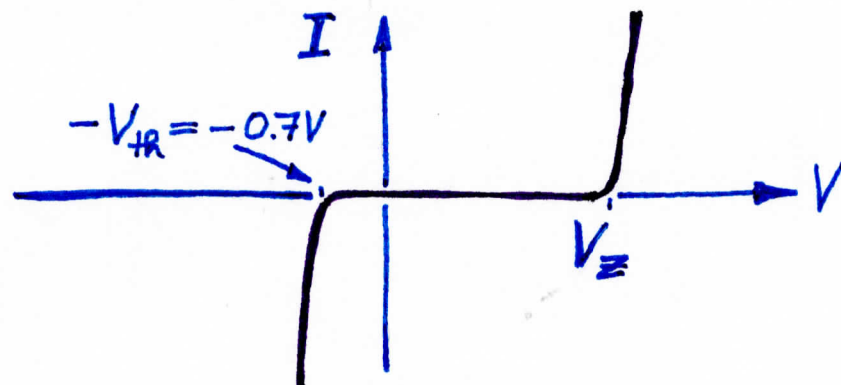
We typically operate Zener diode in reverse direction



Circuit symbol



Why this circuit symbol  ?

V_Z can be 5V, 10V, 18V...

$$V < V_Z \Rightarrow r_{\text{Zener}} = \frac{dV}{dI} \approx \infty$$

$$V \geq V_Z \Rightarrow r_{\text{Zener}} = \frac{dV}{dI} \approx 0$$

IV characteristic (quantitative)


$$I \approx I_0 e^{(V-V_Z)/V_t}$$

↳ regular diode

turn-on not included

↳ Can be smaller than 26 mV, so turn-on can be very abrupt.

Basic Zener diode circuit

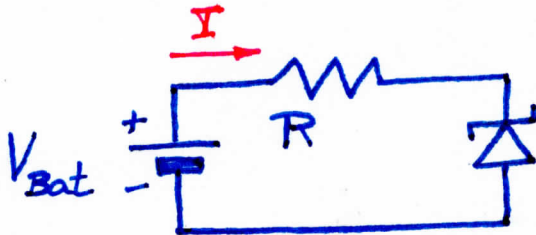


What is current I ? Similar to diode discussion, the equation based on **KVL** cannot be solved analytically.

⇒ We need alternative solutions.


① Graphical solution based on load line ⑤

KVL: $V_{\text{Bat}} = IR + V_Z(I)$
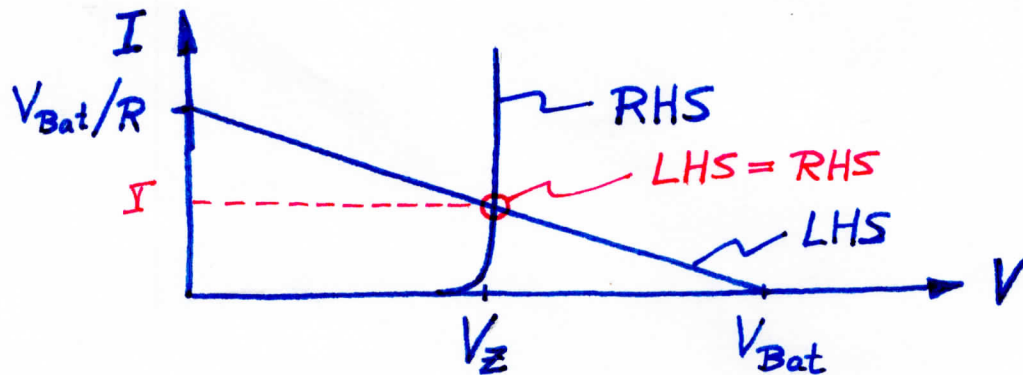
$$\Rightarrow \underbrace{V_{\text{Bat}} - IR}_{\text{LHS}} = \underbrace{V_Z(I)}_{\text{RHS}}$$



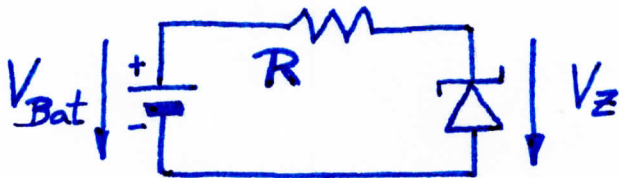② Approximate analytical solution by assuming $V_Z = \text{constant}$ (e.g. $V_Z = 10V$)



$$V_{\text{Bat}} = IR + V_Z$$
$$\Rightarrow I = \frac{V_{\text{Bat}} - V_Z}{R}$$

Example: $V_{\text{Bat}} = 10V$ $V_Z = 5V$ $R = 1k\Omega$

$$\Rightarrow I = \frac{V_{\text{Bat}} - V_Z}{R} = \frac{10V - 5V}{1k\Omega} = 5 \text{ mA}$$