

Hayden Fuller  
Intro to Electronics HW5

1. A bipolar junction transistors (BJT) is characterized by various quantities, for example the thermal voltage ( $V_t$ ), alpha ( $\alpha$ ), beta ( $\beta$ ), and the BE threshold voltage ( $V_{th}$  ).
  - a. Describe the meaning of each of these quantities and give (approximate) associated numerical values.

$V_t$       $kT/q$ , Voltage between p and n junctions due to temperature, 26mV  
 $\alpha$      CE current amplification,  $I_C = \alpha I_E$ ,  $\alpha < 1$ ,  $\alpha \approx 0.99$   
 $\beta$      CB current amplification  $I_C = \beta I_B$   $\beta > 1$ ,  $\beta \approx 100$   
 $V_{th}$     pn junction turn on voltage,  $V_{th} \approx 0.7V$

- b. Which one of these quantities is best suited to help us understand the physical operation of a BJT? Explain your answer.

$V_{th}$ , it helps us understand the pn junctions that the BJT is made of

- c. Which one of these quantities is most relevant in the practice of BJTs? Explain your answer.


$\beta$ , it is what is often how we amplify our signal

- d. Which of these quantities depends strongly on a geometrical dimension (thickness of the base layer) of the BJT? Explain your answer.

$\alpha$  and  $\beta$ , amplification increases with a thinner base layer

2. This problem relates to a bipolar junction transistor (BJT).

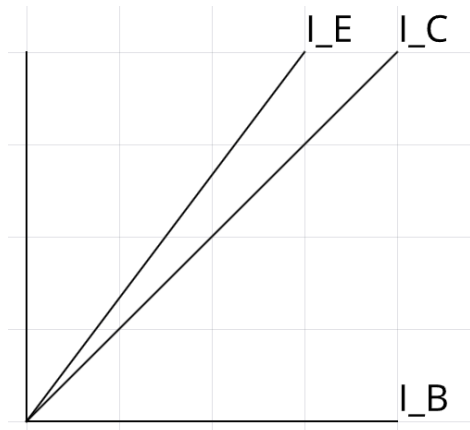
- a. Draw the  $I_E$ -versus- $I_B$  characteristic ( $I_E$  vertical axis (ordinate) and  $I_B$  horizontal axis (abscissa)) of a generic BJT. In the same diagram, draw the  $I_C$  -versus- $I_B$  characteristic of a BJT. Explain the characteristic.



$$I_C = \beta \cdot I_B$$


$$I_E = I_B + I_C = (\beta + 1) \cdot I_B$$

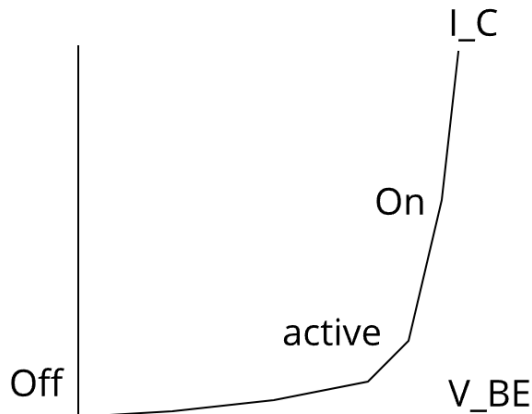- b. Draw the  $I_C$  -versus- $V_{BE}$  characteristic of a BJT. In the drawing, show the BJT's forward active region (ON region) and cutoff region (OFF region). Explain the characteristic.




There's a diode like characteristic where once  $V_{BE}$  hits a threshold,  $I_C$  is allowed to flow with little resistance.

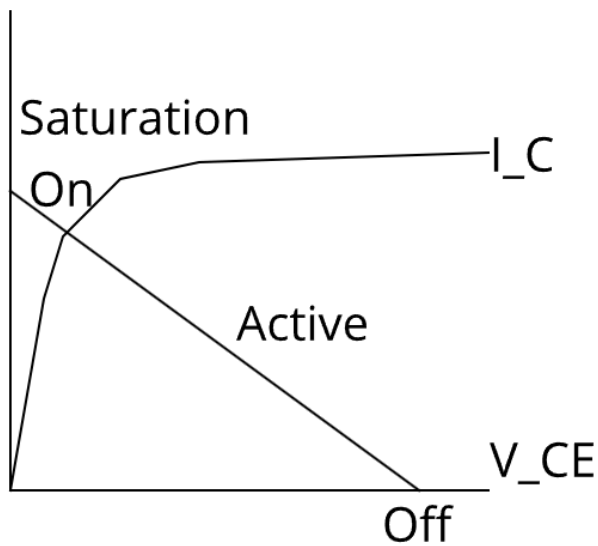- c. Draw the output characteristic  $I_C$  -versus- $V_{CE}$  of a BJT. In the drawing, show the BJT's forward active region (ON region), cutoff region (OFF region), and saturation region.




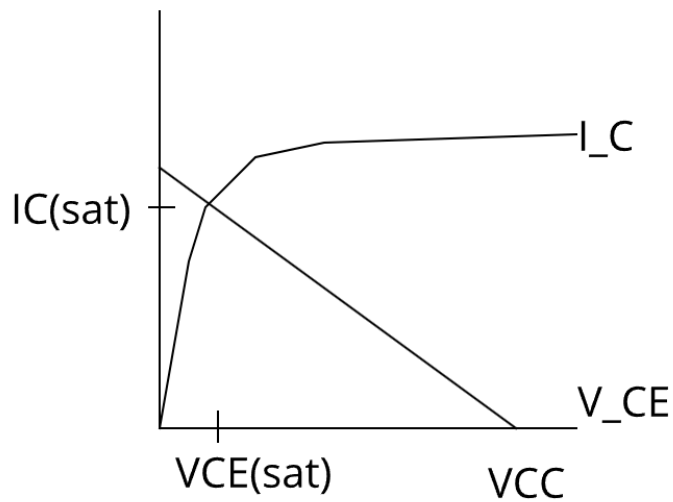- d. Sketch the  $I_C$  -versus- $V_{CE}$  characteristic and indicate the saturation voltage. A typical value of the saturation voltage is 0.2 V. Can you give a quantitative justification of that typical value?





I won't lie, I've spent over an hour researching an equation for  $V_{CE(sat)}$  or BJT knee voltage, I've found absolutely nothing. It's between 0.1V and 0.3V, often said to be 0.2V.

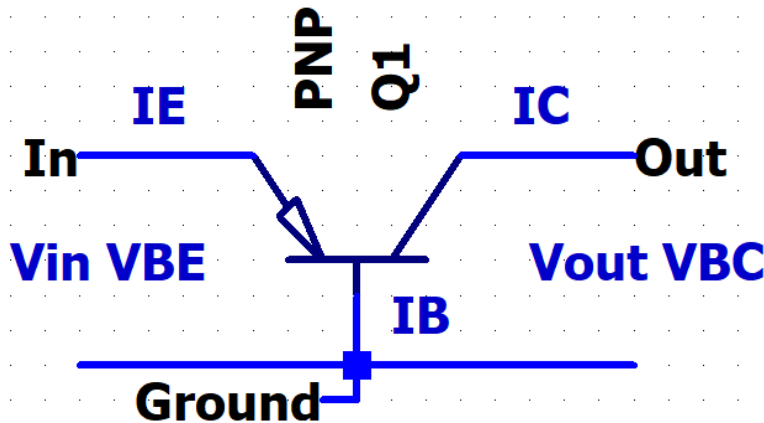3. This problem relates to a bipolar junction transistor (BJT) having a current amplification  $\alpha$  in common-base (common-B) configuration.
- Draw a common-B BJT amplifier circuit of a pnp BJT (without sources and without resistors). Label all input and output quantities.



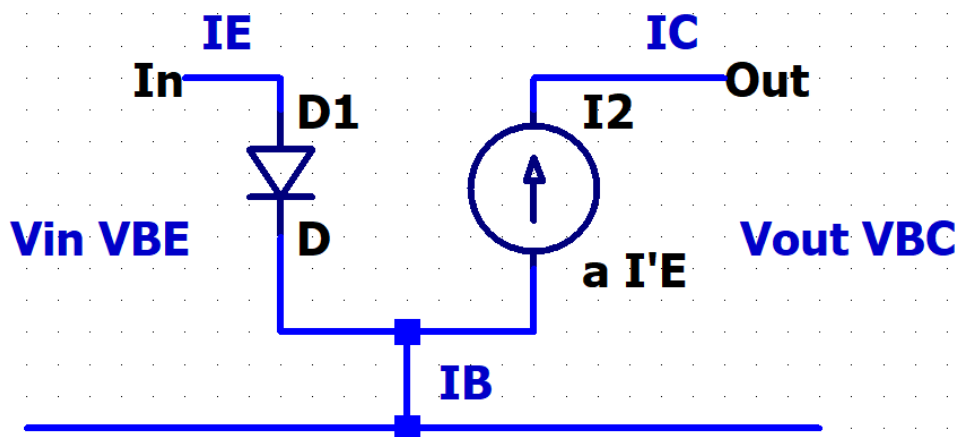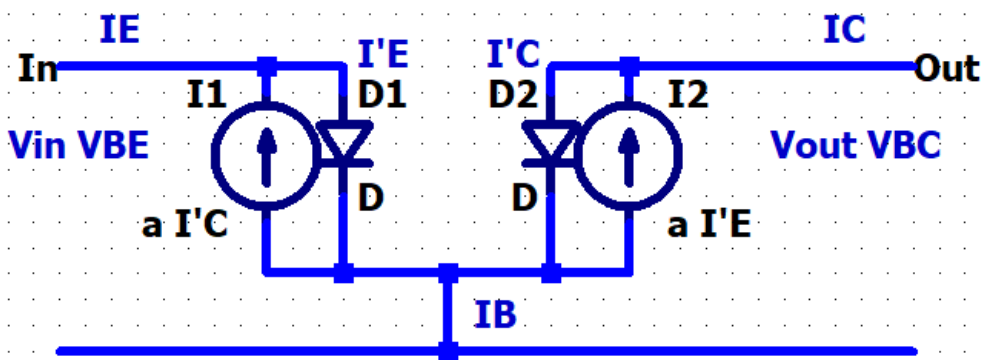- Draw the large-signal equivalent circuit of the transistor circuit (for the forward active operating regime); the equivalent circuit should not use the transistor circuit symbol. Define all quantities used in the equivalent circuit.




$V_{in}=V_{BE}$ , Voltage between the Base and Emitter

$V_{out}=V_{BE}$ , Voltage between Base and Collector

$a * I_E$ , output = amplification \* input

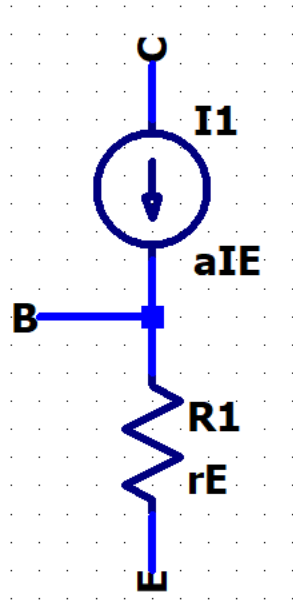- c. Draw the AC small-signal equivalent circuit (for the forward active operating regime). Define all quantities used in the circuit.



$$r_E = V_t / I_E$$

$$I_C = a * I_E$$

- d. Can you comment on the input resistance of the circuit? Do we generally prefer an amplifier having a small or large input resistance?
- Smaller input resistances are preferred because that gives a more ideal source and higher amplification.