

Differential mode and common mode

①

Differential mode amplification ("Diff")

$$V_{out} = A_{diff} (V_+ - V_-)$$

Common mode amplification ("CM")

$$V_{out} = A_{CM} \frac{1}{2} (V_+ + V_-)$$

Total amplification

$$V_{out} = \underbrace{A_{diff} (V_+ - V_-)}_{\text{Desired}} + \underbrace{A_{CM} \frac{1}{2} (V_+ + V_-)}_{\text{Undesired}}$$

Ideal op amp : $A_{CM} = 0$

Example:

Assume $V_+ = V_- = 1.0V$

$\Rightarrow V_{out}$ should be zero but it is not
due to A_{CM}

Why is $A_{CM} \neq 0$?

Common mode rejection ratio (CMRR)

$$CMRR = \frac{A_{diff}}{A_{CM}} \quad (\Rightarrow 20 \log \left(\frac{A_{diff}}{A_{CM}} \right) \text{ dB})$$

②
⇒ We need to check if A_{CM} has an influence. A_{CM} will falsify result.

Example:

Consider op amp with $A_{Diff} = 100$ and $A_{CM} = 1$

CMRR = ? (100 or 40 dB)

Assume $V_- = 5.0V$ $V_+ = 5.005V$

$V_{out} = ?$

$$V_{out} = A_{Diff} (V_+ - V_-) + A_{CM} \frac{1}{2} (V_+ + V_-) = 0.5V + 5V$$

⇒ Result is not acceptable.

Further considerations

⇒ Some circuits are more sensitive and some circuits are less sensitive to A_{CM} .

⇒ Further discussion

⇒ Textbook

⇒ Advanced courses