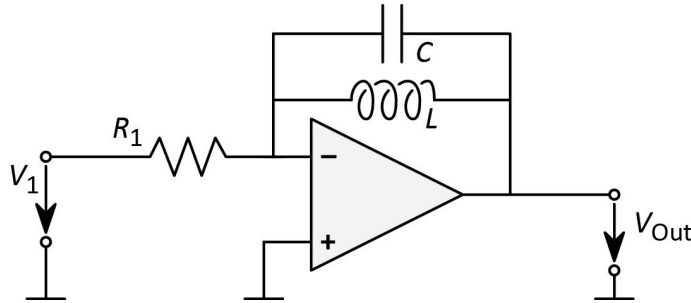


Homework 03

1. Consider an op amp circuit as shown in the figure below. The non-inverting input terminal is connected to ground. The feedback impedance is a capacitor C parallel to an inductor L .



- Calculate and sketch the impedance of the feedback impedance as a function of angular frequency ω .
 - What is the resonance angular frequency (ω_0) of the feedback circuit?
 - Calculate the transfer function $|H(\omega)| = |V_{out}/V_1|$. Sketch the transfer function.
 - Next, a resistor R_F is added in parallel to the L and C . Draw the feedback circuit. Calculate the impedance.
 - What is the feedback impedance at the resonance frequency ω_0 ? Sketch the impedance of the feedback impedance as a function of ω .
 - Assume that $R_1 = R_F$. What is the amplification of the amplifier at the resonance frequency?
2. An Op Amp has an open-circuit voltage gain of A_{VOC} (that can be adjusted by the feedback resistor) and a slew rate of $SR = 1 \text{ V}/\mu\text{s}$.
- Define the slew rate in your own words. Does the slew-rate limitation apply to the Op Amp's input or output voltage?
 - A triangular wave with period $1 \mu\text{s}$ and amplitude of 1 V is applied to the input of an Op Amp with an open-circuit voltage amplification of $A_{VOC} = 5$. Sketch the input waveform. Sketch the output waveform of the Op Amp. Is the output signal distorted?
 - For an Op Amp with $A_{VOC} = 1$, can you determine the maximum frequency of an input triangular wave with amplitude 100 mV that can be amplified with high fidelity?
 - For an Op Amp with $A_{VOC} = 10$, can you determine the maximum frequency of an input triangular wave with amplitude 100 mV that can be amplified with high fidelity?
 - For an Op Amp with $A_{VOC} = 100$, can you determine the maximum frequency of an input triangular wave with amplitude 100 mV that can be amplified with high fidelity?
 - Assume that the bandwidth of an Op Amp is the maximum frequency at which a signal is amplified with high fidelity. What is the mathematical product of (Op Amp gain) \times (Op Amp bandwidth) for the previous 3 questions? Is the mathematical product a constant?
 - Is the constancy of the gain-bandwidth product a direct consequence of the finite slew rate of an Op Amp?

3. Are the statements **True** or **False**? Justify your answer with one or two sentences.
- (a) A forward biased diode converts to heat the power of $V_f \times I$, where V_f is the forward voltage and I is the diode current.
 - (b) A reverse-biased pn-junction diode generally consumes no or very little power.