

ITE - Homework 8 - Solution

①

Problem 1

Current mirror

(a) $V_{BE1} = 0.7V$

Note that $V_{BE1} = V_{BE2} = V_{BE} = 0.7V$

$\Rightarrow I_{B1} = I_{B2} = I_B$ (T_1 and T_2 are identical)

Voltage drop across R_1

$$V_{R1} = \underline{V_{CC} - V_{BE}} = \underline{V_{CC} - 0.7V}$$

(b) Current through R_1

$$V_{R1} = I_{R1} R_1 = V_{CC} - V_{BE}$$

$$\Rightarrow \underline{I_{R1} = \frac{V_{CC} - V_{BE}}{R_1}}$$

$$\begin{aligned} I_{E1} &= I_{C1} + I_{B1} = I_{C1} + I_B = \beta I_B + I_B \\ &= (\beta + 1) I_B \end{aligned}$$

$$\begin{aligned} I_{R1} &= I_{C1} + I_{B1} + I_{B2} = I_{C1} + 2I_B \\ &= \beta I_B + 2I_B = (\beta + 2) I_B \end{aligned}$$

Eliminating I_B from the two eqns. above yields

(2)

$$I_{E1} = (\beta + 1) I_B = (\beta + 1) \frac{I_{R1}}{\beta + 2}$$

$$= \underline{\underline{I_{R1} \frac{\beta + 1}{\beta + 2} \approx I_{R1}}}$$

$$(c) \quad I_{B1} = \frac{I_{E1}}{\beta + 1} = \frac{I_{R1} \frac{\beta + 1}{\beta + 2}}{\beta + 1} = \underline{\underline{\frac{I_{R1}}{\beta + 2}}} \approx \underline{\underline{\frac{I_{R1}}{\beta}}}$$

$$I_{C1} = I_{B1} \beta = \frac{I_{R1}}{\beta + 2} \beta = \underline{\underline{I_{R1} \frac{\beta}{\beta + 2}}} \approx \underline{\underline{I_{R1}}}$$

(d) V_{B1} and V_{B2} are the same

T_1 and T_2 are identical transistors

$$\Rightarrow I_{B1} = I_{B2} = I_B$$

$$\Rightarrow I_{E1} = I_{E2}$$

$$\Rightarrow I_{C1} = I_{C2}$$

(e) Current through load = I_{C2}

$$I_{C2} = \beta I_B = I_{C1} = \underline{\underline{I_{R1} \frac{\beta}{\beta + 2}}} \approx \underline{\underline{I_{R1}}}$$

$\downarrow = I_{Load}$

$$\Rightarrow I_{Load} \approx I_{R1}$$

(f) Current I_{R1} is "mirrored" to load

$$\Rightarrow \underline{\underline{I_{Load} \approx I_{R1}}}$$

(3)

(g) Yes, Z_{Load} can be zero. The eqns. derived above are valid for $Z_{Load} = 0$.

(h) No, Z_{Load} cannot be ∞ . No I_{C2} current would flow and the current I_{R1} would not be "mirrored".

(i) Maximum voltage across Z_{Load} must be less than $(V_{CC} - \underbrace{V_{CE,sat}}_{0.2V})$

$$\Rightarrow Z_{Load} I_{R1} < V_{CC} - V_{CE,sat}$$

$$\Rightarrow \underline{\underline{Z_{Load} < \frac{1}{I_{R1}} (V_{CC} - \underbrace{V_{CE,sat}}_{0.2V})}}$$


(j) $V_{CC} = 10V$ $\beta = 100$ $R_1 = 500\Omega$

$$\Rightarrow I_{R1} = \frac{10V - 0.7V}{500\Omega} = \frac{9.3V}{500\Omega} = \underline{\underline{18.6mA}}$$

$$I_{C1} = I_{R1} \frac{\beta}{\beta + 2} = 18.6mA \frac{100}{100 + 2} = \underline{\underline{18.2mA}}$$


$$I_{C2} = I_{C1} = I_{Load} = \underline{\underline{18.2mA}}$$

(k)

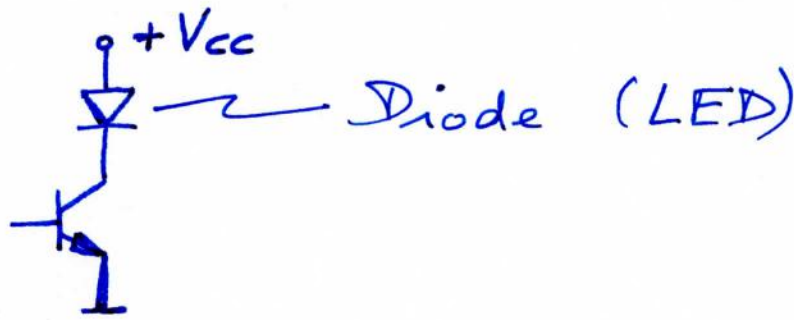


$$I_{\text{Diode}} = I_{C2} = I_{C1} = \underline{\underline{18.2 \text{ mA}}}$$

(l)

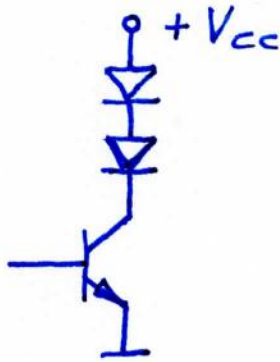

$$I_{\text{Diode 1}} = I_{\text{Diode 2}} = I_{C1} = \underline{\underline{18.2 \text{ mA}}}$$

(m)

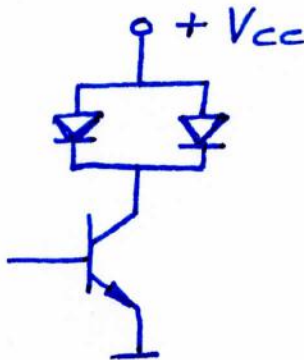

Due to symmetry, each diode carries $I_{C1}/2$

$$= 18.2 \text{ mA} / 2 = \underline{\underline{9.1 \text{ mA}}}$$

(n) We appreciate that the current through the load is 18.2 mA, independent of the type of load.

Problem 2

SRAM cell

4R

2T


↳ 4 resistors ↳ 2 transistors

$$V_{CC} = 5V$$


$$\beta = 50$$

$$V_{CE,sat} = 0.2V$$

(a) Circuit diagram

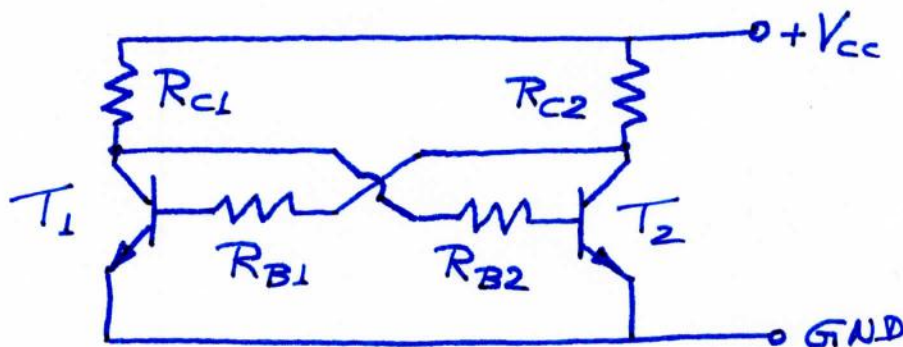

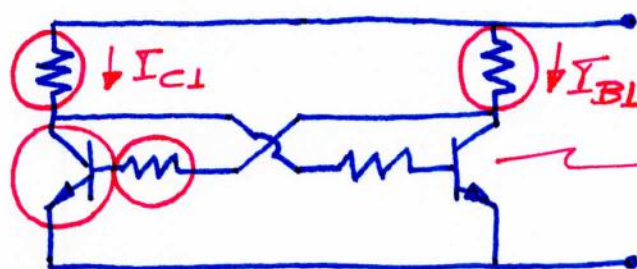(b) Let us choose the state where T_1 is conductive $\Rightarrow T_1$ is ON $\Rightarrow V_{CE1,sat} = 0.2V$
 $\Rightarrow T_2 = \text{OFF}$. Which elements consume power?



Circled elements consume power

$$(c) R_{C1} \Rightarrow P = I_{C1}^2 R_{C1}$$

$$R_{B1} \Rightarrow P = \left(\frac{I_{C1}}{\beta}\right)^2 R_{B1} \Rightarrow \text{small}$$

$$R_{C2} \Rightarrow P = \left(\frac{I_{C1}}{\beta}\right)^2 R_{C2} \Rightarrow \text{small}$$

$$T_1 \Rightarrow P = V_{CE,sat} \times I_C \Rightarrow \text{small}$$

↳ 0.2V

Total power

$$P = P_{RC1} + P_{RB1} + P_{RC2} + P_{T1}$$

↳ Dominant summand

(d) R_{C1} is greatest consumer of power.

$$P \approx 1 \mu W = I_{C1}^2 R_{C1}$$

$$P \approx 1 \mu W = \frac{V_{RC1}^2}{R_{C1}} = \frac{(V_{CC} - V_{CE,sat})^2}{R_{C1}}$$

$$= \frac{(5V - 0.2V)^2}{R_{C1}}$$

$$\text{Solve for } R_{C1}: R_{C1} = \frac{(5V - 0.2V)^2}{1 \mu W} = \frac{(4.8V)^2}{1 \mu W}$$

$$= \underline{\underline{23.0 \text{ M}\Omega}}$$

$$\Rightarrow I_{C1} = \frac{1 \mu W}{4.8V} = \underline{\underline{0.208 \mu A}}$$

$$\Rightarrow I_{B1} = \frac{0.208 \mu A}{\beta} = \underline{\underline{4 \text{ nA}}} \quad (\text{very small})$$

How to choose R_{B1} ? The choice is not critical as long as it keeps T_1 in the ON state. We therefore choose $R_{B1} = 23 \text{ M}\Omega$ (same value as R_{C1}). Other choices are acceptable.

$$\Rightarrow R_{C1} = R_{C2} = \underline{\underline{23 \text{ M}\Omega}}$$

$$R_{B1} = R_{B2} = \underline{\underline{23 \text{ M}\Omega}}$$

(e) $1 \text{ Gbit} = 10^9 \text{ bit}$

SRAM memory would consume

$$10^9 \times 1 \mu\text{W} = \underline{\underline{1 \text{ kW}}}$$

Power is too high. Circuit consumes too much power for large-scale memory.