

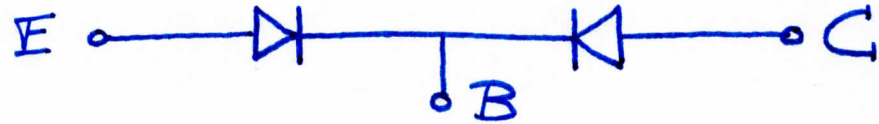


BJT equivalent circuit

BJT (pnp)

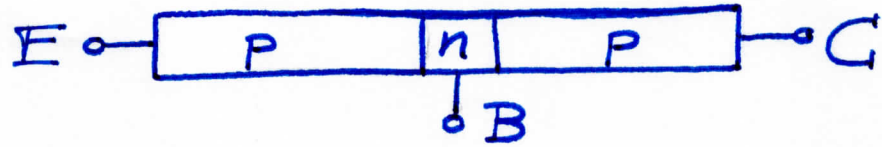


Equivalent circuit

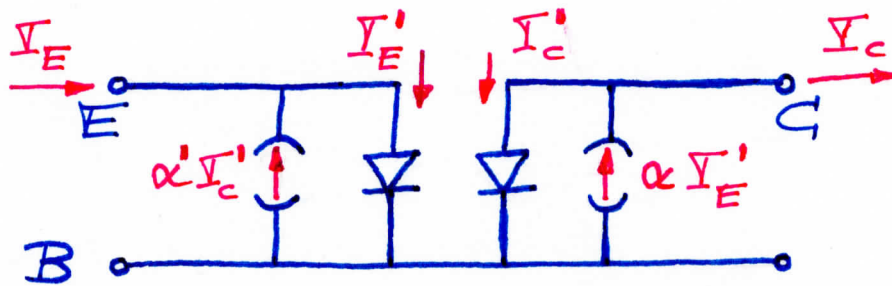

Typically $\alpha' < \alpha$ (Why?)

Note $\alpha I_E = I_C = \beta I_B$


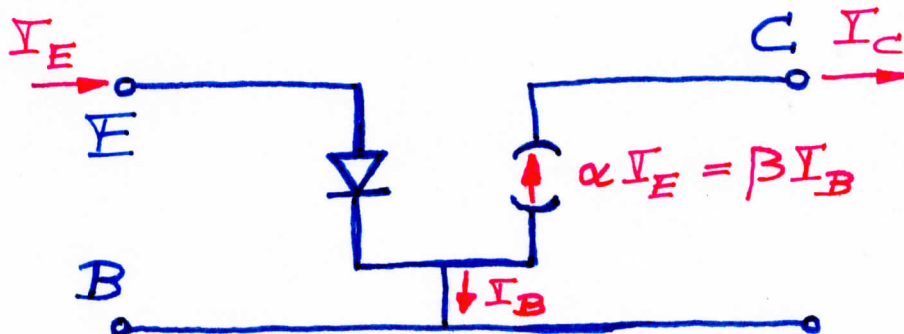
Active regime \Rightarrow CB diode is reverse biased
 \Rightarrow CB diode = OC (open circuit)





(2)

Redrawing equivalent circuit for pnp and npn transistor


pnp

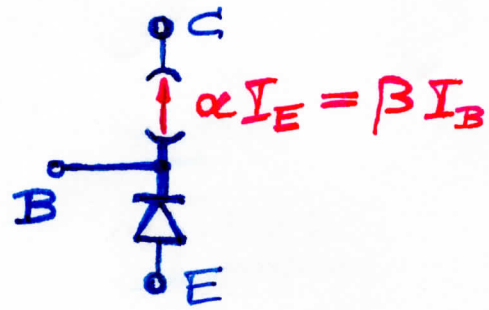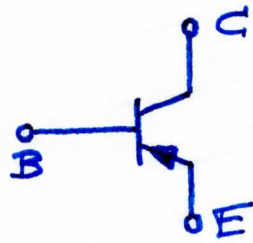

nnp

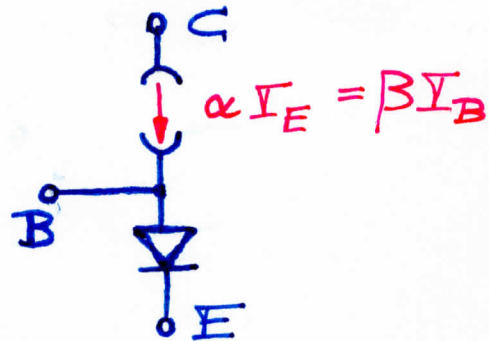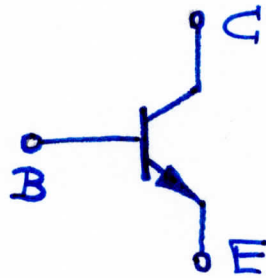

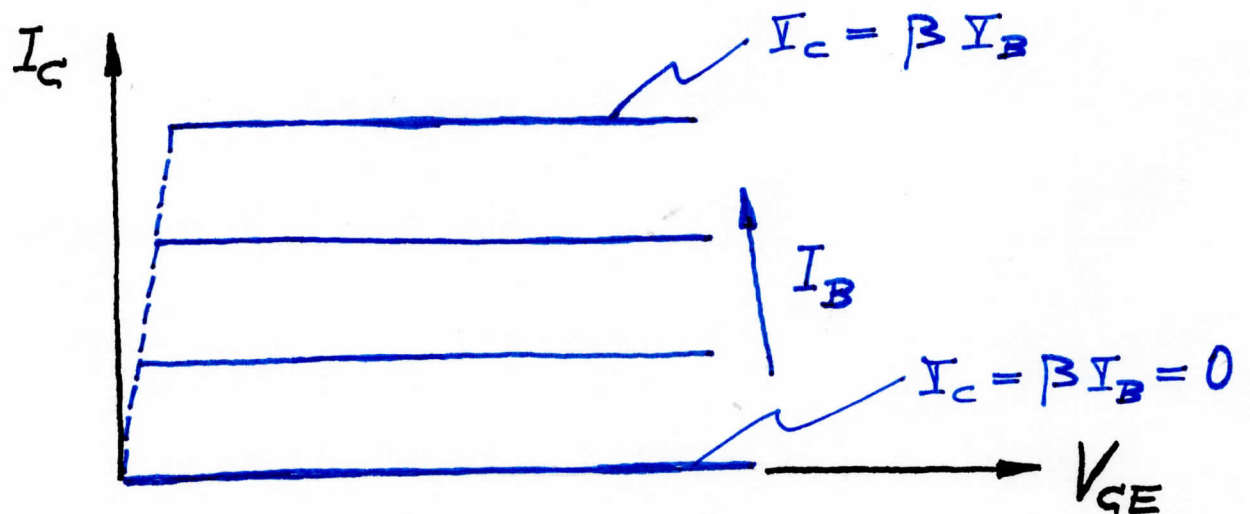Output characteristic based on equivalent circuit



Output characteristic \Rightarrow Current source \Rightarrow

Current I_C for any voltage V_{CE} .

What is output resistance of transistor?