

1c $I_S = I_D$

1d The FET "turns on" allowing current through.

2a Essentially zero.

2b The input power of a FET is $V_{gate} \cdot I_{gate}$.

However, BJTs consume more power since I_S for FETs is essentially 0.


2c It takes less energy to run FETs, saving power is good.

2.2 Both have three terminals, can be turned ON or OFF, and can amplify signals.

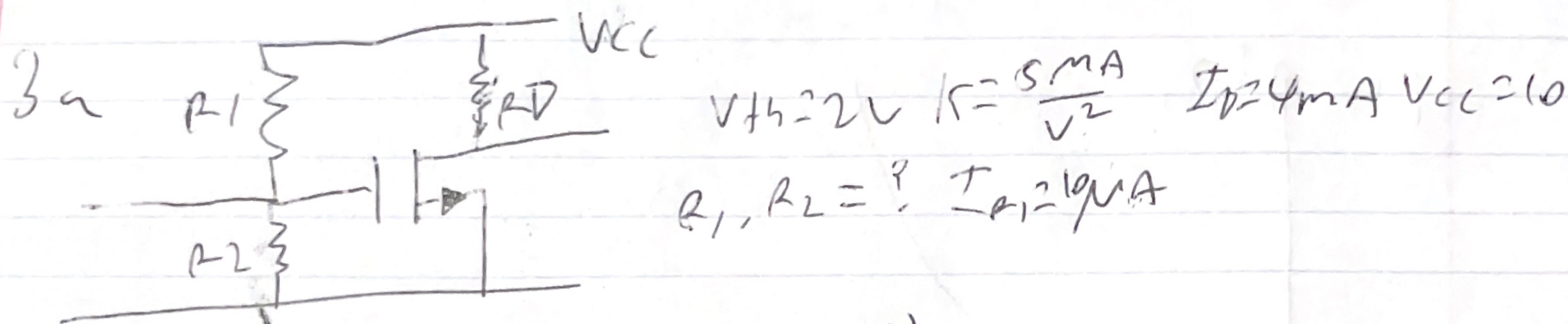2.3 BJTs require an input current, FETs don't.

BJTs have high power consumption, FETs don't.

BJTs have low input impedance, FETs have high input impedance.



1.4 n-channel FET biasing circuit.

$$4mA = \frac{1}{2} \cdot 5mA \left(\frac{R_2}{R_1 + R_2} \cdot 10 - 2 \right)^2 \quad I_{R1} = 10\mu A$$

No input current so I_{R2} must equal I_{R1} too

$$10V = I_{R1} \cdot R_1 + I_{R2} \cdot R_2 = 10 = 10\mu A (R_1 + R_2)$$

$$R_1 + R_2 = 1000000 \quad \frac{R_2}{R_1 + R_2} = 0.325$$

$$R_1 = 325K$$


$$R_2 = 675K$$

3b $V_{DS} = V_{CC} - I_D R_D$ $V_{DS} = 10 - R_D \cdot 4mA$

$\frac{V_{CC}}{2}$ roughly Q point so $V_{DS} = \frac{V_{CC}}{2}$

$$5 = 10 - R_D \cdot 4mA$$

$$R_D = 1250\Omega$$

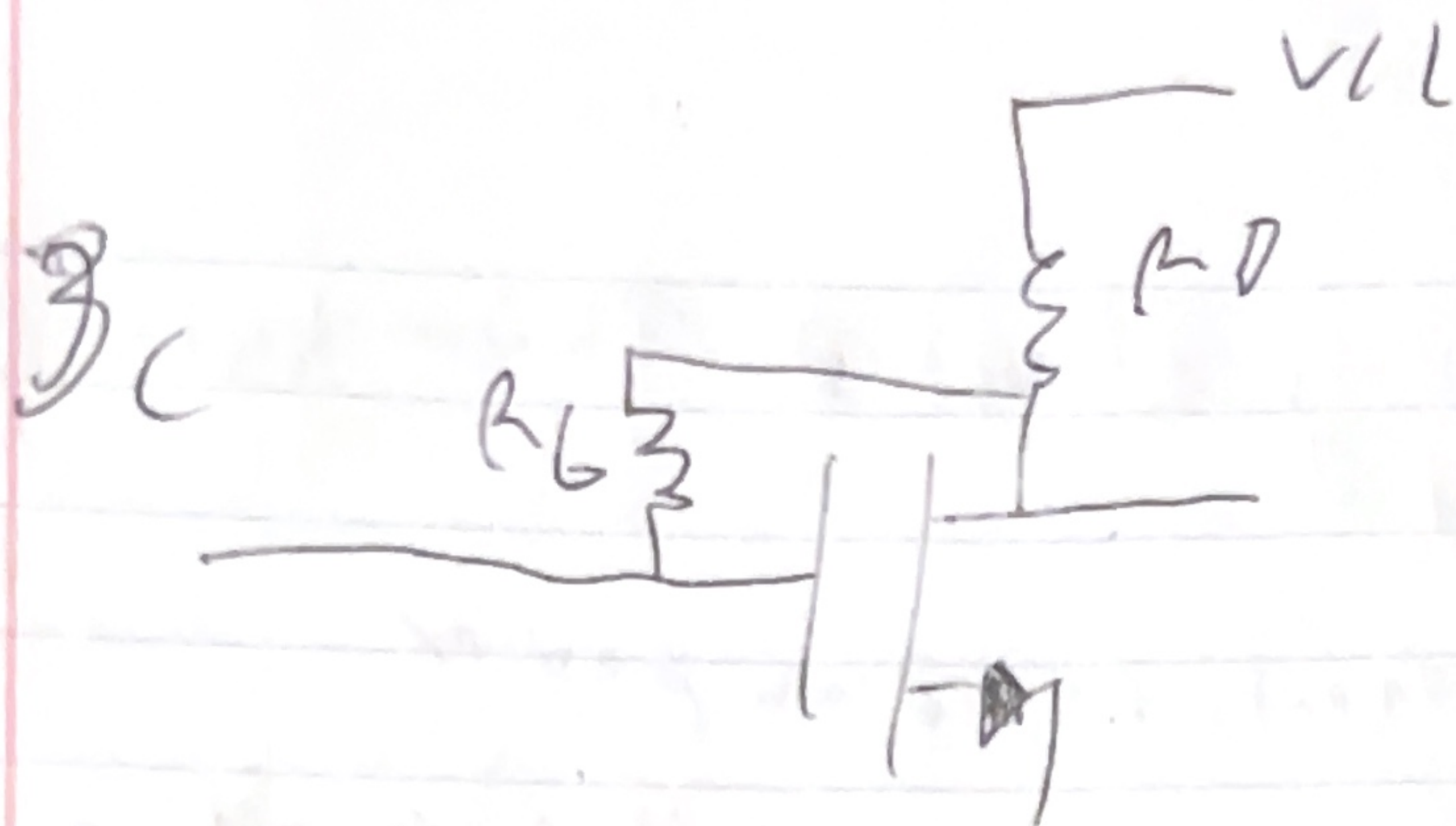

$$V_{th} = 2V \quad V_{CC} = 10V$$

$$k = 5 \text{ mA/V}^2$$

$$I_D = 4 \text{ mA}$$

$$R_D, R_G = ?$$

this is also a FET biasing circuit.

$$V_{GS} = V_{CC} - I_D R_D$$

$$I_D = \frac{1}{2} k (V_{GS} - V_{th})^2$$

$V_{GS} = V_{DS}$ No voltage drop over R_G . Also no current through R_G . $R_G = ?$

$$I_D = \frac{1}{2} k (V_{GS}^2 - V_{GS} V_{th} + V_{th}^2)$$

$$\frac{V_{GS} - V_{CC}}{-I_D} = R_D$$

$$V_{GS} - V_{CC} = -R_D I_D$$

$$V_{GS} = V_{CC} - I_D R_D$$

$$-\frac{1}{2} k (V_{GS}^2 - V_{GS} V_{th} + V_{th}^2)$$

$$\frac{V_{CC} - I_D R_D - V_{CC}}{-I_D} = R_D$$

unknown

$$-\frac{1}{2} k (V_{CC} - I_D R_D)^2 - (V_{CC} - I_D R_D) V_{th} + V_{th}^2$$

$$R_G = R_D = R$$

3) R_2 and R_1 act as a voltage divider, letting a variable amount of voltage reach the FET based on their resistances.

3) V_{GS} and V_{DS} are equal which allows for easier calculations to be done.

4a False. Gate current is almost 0. This makes the input power very small, but not 0

4b True. Other components can draw power

4c False $I_s \geq I_D$ due to the control circuit of a FET.