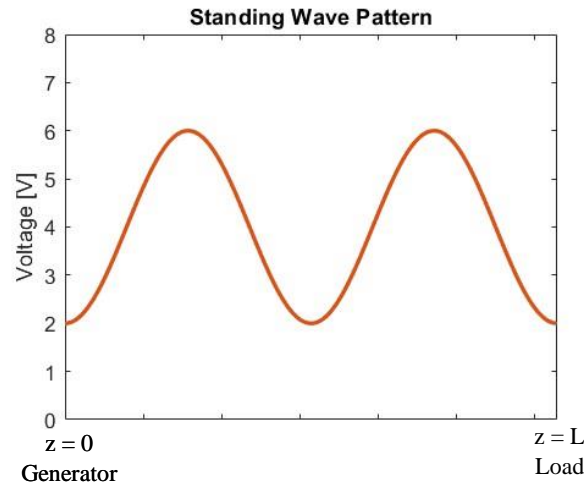


Homework 2

Due: 11:59pm January 31st

1. Standing Wave Patterns on Lossless Transmission Lines


All parts of Problem 1 refer to the standing wave pattern below. The characteristic impedance of the transmission line is $Z_0 = 60\Omega$.




- Simply by inspecting the features of the standing wave pattern, determine if Z_L is purely real (resistive), purely imaginary (reactive), or a combination of both. How can you tell?
- Again, simply by inspecting features of the standing wave pattern, determine the sign of Γ_L , the reflection coefficient at the load.
- Calculate the standing wave ratio (SWR) for this standing wave pattern.
- Keeping in mind your result from b), calculate Γ_L , the reflection coefficient at the load.
- Calculate Z_L , the load impedance.
- What is the value of V_0^+ , the amplitude of the incident voltage wave?

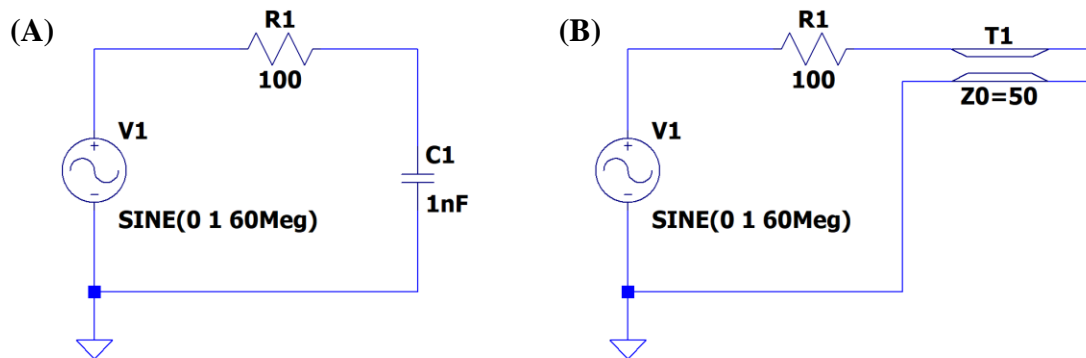2. Input Impedance of Lossless Transmission Lines

- What is the wavelength of a 60 MHz voltage signal on a transmission line with a characteristic impedance $Z_0 = 75\Omega$ and velocity factor $v_f = 0.7$?
- You are tasked with replacing the capacitor in circuit A below with a short-circuited transmission line, resulting in circuit B.




- Using the same transmission line properties as in (a) and a source voltage frequency of 60MHz, what is the minimum length of the transmission line that would present the same input impedance to the generator circuit as the capacitor in circuit A?
- Suppose instead that you were given an open-circuited transmission line with which to replace the capacitor in circuit A of part (b). What is the minimum length of the transmission line that would present the same input impedance as the capacitor in circuit A?
- Given the circuit below, what is the minimum length of the transmission line $T1$ (same properties as in part a) that can be used to prevent reflection from occurring between the generator resistance $R1$ and the input of the transmission line? Will reflections still occur on the transmission line at the load?

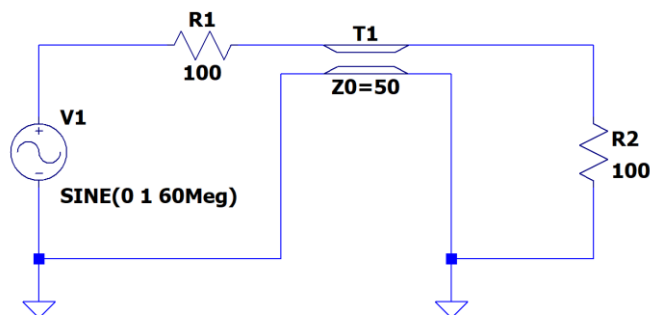

- If $R2$ in the circuit above is instead 150Ω and transmission line $T1$ is a quarter wave transformer, what characteristic impedance Z_0 of $T1$ will ensure that no reflection occurs between the generator impedance $R1$ and the transmission line? Will reflections still occur on the transmission line at the load?
- If the frequency of the source voltage in the circuit you designed in part f is changed, will the quarter wave transformer still ensure that no reflections occur between $R1$ and the input to the transmission line? Why or why not?

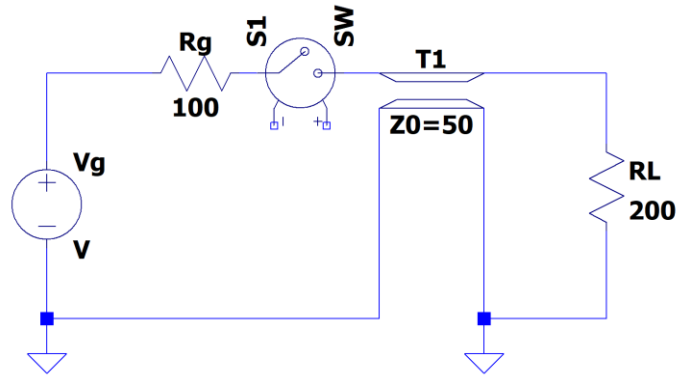3. Transient Signals on Lossless Transmission Lines

All parts of Problem 3 refer to the circuit below. At time $t=0$, the switch $S1$ closes and a 3V DC source supplies voltage to the circuit. The transmission line has a characteristic impedance of $Z_0 = 50\Omega$.



- What is the amplitude of the forward-traveling voltage wave V_0^+ that enters the transmission line at $t = 0$?
- What are Γ_L , the reflection coefficient at the load, and Γ_g , the reflection coefficient at the input to the transmission line?
- Draw a bounce diagram for the circuit above from $t = 0$ to $t = 4T$, where T is the time delay on the transmission line. Be sure to label both the time axis and distance axis, voltage wave amplitudes and directions of travel, and the voltages at the load and generator during reflection.
- Sketch the voltage amplitude at the load vs. time for the timespan $t = 0$ to $t = 4T$. Be sure to label voltage amplitudes and critical times.
- Assuming enough time has elapsed, what are the steady-state voltage and current on the line? Does this agree with the result you expect from DC circuit theory?
- If you were to replace RL with a capacitor instead, what would you expect the steady-state voltage and current to be? Why?

4. Conceptual Questions

- a) The standing wave ratio can be found using the absolute value of reflection coefficient at the load. Why is the absolute value used? Why doesn't the sign of the reflection coefficient matter?
- b) Suppose that in Problem 1, the frequency of the sinusoidal input voltage signal were increased by 50%. Would this change the standing wave pattern? If so, describe how.
- c) Why don't standing wave patterns ever have values below 0?
- d) In principle, a standing wave pattern could exist for a non-sinusoidal input signal as well. Choose some non-sinusoidal input signal, length of line, Z_0 , and load impedance and draw the standing wave pattern that will result from it. Show calculations to justify the correctness of your drawing.