

## Laboratory 8 (1 day): Digital circuits

### Material covered:

- This laboratory has **one session** allocated for completion:
  - Mandatory: Pre-Lab Exercise 1 and Exercise 1. Optional: Exercise 2
- Transistor-resistor logic
- Transistor-transistor logic
- Digital circuits

### Propagation delay:

The **propagation delay** is the time it takes for the digital output to change after the digital input changes. It is defined as the time difference between when the input is halfway between  $V_{In,Low}$  and  $V_{In,High}$  to when the output is halfway between  $V_{Out,Low}$  and  $V_{Out,High}$ . The two times are defined as  $t_{p,LH}$  (output transitions from LO to HI) and  $t_{p,HL}$  (output transitions from HI to LO). An example for an inverter circuit is shown below. The **red line is the input** and the **green line is the output**.


 


Figure 1: Inverter timing diagram (input and output)


## Pre-Lab Exercise 1

 

**Figure 2: CMOS inverter (M1 = N-channel FET; M2 = P-channel FET)**

1. Simulate the circuit shown above. Note, the PMOS transistor needs to be ‘mirrored vertically’ so that the source is on the ‘top’. You can change the orientation of a component by right clicking on it. Set the simulation to a DC voltage sweep for  $0 < V_{in} < 5$  V.

*Estimate the output high voltage, the output low voltage, the low noise margin and the high noise margin.*

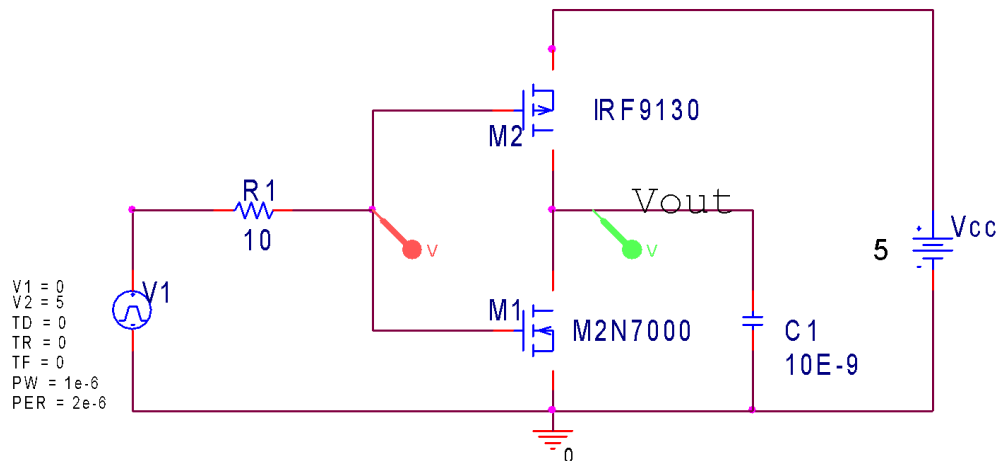

**Figure 3: CMOS inverter (M1 = N-channel FET; M2 = P-channel FET)**

2. Add an input side resistance and an output side capacitance. Set  $V_{in}$  to a pulse stream with a 50% duty cycle and a 2  $\mu$ s period.

*Estimate the propagation delay as the output switches from LO to HI and from HI to LO.*

## Exercise 1: CMOS inverter

 


Figure 4: CMOS inverter

1. Build the circuit above using the IRF9120 PMOS and 2N7000 NMOS transistors. Set the input signal to a 10 Hz sawtooth triangle wave, oscillating between 0 V and 5 V.
2. Use the x-y channel to plot the voltage transfer function,  $V_{out}$  versus  $V_{in}$ .

*Determine the LO and HI output voltages,  $V_{Out,Low}$  and  $V_{Out,High}$ .*

*Estimate the high and low noise margins.*

3. Add a 10 nF capacitor at the load ( $V_{out}$ ) and change the input signal to a square wave. You will need to 'zoom in' to see the  $t_{PLH}$  and  $t_{PHL}$ . In order to do that, you need to set the horizontal axis to ~100 ns/div. The triggering must also be set correctly. Set the triggering source to the oscilloscope channel connected to the input and the triggering level to ~2 V. You can change the condition ("Cond.") to Rising and Falling, giving you the two different propagation delays.

*Estimate the propagation delays.*

$V_{OL}$ (Output voltage – Low)	
$V_{OH}$ (Output voltage – High)	
$NM_{Low}$ (Noise margin – Low)	
$NM_{High}$ (Noise margin – High)	
$t_{PLH}$ (Propagation delay – L-to-H)	
$t_{PHL}$ (Propagation delay – H-to-L)	

## Exercise 2: Logic circuits

Design an OR or an AND gate (you choose). You may use any type of circuit design. Build the circuit and verify the truth table.

*Estimate the propagation delays for the gate. You only need to change one input such that the output toggles.*