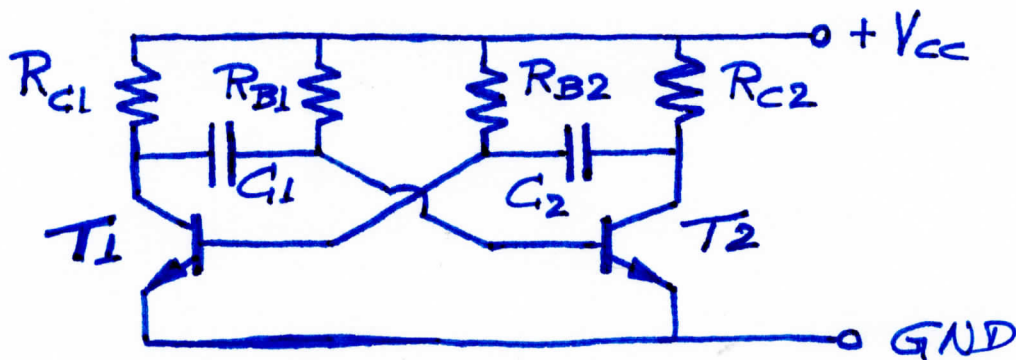


Iconic circuit: Astable flip-flop circuit ①

Circuit with two states, none stable, always switching between states. \Rightarrow Astable flip-flop (non-stable flip-flop).

Historical name: Multivibrator circuit. \Rightarrow Oscillation at a range of frequencies and containing harmonics. Also: First product of the **HP** Company.



General observation: $R_B \gg R_C$

If C charges through $R_C \Rightarrow$ Fast charge

If C charges through $R_B \Rightarrow$ Slow charge

Transistors are either ON or OFF

\hookrightarrow Saturation

(2)

How does the circuit work ?

\Rightarrow Assume $T_1 = \text{ON}$ $T_2 = \text{OFF}$

$\Rightarrow C_2$ charged to $(V_{CC} - 0.7V)$.

C_1 charges (slowly) through $R_{B1} \Rightarrow$ Then T_2 's V_{BE} becomes $> 0.7V \Rightarrow T_2 = \text{ON}$

$\Rightarrow T_2$'s $V_C \approx 0 \Rightarrow C_2$ (which is charged) causes T_1 's V_{BE} to be negative $\Rightarrow T_1 = \text{OFF}$


$\Rightarrow C_1$ charged to $(V_{CC} - 0.7V)$.

C_2 charges (slowly) through $R_{B2} \Rightarrow$ Then T_1 's V_{BE} becomes $> 0.7V \Rightarrow T_1 = \text{ON}$

$\Rightarrow T_1$'s $V_C \approx 0 \Rightarrow C_1$ (which is charged) causes T_2 's V_{BE} to be negative $\Rightarrow T_2 = \text{OFF}$

... this completes one full cycle of oscillation

Circuit output:

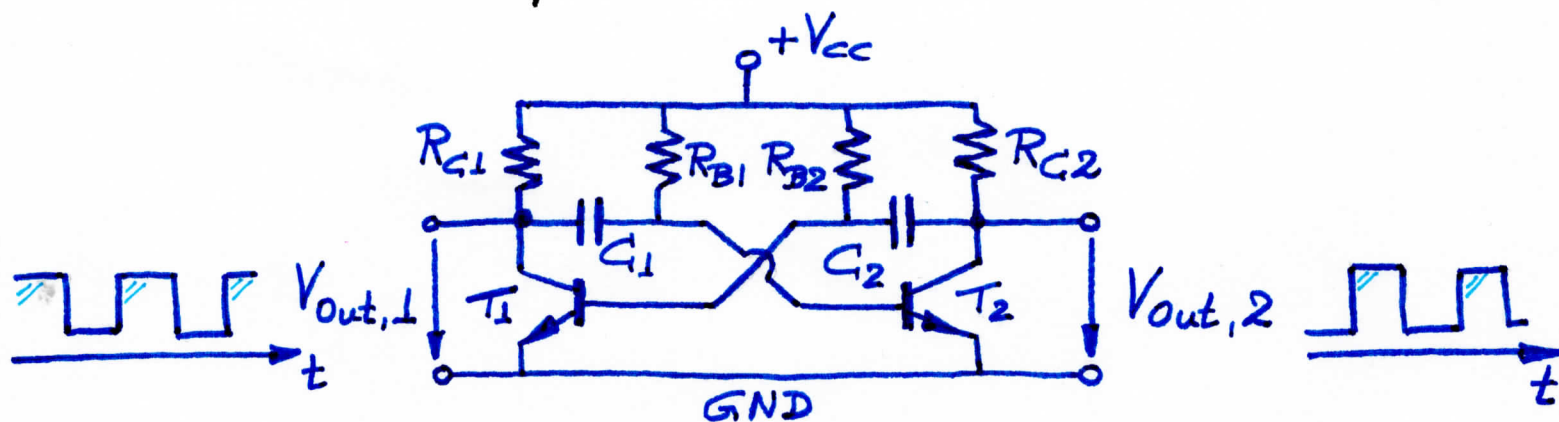

$V_{out,1}$ and $V_{out,2}$ are complementary.

Switching time for symmetric circuit

$$\tau = RC = R_{B1}C_1 = R_{B2}C_2$$

Period of oscillation

$$T = 2\tau = 2 R_B C$$


$\begin{matrix} \text{---} \rightarrow C_1 = C_2 \\ \text{---} \rightarrow R_{B1} = R_{B2} \end{matrix}$

Applications for astable flip-flop circuit:

- * Audio signals and sounds
- * Signal generator
- * Frequency synthesizer

How can we change the frequency ?

* Change of R_{B1} and R_{B2}

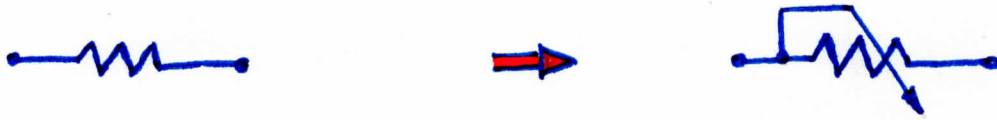

* Change of C_1 and C_2

