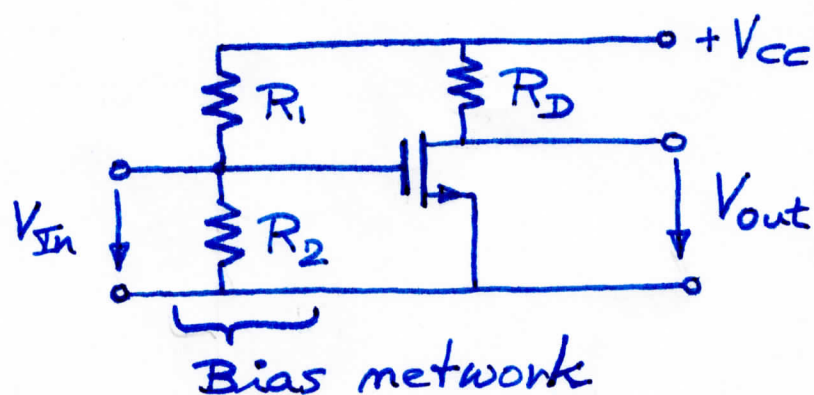



# FET Amplifiers

## Common Source amplifier



Q: Explain name: Common Source amplifier.

## Common Drain amplifier

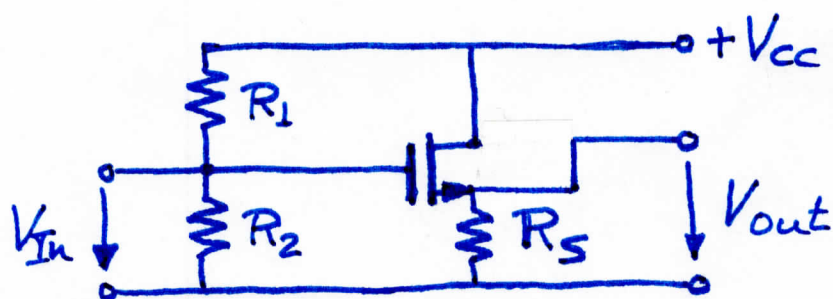


Q: Is D common?  $\Rightarrow$  Yes

Q: Why is D common?

Alternative name: Source follower

# Common Gate amplifier

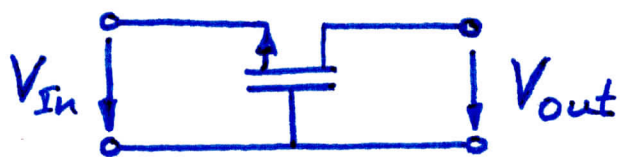


Q: Current amplification ?  $\Rightarrow 1.0$

Q: Why ?

$\Rightarrow$  Current follower (alternative name)

# Common Source amplifier

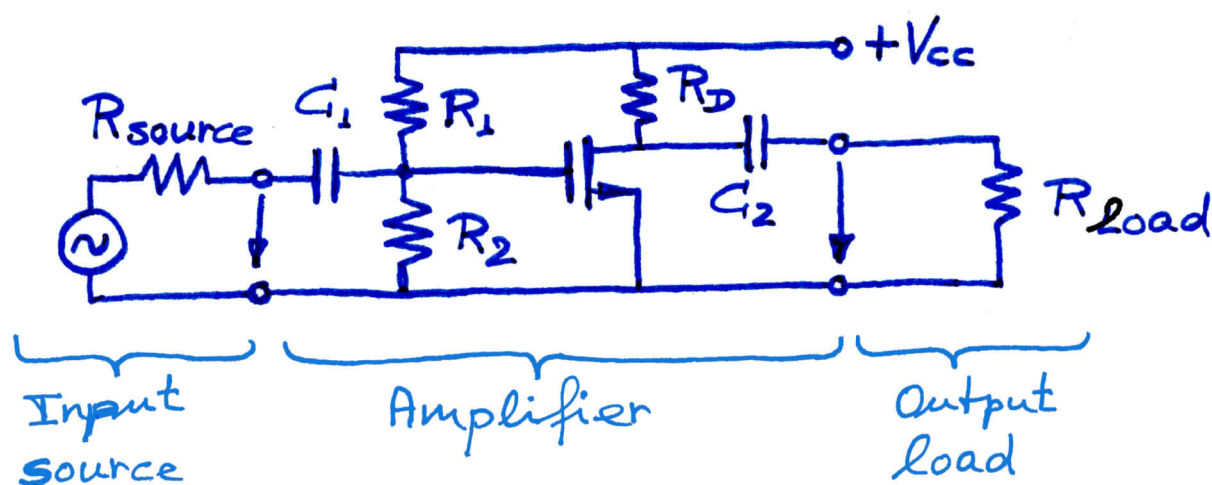


Q: For analysis of amplifier, will  $R_{source}$  and  $R_{load}$  matter?  $\Rightarrow$  No. Why?

Q: How are  $C_1$  &  $C_2$  dimensioned?  $\Rightarrow C_1 \rightarrow \infty$   
 $C_2 \rightarrow \infty$  so that  $Z_C = \frac{1}{j\omega C} = 0$

Q: How are  $C_1$  &  $C_2$  dimensioned in practice?  
 $\Rightarrow$  Dimension  $C_1$  &  $C_2$  to let pass all relevant frequencies.

# Small-signal equivalent circuit

④

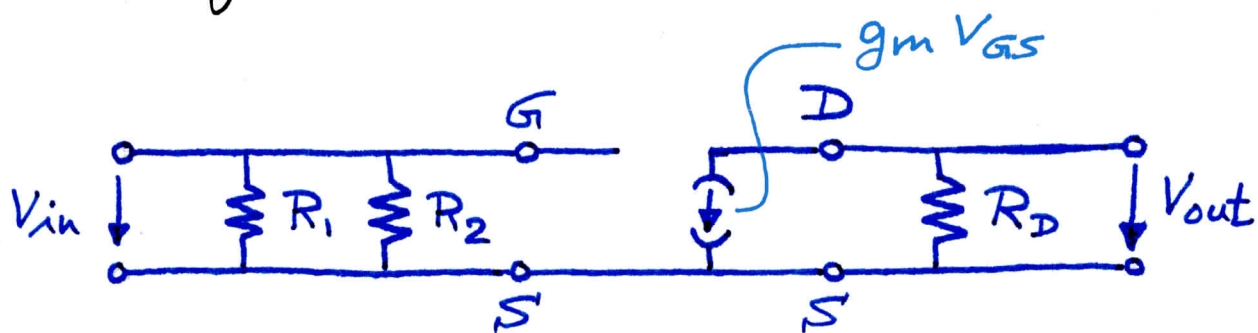

Input impedance

$$Z_{in} = \underline{R_1 \parallel R_2}$$

Output impedance

$$Z_{out} = \underline{R_D} \quad (\text{or } R_D \parallel R_{DS} \text{ if } R_{DS} \neq \infty)$$

Current amplification

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{g_m V_{GS}}{V_{GS} / (R_1 \parallel R_2)} = \underline{g_m (R_1 \parallel R_2)}$$

Note:  $R_1$  &  $R_2$  can be very large. Why?


$\Rightarrow A_{ISC}$  can be very large.

Voltage amplification


$$A_{VOC} = \frac{V_{out}}{V_{in}} = \frac{g_m V_{GS} R_D}{V_{in}} = \underline{g_m R_D}$$

$\xrightarrow{V_{GS}}$

Let us add a source resistance

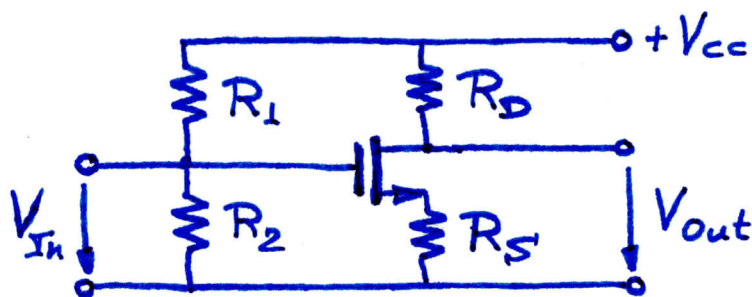

Small signal equivalent circuit

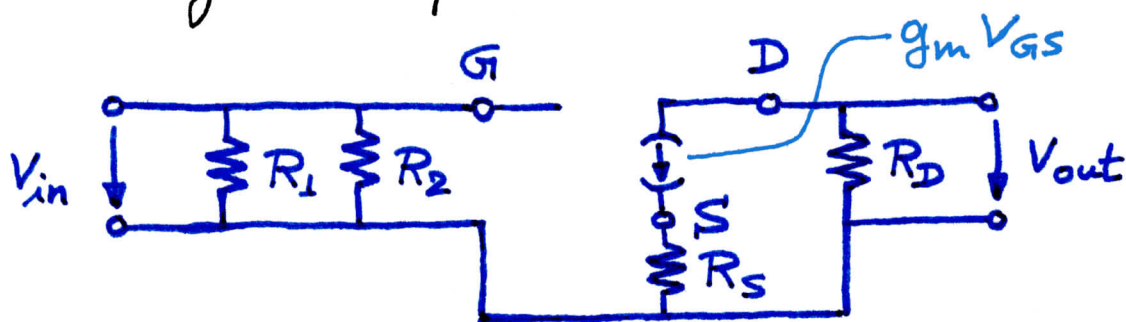

$$Z_{in} = \underline{R_1 \parallel R_2}$$

$$Z_{out} = \underline{R_D}$$

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{g_m V_{GS}}{V_{in} / (R_1 \parallel R_2)} = \frac{g_m (R_1 \parallel R_2)}{1 + g_m R_S}$$

$\hookrightarrow V_{GS} + R_S g_m V_{GS}$


$\Rightarrow R_S$  reduces amplification

$$A_{VOC} = \frac{V_{out}}{V_{in}} = \frac{g_m \underline{V_{GS}} R_D}{\underline{V_{GS}} + R_S g_m \underline{V_{GS}}} = \underline{\underline{\frac{g_m R_D}{1 + g_m R_S}}}$$

$\Rightarrow R_S$  reduces amplification


# Common Drain amplifier

(also called Source Follower)

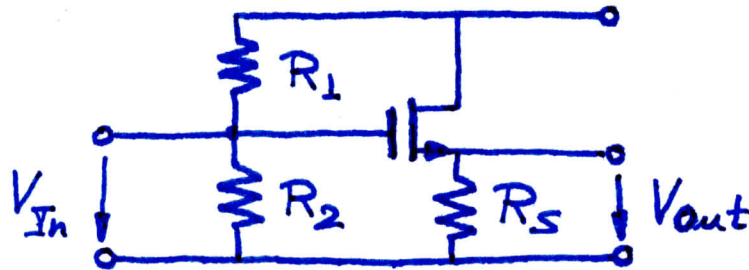

Q: Why is this called a common-Drain amplifier ?

Small signal equivalent circuit

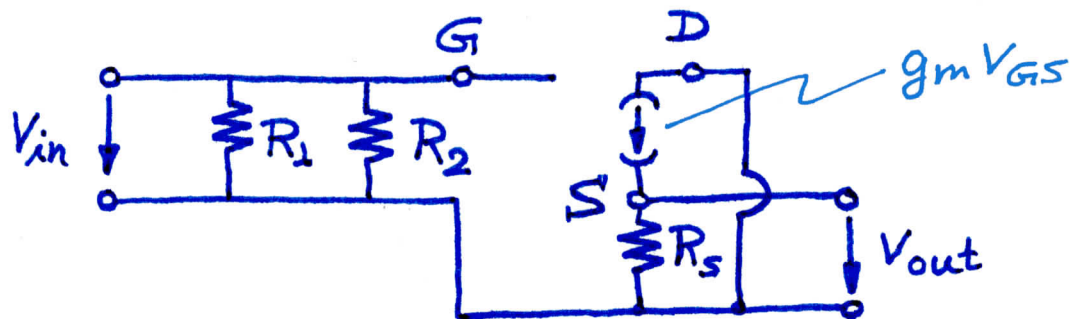

$$Z_{in} = \underline{\underline{R_1 \parallel R_2}}$$

$$Z_{out} = \underline{\underline{R_S}}$$



(7)

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{g_m V_{GS}}{V_{in} / (R_1 \parallel R_2)} = \underline{\underline{g_m (R_1 \parallel R_2)}}$$

$\downarrow$   
 $V_{GS}$

$\Rightarrow$  For high values of  $R_1$  &  $R_2 \Rightarrow A_{ISC} \gg 1$

$$A_{VOC} = \frac{V_{out}}{V_{in}} = \frac{g_m V_{GS} R_s}{V_{GS} + g_m V_{GS} R_s} = \underline{\underline{\frac{g_m R_s}{1 + g_m R_s}}}$$

$\downarrow$   
 $V_{GS} + g_m V_{GS} R_s$

$\Rightarrow$  For large  $R_s \Rightarrow A_{VOC} \approx 1.0$

$\Rightarrow$  S voltage follows G voltage

$\Rightarrow$  Alternative name: Source follower