

①


# DC - biasing of FET

⇒ DC biasing circuit

⇒ Note:  $I_G = 0$  Why?  $I_D = I_S$  Why?

⇒ Mostly resistors. Some capacitors. Why?

## ① FET biasing circuit

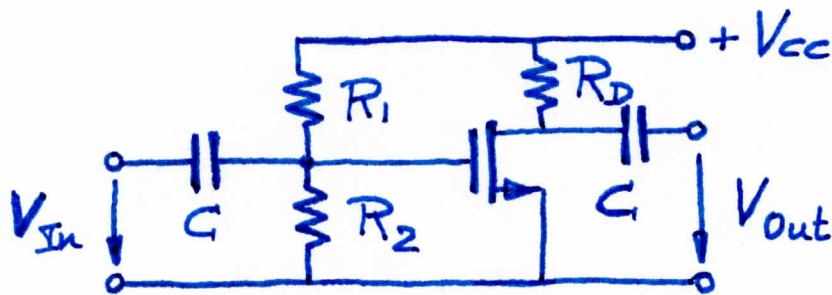

Assume that we know all circuit elements.

Quiescent-point determination

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{CC} \quad (\text{Voltage divider}) \quad (1)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_{th})^2 \quad (\text{Saturation}) \quad (2)$$

⇒ 2 eqns. 2 unknowns ( $I_D$  and  $V_{GS}$ )

⇒ Eqn. (1) yields  $V_{GS}$ . Eqn. 2 yields  $I_D$

⇒  $V_{DS} = V_{CC} - R_D I_D$  ⇒ Verify that FET is in saturation. Saturation:  $V_{DS} \geq V_{GS} - V_{th}$

⇒ We solved the DC biasing problem ②

---

Numerical example:  $V_{CC} = 10V$   $R_1 = 800k\Omega$   
 $R_2 = 200k\Omega$   $R_D = 500\Omega$   $k = 10 \frac{mA}{V^2}$   $V_{th} = 1V$

Determine Q-point of FET

$$\Rightarrow V_{GS} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{200k\Omega}{1000k\Omega} 10V = 2.0V$$

$$\begin{aligned}\Rightarrow I_D &= \frac{1}{2} k (V_{GS} - V_{th})^2 = \frac{1}{2} 10 \frac{mA}{V^2} (2V - 1V)^2 \\ &= \frac{1}{2} 10 \frac{mA}{V^2} (1V)^2 = 5.0 mA\end{aligned}$$


$$\begin{aligned}\Rightarrow V_{DS} &= V_{CC} - R_D I_D = 10V - 500\Omega \times 5mA \\ &= 10V - 2.5V = 7.5V\end{aligned}$$

$$\Rightarrow \underbrace{V_{DS}}_{7.5V} \geq \underbrace{V_{GS} - V_{th}}_{1V} \Rightarrow \text{Yes} \Rightarrow \text{Saturation}$$

---

(3)

## ② FET biasing circuit

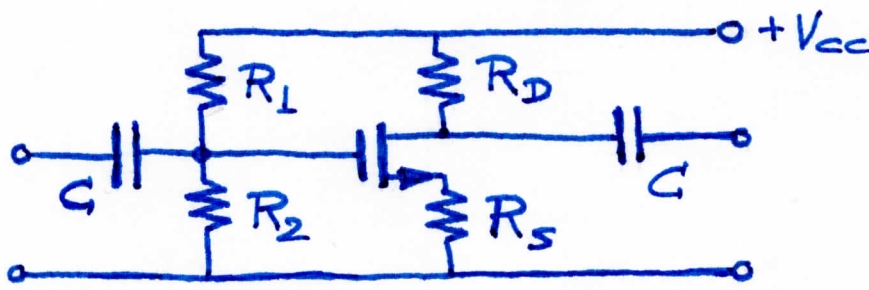

$$V_G = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_S = R_S I_D$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{CC} - R_S I_D \quad (1)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_{th})^2 \quad (\text{Saturation}) \quad (2)$$

$\Rightarrow$  2 eqns      2 unknowns      ( $V_{GS}$  and  $I_D$ )

Insert Eqn(2) into Eqn(1)  $\Rightarrow$

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{CC} - R_S \times \frac{1}{2} k (V_{GS} - V_{th})^2$$

$\Rightarrow$  1 eqn      1 unknown      ( $V_{GS}$ )

Rearrange eqn:

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{CC} - \frac{1}{2} k R_S (V_{GS}^2 - 2V_{GS} V_{th} + V_{th}^2)$$

$$\underbrace{\frac{1}{2} k R_S V_{GS}^2}_{ax^2} + \underbrace{(1 - k R_S V_{th}) V_{GS}}_{bx} + \underbrace{\frac{1}{2} k R_S V_{th}^2 - \frac{R_2}{R_1 + R_2} V_{CC}}_c = 0$$

... this is a quadratic eqn.

Recall:


Quadratic eqn.  $ax^2 + bx + c = 0$

Solution  $x_{1/2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

Q: Why does a quadratic eqn. have two solutions?

Q: Does it help writing the quadratic eqn as follows?
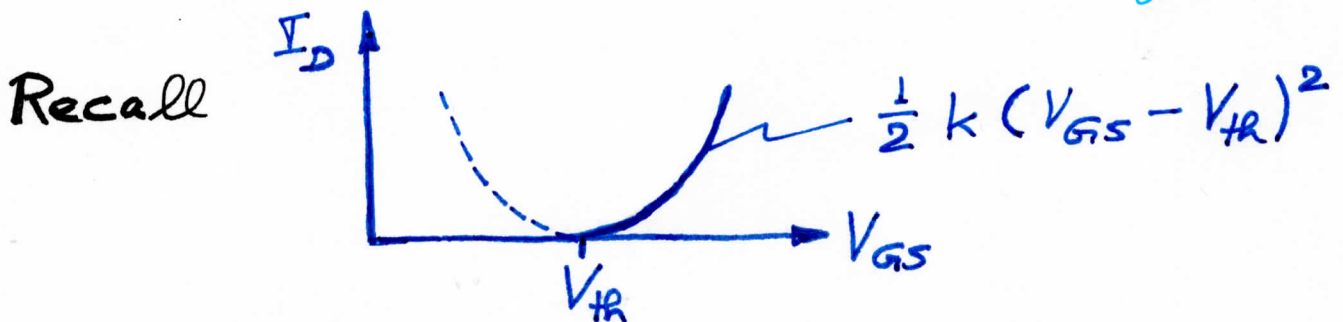
$$\underbrace{ax^2}_{\text{Parabola}} = \underbrace{-bx - c}_{\text{Straight line}}$$




For the "right" solution, it is  $V_{GS} > V_{TH}$

Note: It may be prudent to determine the numerical values of  $a$ ,  $b$ , and  $c$  and then solve the quadratic equation.



# Numerical example

⑤

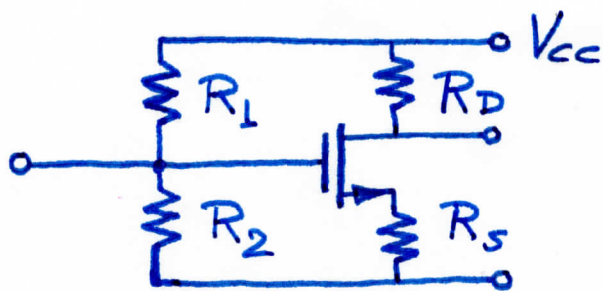

$$V_{CC} = 10V$$

$$R_1 = R_2 = 100 k\Omega$$

$$R_S = 100 \Omega \quad R_D = 400 \Omega$$

$$V_{th} = 2V$$

$$k = 5 mA/V^2$$

We use quadratic eqn derived above  $aV_{GS}^2 + bV_{GS} + c = 0$

$$a = \frac{1}{2} k R_S = \frac{1}{2} 5 \frac{mA}{V^2} 100 \Omega = 0.25 \frac{1}{V}$$

$$b = 1 - k R_S V_{th} = 1 - 5 \frac{mA}{V^2} 100 \Omega 2V = 1 - 1 = 0$$

$$c = \frac{1}{2} k R_S V_{th}^2 - \frac{R_2}{R_1 + R_2} V_{CC} = \frac{1}{2} 5 \frac{mA}{V^2} 100 \Omega 4V^2 - \frac{1}{2} 10V$$

$$= 1V - 5V = -4V$$

$$\Rightarrow \text{Quadratic eqn} \quad 0.25 \frac{1}{V} V_{GS}^2 - 4V = 0$$

$$\Rightarrow V_{GS}^2 = 16V^2 \Rightarrow \underline{V_{GS} = 4V}$$

$$\Rightarrow \underline{I_D} = \frac{1}{2} k (V_{GS} - V_{th})^2 = \frac{1}{2} 5 \frac{mA}{V^2} (2V)^2 = \underline{10mA}$$

$$\Rightarrow \underline{V_{DS}} = V_{CC} - R_D I_D - R_S I_D = 10V - 400 \Omega 10mA - 100 \Omega 10mA$$


$$= 10V - 4V - 1V = \underline{5V}$$

$$\underbrace{V_{DS}}_{5V} > \underbrace{V_{GS} - V_{th}}_{2V} \Rightarrow \text{FET is in saturation}$$

$\Rightarrow$  To conclude, we determined the Q-point

### ③ FET biasing circuit

⑥

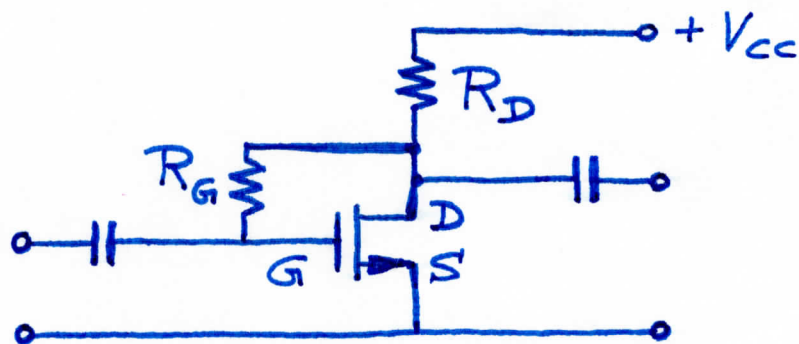

Q: What is the value of the current flowing through  $R_G$ ?  $\Rightarrow$  Zero  $\Rightarrow$  Why?

$$\underline{V_{GS}} = V_D = V_{CC} - \underline{I_D} R_D \quad (1)$$

$$\underline{I_D} = \frac{1}{2} k (\underline{V_{GS}} - V_{th})^2 \quad (2)$$

Two eqns. and two unknowns. Insert Eqn.(2) into Eqn(1) yields

$$V_{GS} = V_{CC} - \frac{1}{2} k R_D (V_{GS}^2 - 2V_{th}V_{GS} + V_{th}^2)$$

Rearranging the eqn. yields

$$\underbrace{\frac{1}{2} k R_D V_{GS}^2}_{a V_{GS}^2} + \underbrace{(1 - k R_D V_{th}) V_{GS}}_{b V_{GS}} + \underbrace{\frac{1}{2} k R_D V_{th}^2 - V_{CC}}_c = 0$$

$\Rightarrow$  Quadratic eqn.  $\Rightarrow V_{GS}$  is unknown  $\Rightarrow$

We can solve the problem.

$V_{GS}$  has two solutions. For the meaningful solution  $V_{GS} > V_{th}$

⇒ Then calculate  $I_D$

⇒ Then calculate  $V_{DS} = V_{CC} - I_D R_D$

⇒ Verify that FET is in saturation  
(which requires  $V_{DS} \geq V_{GS} - V_{th}$ )