

Memory circuits

Memory is organized in bits and words (e.g. one word is 1 byte = 8 bit)

Memory organization

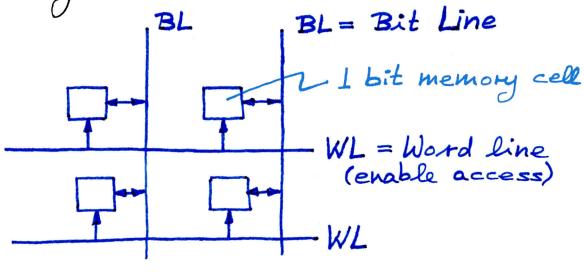


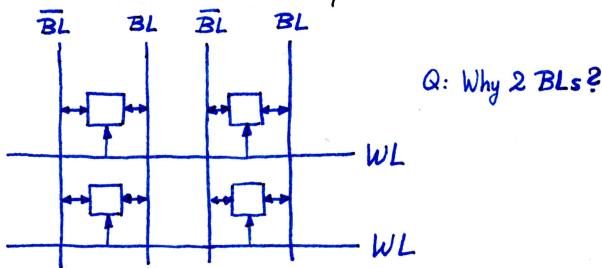Sometimes there are two Bit Lines per bit



WL enables memory cell to communicate with BL

Flip-flop circuit (bistable)

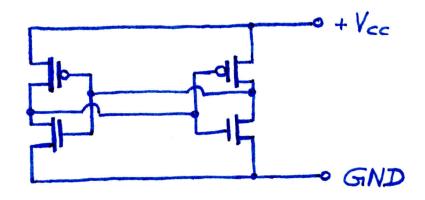

Convince yourself that this is a bistable circuit.


Q: How many transistors? > 4 FEVS

SRAM circuit

RAM = Random Access Memory

SRAM = Static RAM

- Using flip-flop as memory

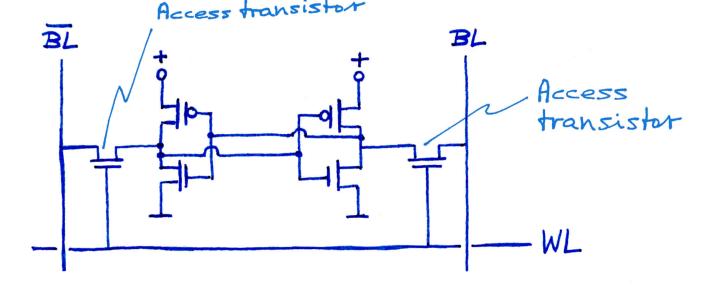

Q: Static power consumption? => Zero

Q: How many transistors? => Six

Q: Which regime does Access Transistor operate in ? Ohmic (ON) and Saturation (OFF)

Q: Advantage of SRAM? => Fast

Q: Disadvantage of SRAM? => 6 transistors


Q: SRAM volatile or non-volatile? => Volatile

DRAM circuit

DRAM = Dynamic RAM

Storage element is capacitor G => Prischarges over time => Needs to be recharged => "Dynamic"

I transistor I capacitor => 1719

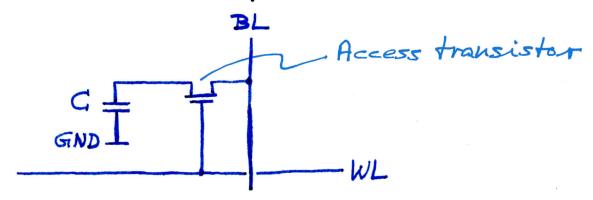

Cis a bit leaky - Ci self-discharges - Information needs to be "refreshed".

Q: Refresh time? => 64 ms

0: As an engineer, do you prefer SRAM or DRAM?

Q: As an economist, do you prefer SRAM (6T) or DRAM (ITIG)?

(5)


Q: Is SRAM a volotile memory?

Q: Is DRAM a valatile memory?


Flash memory

Flash memory = Non-volatile memory

Regular FET

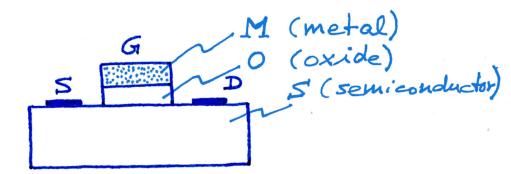



Flash memory FET

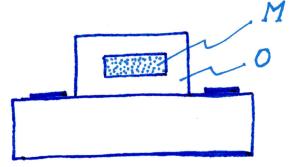

Gate metal is completely surrounded by oxide (SiO2 insulator) so that the charge on the gate is kept for 10~20 years.

Gate charge:

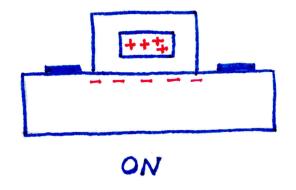

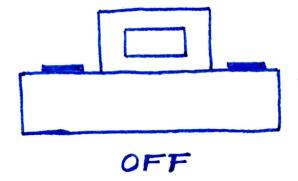

Due to the permanent (10~20 years) charge on the Gate, the FET is "frozen" in its ON or OFF state.

How do we change the Gate charge? We need a high-energy pulse ("flash") to transfer charge (through the insulator) to the gate.

What is the "flash"? => A very high voltage pulse between S and D. During the pulse some charge end up on the G.

- Q: Is flash memory volatile? No.
- Q: Name some examples where flash memory is used.