

2.) Input Impedance, Reflection, and Power

$$a.) \quad 1V + \Gamma_L (1V) = 0.75V$$

$$\Gamma_L = -0.25$$

$$-0.25 = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L - 50}{Z_L + 50}$$

$$Z_L = 30\Omega$$

$$b.) \quad \text{velocity factor} = 0.6, \quad \text{light speed} = 3.0 \times 10^8 \text{ m/s}$$

$$\frac{0.6 \times 3 \times 10^8 \text{ m/s}}{10^6 \text{ Hz}} = 180 \text{ m}$$

$$c.) \quad \beta = \frac{2\pi}{\lambda} = \frac{\pi}{90} \quad L = 300 \text{ m}$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta L}{Z_0 + jZ_L \tan \beta L}$$

$$Z_{in} = 50 \frac{(30) + j(50) \tan \left(\frac{300\pi}{90} \right)}{(50) + j(30) \tan \left(\frac{300\pi}{90} \right)} = 57.7 + j26.6\Omega$$

d.) $\frac{270\text{m}}{\lambda} = \frac{270}{180} = 3/2$. The new section of line has length $3/2\lambda$. Since this is a multiple of $\frac{\lambda}{2}$, $Z_{in} = Z_L$. So the Z_{in} will be the same as in part c.

e.)

$$P_{av} = \frac{|V_o^+|^2}{2Z_0} [1 - |\Gamma_L|^2]$$

$$P_{av} = \frac{(1)^2}{2(50)} [1 - 0.25^2] = 9.375 \text{ mW}$$

If the load were matched,


Γ_L would be 0.

$$P_{av} = \frac{(1)^2}{2(50)} = 10 \text{ mW}$$

3.) Standing Waves

a.) This is not a standing wave pattern. Standing wave patterns are defined by the equation 2.64 on page 70 of Ulaby. This pattern has magnitude 0 at some wavelengths, which suggests that it must correspond to a reflection coefficient of 1 or -1. But reflection coefficients of 1 and -1 generate standing wave patterns that look different from this. You can see this by playing with the standing wave simulator (https://www.rfmentor.com/node/138?no_cache=1612764476). You'll note that there is no value of reflection coefficient for which you can generate a standing wave pattern that has this shape.

b.)

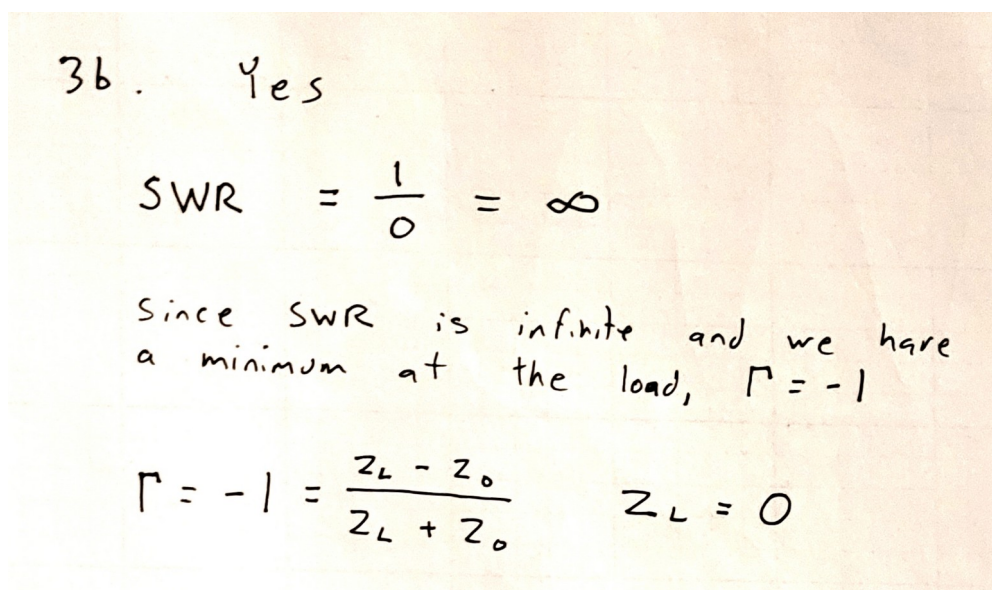

Handwritten text on a piece of paper:

3b. Yes

$$SWR = \frac{1}{0} = \infty$$

Since SWR is infinite and we have a minimum at the load, $\Gamma = -1$

$$\Gamma = -1 = \frac{Z_L - Z_0}{Z_L + Z_0} \quad Z_L = 0$$

4.) Lossy Transmission Line

4.

$$5e^{-\alpha(50)} = 2$$

$$e^{-\alpha(50)} = \frac{2}{5}$$

$$-\alpha(50) = \ln \frac{2}{5}$$

$$50\alpha = 0.916$$

$$\alpha = 0.0183$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{25} = 0.251$$

5.) Low-Loss Transmission Line

5a. Series impedance is $r' + j\omega l'$
 $r = 0.2 \, \Omega/\text{m}$
at 1 K , $j\omega l' = j(2\pi \cdot 1000)(100 \times 10^{-6})$
 $= j 0.628$

Low-loss approximation holds
for $\frac{r'}{j\omega l'} \ll 1$. But at 1 K , it
does not hold.

5b. At 1 MHz , $j\omega l' = j(2\pi \times 10^6)(100)(10^{-6})$
 $\approx j 628$

$$\frac{r'}{j\omega l'} = \frac{0.2}{j 628} \ll 1,$$

so low-loss approximation holds.

Sc. We need to choose g such that the Heaviside condition is satisfied:

$$\frac{r'}{l'} = \frac{g'}{c'}$$

given the specified parameters for this line:

$$\frac{0.2}{100 \times 10^{-6}} = \frac{g'}{100 \times 10^{-12}}$$

$$g' = 2 \times 10^{-7} \text{ S/m}$$

$$(2 \times 10^{-7} \text{ S/m})(10 \text{ m}) = 2 \times 10^{-6} \text{ S}$$

$$\frac{1}{g'} = 500 \text{ k}\Omega$$