

## Laboratory 8 (1 day): Digital circuits

### Material covered:

- This laboratory has **one session** allocated for completion:
  - Mandatory: Pre-Lab Exercise 1 and Exercise 1. Optional: Exercise 2 •

Transistor-resistor logic

- Transistor-transistor logic
- Digital circuits

### Propagation delay:

The **propagation delay** is the time it takes for the digital output to change after the digital input changes. It is defined as the time difference between when the input is halfway between

$V_{In,Low}$  and  $V_{In,High}$  to when the output is halfway between  $V_{Out,Low}$  and  $V_{Out,High}$ . The two times are defined as  $t_{p,LH}$  (output transitions from LO to HI) and  $t_{p,HL}$  (output transitions from HI to LO). An example for an inverter circuit is shown below. The **red line is the input** and the **green line is the output**.


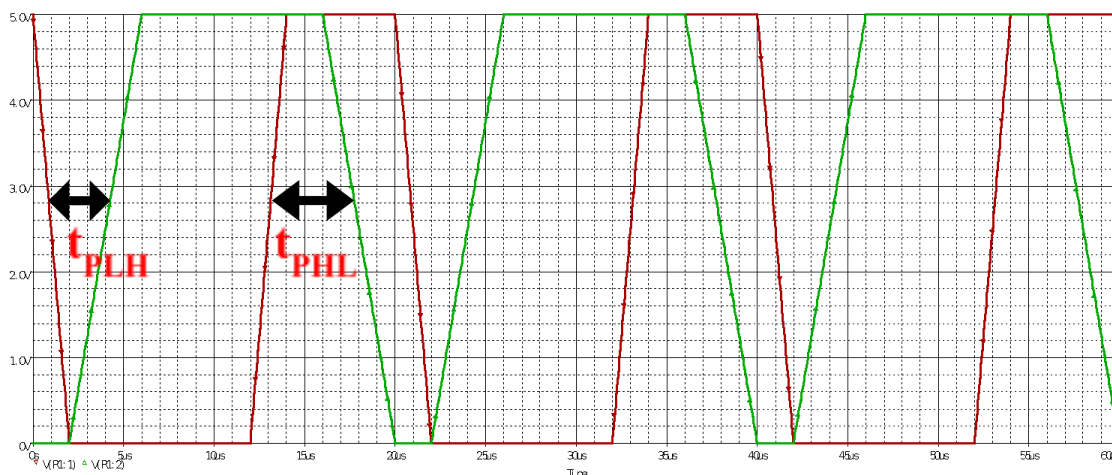


Figure 1: Inverter timing diagram (**input** and **output**)


## Pre-Lab Exercise 1

 

**Figure 2: CMOS inverter (M1 = N-channel FET; M2 = P-channel FET)**

1. Simulate the circuit shown above. Note, the PMOS transistor needs to be ‘mirrored vertically’ so that the source is on the ‘top’. You can change the orientation of a component by right clicking on it. Set the simulation to a DC voltage sweep for  $0 < V_{in} < 5$  V.

*Estimate the output high voltage, the output low voltage, the low noise margin and the high noise margin.*

 

**Figure 3: CMOS inverter (M1 = N-channel FET; M2 = P-channel FET)**

2. Add an input side resistance and an output side capacitance. Set  $V_{in}$  to a pulse stream with a 50% duty cycle and a 2  $\mu$ s period.

*Estimate the propagation delay as the output switches from LO to HI and from HI to LO.*

## Exercise 1: CMOS inverter

 


Figure 4: CMOS inverter

1. Build the circuit above using the IRF9120 PMOS and 2N7000 NMOS transistors. Set the input signal to a 10 Hz sawtooth triangle wave, oscillating between 0 V and 5 V.
2. Use the x-y channel to plot the voltage transfer function,  $V_{out}$  versus  $V_{in}$ .



The transfer function matches the inverter's expected behavior!  
When  $V_{in}$  is low (0V),  $V_{out}$  is high (up to ~925 mV).

When  $V_{in}$  is high,  $V_{out}$  is low (down to 0V)


Determine the LO and HI output voltages,  $V_{\text{Out,Low}}$  and  $V_{\text{Out,High}}$ . Estimate the high and low noise margins.

$$V_{\text{Out,Low}} = 0 \text{ V}$$

$$V_{\text{Out,High}} = 925 \text{ mV}$$

$$\text{NM}_{\text{low}} = V_{\text{IL}} - V_{\text{OL}} = 1.4 \text{ V} - 0.05 \text{ V} = 1.35 \text{ V}$$
 
$$\text{NM}_{\text{high}} = V_{\text{OH}} - V_{\text{IH}} = 0.7 \text{ V} - 2 \text{ V} = -1.3 \text{ V} = 1.3 \text{ V}$$



So the Noise Margins are mostly symmetrical

3. Add a 10 nF capacitor at the load ( $V_{\text{out}}$ ) and change the input signal to a square wave. You will need to 'zoom in' to see the  $t_{\text{PLH}}$  and  $t_{\text{PHL}}$ . In order to do that, you need to set the horizontal axis to  $\sim 100 \text{ ns/div}$ . The triggering must also be set correctly. Set the triggering source to the oscilloscope channel connected to the input and the triggering level to  $\sim 2 \text{ V}$ . You can change the condition ("Cond.") to Rising and Falling, giving you the two different propagation delays.

Estimate the propagation delays.

$V_{\text{OL}}$ (Output voltage – Low)	31.25 mV
$V_{\text{OH}}$ (Output voltage – High)	775 mV to 1 V (depending on L-to-H or H-to-L)
$\text{NM}_{\text{Low}}$ (Noise margin – Low)	Was not able to measure successfully, impedance of probes and input of oscilloscope were very wonky (hard to get trustable values)
$\text{NM}_{\text{High}}$ (Noise margin – High)	Same as above^
$t_{\text{PLH}}$ (Propagation delay – L-to-H)	60 ns (measured via cursors)
$t_{\text{PHL}}$ (Propagation delay – H-to-L)	64 ns (measured via cursors)