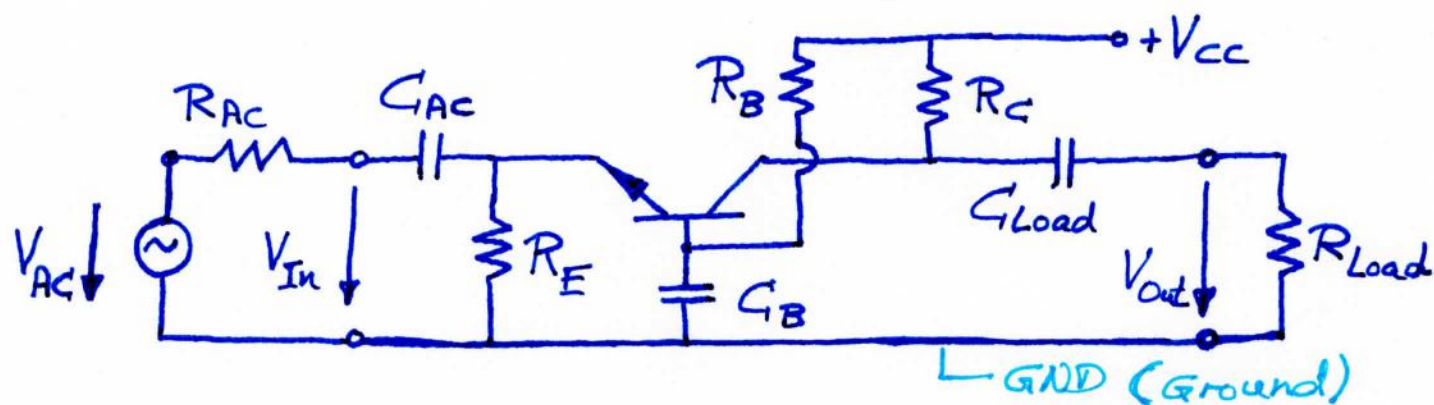


Problem 1 Amplifier

- (a) β = Current amplification in common-emitter configuration

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = \frac{0.99}{0.01} = 99 \approx \underline{\underline{100}}$$

- (b) Redraw circuit diagram



- (c) Base is shared (common) for AC signals.
 \Rightarrow Circuit is common-base configuration.

- (d) $R_C = R_E = 500\Omega$ $V_{RC} = 3.0V$ Q-point ?

$$\Rightarrow I_C = \frac{V_{RC}}{R_C} = \frac{3.0V}{500\Omega} = \underline{\underline{6\text{ mA}}}$$

$$\Rightarrow I_B = \frac{I_C}{\beta} = \frac{6\text{ mA}}{100} = 0.06\text{ mA} = \underline{\underline{60\mu\text{A}}}$$

$$\Rightarrow I_E = I_C + I_B = 6\text{ mA} + 60\mu\text{A} = \underline{\underline{6.06\text{ mA}}}$$

$$\Rightarrow V_{RE} = 500\Omega \times 6.06\text{ mA} = 3.03V$$


$$\Rightarrow V_{Base} = V_{RE} + V_{BE} = 3.03V + 0.7V = 3.73V \quad (2)$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{Base}}{I_{Base}} = \frac{12V - 3.73V}{60\mu A} = \underline{\underline{138k\Omega}}$$

(e) Differential emitter resistance


$$r_E = \frac{V_t}{I_E} = \frac{26mV}{6.06mA} = \underline{\underline{4.29\Omega}}$$

(f) AC small-signal equivalent circuit

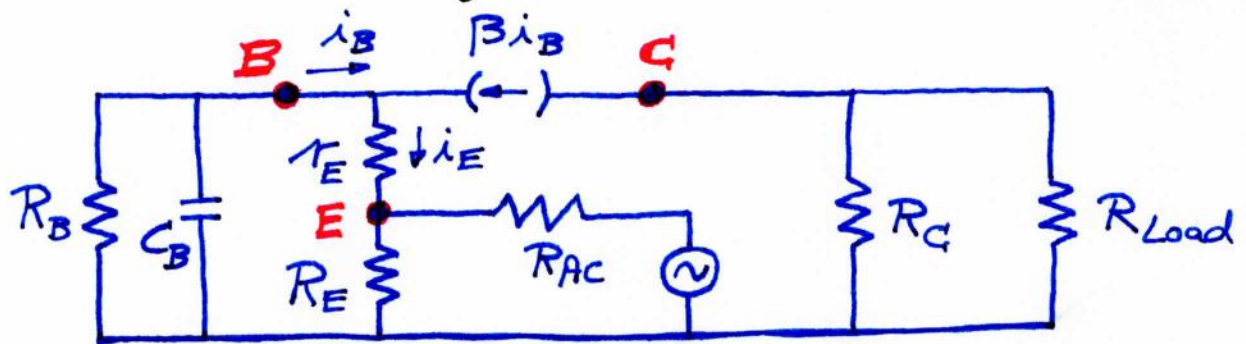

Note: R_B is shorted by $C_B \Rightarrow$ Base is connected to GND.

(g) Redraw circuit diagram

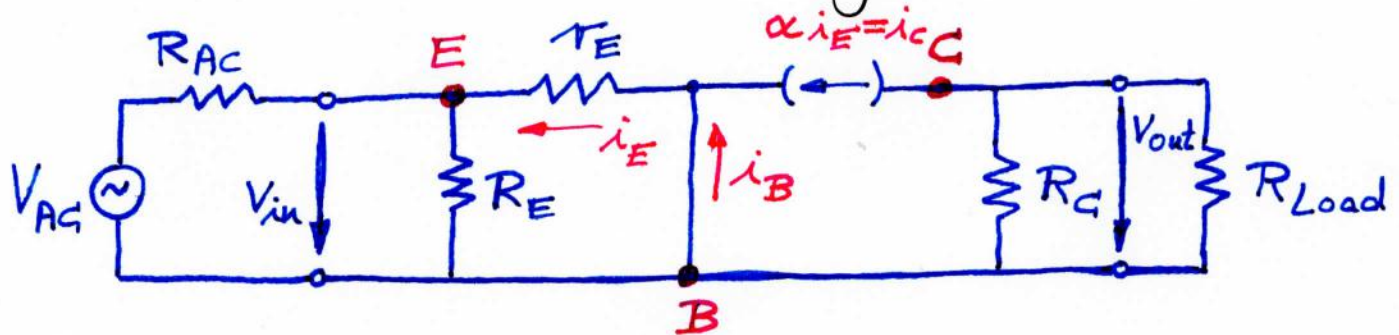

\Rightarrow Linear circuit. \Rightarrow We can analyze effect of one source without considering other sources.

③

$$(h) \quad Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{i_{RE} + i_{TE}} = \frac{V_{in}}{\frac{V_{in}}{R_E} + i_E}$$

$$= \left(\frac{V_{in}/R_E + i_E}{V_{in}} \right)^{-1} = \left(\frac{1}{R_E} + \frac{1}{r_E} \right)^{-1} = \underline{\underline{R_E \parallel r_E}}$$

$$\Rightarrow \text{Note } r_E \ll R_E \Rightarrow Z_{in} \approx r_E$$

$$\Rightarrow \underline{\underline{Z_{in} \approx r_E}} \quad r_E = 4.29 \Omega$$

$Z_{in} \approx r_E = 4.29 \Omega$ is relatively low value

$$(i) \quad Z_{out} = \frac{V_{out}}{i_{out}} = \frac{i_{out} R_C}{i_{out}} = \underline{\underline{R_C}}$$

$$(j) \quad A_{voc} = \frac{V_{out}}{V_{in}} \quad \text{when } R_{Load} = \infty \text{ (OC)}$$

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{i_C R_C}{i_E r_E} = \frac{\alpha i_E R_C}{i_E r_E} = \alpha \frac{R_C}{r_E} \approx \underline{\underline{\frac{R_C}{r_E}}}$$

$$= \frac{500 \Omega}{4.29 \Omega} = \underline{\underline{117}}$$

$$(k) \quad A_{isc} = \frac{i_{out}}{i_{in}} \quad \text{when } R_{Load} = 0 \text{ (SC)}$$

$$A_{isc} = \frac{i_{out}}{i_{in}} = \frac{i_C}{i_E + i_{RE}} \approx \frac{i_C}{i_E} = \underline{\underline{\alpha}} = \underline{\underline{0.99}}$$

$$(l) \quad A_v = ? \quad R_{Load} = 500 \Omega \quad R_C = 500 \Omega$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{i_C (R_C \parallel R_{Load})}{i_E r_E} \approx \frac{R_C \parallel R_{Load}}{r_E}$$

$$= \frac{500 \Omega \parallel 500 \Omega}{4.29 \Omega} = \frac{250 \Omega}{4.29 \Omega} = \underline{\underline{58.5}}$$


(m) The resistances R_C and R_{Load} act as ④
current divider. Which part of i_c will
flow through R_{Load} ?

$$\Rightarrow i_{Load} = i_c \frac{\frac{1}{R_{Load}}}{\frac{1}{R_{Load}} + \frac{1}{R_C}} = i_c \frac{(500\Omega)^{-1}}{(500\Omega)^{-1} + (500\Omega)^{-1}}$$

$$= \frac{1}{2} i_c$$

$$A_I = \frac{i_{out}}{i_{in}} = \frac{\frac{1}{2} i_c}{i_E} \approx \frac{1}{2} \alpha \approx \underline{\underline{0.5}}$$

(n)

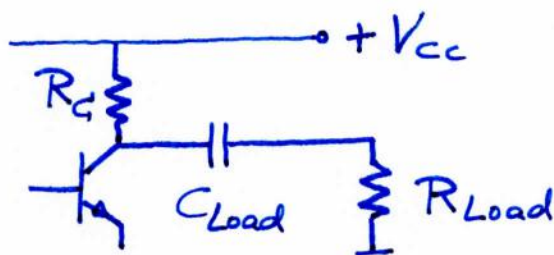

C_{Load} blocks DC
 C_{Load} lets pass AC
 }
 This is a high-frequency pass filter

Relevant R is the R that C_{Load} will discharge through.

Inspection of circuit diagram reveals that relevant $R = R_C + R_{Load} = 1\text{ k}\Omega$

Recall $\omega_{3dB} = \omega_{cutoff} = \frac{1}{RC}$

$$\Rightarrow f_{3dB} = f_{cutoff} = \frac{1}{2\pi RC}$$

(0) $f_{\text{cutoff}} = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi R f_{3dB}}$

$\hookrightarrow f_{3dB}$


$$C = \frac{1}{2\pi \cdot 1k\Omega \cdot 1kHz} = \underline{\underline{159 \text{ nF}}}$$

(5)

Problem 2

Differential amplifier

(a) Circuit diagram

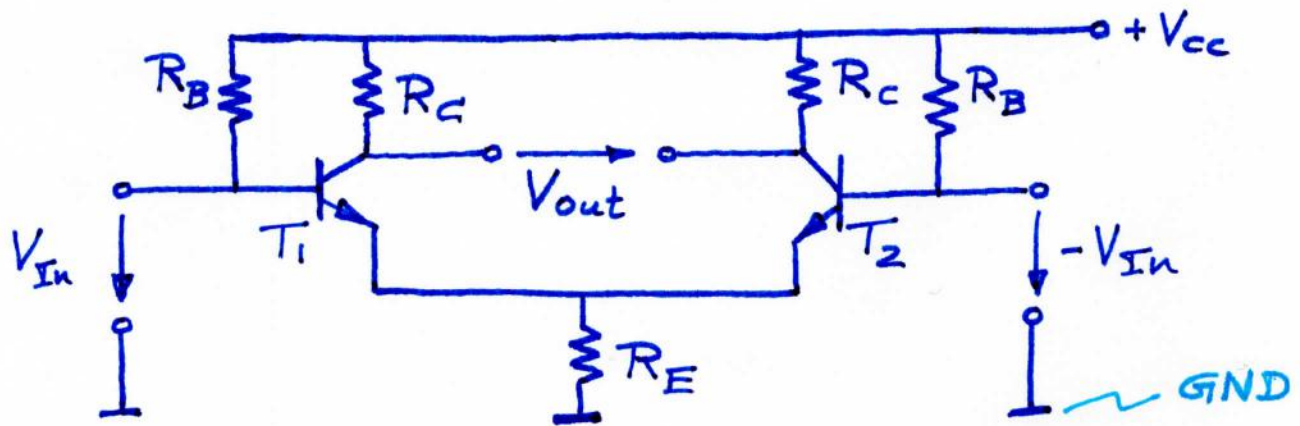(b) Q-point $V_{RE} = 1V$ $V_{CE} = 5V$ $V_{CC} = 12V$ Current through $R_E = I_{RE} = 20mA$

$$\Rightarrow R_E = \frac{V_{RE}}{I_{RE}} = \frac{1V}{20mA} = \underline{\underline{50\Omega}}$$

$$I_{C1} \approx I_{E1} = \frac{1}{2} I_{RE} = \underline{\underline{10mA}}$$

$$\text{KVL } V_{CC} = V_{RE} + V_{CE} + V_{RC}$$

$$\Rightarrow V_{RC} = V_{CC} - V_{CE} - V_{RE} = 12V - 5V - 1V = 6V$$

$$\Rightarrow R_C = \frac{V_{RC}}{I_{RC}} = \frac{6V}{10mA} = \underline{\underline{600\Omega}}$$

$$I_B = \frac{I_C}{\beta} = \frac{10mA}{100} = \underline{\underline{0.1mA}}$$


$$V_{RB} = V_{CC} - V_{RE} - V_{BE} = 12V - 1V - 0.7V = 10.3V$$

$$\Rightarrow R_B = \frac{V_{RB}}{I_{RB}} = \frac{10.3V}{0.1mA} = \underline{\underline{103k\Omega}}$$

(c) At Q-point: $V_E = 1V$ $V_C = 6V$ $V_{CE} = 5V$
 $I_C = 10mA$ $I_E = 10mA$

V_E can be considered "virtual ground" because V_E does not change. Currents through transistors change but sum $I_{E1} + I_{E2} = I_{RE}$ does not $\Rightarrow V_E = \text{constant}$


Output characteristic

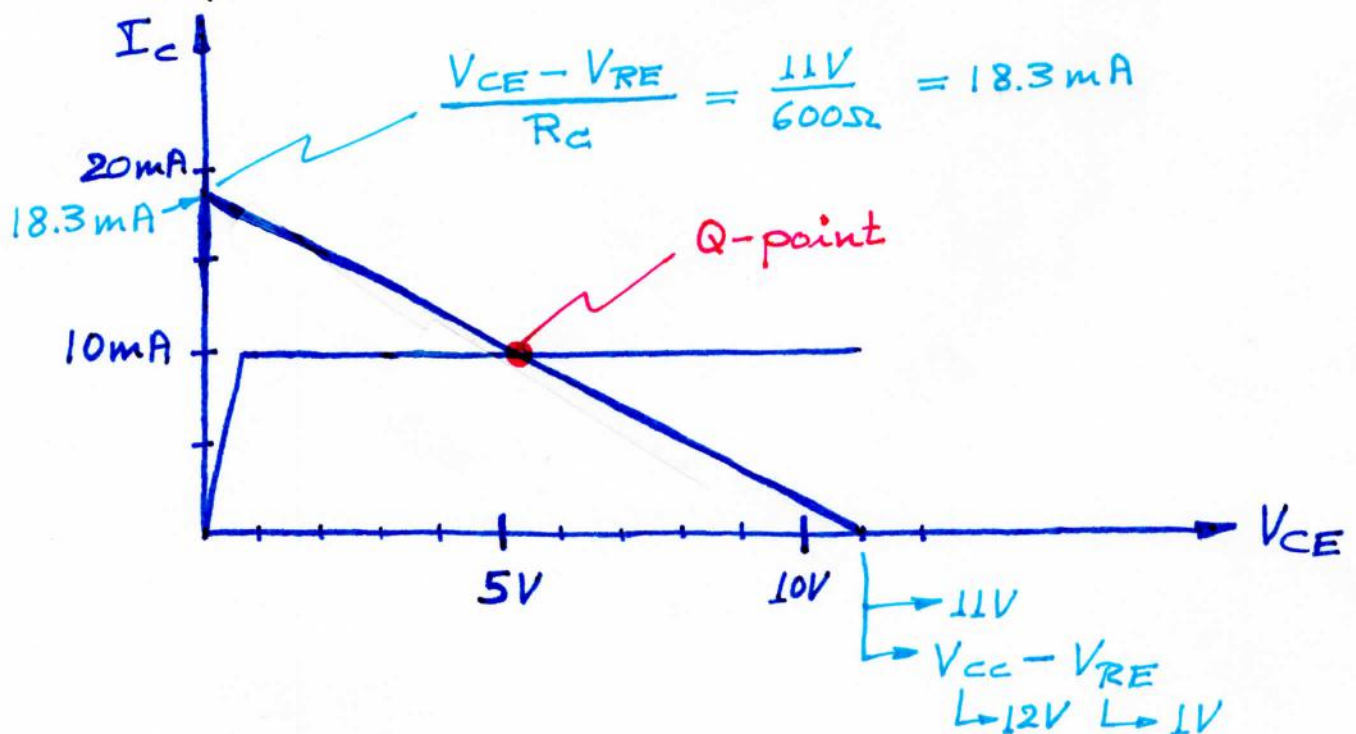


(d) Differential emitter resistance r_E
 (may also be called dynamic emitter resistance)

$$r_E = \frac{V_t}{I_E} = \frac{26mV}{10mA} = \underline{\underline{2.6\Omega}}$$


Small-signal equivalent circuit

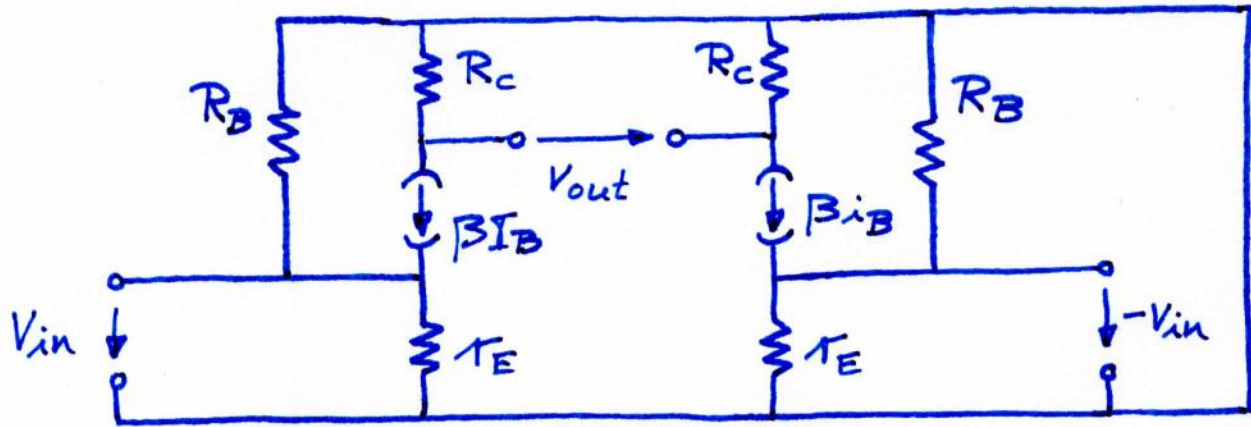

Redrawing (simplifying) the circuit

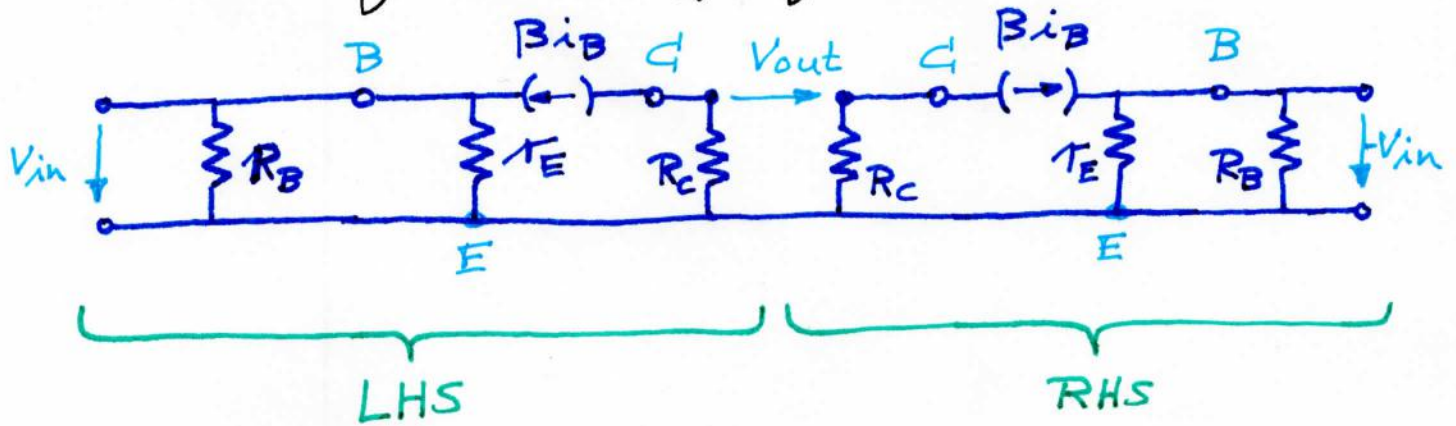

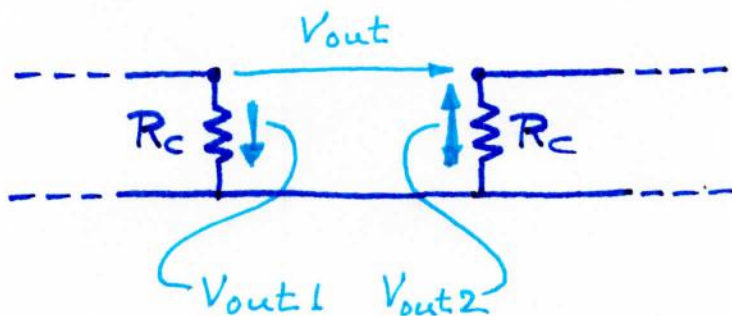LHS and RHS are identical. We therefore analyze only the LHS and double the output voltage



$$V_{out} = V_{out1} + V_{out2} = 2 V_{out1}$$

(9)

(e) LHS circuit:

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{\beta i_B R_c}{(\beta + 1) i_B r_E} \approx \frac{R_c}{r_E}$$

Same A_{voc} for RHS circuit due to symmetry

$$\Rightarrow \text{Total amplification } A_{voc} = \frac{2V_{out}}{V_{in}} = \underline{\underline{\frac{2R_E}{r_E}}}$$

(f) Numerical value

$$A_{voc} = 2 \frac{R_E}{r_E} = 2 \frac{600\Omega}{2.6\Omega} = \underline{\underline{461}}$$

(g) Two amplifier stages in series

$$A_{voc} \Big|_{2 \text{ stages}} = A_{voc}^2 = 461^2 = \underline{\underline{212\,000}}$$

Problem 3

True/false questions

- (a) True
- (b) True
- (c) True
- (d) False
- (e) True
- (f) True
- (g) True

$$I_C = \alpha I_E$$

↳ ≈ 1.0

Will not work properly

α and β are reduced

Circuit will likely still work

α and β are reduced

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{\beta + 1}$$

$$\Rightarrow I_B \ll I_C \text{ and } I_B \ll I_E$$

BE \Rightarrow Forward bias

CE \Rightarrow Reverse bias.