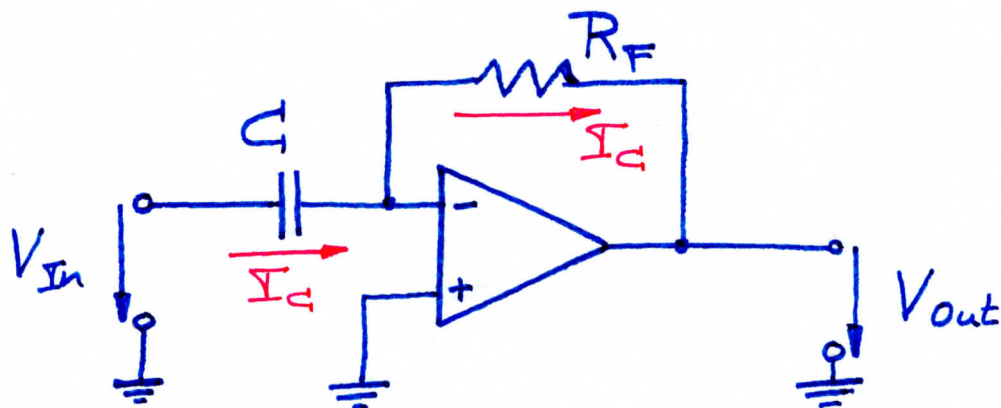


Op amp as differentiator



We can write:

$$V_{In} = V_C \quad (\text{KVL})$$

$$\text{Recall: } Q = CV \Rightarrow \dot{Q} = C\dot{V}$$

\downarrow I_C

$$\Rightarrow I_C = C\dot{V}_C = C\dot{V}_{In}$$

Furthermore:


$$\begin{aligned} V_{Out} &= -I_C R_F \quad (\text{KVL}) \\ &= -C\dot{V}_{In} R_F \end{aligned}$$

$$\Rightarrow \boxed{V_{Out} = -R_F C \dot{V}_{In}}$$

$\Rightarrow V_{Out}$ is temporal derivative of V_{In}

\Rightarrow Op amp works as mathematical differentiator

Op amp as integrator

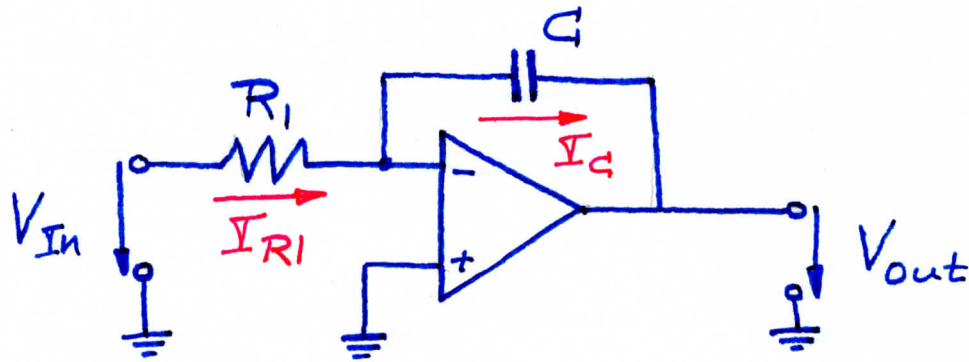

We can write:

$$I_C = I_{R1}$$

$$I_{R1} = \frac{V_{In}}{R_1} \quad (\text{Ohm})$$

Recall: $Q = CV \Rightarrow \dot{Q} = C\dot{V} \Rightarrow \dot{V} = \frac{I_C}{C}$

$$\Rightarrow V = V_C = \int_t \frac{1}{C} I_C dt$$

Furthermore:

$$\begin{aligned} V_{out} &= -V_C = -\frac{1}{C} \int I_C dt \\ &= -\frac{1}{C} \int \frac{V_{In}}{R_1} dt = -\frac{1}{R_1 C} \int_0^t V_{In} dt \end{aligned}$$

$$\Rightarrow \boxed{V_{out} = -\frac{1}{R_1 C} \int_0^t V_{In} dt}$$

$\Rightarrow V_{out}$ is temporal integral of V_{In}

\Rightarrow Op amp works as mathematical integrator