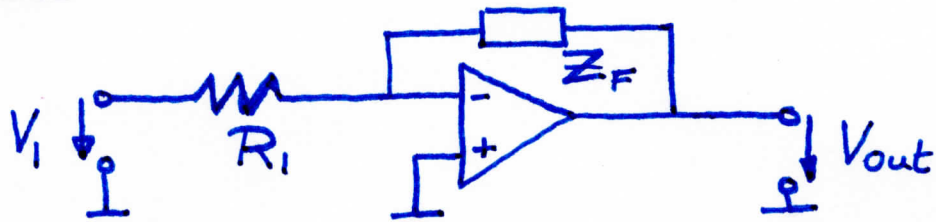


ITE - Homework 03 - Solution

①

Problem 01 Operational amplifier



(a) Feedback 

$$Z_F = \left(\frac{1}{j\omega L} + j\omega C \right)^{-1} = \left(\frac{1 + j^2 \omega^2 LC}{j\omega L} \right)^{-1}$$


$$= \frac{j\omega L}{1 - \omega^2 LC}$$

$$\omega \rightarrow 0 \Rightarrow Z_F \rightarrow 0$$

$$\omega = \frac{1}{\sqrt{LC}} \Rightarrow Z_F \rightarrow \infty$$

$$\omega \rightarrow \infty \Rightarrow Z_F \rightarrow 0$$

Sketch

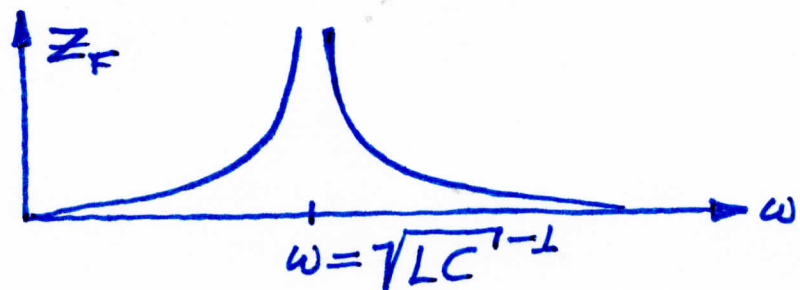

(b) Resonance angular frequency $\omega_0 = \frac{1}{\sqrt{LC}}$

(2)


(c) Recall $A_{voc} = -\frac{Z_F}{R_L}$

$$= -\frac{1}{R_L} \frac{j\omega L}{1 - \omega^2 LC} = \frac{V_{out}}{V_L}$$


$$H(\omega) = \frac{V_{out}}{V_L} = -\frac{1}{R_L} \frac{j\omega L}{1 - \omega^2 LC}$$

$$\Rightarrow |H(\omega)| = \frac{1}{R_L} \frac{\omega L}{1 - \omega^2 LC}$$

Sketch

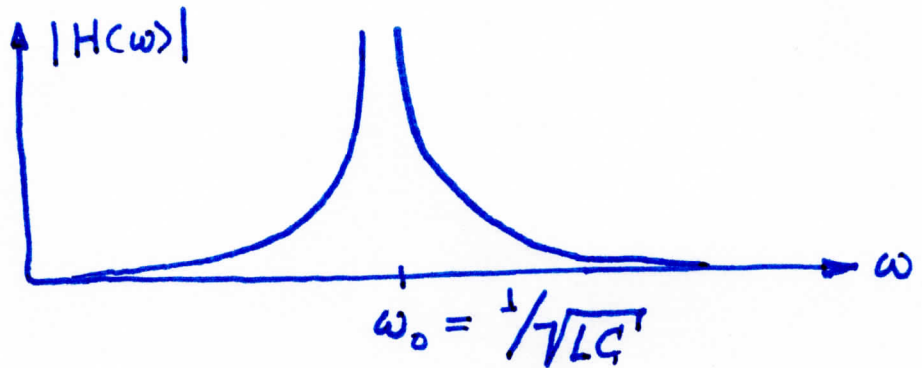

(d) Addition of R_F

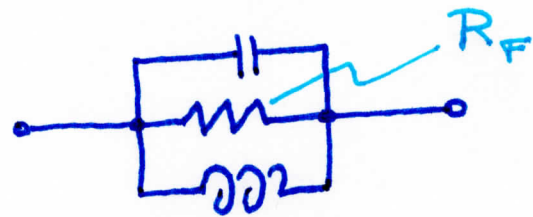

Impedance


$$\begin{aligned} Z_F &= \left(\frac{1}{j\omega L} + j\omega C + \frac{1}{R_F} \right)^{-1} \\ &= \left(\frac{R_F + j^2\omega^2 LCR_F + j\omega L}{j\omega L R_F} \right)^{-1} \\ &= \frac{j\omega L R_F}{R_F - \omega^2 LCR_F + j\omega L} \end{aligned}$$

(e) Impedance at resonance frequency

③

$$\omega = \omega_0 = 1/\sqrt{LC}$$
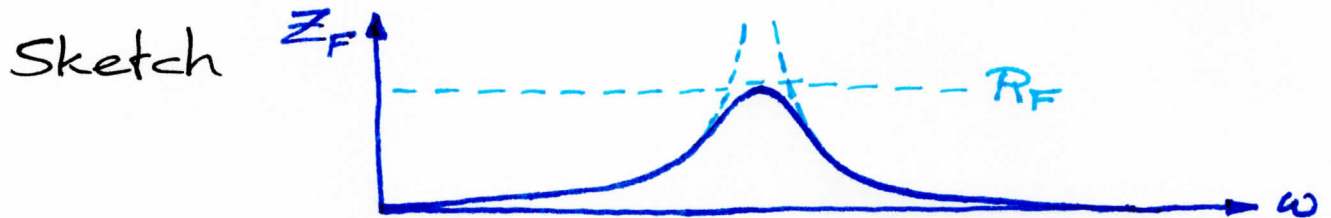
$$\begin{aligned}\Rightarrow Z_F &= \frac{j\omega_0 L R_F}{R_F - \frac{1}{\underline{LC}} \underline{LC} R_F + j\omega_0 L} \\ &= \frac{j\omega_0 L R_F}{j\omega_0 L} = \underline{R_F}\end{aligned}$$



(f) At resonance $Z_F = R_F$

$$\Rightarrow A_{voc} = -\frac{Z_F}{R_i} = -\frac{R_F}{R_i} = \underline{\underline{-1}}$$

Problem 02



$$\text{Slew rate} = SR = 1 \frac{V}{\mu s}$$

(4)

(a) Slew rate is maximum of $\frac{dV_{out}}{dt}$

Slew rate applies to OpAmp's output voltage.

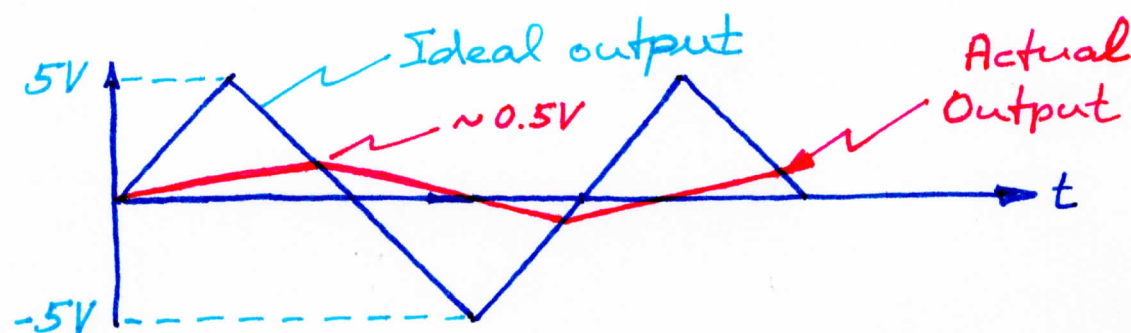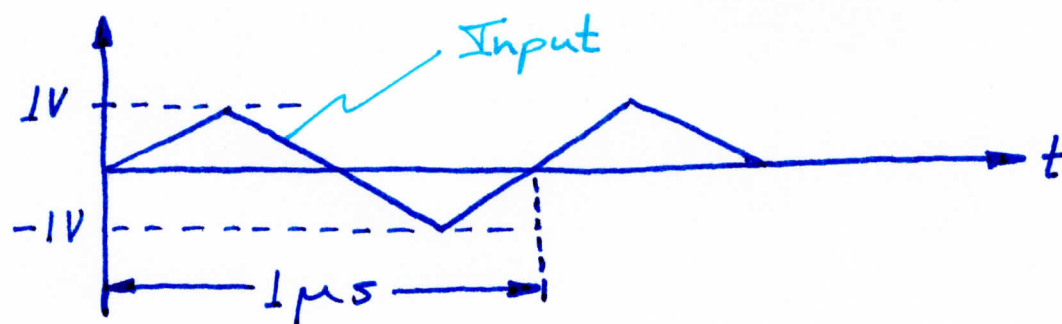(b) Triangular wave $T = 1 \mu s$ $V_o = 1V$
 $A_{voc} = 5$ $V_{out} = 5V$



⇒ Output signal is strongly distorted

(c) $V_{o,in} = 0.1V$ $A_{voc} = 1$ $V_{o,out} = 0.1V$

$$\text{Slew rate} = \frac{\Delta V}{\Delta t} = \frac{100mV}{T/4} = \frac{400mV}{T} = 1 \frac{V}{\mu s}$$

$$\text{Solve for } T \Rightarrow T = 400mV / 1 \frac{V}{\mu s} = 0.4 \mu s$$

$$\Rightarrow f = \frac{1}{T} = \frac{1}{0.4 \mu s} = \underline{\underline{2.5 MHz}}$$

Op Amp
value

(5)

$$(d) \quad V_{o,in} = 0.1V \quad A_{voc} = 10 \quad V_{o,out} = 1V$$

$$\text{Slew rate} = SR = \frac{\Delta V}{\Delta t} = \frac{1V}{T/4} = \frac{4V}{T} = 1 \frac{V}{\mu s}$$

$$\text{Solve for } T \Rightarrow T = \frac{4V}{1 \frac{V}{\mu s}} = 4 \mu s$$

$$\Rightarrow f = \frac{1}{T} = \frac{1}{4 \mu s} = \underline{\underline{0.25 \text{ MHz}}}$$

$$(e) \quad V_{o,in} = 0.1V \quad A_{voc} = 100 \quad V_{o,out} = 10V$$

$$\text{Slew rate} = SR = \frac{\Delta V}{\Delta t} = \frac{10V}{T/4} = \frac{40V}{T} = 1 \frac{V}{\mu s}$$

$$\Rightarrow T = \frac{40V}{1V/\mu s} = 40 \mu s$$

$$\Rightarrow f = \frac{1}{T} = \frac{1}{40 \mu s} = \underline{\underline{0.025 \text{ MHz}}}$$

(f) Gain \times Bandwidth

$$(c): \quad 1 \times 2.5 \text{ MHz} = 2.5 \text{ MHz}$$

$$(d): \quad 10 \times 0.25 \text{ MHz} = 2.5 \text{ MHz}$$

$$(e): \quad 100 \times 0.025 \text{ MHz} = 2.5 \text{ MHz}$$

\hookrightarrow Gain \hookrightarrow Bandwidth


In each case: 2.5 MHz

\Rightarrow We see that Gain \times Bandwidth = constant

(g) Yes, the present problem shows that this is indeed the case.

Problem 3

(a) True.

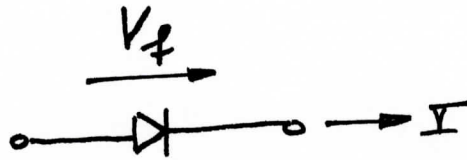

Power dissipated in the diode is $P = V_f I$

(b) True.

Reverse current is very small. $\Rightarrow P = VI$ is very small as well.