


## ITE - Homework 01 - Solution

Problem 1: Voltage source and current source

(a) Output voltage of voltage source

$$V_{out} = V_{source} - I_{out} R_{source}$$


Sketch

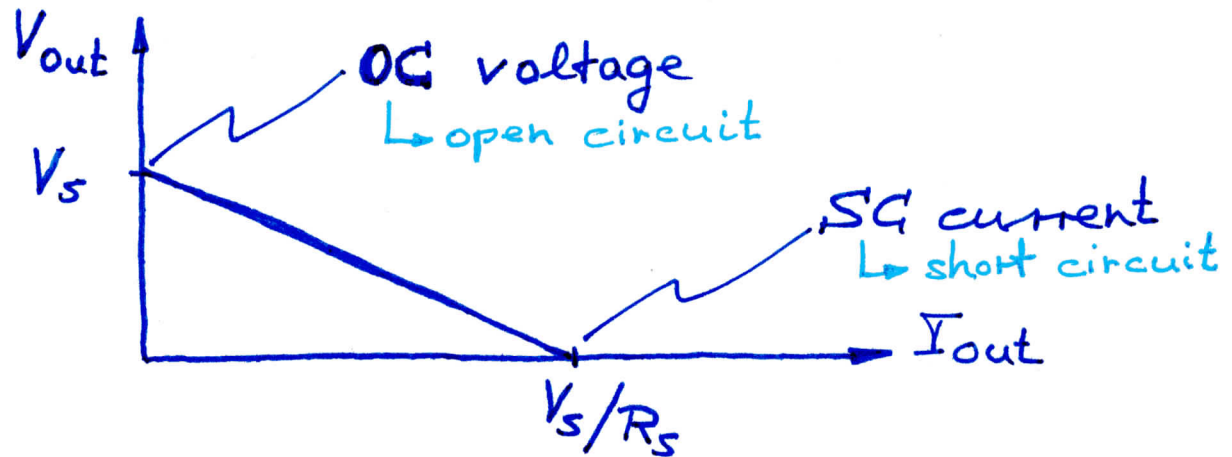

(b) Output current of current source

$$I_{out} = I_{source} - V_{out} G_{source}$$

Sketch

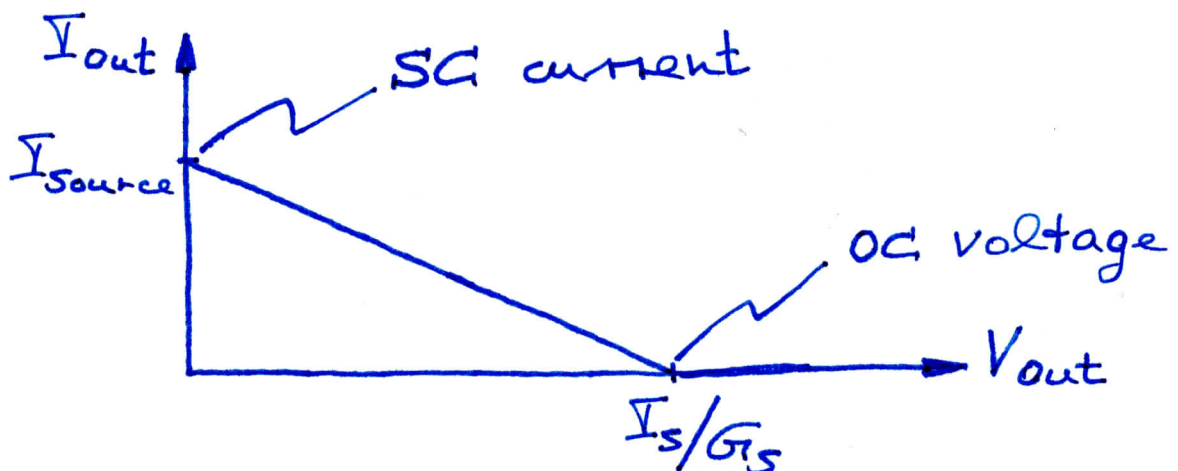

Note:  $V_{source} = V_s$        $I_{source} = I_s$

- (c) The two functions are two straight lines. Yes, the two straight lines can be identical <sup>②</sup>
- (d) Two straight lines are identical if two points are identical
- (e) If the OC voltage and the SC current are identical, then the two straight lines are identical and the two sources are equivalent

## Problem 2: Linear and non-linear circuits <sup>③</sup>

- (a) A linear circuit is a circuit that, when stimulated, gives a response that is proportional to the stimulus.

Response  $\propto$  Stimulus

Effect  $\propto$  Cause

Output  $\propto$  Input

- (b) A non-linear circuit is a circuit that, when stimulated, gives a response that is not proportional to the stimulus.

Response  $\npropto$  Stimulus

Effect  $\npropto$  Cause

Output  $\npropto$  Input

(c)  R       C       L

(d)  Diode       Transistors


(e) Yes. A circuit that includes a voltage source fits the definition of a linear circuit (given above).

(f) Yes. A circuit that includes a current source meets the definition of a linear circuit (given above).

(g) Example of linear circuit



(h) Example of non-linear circuit

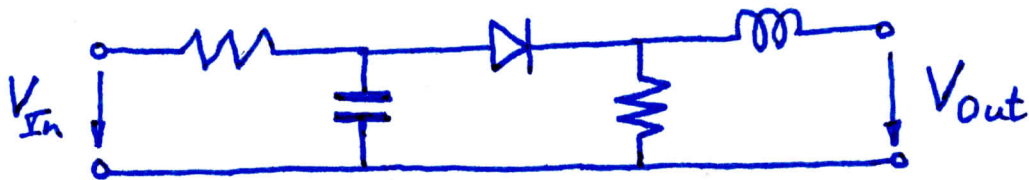

(i) The analysis of linear circuits is generally simpler. This is because a system of linear equations is generally simpler to solve than a system of non-linear equations (quadratic, exponential...)

### Problem 3: Superposition principle

- (a) A circuit must be a linear circuit to allow for the application of the superposition principle.
- (b) The total output of a linear circuit is the sum (superposition) of multiple individual outputs with each individual output being caused by an individual input.
- (c) Individual inputs and outputs
- $$\begin{aligned}\text{Input 1} &\Rightarrow \text{Output 1} \\ \text{Input 2} &\Rightarrow \text{Output 2} \\ \text{Input } i &\Rightarrow \text{Output } i\end{aligned}$$

Then

$$\underline{\underline{\text{Output} = \sum_i \text{Output } i}}$$

- (d) We cannot apply the Superposition Principle to non-linear circuits.