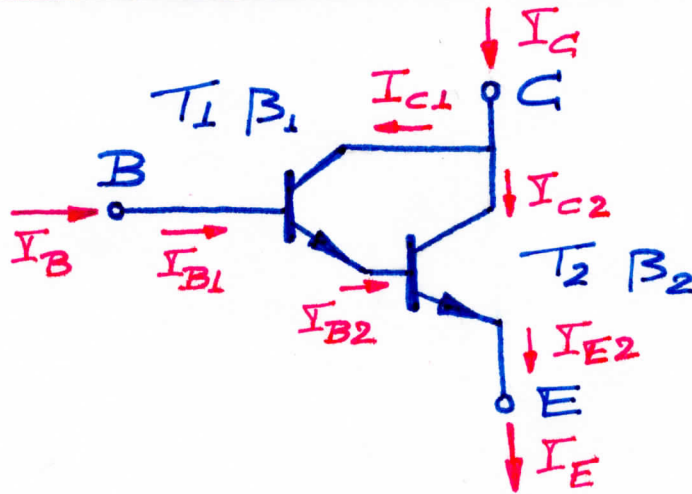


①

# Iconic circuit: Darlington transistor



⇒ Darlington transistor with **B**, **C** and **E**

⇒ Three-terminal device

⇒ Q: What is **BE** voltage of Darlington?

$$\Rightarrow V_{BE} = V_{BE1} + V_{BE2} = 0.7V + 0.7V = \underline{\underline{1.4V}}$$

Equations:

$$I_C = I_{C1} + I_{C2}$$

$$I_B = I_{B1}$$

$$I_E = I_{E2}$$

$$I_{E1} = I_{B2}$$

# Amplification

$$I_{E1} = I_{B1} (\beta_1 + 1)$$

$$\begin{aligned} I_{C2} &= I_{B2} \beta_2 \\ &= I_{B1} (\beta_1 + 1) \beta_2 \end{aligned}$$

$$\begin{aligned} I_C &= I_{C1} + I_{C2} \\ &= I_{B1} \beta_1 + I_{B1} (\beta_1 + 1) \beta_2 \\ &\quad \quad \quad \downarrow \text{ } I_B \\ &= I_B (\beta_1 \beta_2 + \beta_1 + \beta_2) \end{aligned}$$

$$\Rightarrow \boxed{\beta = \beta_1 \beta_2 + \beta_1 + \beta_2 \approx \beta_1 \beta_2}$$

$\rightarrow \beta$  of Darlington

Example:  $\beta_1 = 100 \quad \beta_2 = 80 \Rightarrow \beta \approx 8,000$

Note: Darlington has high current amplification

Darlington has BE voltage of 1.4V

Also note:

$$V_{CE2} = V_{BE2} + V_{CE1} \geq 0.9V$$

$\rightarrow \text{Saturation} \Rightarrow \approx 0.2V$

$T_2$  cannot enter saturation.

Can be an advantage for high-speed operation.

Q: Where are Darlington transistors used? ③

⇒ Amplifiers with high amplification

⇒ Audio amplifier

⇒ Cell phone RF amplifier  
↳ radio frequency