

# FET as an ON/OFF switch

①

Switch



ON

→ Closed

OFF

→ Open




ON


OFF

Switching loads (Motor, lights, TV, PC, electromagnet...)


\* ON and OFF (not dimmed)

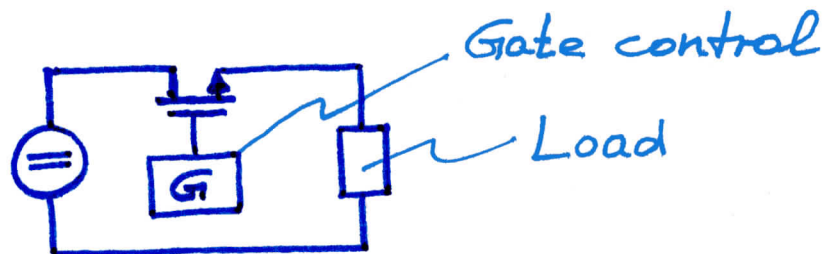

\* Dimming with a resistor

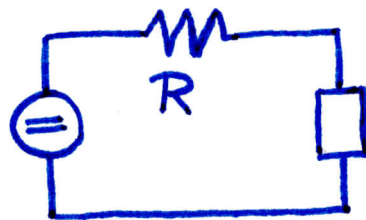

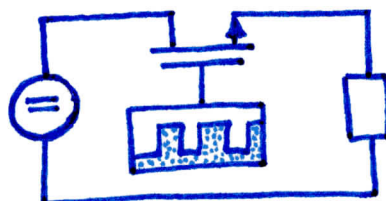\* Dimming with a switch (e.g.  $f = 1\text{kHz}$  50% duty cycle)




Q: Which of the two dimming methods is better? ②

⇒ Switched dimming is better because power is not wasted in a resistor.


⇒ We need a good switch

Perfect switch:  $R_{ON} = 0\Omega$   $R_{OFF} = \infty\Omega$

An FET can be used as a switch

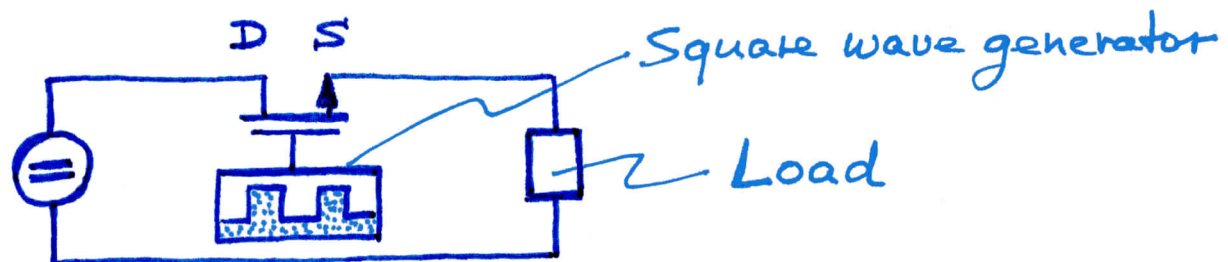

FET output characteristic

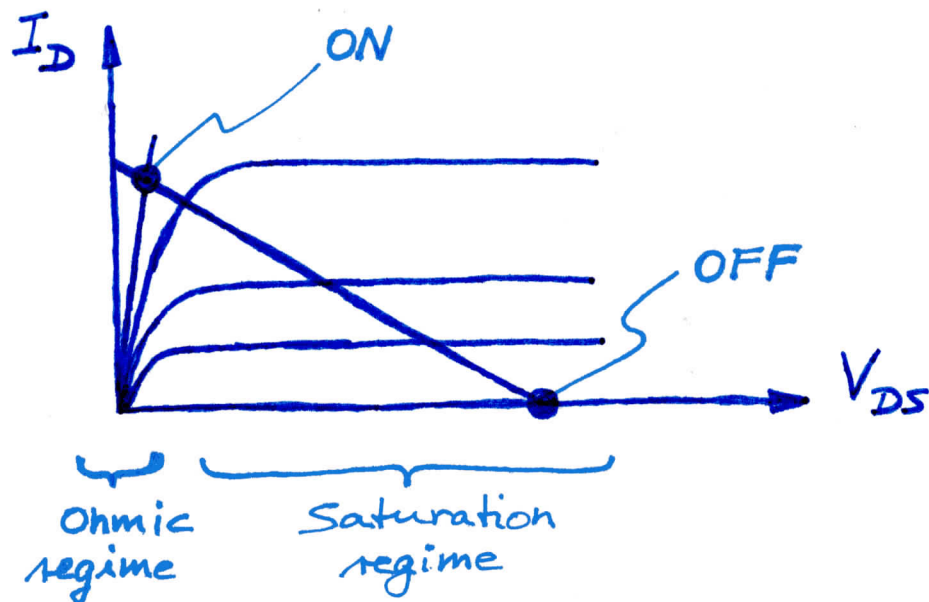

ON ⇒ Ohmic regime ⇒  $R_{ON}$

OFF ⇒ Saturation regime ⇒  $R_{OFF}$

## OFF state

FET operates in saturation regime

Recall:

$$I_D = \frac{1}{2} k (V_{GS} - V_{th})^2$$

$$V_{GS} < V_{th} \Rightarrow I_D = 0$$

$$\Rightarrow \boxed{R_{OFF} = \infty}$$

$\Rightarrow$  Perfect OFF state

## ON state

FET operates in ohmic regime

Recall:

$$I_D = k (V_{GS} - V_{th}) V_{DS}$$

$$\Rightarrow G_{ON} = \frac{1}{R_{ON}} = \frac{dI_D}{dV_{DS}} = k (V_{GS} - V_{th})$$

$$\Rightarrow \boxed{R_{ON} = \frac{1}{k (V_{GS} - V_{th})}}$$

$$\Rightarrow R_{ON} > 0 \Rightarrow \text{Not perfect}$$

(4)

Q: How can we minimize  $R_{ON}$  ?

$$\Rightarrow V_{GS} \gg V_{th}$$

$$\Rightarrow \text{Geometry of FET} \Rightarrow k = k' \frac{W_G}{L_G} \Rightarrow$$

Wide  $W_G$  and short  $L_G$  will increase  $k$  and decrease  $R_{ON}$ .

Example:

$$\text{Switching FET: } k = 10 \frac{\text{A}}{\text{V}^2} \quad V_{th} = 2 \text{ V}$$

$$\text{Choose } V_{GS} \text{ so that } R_{ON} = 10 \text{ m}\Omega = 0.01 \Omega$$

$$\text{Solution: } R_{ON} = \frac{1}{k(V_{GS} - V_{th})}$$

$$\Rightarrow V_{GS} = \frac{1}{k R_{ON}} + V_{th} = \frac{1}{10 \frac{\text{A}}{\text{V}^2} 10 \text{ m}\Omega} + V_{th}$$

$$= 10 \text{ V} + 2 \text{ V} = \underline{\underline{12 \text{ V}}}$$

Switching FETs (Switching MOSFETs) are <sup>⑤</sup>  
common in all kinds of appliances:

TV, Washing machine, Dryer, Cell phone,  
Cars, Lights, IOT, etc.

There is a transition

Mechanical switch  $\Rightarrow$  FET switch