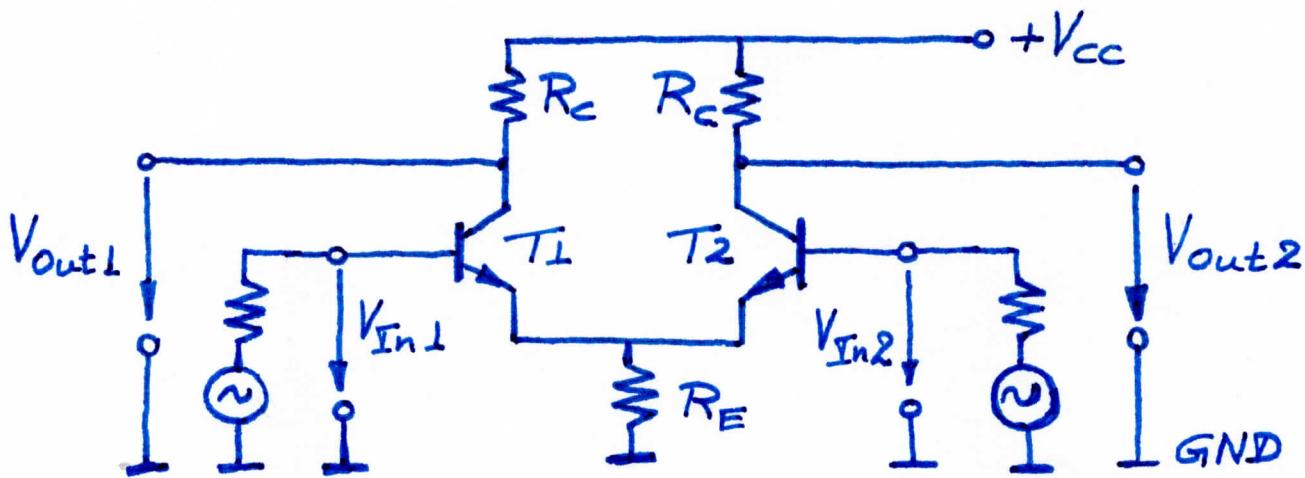


Ionic circuit: Differential amplifier

- * Differential amplifier is physical basis of Operational Amplifier (Op Amp).
- * Two inputs. Two outputs.
- * Amplifies difference in input voltages.




- * Emitters are coupled and share R_E .
- * 1 or 2 inputs (unused input can be grounded)
- * 1 or 2 outputs (unused output can be floating)
- * Two modes of operation

Common mode: $V_{In1} = V_{In2}$

Differential mode: $V_{In1} \neq V_{In2}$ Difference $\neq 0$

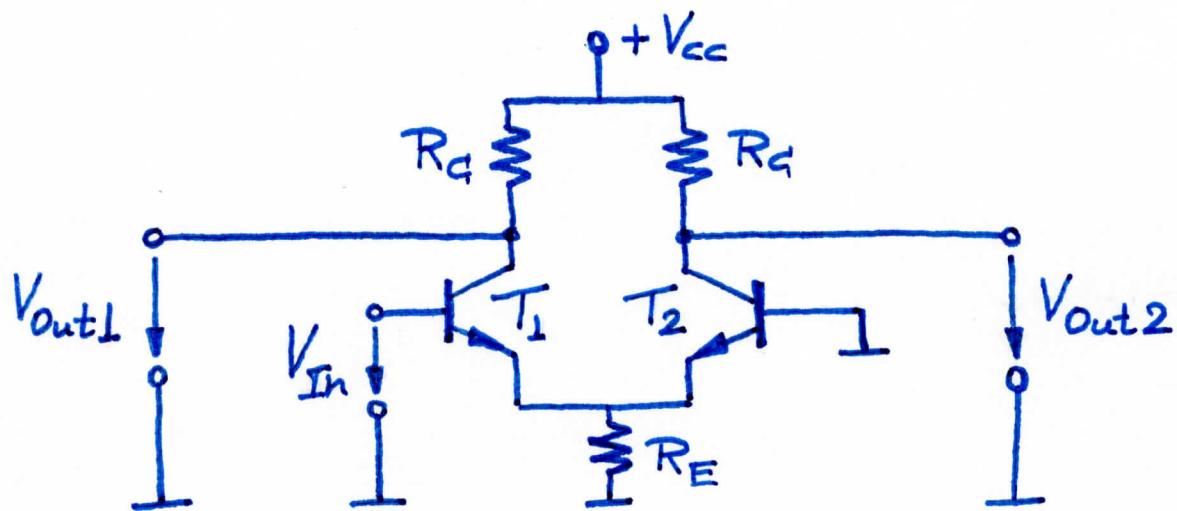
Inverting output and non-inverting output ②



Q: Which output is inverting output ?
⇒ Output 1 is inverting.

Q: Which output is non-inverting output
⇒ Output 2 is non-inverting.

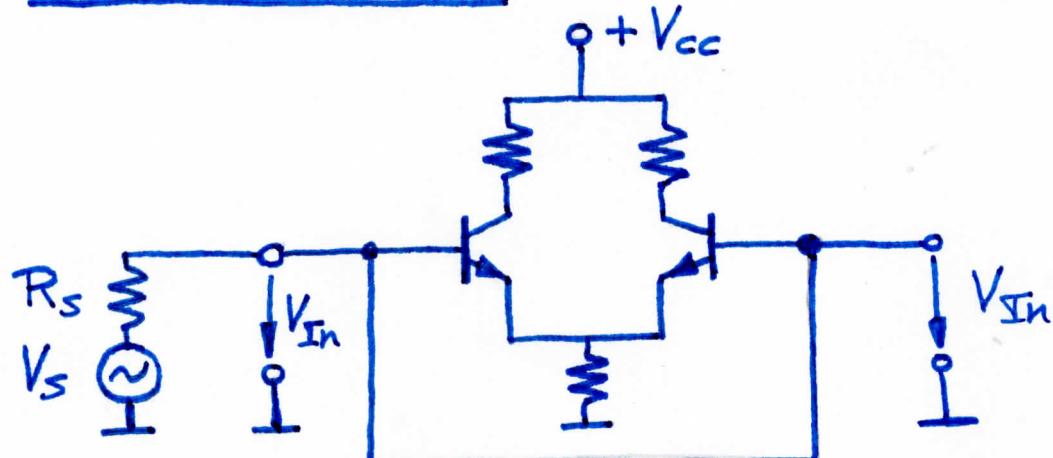
Common mode (CM): Both inputs at same voltage



$$\Rightarrow V_{in1} = V_{in2} = V_{in}$$


Input and output configurations

- * Single input & single output

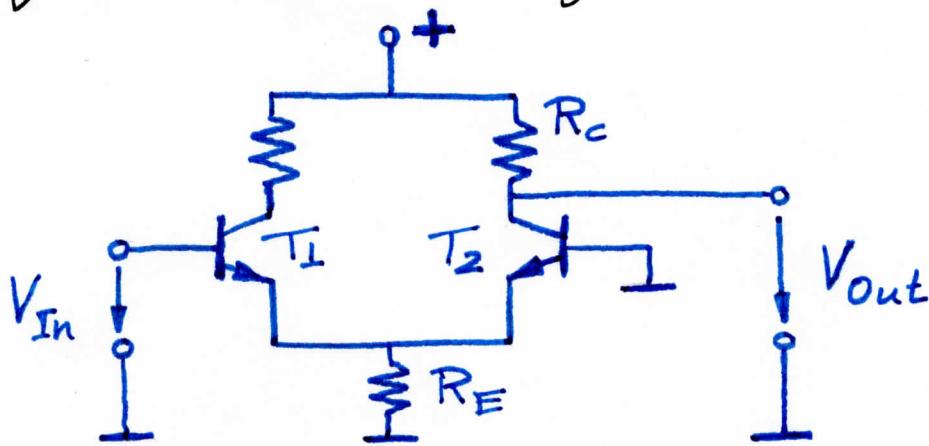


$$\Rightarrow \text{To be shown: } A = \frac{R_C}{2r_E}$$

- * Single input & differential output

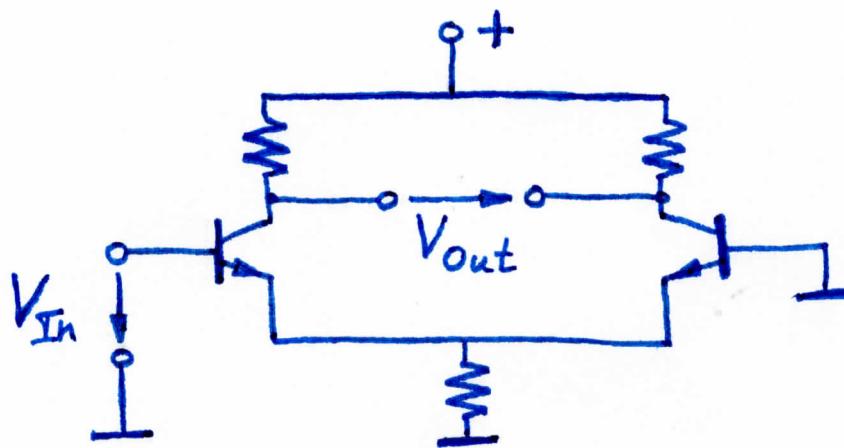


$$\Rightarrow \text{To be shown: } A = \frac{R_C}{r_E}$$

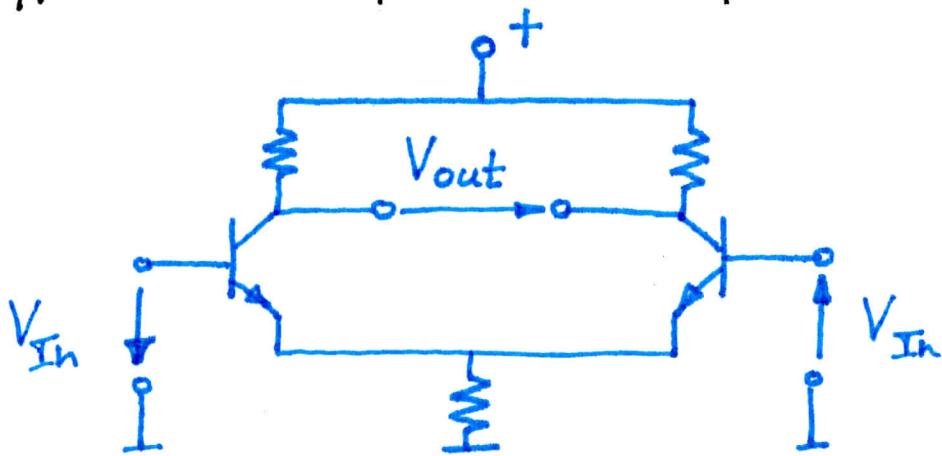* Differential input & differential output




\Rightarrow To be shown: $A = \frac{2R_c}{r_E}$

Note on input voltage representation

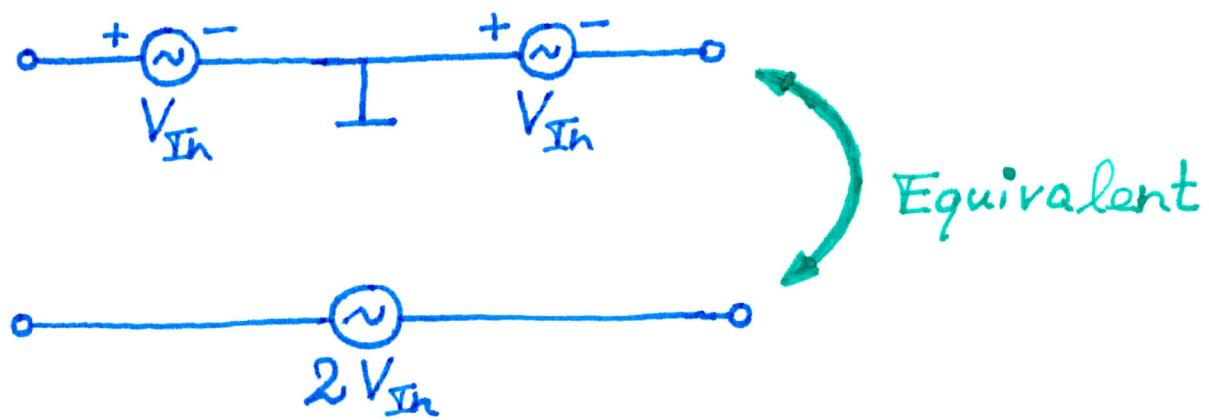

Quiescent point (Q-point)

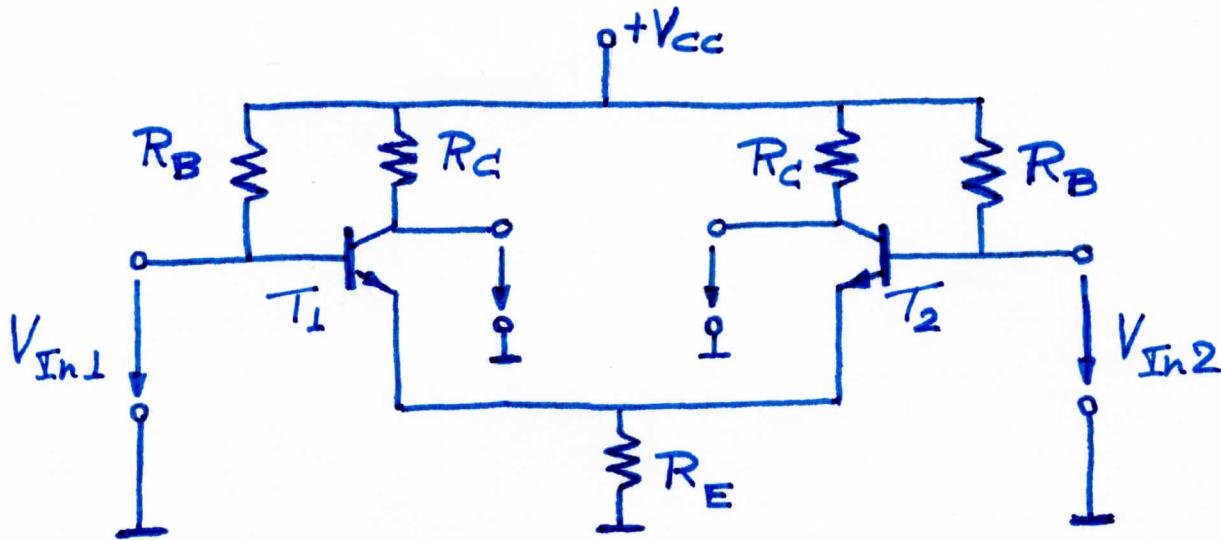

⇒ Symmetric circuit

$$\Rightarrow \text{Q-point: } I_{B1} R_B + V_{BE} + 2(\beta+1) I_{B1} R_E = V_{CC}$$

$$\Rightarrow I_{B1} = \frac{V_{CC} - 0.7V}{R_B + 2(\beta+1) R_E}$$

$$\Rightarrow I_{E1} = (\beta+1) I_{B1} \quad I_{C1} = \beta I_{B1}$$

$$\Rightarrow V_E = 2 I_{B1} (\beta+1) R_E$$

$$V_C = V_{CC} - \beta I_{B1} R_C$$

$$\Rightarrow V_{CE} = V_C - V_E = V_{CC} - \beta I_{B1} R_C - 2 I_{B1} (\beta+1) R_E \\ \approx V_{CC} - \beta I_{B1} (R_C + 2 R_E)$$

... this concludes our Q-point calculation.


Q: What would be a good value of V_{CE} ?

Qualitative discussion

* Common mode: $V_{In1} = V_{In2} \Rightarrow$ Due to symmetry of circuit $I_{C1} = I_{C2} \Rightarrow V_{out} = 0$
 $\Rightarrow \underline{\underline{A_{CM} = 0}}$

* Differential mode: Assume $V_{In1} \uparrow \Rightarrow$
 $\Rightarrow V_{BE1} \uparrow$ and $V_E \uparrow \Rightarrow V_{BE2} \downarrow \Rightarrow$
 $\qquad\qquad\qquad \text{L} \hookrightarrow \sim 0.7V \qquad\qquad\qquad \text{L} \hookrightarrow \sim 0.7V$
 $\Rightarrow I_{E1} \uparrow$ and $I_{E2} \downarrow \Rightarrow I_{C1} \uparrow$ and $I_{C2} \downarrow$
 $\Delta I_{C1} = \Delta I_{C2}$ due to linearization of circuit.
 \Rightarrow Current is "steered" through T_1 & T_2

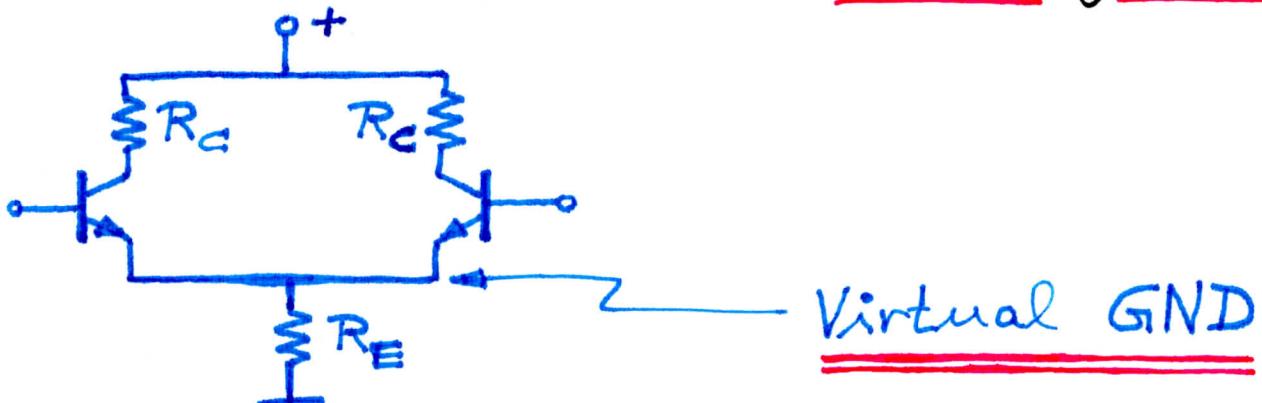* $I_{RE} = I_{E1} + I_{E2}$. Since $I_{E1} \uparrow$ and $I_{E2} \downarrow$
 (by same amount) $\Rightarrow I_{RE} = \text{constant} \Rightarrow$
 $V_{RE} = \text{constant} \Rightarrow V_E = \text{constant} \Rightarrow$ Emitters
 are at constant potential \Rightarrow "virtual ground"



Amplification


$$A_{CM} = \frac{V_{out}}{\frac{1}{2}(V_{in1} + V_{in2})} = 0 \quad (\text{already shown})$$

Single input & single output $A = \frac{V_{out1}}{V_{in1}} = ?$


Single input & differential output $A = \frac{V_{out1} - V_{out2}}{V_{in1}} = ?$

Differential input & output $A = \frac{V_{out1} - V_{out2}}{V_{in}} = ?$

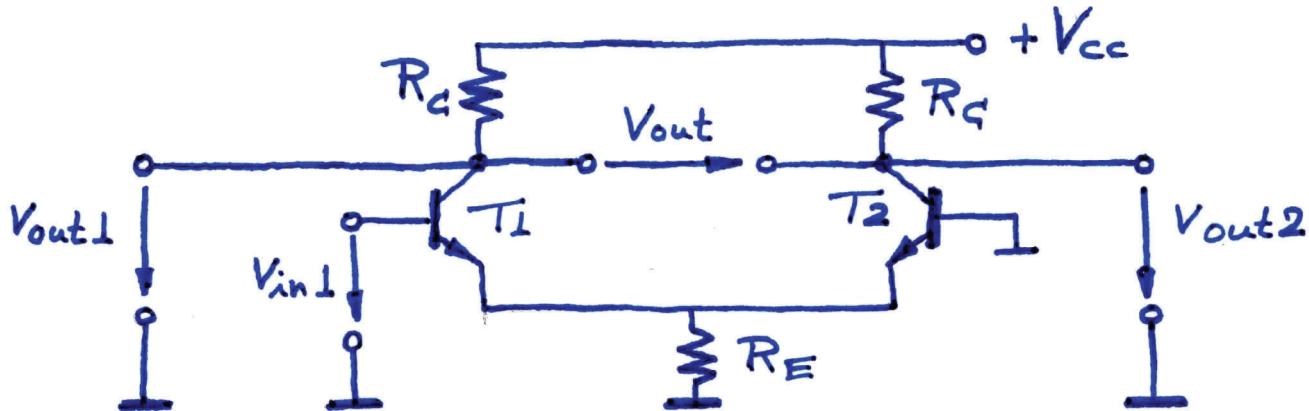Next, we consider single input & differential output
 \Rightarrow Circuit diagram



Small-signal equivalent circuit

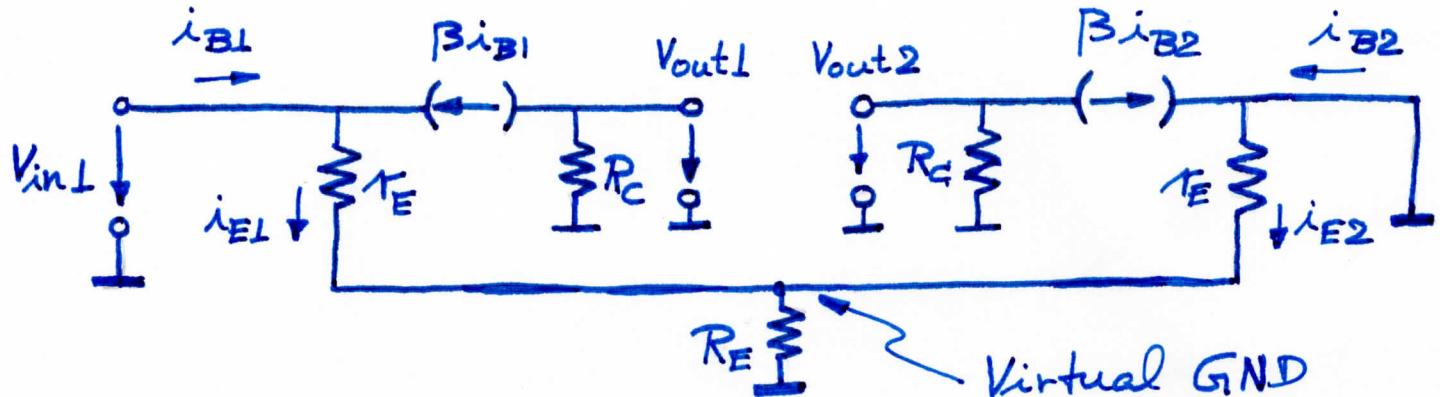

$$V_{out1} = \beta i_{B1} R_C$$

Virtual GND
 \Rightarrow constant potential
 $\Rightarrow V_{RE} = \text{constant}$
 \Rightarrow No small-signal current through R_E

$$V_{out2} = \beta i_{B2} R_C$$

$$V_{in1} = i_{E1} \tau_E + i_{E1} \tau_E = 2 i_{E1} \tau_E$$

$$A = \frac{V_{out1} - V_{out2}}{V_{in1}} = \frac{\beta i_{B1} R_C - \beta i_{B2} R_C}{2 i_{E1} \tau_E}$$

$$= \frac{2 \beta i_{B1} R_C}{2 (\beta + 1) i_{B1} \tau_E} \approx \frac{R_C}{\tau_E}$$

* Single input & single output: $A = \frac{R_C}{2 \tau_E}$ Why?

* Differential input & output: $A = \frac{2 R_C}{\tau_E}$ Why?

Summary table

Input	Output	Gain
single	single	$R_C/2 r_E$
single	differential	R_C/r_E
differential	differential	$2R_C/r_E$

Example: Consider a differential amplifier with differential input & output. $V_{cc} = 12V$. Assume $R_C = 500\Omega$ and $I_{C1} = 10mA$.

* Determine the voltage gain. $I_{E1} \approx I_{C1} = 10mA$

$$\Rightarrow r_E = \frac{V_t}{I_{E1}} = \frac{26mV}{10mA} = 2.6\Omega$$

$$\Rightarrow A = \frac{2R_C}{r_E} = \frac{1000\Omega}{2.6\Omega} = \underline{\underline{384}}$$

* What is the gain of a 2-stage amplifier?

$$\Rightarrow A = A_{1st\text{-stage}} \times A_{2nd\text{-stage}} = 384 \times 384 = \underline{\underline{148\,000}}$$

\Rightarrow Reasonable value for Op Amp.

Applications

- * Operational amplifier. The basic internal circuit of an Op Amp is a 2-transistor differential amplifier. Amplification of Op Amp $\approx 100,000$. Amplification of differential amplifier ≈ 200 . \Rightarrow Multiple stages needed.
- * Emitter-coupled logic (ECL). Also called current steering logic (CSL).
ECL is very fast. But: Power consumption is high. ECL consumes power at the quiescent point (Q-point).