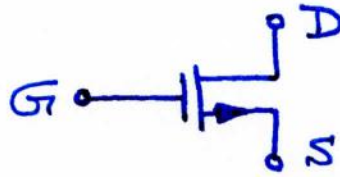


ITE - Homework 10 - Solution

Problem 1 FET linear amplifier circuits


(a) n-channel FET

Source = Source of electrons




⇒ Current flows out of the source


Small-signal equivalent circuit

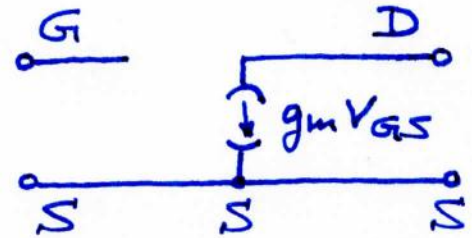

(b) Common-S amplifier

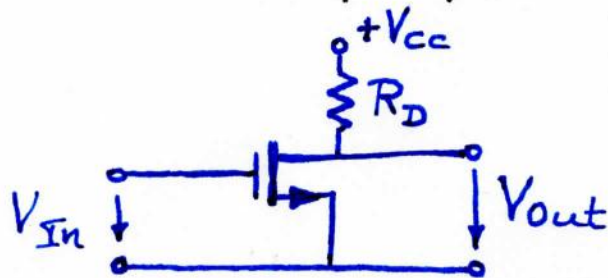

Equivalent circuit

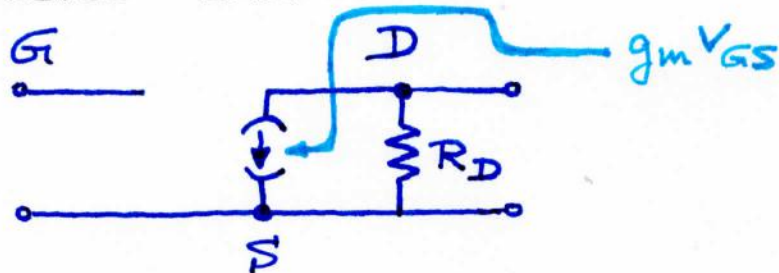


$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{0} = \underline{\underline{\infty}}$$

$$Z_{out} = \frac{V_{out}}{i_{out}} = \underline{\underline{R_D}}$$


$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{-g_m V_{GS} R_D}{V_{GS}} = \underline{\underline{-g_m R_D}}$$

$$A_{Isc} = \frac{i_{out}}{i_{in}} = \frac{g_m V_{GS}}{0} = \underline{\underline{\infty}}$$


(c) Common - D amplifier

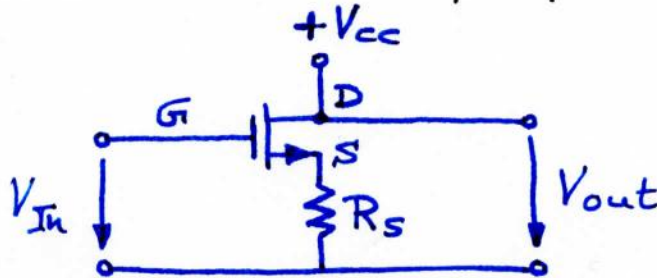

Equivalent circuit

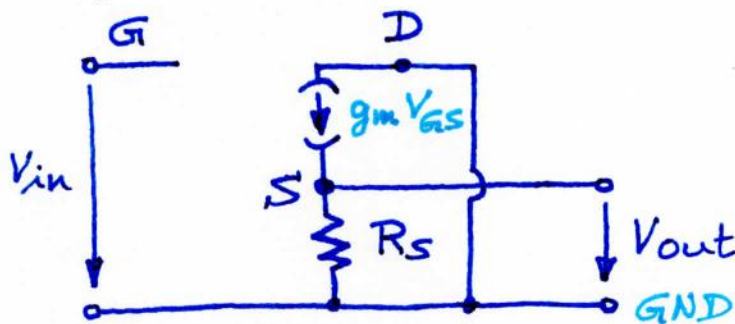

Redraw equivalent circuit

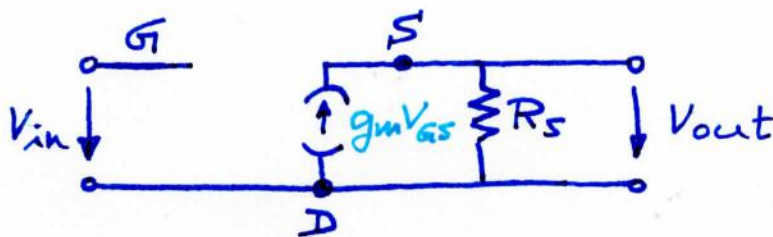

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{0} = \underline{\underline{\infty}}$$


$$Z_{out} = \frac{V_{out}}{i_{out}} = \underline{\underline{R_S}}$$

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{g_m V_{GS} R_S}{V_{GS} + g_m V_{GS} R_S} = \frac{g_m R_S}{1 + g_m R_S} \approx \underline{\underline{1}}$$


$$A_{Isc} = \frac{i_{out}}{i_{in}} = \frac{i_{out}}{0} = \underline{\underline{\infty}}$$

For large g_m or R_S

(d) Common - G amplifier

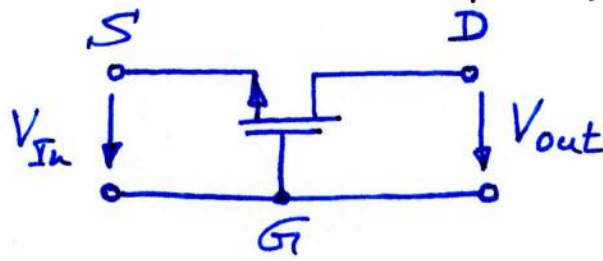

Equivalent circuit

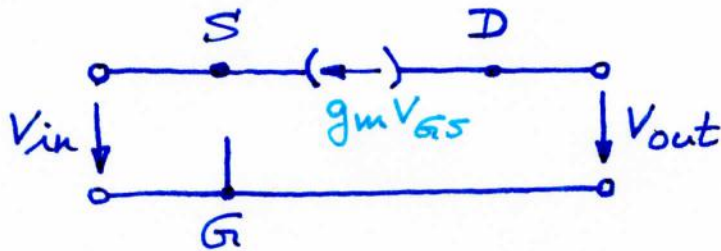

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{g_m V_{GS}} = \frac{V_{GS}}{g_m V_{GS}} = \underline{\underline{\frac{1}{g_m}}}$$

$$Z_{out} = \frac{V_{out}}{i_{out}} = \frac{\infty}{g_m V_{GS}} = \underline{\underline{\infty}}$$

Why is $V_{out} = \infty$? Circuit has an ∞ load resistance ($R_{Load} = \infty$). The voltage across the load is $g_m V_{GS} R_{Load} = \infty$

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{\infty}{V_{in}} = \underline{\underline{\infty}}$$

$$A_{isc} = \frac{i_{out}}{i_{in}} = \frac{i_D}{i_S} = \underline{\underline{1}}$$

(e) Table

	Common-S	Common-D	Common-G
Z_{in}	∞	∞	$1/g_m$
Z_{out}	R_D	R_S	∞
A_{voc}	$-g_m R_D$	1	∞
A_{isc}	∞	∞	1

(f) Lowest output impedance:
Common-S and common-D
 $\hookrightarrow R_D$ $\hookrightarrow R_S$

Yes, low output impedance is desirable

(g) Lowest input impedance:
Common-G
 $\hookrightarrow 1/g_m$

No, low input impedance is not desirable

(h) $A_{voc} \approx 1$

\Rightarrow Common-D configuration
 $\rightarrow = S$ follower

(i) Common-S and common-D configurations are the most useful ones.

They have no undesirable characteristics.

Problem 2

Miller capacitance

FET $k = 20 \frac{\text{mA}}{\text{V}^2}$ $V_{th} = 1.0\text{V}$ n-channel FET

(a) This is a common-source amplifier

$$\begin{aligned} \text{Voltage at } G \quad V_G = V_{GS} &= V_{CC} \frac{R_2}{R_1 + R_2} \\ &= 10\text{V} \frac{20\text{k}\Omega}{20\text{k}\Omega + 80\text{k}\Omega} = 10\text{V} \frac{20}{100} = \underline{\underline{2\text{V}}} \end{aligned}$$

Drain current

$$\begin{aligned} I_D &= \frac{1}{2} k (V_{GS} - V_{th})^2 = \frac{1}{2} 20 \frac{\text{mA}}{\text{V}^2} (2\text{V} - 1\text{V})^2 \\ &= \frac{1}{2} 20 \frac{\text{mA}}{\text{V}^2} (1\text{V})^2 = \underline{\underline{10\text{mA}}} \end{aligned}$$

(b) Choice of R_D

$$V_{RD} = V_{CC} - V_{DS} = 10\text{V} - 5\text{V} = 5\text{V}$$


$$R_D = \frac{V_{RD}}{I_{RD}} = \frac{5\text{V}}{10\text{mA}} = 0.5\text{k}\Omega = \underline{\underline{500\Omega}}$$

(c) Transconductance

$$\begin{aligned} \text{Recall } g_m &= k (V_{GS} - V_{th}) = 20 \frac{\text{mA}}{\text{V}^2} (2\text{V} - 1\text{V}) \\ &= 20 \text{ mA/V} = \underline{\underline{20 \text{ mS}}} \end{aligned}$$

→ S = Siemens

(d) AC small-signal circuit

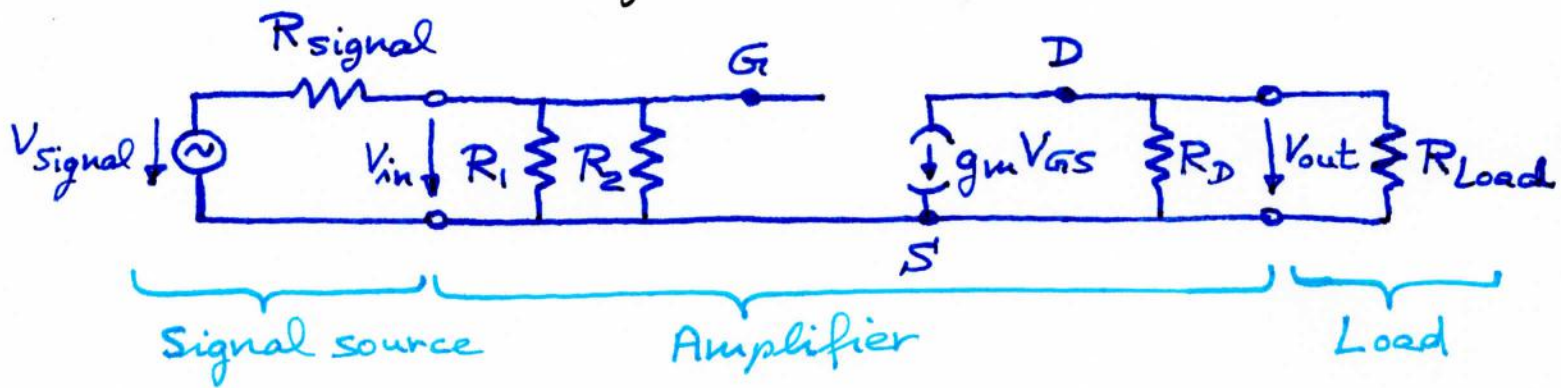

(e) Calculate A_{Voc} and A_V

$$A_{Voc} = \frac{V_{out}}{V_{in}} = \frac{g_m V_{GS} R_D}{V_{GS}} = \underline{\underline{g_m R_D}}$$

$$= 20 \text{ mS} \times 500 \Omega = \underline{\underline{10}}$$


$$R_{Load} = 1 \text{ k}\Omega$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{g_m V_{GS} (R_D \parallel R_{Load})}{V_{GS}} = \underline{\underline{g_m (R_D \parallel R_{Load})}}$$


$$= g_m (500 \Omega \parallel 1 \text{ k}\Omega) = 20 \text{ mS} \times 333 \Omega = \underline{\underline{6.66}}$$

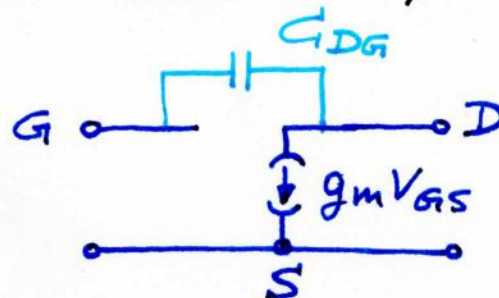(f) $C_{DG} \Rightarrow$ Physical capacitance between D & G.


This is a capacitance we can measure with a capacitance meter



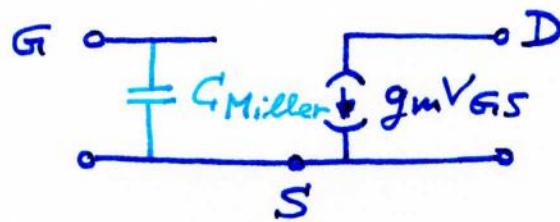$C_{\text{Miller}} \Rightarrow$ Equivalent capacitance relevant^⑧
("seen") at the input terminals
of the FET.



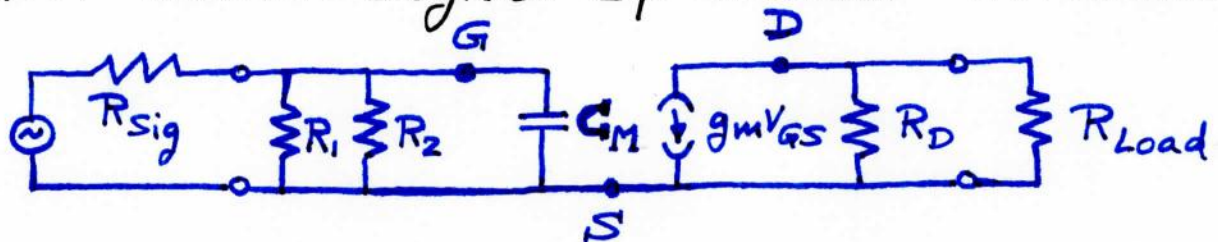(g) Cutoff frequency = 20 MHz
AC small-signal equivalent circuit



RC time constant. What is the relevant R ?
Through which resistors will C_M discharge?

$$R = R_1 \parallel R_2 \parallel R_{\text{signal}} = 80\text{k}\Omega \parallel 20\text{k}\Omega \parallel 5\text{k}\Omega$$

\hookrightarrow Relevant R

$$= \underline{\underline{3.81\text{k}\Omega}}$$

Recall $\omega_{\text{cutoff}} = \frac{1}{RC} = \frac{1}{\tau}$

$$\Rightarrow \tau = RC = \frac{1}{\omega_{\text{cutoff}}} = \frac{1}{2\pi f_{\text{cutoff}}} = \frac{1}{2\pi \cdot 20\text{MHz}}$$

$$= \frac{1}{126 \times 10^6 \frac{1}{\text{s}}} = \underline{\underline{7.94\text{ns}}}$$

(h) $\tau = RC_M \Rightarrow C_M = \frac{\tau}{R} = \frac{7.94\text{ns}}{3.81\text{k}\Omega} = \underline{\underline{2.08\text{pF}}}$

Recall $C_M = (1 + A_v) C_{DG}$

$$\Rightarrow C_{DS} = \frac{C_M}{1 + A_V} = \frac{2.08 \mu F}{1 + 6.66} = \underline{\underline{0.272 \mu F}} \quad (9)$$

(i) Yes. The common-D configuration does not suffer from the limitations of the Miller capacitance.