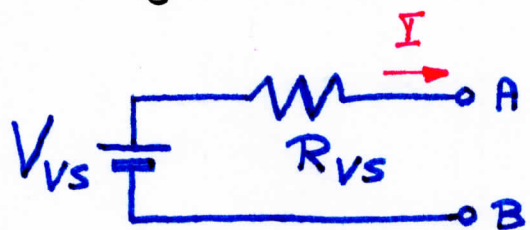


Equivalent sources


(Method 1)

①


Voltage source (VS)



$$V_{AB} = V_{VS} - I R_{VS}$$

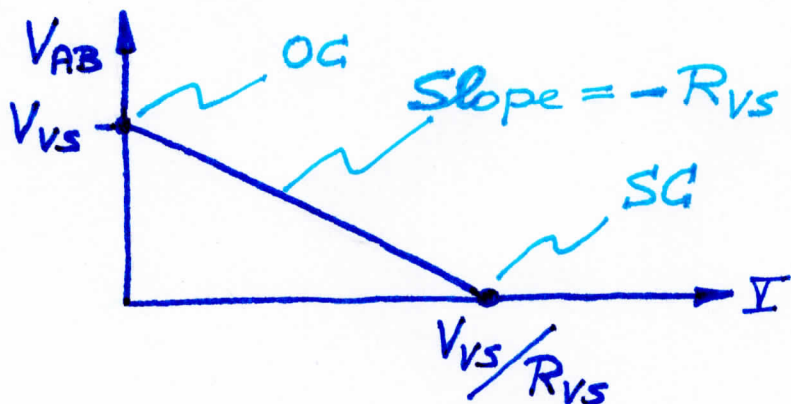


Current source

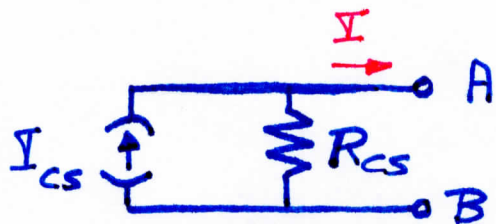

$$I = I_{CS} - V_{AB} / R_{CS}$$
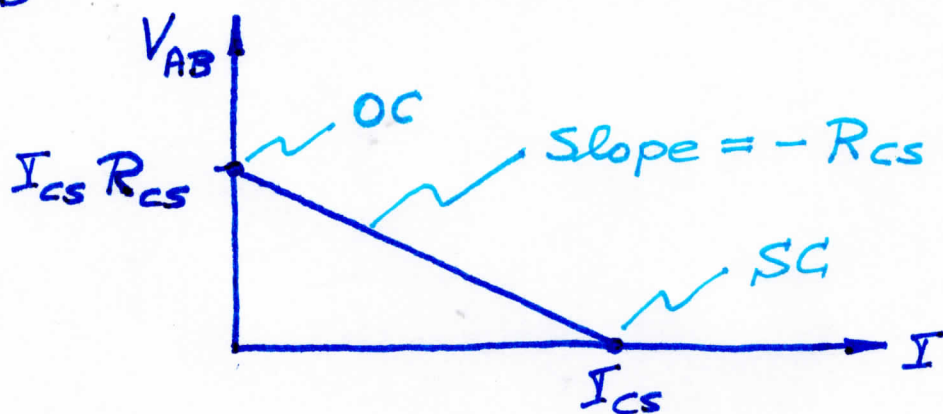
$$\Rightarrow V_{AB} = (I_{CS} - I) R_{CS}$$



If the two sources are equivalent, then their OC voltages and SC currents must be the same.

(2)

$$V_{VS} = I_{CS} R_{CS} \Rightarrow I_{CS} = V_{VS} / R_{CS}$$

OC voltages

$$I_{CS} = V_{VS} / R_{VS}$$

SC currents

Comparison of the last two eqns. yields



$$R_{VS} = R_{CS} = R$$

Internal resistance

"Looking into" the power sources, we "see" that they have the same internal resistance.

\Rightarrow Two equivalent power sources have the same internal resistance.

Complex source

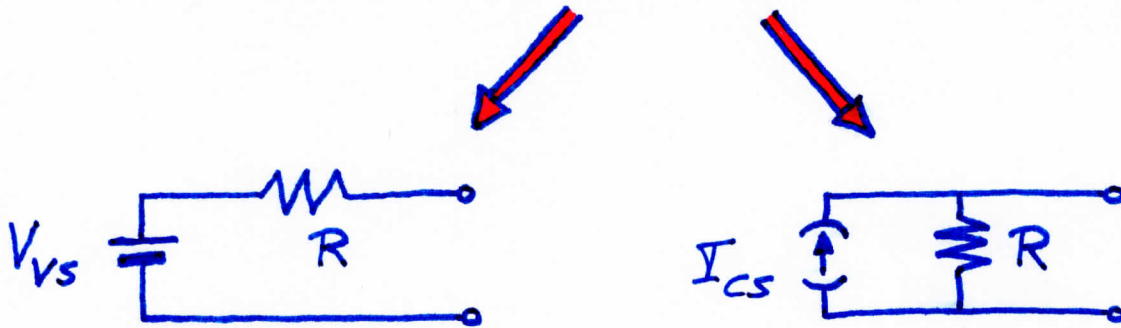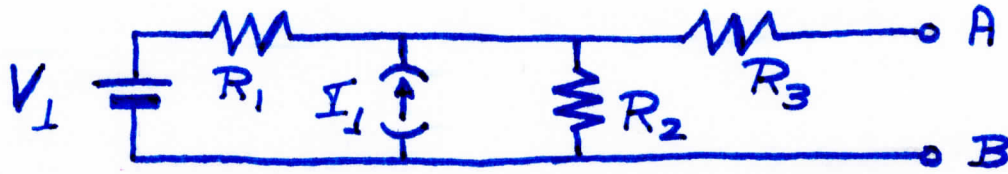

$$\Rightarrow R = R_3 + (R_1 \parallel R_2)$$

└ Internal resistance

Equivalent V source

$$V_{Vs} = V_{oc} \text{ of complex source}$$

Equivalent I source

$$I_{Cs} = I_{sc} \text{ of complex source}$$



Equivalent sources

(Method 2)



①

Any DC power source can be represented by a real voltage source (= ideal V source plus internal R) or a real current source (= ideal I source plus internal G)



Complex DC source

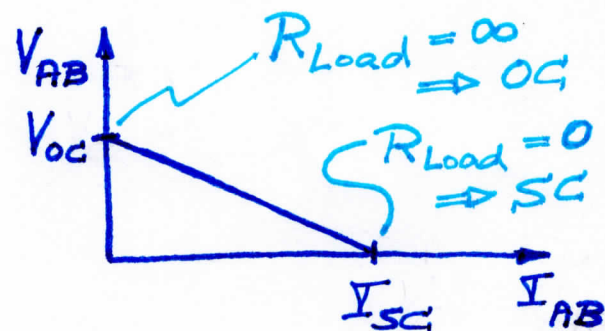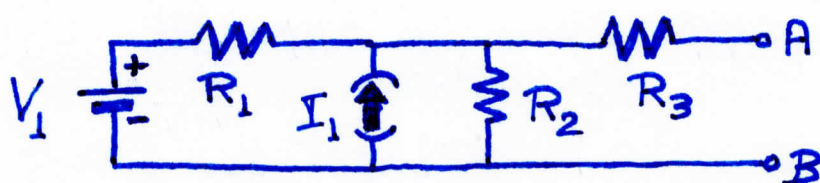

Equivalent V source

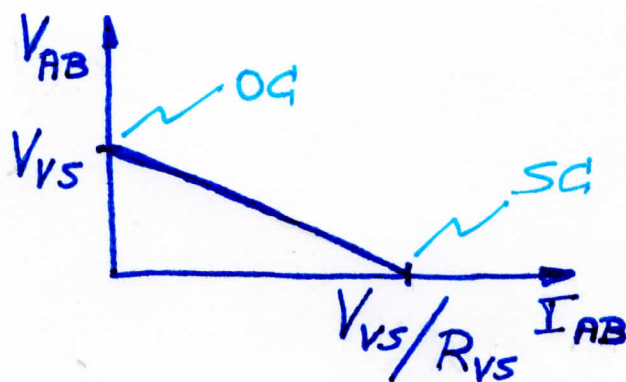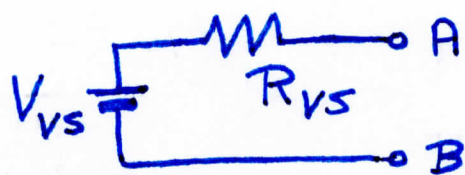

Equivalent I source

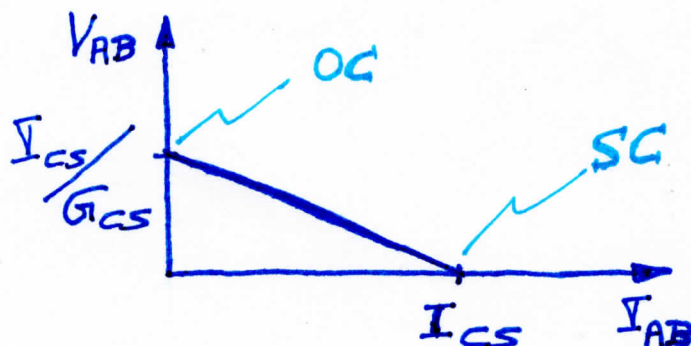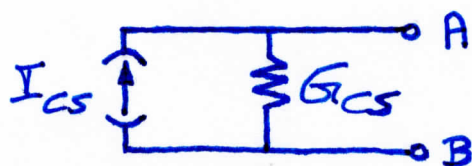

Voltage source (V_S) is equivalent if... (2)

$$\underline{V_{VS}} = V_{OC} \quad \rightarrow \text{of complex DC source}$$

$$I_{SC} = V_{VS} / R_{VS} \Rightarrow \underline{R_{VS}} = V_{VS} / I_{SC}$$

\rightarrow of complex DC source

Current source (G_S) is equivalent if...

$$\underline{I_{CS}} = I_{SC} \quad \rightarrow \text{of complex DC source}$$

$$V_{OC} = I_{CS} / G_{CS} \Rightarrow \underline{G_{CS}} = I_{CS} / V_{OC}$$

\rightarrow of complex DC source

Determination of V_{OC} \rightarrow of complex DC source

\Rightarrow Superposition principle

$\Rightarrow V_{OC} = \text{Effect of } V_1 + \text{Effect of } I_1$

$$\text{Effect of } V_1 = V_1 \frac{R_2}{R_1 + R_2}$$

$$\text{Effect of } I_1 = I_1 (R_1 \parallel R_2)$$

$$\Rightarrow \underline{V_{OC}} = V_1 \frac{R_2}{R_1 + R_2} + I_1 (R_1 \parallel R_2)$$

(3)

Determination of I_{sc} ~ of complex DC source

⇒ Superposition principle

⇒ $I_{sc} = \text{Effect of } V_1 + \text{Effect of } I_1$

Effect of V_1

$$\text{Ohm } V_1 = I_{R1} (R_1 + (R_2 \parallel R_3))$$

$$\text{Also: } I_{R2} R_2 = I_{R3} R_3 \Rightarrow I_{R2} = I_{R3} \frac{R_3}{R_2}$$

$$\begin{aligned} \Rightarrow V_1 &= I_{R1} (R_1 + (R_2 \parallel R_3)) \\ &= \left(I_{R3} \frac{R_3}{R_2} + I_{R3} \right) (R_1 + (R_2 \parallel R_3)) \\ &= I_{R3} \left(\frac{R_3}{R_2} + 1 \right) (R_1 + (R_2 \parallel R_3)) \end{aligned}$$

$$\Rightarrow I_{R3} = \frac{V_1}{\left(\frac{R_3}{R_2} + 1 \right) (R_1 + (R_2 \parallel R_3))}$$

Effect of I_1

$$\text{Current divider } I_{R3} = I_1 \frac{G_3}{G_1 + G_2 + G_3} \quad \sim 1/R_3$$

Total effect (due to V_1 and I_1) is the sum

$$\underline{I_{sc}} = \frac{V_1}{\left(\frac{R_3}{R_2} + 1 \right) (R_1 + (R_2 \parallel R_3))} + I_1 \frac{G_3}{G_1 + G_2 + G_3}$$

We now determined V_{oc} and I_{sc} of complex DC source

⇒ Equivalent V source (V_S)




$$\Rightarrow \underline{V_{VS}} = V_{oc}$$

$$\Rightarrow V_{VS} / R_{VS} = I_{sc}$$

$$\Rightarrow \underline{R_{VS}} = V_{VS} / I_{sc}$$

⇒ Equivalent I source (I_S)

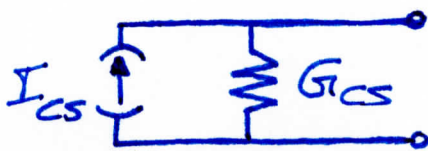

$$\Rightarrow \underline{I_{CS}} = I_{sc}$$

$$\Rightarrow V_{oc} = I_{CS} / G_{CS}$$

$$\Rightarrow \underline{G_{CS}} = I_{CS} / V_{oc}$$