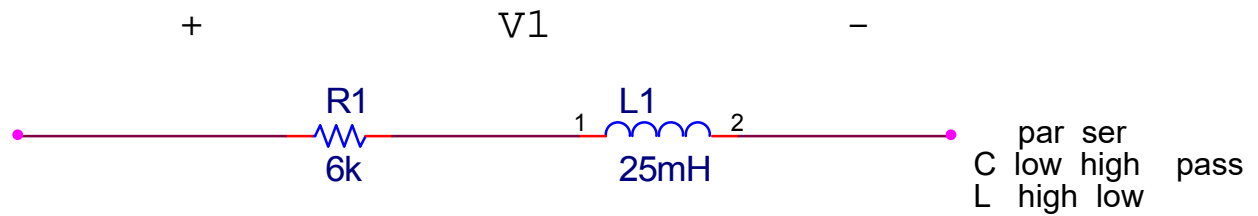


1) Equivalent circuits



1.1: For $I = 8\angle 45^\circ \text{mA}$ in phasor form with a 1.59kHz frequency, determine the voltage $V1$ in the time domain form.
 $\omega = 2\pi f$ $\omega = 10\text{k}$

$$Z = Z_R + Z_L = 6\text{k} + j \cdot 10\text{k} \cdot 25\text{m} = 6\text{k} + j250$$

$$V = I \cdot Z$$


$$V = 48.04 \angle 47.38$$

$$V = 48.04 \cdot \cos(10\text{E}3 \cdot t + 47.38)$$

$$d = r / (2\pi) \cdot 360$$

$$r = d / 260 \cdot 2\pi$$

2) First order circuits

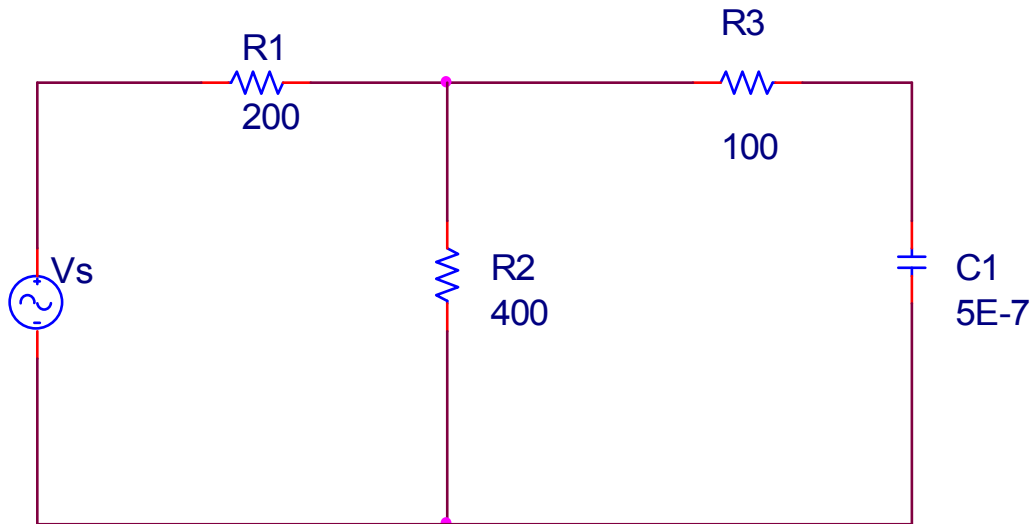

The source is a 10V sinusoidal signal with a frequency of 636.6Hz and has zero phase.
 $\omega = 4k$

2.1: Determine the phasor expression for the voltage source.

$$V = 10 \angle 0$$

2.2: Determine the equivalent impedance seen by the source.

$$Z = Z_1 + (Z_2^{-1} + (Z_3 + Z_C)^{-1})^{-1} = 468.18e^{-19.98j}$$

$$Z_C = 1 / (j \cdot 4E3 \cdot 5E-7)$$

2.3: Determine the phasor expression for the current through the source.


2.4: Determine the phasor expression for the voltage across C_1 .

2.5: Determine the time domain expression for the voltage across C_1 .

2.6: Determine the transfer function, $H(s) = V_{C1}(s) / V_s(s)$, for the above RC circuit.

2.7: Verify your solution to part d. using the transfer function (remember $s = j\omega$ in AC steady state).

3) Phasors- RLC

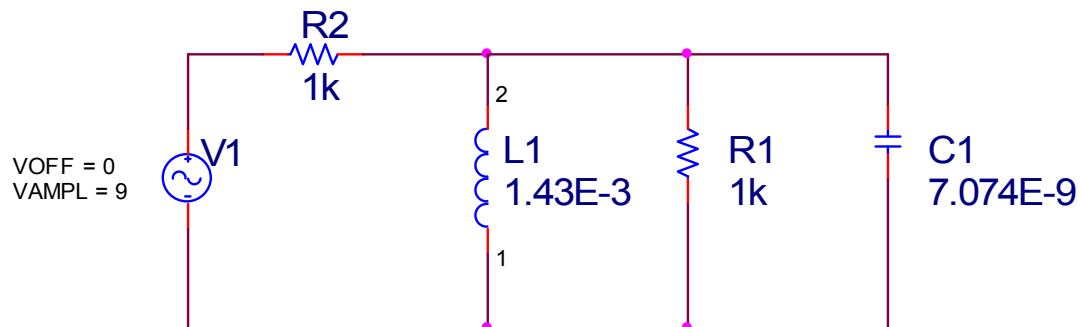


3.1: Using phasor analysis, determine the voltage across the capacitor when the source is 50kHz.

3.2: Using phasor analysis, determine the voltage across the capacitor when the source is 50 Hz.
(reminder: -90degrees is -j) **Partial answer check: $Z_{RLC} = 0.45j$**

3.3: Using phasor analysis, determine the voltage across the capacitor when the source is 50MHz
(50E6Hz).(reminder: 90degrees is j)

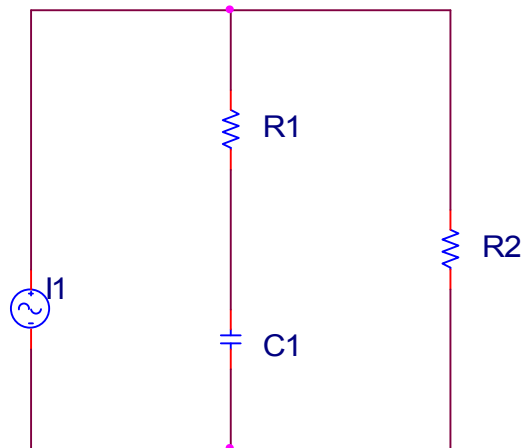4) Transfer functions


Determine the transfer functions in the following circuit. Determine the behavior of the transfer function as $\omega \rightarrow 0$ and $\omega \rightarrow \infty$



4.1: Voltage across C1 relative to the source voltage $H(s) = \frac{V_{C1}(s)}{I_1(s)}$
Using the current divider formula (then ohms law)

4.2: Determine the magnitude of the transfer function as frequency approaches zero, $|H(s \rightarrow 0)|$

4.3: Determine the magnitude of the transfer function as frequency approaches infinity, $|H(s \rightarrow \infty)|$

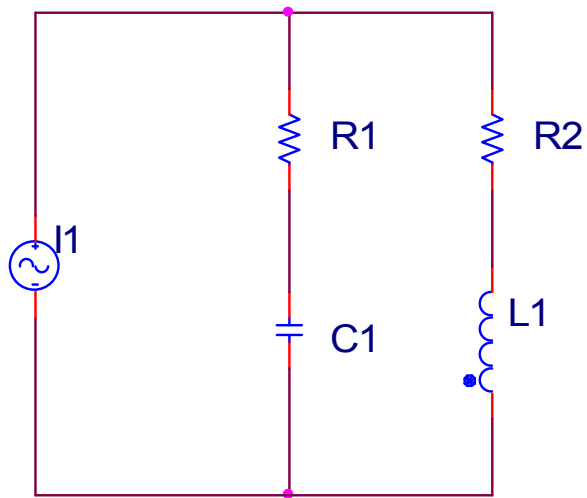

4.4: Voltage across L_1 relative to the source current $H(s) = \frac{V_{L1}(s)}{I_1(s)}$

4.5: Determine the magnitude of the transfer function as frequency approaches zero, $|H(s \rightarrow 0)|$

4.6: Determine the magnitude of the transfer function as frequency approaches infinity, $|H(s \rightarrow \infty)|$