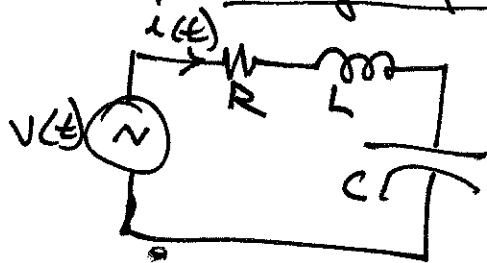


ECSE 2110 Elec. Energy Systems

Final Examination, Spring 2018
May 8, 2018, LOW 3051, 3-6 PM


① ① Single-phase AC Circuit

$$V(t) = 100 \sin(\omega t)$$

$$R = 1 \Omega, L = 1 \text{ mH}, C = 10 \mu\text{F}$$

- ⑩ (i) $\omega = 100 \text{ rad/sec}$, Calculate $i(t)$, $S = P + jQ$
(ii) $\omega = 10000$ " " " "

Explain the differences in the two results.

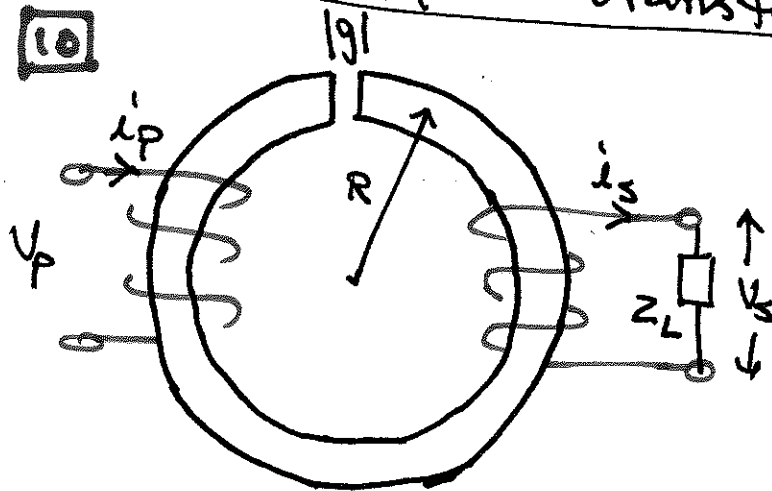① ② Coupled Transformer

$$R = 10 \text{ cm}, g = 1 \text{ mm}$$

$$\text{Core cross-section} = 2 \text{ cm}^2$$

$$\mu_r = 1000, \omega = 300 \text{ rad/sec.}$$

- Neglect leakage flux.
- " flux fringing at gap.
- " core & copper losses

$$V_p(t) = 100 \sin(\omega t)$$

$$N_p/N_s = 0.2, N_p = 1000, N_s = 5000$$


- (i) Calculate magnetizing current ($i_{p \text{ no load}}$) i.e. open secondary (wdg)
(ii) For $Z_L = 10 \Omega$, calculate i_s, i_p

(2) Synchronous Motor

300 kW, 480 V, Y-connected, $X_s = 1 \Omega$, $R_A \approx 0$, 8 pole, 60 Hz
Assume P_{FW} , P_{core} , P_{LL} are negligible

- (a) Motor is operating at rated load and 0.9 lagging pf.
Calculate E_A , I_A , Torque, Max Torque
- (b) If $|E_A|$ is increased by 20%, how do E_A , I_A , Torque, Torque(max) change?

(3) Transmission Lines $T = 40^\circ C$


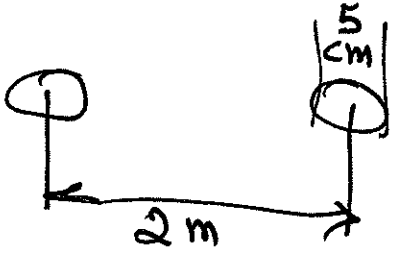
(25)  $S_{DOL} = 2 \times 10^{-8} \Omega \cdot m$, $M = 250$
 $R_{AC} = (1.05) R_{DC}$, $f = 60 \text{ Hz}$, $V_S = 8 \text{ kV}$
Length = 100 km

- (a) Calculate R, L, C for the overhead single-phase line
(b) Calculate the A, B, C, D constants and then calculate the line charging current for short, medium and long lines.

RLC \rightarrow (5)

ABCD \rightarrow $\begin{matrix} 2.5 \\ 5 \\ 7.5 \end{matrix}$ } Charging (5)

④ Wind power

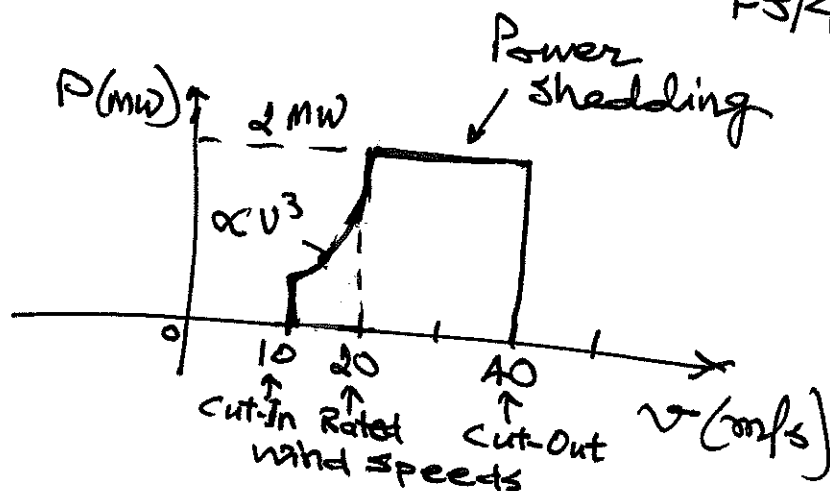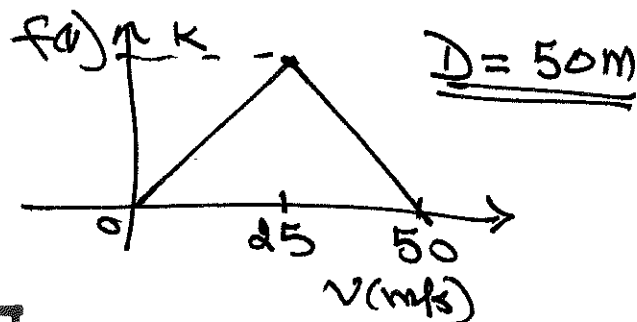


24

- Calculate K
- " $(V_{av})^3$ and $(V^3)_{av}$. Compare.
- P_{av} in wind assuming $15^\circ C$ and 1 ATM
- Energy delivered by wind turbine in a year assuming efficiency @ $V = 20 \text{ m/s}$ valid from $V = 10$ to 20 m/sec .
- Maximum energy wind turbine can deliver in a year.

⑤ Solar Energy

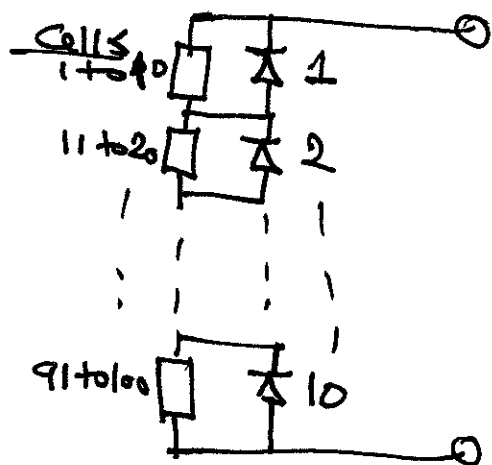100 solar cells are connected in series to form a module. A bypass diode is connected to a sub-module consisting of 10 cells in series (to save cost).



$$T = 50^\circ C$$

$$I_{sc} = 4 \text{ A}, I_0 = 10^{-9} \text{ A}, V_d = 0.5 \text{ V}, R_p = 10 \Omega, R_s = 0.01 \Omega$$

$$V_{d \text{ bypass}} = 0.6 \text{ V}$$

Calculate

I_0, V_{module} and Power for

- Healthy system
- Two shaded cells covered by the same bypass diode
 - without bypass diode
 - with "

5(c) Two shaded cells, each belonging to different sub-modules i.e. they do not share the same bypass diode

- (i) without bypass diode
- (ii) with " "

F4/4

Hint: Answers to b(i) and c(i) are the same.

$$V = \frac{100}{\sqrt{2}} \angle 0$$

$$R = 1 \Omega, L = 10^{-3} \text{ H}, C = 10^{-5} \text{ F}$$

$$\textcircled{1} V = I(R + j\omega L - \frac{j}{\omega C})$$

$$\textcircled{1} \omega = 100 \text{ rad/sec}$$

$$I = \frac{\frac{100}{\sqrt{2}} \angle 0}{1 + j100 \times 10^{-3} - \frac{j}{100 \times 10^{-5}}} = \frac{70.71 \angle 0}{1 + j(0.1 - 10^3)} = \frac{70.71 \angle 0}{1 - j999.9}$$

$$I = 7.0725 \times 10^{-5} \angle 0 + j 7.071768 \times 10^{-2} = 0.070718 / 89.943^\circ \angle 0 = 0.001 \sin(\omega t + 89.943^\circ)$$

$$S = VI^* = (70.71 \angle 0)(7.0725 \times 10^{-5} \angle 0 - j 7.072 \times 10^{-2}) = 5.001 \times 10^{-3} - j 5.0005 (P + jQ)$$

$$\textcircled{II} \omega = 10000 \text{ rad/sec}$$

$$I = \frac{70.71 \angle 0}{1 + j10^4 \times 10^{-3} - \frac{j}{10^4 \times 10^{-5}}} = \frac{70.71 \angle 0}{1 + j10 - j10} = \frac{70.71 \angle 0}{1}$$

$$\textcircled{II} I = 70.71 \angle 0 \text{ Amps} \Rightarrow i(t) = 100 \sin(\omega t) \text{ A}$$

$$S = VI^* = 70.71 \angle 0 * 70.71 \angle 0 = 5 \times 10^3 + j0 = P + jQ$$

The low frequency ($\omega = 100$) increased the capacitive reactance to reduce the current magnitude with virtually a 90° leading current. As frequency increased ($\omega = 10000$), it coincided with L-C series resonance and reduced impedance down to its resistance value enabling source to deliver real power at unity pf.

$$Q = \frac{l}{\mu_0 A} + \frac{l_{Fe}}{\mu_0 \mu_r A}$$

$$= \frac{10^{-3}}{\mu_0 \times 2 \times 10^{-4}} + \frac{0.2\pi - 10^{-3}}{\mu_0 \times 10^3 \times 2 \times 10^{-4}}$$

$$\therefore Q = \frac{1}{\mu_0} [5 + \pi - 5 \times 10^{-3}] = \frac{(4.995 + \pi)}{\mu_0}$$

$$l = 1 \text{ mm} = 10^{-3} \text{ m}$$

$$A = 2 \text{ cm}^2 = 2 \times 10^{-4} \text{ m}^2$$

$$l_{Fe} = (2 \times \pi \times 10 - 0.1) \times 10^{-2} \text{ m}$$

$$\mu_r = 1000$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$\omega = 300 \text{ rad/sec}$$

$$L = N^2 P = (1000)^2 \times \frac{4\pi \times 10^{-7}}{(4.995 + \pi)} = \frac{0.4\pi}{4.995 + \pi} = \underline{\underline{0.15444 \text{ H}}}$$

$$X_m = \omega L = 300 \times L = \frac{120\pi}{4.995 + \pi} = \underline{\underline{46.3328 \Omega}}$$

$$V_p = \frac{100}{\sqrt{2}} = 70.71 \text{ V}$$

$$(i) \text{ } I_{\text{magnetizing}} = \frac{70.71}{j 46.3328} = -j 1.526147 \text{ Amps}$$

$$I_p = 2.1583 \sin(\omega t - 90^\circ)$$

primary side

$$(ii) V_p = \frac{100}{\sqrt{2}} = 70.71 \text{ V}, \frac{N_p}{N_s} = 0.2 \Rightarrow V_s = \frac{500}{\sqrt{2}} = 353.55 \text{ V}$$

$$Z_L = R_L = 10 \Omega \Rightarrow I_s = \frac{500/\sqrt{2}}{10} = \frac{50}{\sqrt{2}} \text{ Amps} = \underline{\underline{35.35534 \text{ A}}}$$

$$I_s(t) = 50 \sin(\omega t)$$

secondary side

$$\text{Then } I_s' = \frac{I_s}{a} = \frac{50/\sqrt{2}}{0.2} = 250/\sqrt{2} \text{ Amps} = \underline{\underline{176.7767 \text{ Amps}}}$$


$$\therefore I_p = \left(\frac{250}{\sqrt{2}} - j 1.526147 \right) = \underline{\underline{176.7833 \angle -0.4946^\circ}}$$

$$I_p(t) = \underline{\underline{250.00932 \sin(\omega t - 0.4946^\circ)}}$$

primary side

② 300 kW, 480V, Y-connected, $X_s = 1 \Omega$, $R = 0$, 8 pole, 60 Hz
(Negligible losses) Syn. motor

(a) Rated load @ 0.9 lagging pf

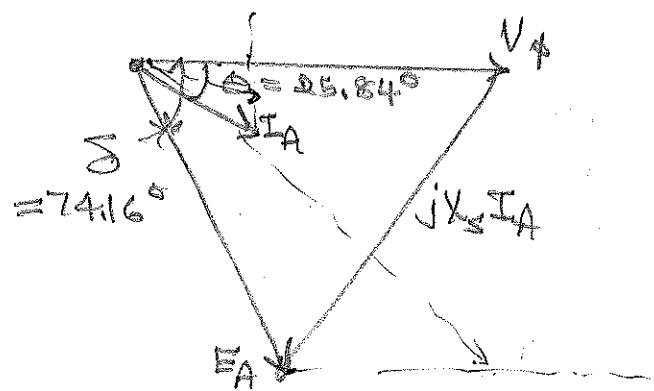

$$\begin{aligned} \bar{E}_A &= \bar{V}_\phi - jX_s \bar{I}_A \\ &= 160\sqrt{3} \angle 0^\circ - \frac{1 \times 1000}{1.44\sqrt{3}} \angle 90 - \cos^{-1}(0.9) \\ &= 375.08 \angle -74.1625^\circ \end{aligned}$$

$$\begin{aligned} V_\phi &= \frac{480}{\sqrt{3}} \angle 0^\circ = 277.13 \angle 0^\circ \\ I_A &= \frac{300 \times 10^3}{\sqrt{3} \times 480 \times 0.9} \angle -\cos^{-1}(0.9) = \frac{1000}{1.44\sqrt{3}} \angle -\cos^{-1}(0.9) = 400.94 \angle -25.84^\circ \end{aligned}$$

$$\begin{aligned} T_{\text{orque}} &= \frac{P}{\omega_m}, \quad \omega_m = \frac{\pi}{30} \times \frac{f_p \times 120}{P} = \frac{\pi}{30} \times \frac{60 \times 120}{8} = 30\pi \text{ rad/sec} \\ &= \frac{300 \times 10^3}{30\pi} = \frac{10^4}{\pi} = \underline{\underline{3183.1 \text{ N-m}}} \end{aligned}$$

$$T_{\text{max}} = \frac{T_{\text{orque}}}{\sin(74.16)} = \underline{\underline{3308.7 \text{ N-m}}}$$

(b) $|E_A|$ increased by 20%

Since $P = \frac{3V_\phi \cdot E_A}{X_s} \cdot \sin \delta$ is a constant, $E_A \sin \delta_1 = E_A \sin \delta_2$


$$\sin \delta_2 = \left(\frac{E_{A1}}{E_{A2}} \right) \sin \delta_1 = \frac{\sin(74.16)}{1.2} = 0.8017 \Rightarrow \delta_2 = \underline{\underline{53.293^\circ}}$$

$$\bar{I}_A = \frac{\bar{V}_\phi - \bar{E}_A}{jX_s} = \frac{277.13 \angle 0^\circ - 375.08 \times 1.2 \angle -53.293^\circ}{1 \angle 90^\circ} = \underline{\underline{360.9346 \angle -1.285^\circ}}$$

Torque remains the same = 3183.1 N-m

$$T_{\text{max}} = \frac{T_{\text{orque}}}{\sin(53.293)} = \underline{\underline{3970.44 \text{ N-m}}} \rightarrow \text{an improvement as } \delta \text{ reduced!}$$

3.

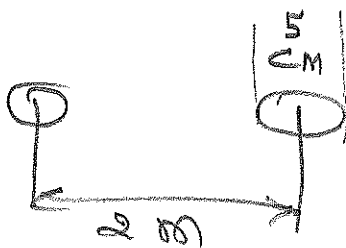

4/10

$$\epsilon_{20^\circ\text{C}} = 2 \times 10^{-8} \text{ } \Omega\text{-m}, M = 250$$

$$R_{AC} = (1.05) R_{DC}, f = 60 \text{ Hz}, V_s = 8 \text{ kV}$$

$$\text{Length} = 100 \text{ km}, T = 40^\circ\text{C}$$

$$= 10^5 \text{ m}$$

(a) R, L, C

Resistance

$$R_{DC} = \frac{58 \times 10^{-8} \times 100 \times 10^3}{\frac{\pi}{4} (5 \times 10^{-2})^2}$$

840°C

$$= \frac{250 + 40}{250 + 20} \times (2 \times 10^{-8}) \text{ } \Omega\text{-m}$$

$$= \frac{58}{27} \times 10^{-8} \text{ } \Omega\text{-m}$$

$$= \frac{58 \times 1.6}{27 \pi} \text{ } \Omega = 1.034 \text{ } \Omega \Rightarrow R_L = (1.05) R_{DC} = 1.15 \text{ } \Omega$$

Inductance

$$L = \frac{\mu}{\pi} \left[\frac{1}{4} + \ln\left(\frac{D}{r}\right) \right] \times 10^5 \text{ H}$$

$$\begin{cases} D = 200 \text{ cm} \\ r = 5/2 = 2.5 \text{ cm} \end{cases}$$

$$= \frac{4 \times 10^{-7} \times 10^5}{\pi} \left[0.25 + \ln\left(\frac{2}{0.025}\right) \right]$$

$$= 0.04 [0.25 + \ln(80)] = 0.185281 \text{ H}$$

Capacitance

$$C = \frac{\pi \epsilon}{\ln(D/r)} \times l = \frac{\pi \times 8.854 \times 10^{-12}}{\ln(80)} \times 10^5 = 6.35 \times 10^{-7} \text{ F}$$

(b) Short line

$$A=1, B=Z=R+jX_L, C=0, D=1$$

$$= 1.15 + j120\pi \times 0.185281$$

$$= 1.15 + j69.85 = 69.86/89.06^\circ$$

Medium line

$$A=D = \frac{Z^2}{2} + 1 = \frac{69.86/89.06 \times 2.392 \times 10^3}{2} + 1$$

$$Y = j\omega C$$

$$= j120\pi \times 6.35 \times 10^{-7}$$

$$= j2.392 \times 10^{-4}$$

$$= 0.99164 \angle 0.008^\circ$$

$$\underline{B = Z = 69.86/89.06^\circ}$$

$$C = Y \left(\frac{Z^2}{4} + 1 \right) = j 2.393 \times 10^{-4} \left[\frac{69.86/89.06^\circ * 2.393 \times 10^{-4}/90}{4} + 1 \right]$$

$$= \underline{2.383 \times 10^{-4} / 90.004^\circ}$$

Long line

$$A = D = \cosh(\gamma d)$$

$$\gamma = \sqrt{ZY}$$

$$B = Z_c \sinh(\gamma d)$$

$$Z_c = \sqrt{\frac{Z}{Y}}$$

$$C = \frac{1}{Z_c} \sinh(\gamma d)$$

$$\underline{d = 100 \text{ km}}$$

$$Z = 0.6986/89.06^\circ \text{ } \Omega/\text{km} \quad Y = \left[0.6986/89.06^\circ * 2.393 \times 10^{-4}/90 \right]$$

$$Y = 2.393 \times 10^{-4} \text{ } S/\text{km} \quad = 1.0631 \times 10^{-5} + j 1.29291 \times 10^{-3}$$

$$Z_c = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{291888.283 - j 4800.4019}{291327.7542 - j 0.9422}} = 540.3034 / -0.4711^\circ$$

$$A = D = \cosh(1.0631 \times 10^{-3} + j 1.29291 \times 10^{-1})$$

$$\cosh(\gamma d) = \frac{e^{\gamma d} + e^{-\gamma d}}{2} = \frac{e^{(\alpha + j\beta)d} + e^{-(\alpha + j\beta)d}}{2} \quad \left\{ \begin{array}{l} \alpha = 1.0631 \times 10^{-3} \\ \beta = 1.29291 \times 10^{-1} \end{array} \right.$$

$$= \frac{(e^\alpha + e^{-\alpha}) \cos \beta + j(e^\alpha - e^{-\alpha}) \sin \beta}{2} = 0.991654 + j 1.37 \times 10^{-4}$$

$$B = Z_c \sinh(\gamma d) = Z_c \left[\frac{e^\alpha - e^{-\alpha}}{2} \cos \beta + j \frac{e^\alpha + e^{-\alpha}}{2} \sin \beta \right] = 1.14235 + j 69.655$$

$$C = \frac{1}{Z_c} \sinh(\gamma d) = \underline{-1.09455 \times 10^{-8} + j 2.386 \times 10^{-4}}$$

Line charging current (I_S) with $I_R=0$, $V_S=8\text{ kV}$

$$\begin{aligned} V_S &= A \cdot V_R + B \cdot I_R^{\angle 0^\circ} \\ I_S &= C \cdot V_R + D \cdot I_R^{\angle 0^\circ} \Rightarrow \boxed{I_S = C \cdot V_R = \frac{C}{A} \cdot V_S} \end{aligned}$$

(i) Short Line $C=0, A=1 \Rightarrow \underline{\underline{I_S=0}}$

(ii) Medium Line $C = 2.383 \times 10^{-4} \angle 90.004^\circ, A = 0.991642 \angle 0.208^\circ$

$$\begin{aligned} \therefore I_S &= \frac{2.383 \times 10^{-4} \angle 90.004^\circ}{0.991642 \angle 1.008^\circ} \times 8000 = 1.338 \times 10^{-4} + j1.92248 \\ &= \underline{\underline{1.92248 \angle 89.996^\circ \text{ A}}} \end{aligned}$$



(iii) Long Line

$$C = -1.09455 \times 10^{-8} + j2.3864 \times 10^{-4}$$

$$A = 0.991654 + j1.371 \times 10^{-4}$$

$$\therefore I_S = \frac{C}{A} V_S = 1.778 \times 10^{-4} + j1.92515 = \underline{\underline{1.92515 \angle 89.9947^\circ \text{ A}}}$$

Note: Medium & Long Line models give similar results.

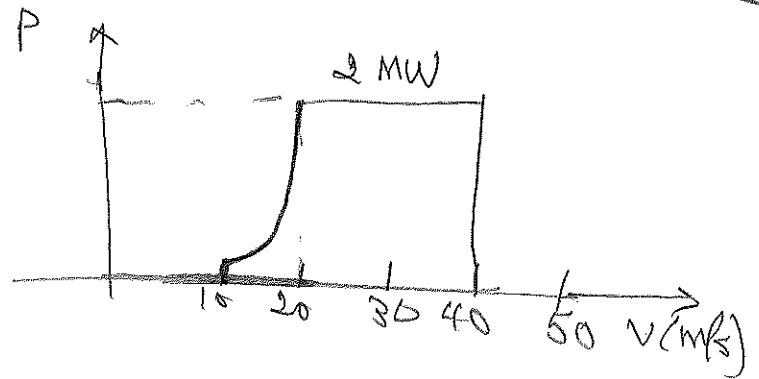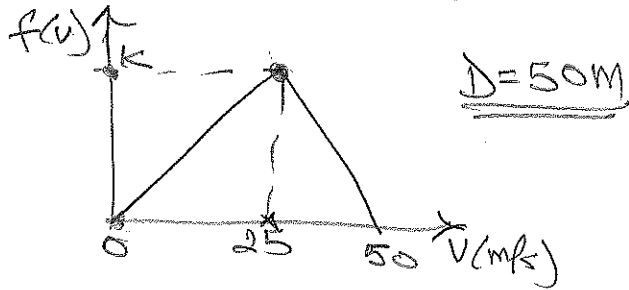④ Wind power(a) K

$$f(v) = \frac{K}{25} v \quad 0 \leq v \leq 25$$

$$= \frac{K(50-v)}{25} \quad 25 \leq v \leq 50$$

$$1 = \int_0^{\infty} f(v) dv = \int_0^{25} \frac{K}{25} v dv + \int_{25}^{50} \frac{K}{25} (50-v) dv$$

$$1 = \frac{K}{25} \left(\frac{25^2}{2} \right) + \frac{K}{25} \left[50(50-25) - \frac{1}{2}(50^2 - 25^2) \right]$$

$$1 = 12.5K + K[50 - 37.5] = 25K$$

$$\therefore \underline{\underline{K = 0.04 \text{ (} = 1/25 \text{)}}}$$

(b) $(V_{av})^3$ and $(V^3)_{av}$

$$V_{av} = \int_0^{\infty} v f(v) dv = \int_0^{25} \frac{K}{25} v^2 dv + \int_{25}^{50} \frac{K}{25} (50v - v^2) dv$$

$$= \frac{K}{25} \left[\frac{25^3}{3} + 50 \left(\frac{50^2 - 25^2}{2} \right) - \frac{50^3 - 25^3}{3} \right] = \underline{\underline{25 \text{ m/sec}}}$$

$$\therefore \underline{\underline{(V_{av})^3 = (25)^3 = 15,625 \text{ (m/sec)}^3}}$$

$$(V^3)_{av} = \int_0^{\infty} v^3 f(v) dv = \frac{K}{25} \left[\int_0^{25} v^4 dv + \int_{25}^{50} (50v^3 - v^4) dv \right]$$

$$= \frac{K}{25} \left[\frac{25^5}{5} + 50 \left(\frac{50^4 - 25^4}{4} \right) - \frac{50^5 - 25^5}{5} \right] = \underline{\underline{1.5 \times 25^3 \text{ (m/s)}^3}}$$

$$= \underline{\underline{23,437.5 \text{ (m/s)}^3}}$$

$(V^3)_{av}$ is greater by 1.5 compared to $(V_{av})^3$!

(c) P_{av} wind

$$P_{av} = \frac{1}{2} \rho A (V^3)_{av} = \frac{1}{2} \times 1.225 \times \frac{\pi}{4} (50)^2 \times 1.5 \times 25^3 \times 10^{-6} \text{ MW}$$

$$= \underline{\underline{28.187 \text{ MW}}},$$

(d) Energy delivered by wind turbine in a year

8/10

$$P_{\text{wind}} = \frac{1}{2} \rho A V^3 = \frac{1}{2} \times 1.225 \times \frac{\pi}{4} (50)^2 \times 20^3 \times 10^{-6}$$

@ 20 m/s

$$= \underline{9.621 \text{ MW}}$$

$$\text{Efficiency @ 20 m/s} = \frac{2}{9.621} \times 100 = \underline{20.7876\%}$$


$$P_{\text{wind}} = \frac{1}{2} \rho A (V^3)_{\text{av}} \quad (10 \leq V \leq 20)$$

$$= \frac{1}{2} \times 1.225 \times \frac{\pi}{4} (50)^2 \times 992 \times 10^{-6}$$

$$= \underline{1.19302 \text{ MW}}$$

$(V^3)_{\text{av}} = \int_{10}^{20} V^3 f(V) dV = \frac{K}{25} \int_{10}^{20} V^4 dV$

$= \frac{K}{25} \left(\frac{20^5 - 10^5}{5} \right) = \underline{992}$



$$\text{Efficiency} = 20.7876\%$$


$$P_{\text{WT}} = 0.248 \text{ MW} \quad (10 \leq V \leq 20) \leftarrow (\text{av. } P_{\text{WT}} \text{ from } 10 \text{ to } 20 \text{ m/s wind})$$

$$P_{\text{prob.}} (10 \leq V \leq 20) = \int_{10}^{20} f(V) dV = \frac{K}{25} \left(\frac{20^2 - 10^2}{2} \right) = \underline{0.24}$$

and

$$P_{\text{prob.}} (20 \leq V \leq 40) = \int_{20}^{40} f(V) dV = \int_{20}^{25} \frac{K}{25} V dV + \int_{25}^{40} \frac{K}{25} (50 - V) dV$$

$$= \frac{K}{25} \left[\frac{25^2 - 20^2}{2} + 50(40 - 25) - \frac{(40^2 - 25^2)}{2} \right]$$
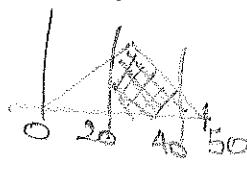
$$= \underline{0.6}$$


$$P_{\text{av}} = 0.248 \times 0.24 + 2 \times 0.6 = \underline{1.25952 \text{ MW}}$$

(WT)

$$\text{Energy delivered by wind turbine in a year}$$

$$= P_{\text{av}} \times 8760 = \underline{11,033.4 \text{ MW-hr}}$$

(WT)

(e) Maximum energy wind turbine can deliver in a year

$$= 2 \text{ MW} \times 8760 = \underline{17,520 \text{ MW-hr}}$$

5) Solar Energy

100 solar cells in series
1 bypass diode every 10 cells

$$T = 50^{\circ}\text{C}$$

$$\begin{aligned} I_{sc} &= 4 \text{ A} \\ I_0 &= 10^{-9} \text{ A} \\ V_d &= 0.5 \text{ V} \\ R_p &= 10 \Omega \\ R_s &= 0.01 \Omega \end{aligned}$$

(a) I , V_{module} , Power - Healthy system

$$\begin{aligned} I &= I_{sc} - I_d - \frac{V_d}{R_p} \\ &= 4 - 0.062381 - \frac{0.5}{10} \\ &= \underline{\underline{3.88762 \text{ A}}} \end{aligned}$$

$$I_d = I_0 \left[e^{\frac{qV_d}{kT}} - 1 \right]$$


$$\begin{aligned} \frac{qV_d}{kT} &= \frac{1.602 \times 10^{-19} \times 0.5}{1.381 \times 10^{-23} \times 323.15} \\ &= 17.949 \end{aligned}$$

$$\therefore I_d = 0.062381$$

$$V_{\text{module}} = 100 [0.5 - 3.88762 \times 0.01] = \underline{\underline{46.11238 \text{ V}}}$$

$$P = I \cdot V_{\text{module}} = \underline{\underline{179.27 \text{ Watts}}} \text{ (Ideal value } 4 \times 50 = 200 \text{ W)}$$

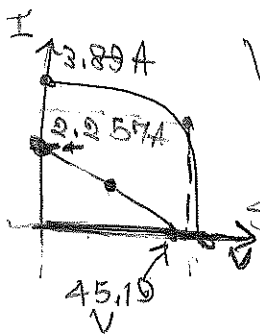(b) Two shaded cells covered by the same bypass diode
(i) without bypass diode, if $I = 3.88762$ were drawn $(V_d = 0.6 \text{ V})$



$$\begin{aligned} V &= \frac{98}{100} \times 46.11238 - 3.88762 [2(10 + 0.01)] \\ &= 45.19 - 77.83 = -32.64 \text{ V} \leftarrow \text{infeasible!} \end{aligned}$$

Since this is not possible as V can at most go to zero, the current will reduce to 2.257 A to $\left(\frac{45.19}{2(10+0.01)} \right)$ render $V=0$. Max Power = $2.257 \times 45.19 = \underline{\underline{25.5 \text{ W}}}$

(ii) with bypass diode, only 90/100 cells are in operation & the V_{bypass} drop.
 $C I = 1.1285 \text{ A}, V = 22.595 \text{ V}$ 4

$$V = \frac{90}{100} \times 46.11238 - 0.6 = \underline{\underline{40.90 \text{ V}}}$$

$$I = \underline{\underline{3.88762 \text{ A}}} \Rightarrow \underline{\underline{P = 159.01 \text{ W}}}$$

(c) (i) \rightarrow Same as b(i)

(ii) With two bypass diodes in action only

80/100 cells are in operation as two sets of 10 cells are bypassed.

$$V = \frac{80}{100} \times 46.11238 - 2 \times 0.6 = \underline{35.69 \text{ V}}$$

$$I = 3.88762 \text{ A} \Rightarrow \underline{P = 138.75 \text{ W}}$$