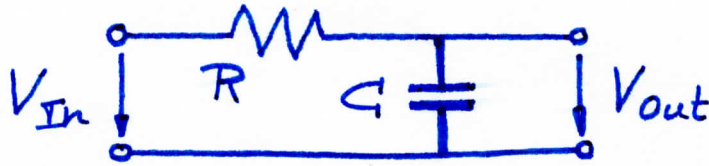


# Gain - bandwidth product of op amp

Preliminary discussion: RC circuit



$$V_{out} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{in} = \frac{1}{1 + j\omega RC} V_{in}$$


$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

$\swarrow$  low  $\omega \Rightarrow H(\omega) = 1$   
 $\searrow$  high  $\omega \Rightarrow H(\omega) = -j\frac{1}{\omega RC}$


$$\Rightarrow \text{low } \omega \Rightarrow |H(\omega)| = 1$$

$$\Rightarrow \text{high } \omega \Rightarrow |H(\omega)| = \frac{1}{\omega RC}$$

$$\Rightarrow \text{any } \omega \Rightarrow |H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

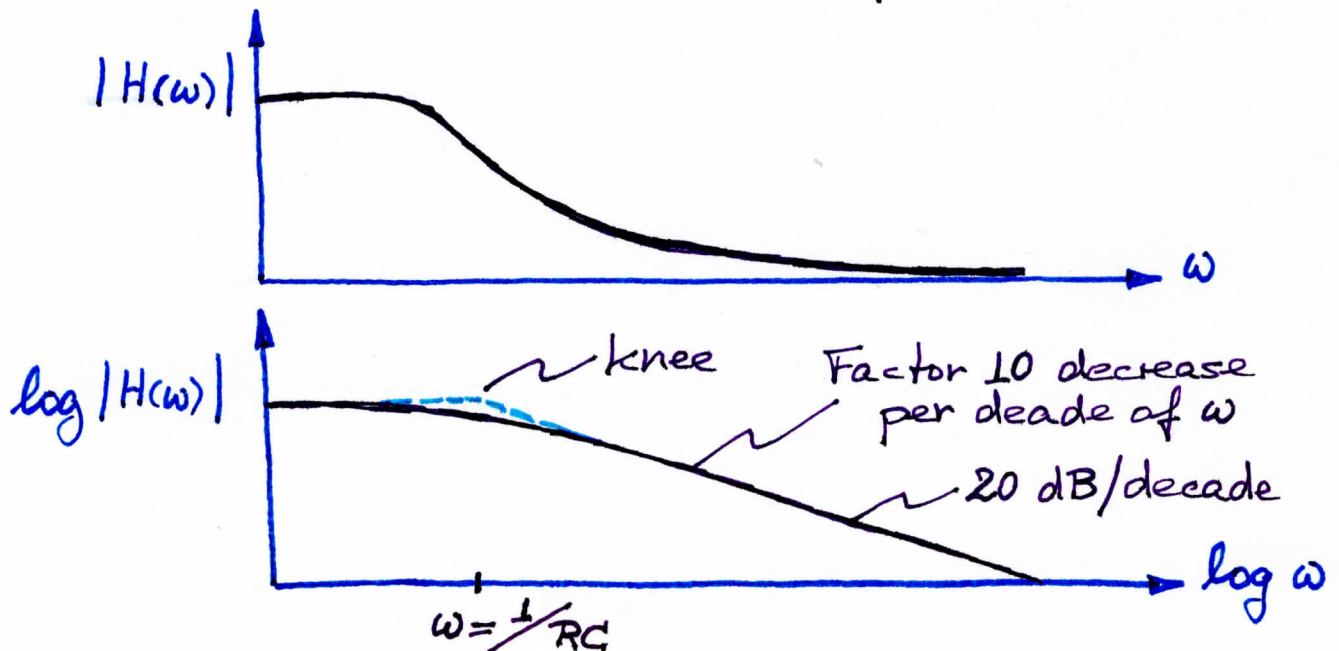

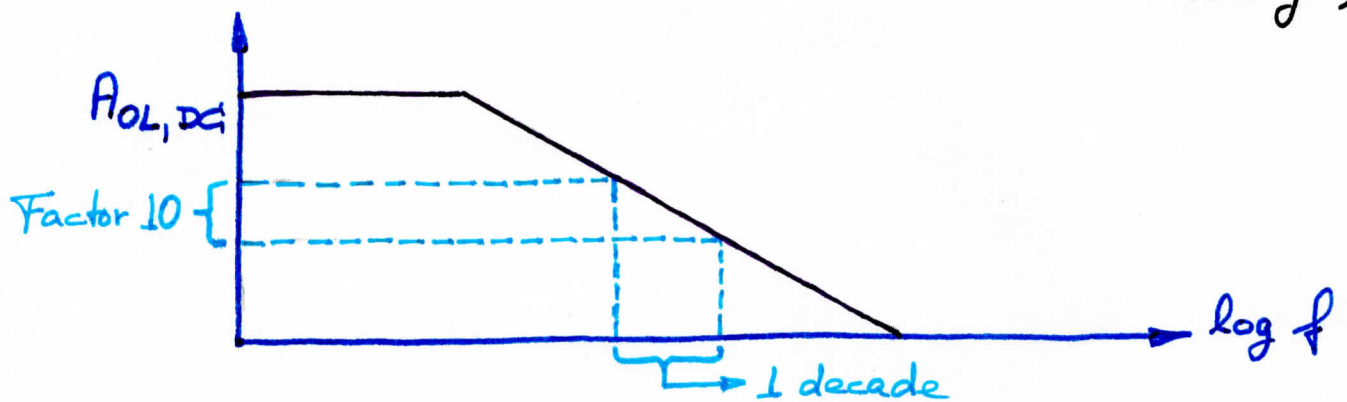Op amps have the basically same transfer function. (Why?) <sup>②</sup>



What do we learn from this curve?

We see:  $f \uparrow \Rightarrow A_{OL} \downarrow$

We also see:  $\underbrace{A_{OL}}_{\text{Gain}=G} \times \underbrace{f}_{\text{Bandwidth}=B} = \text{constant}$

$$\Rightarrow \boxed{G \times B = \text{constant}}$$

e.g.  $10^7 \text{ Hz}$

Example:

Assume op amp with  $G \times B = 10^7 \text{ Hz}$


$$\Rightarrow f = 1 \text{ Hz} \Rightarrow G = 10^7 \quad (G = A_{OL})$$

$$f = 1 \text{ kHz} \Rightarrow G = 10^4$$

$$f = 1 \text{ MHz} \Rightarrow G = 10$$

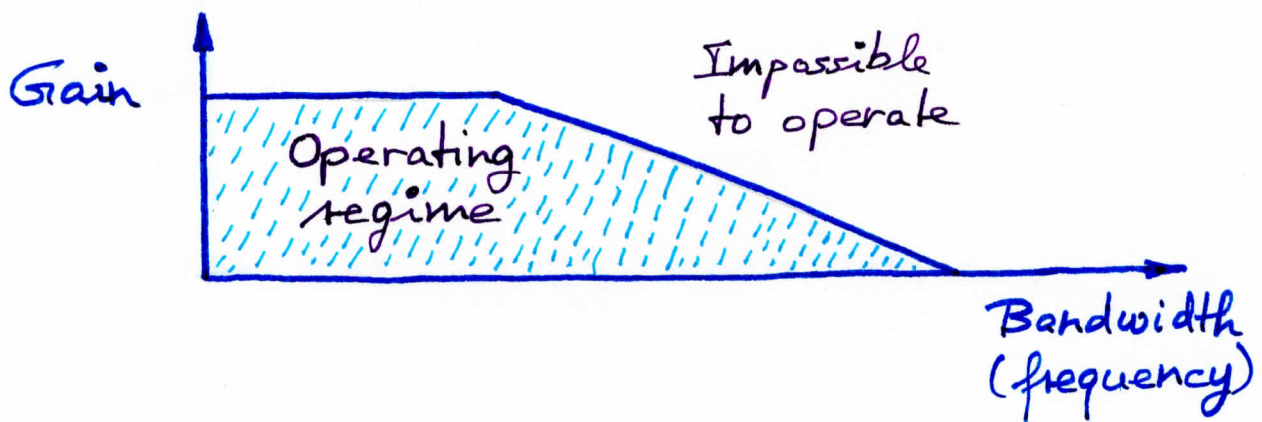
## Consequences for op amp circuit design ③

- \* We cannot exceed gain-bandwidth-product limitations. If  $G \times B = 10^7 \text{ Hz}$ , then  $G = 10^4$  ( $= A_{OL}$ ) at 1 MHz is not possible.
- \* We need to stay within the gain-bandwidth limitations of the op amp.



Recall RC filter transfer function

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

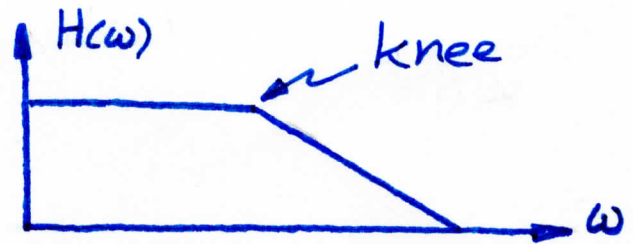

$$\omega = 0 \quad \Rightarrow \quad |H(\omega)| = 1$$

$$\omega = 1/RC \quad \Rightarrow \quad |H(\omega)| = 1/\sqrt{2} \quad (\text{knee})$$

$$\omega = 2/RC \quad \Rightarrow \quad |H(\omega)| = 1/\sqrt{5} \approx 1/2$$


$$\omega = 3/RC \quad \Rightarrow \quad |H(\omega)| = 1/\sqrt{10} \approx 1/3$$

$$\omega = 4/RC \quad \Rightarrow \quad |H(\omega)| \approx 1/4$$

... and so on

$\Rightarrow$  To determine the frequency response of a circuit, we need to identify the RC time constant.

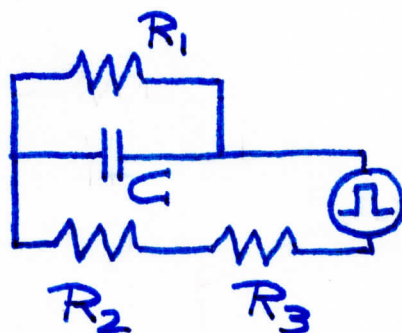Q: What is the time constant of the following circuit?



Pulse source

$\Rightarrow C$  charges & discharges


$\tau = RC$  gives charging & discharging time constant. How will  $C$  discharge?  $C$  will discharge through all resistors. Circuit above:  $R = R_1 \parallel (R_2 + R_3)$

$\Rightarrow \tau = RC$

$\downarrow$  Capacitance  
 $\downarrow$  Resistance "seen" by  $C$

$\Rightarrow$  Knowing  $RC$ , we can calculate frequency response.

Example:

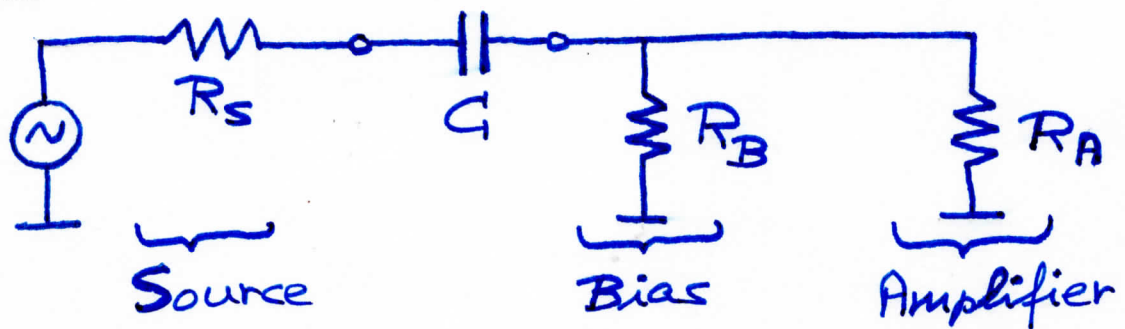



$$RC = ?$$

$$R = R_S + (R_B \parallel R_A)$$



$\downarrow$  Relevant  $R$



Low-pass filter

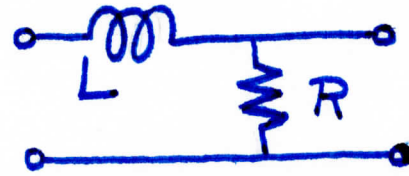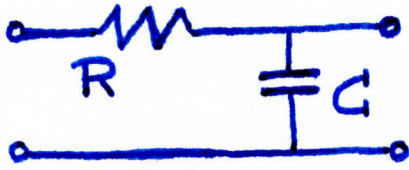

High-pass filter

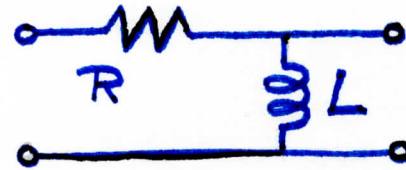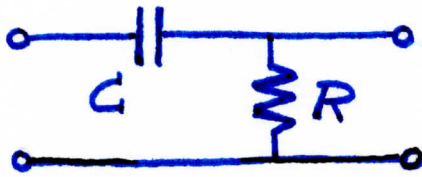

Q: How many low-pass (or high-pass) filters?

Q: Are they mathematically equivalent?

Q: Time constants?  $\Rightarrow \tau = RC$   $\tau = L/R$

Q: Why do we have two filters (of each kind)?

Q: Which one is more common?  $\Rightarrow RC$ ?

Q: Why are  $RC$  filters more common?

Q: Do all filters have a knee frequency?

$$\Rightarrow \omega = 1/RC \quad \omega = R/L$$

# Summary of frequency response

Recall: RC filter

$$\left| \frac{V_{out}}{V_{in}} \right| = |H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Knee frequency  $\Rightarrow \omega = \frac{1}{RC} = \frac{1}{\tau}$   
 $\hookrightarrow$  cutoff frequency  $\Rightarrow f = \frac{1}{2\pi RC} = \frac{1}{2\pi \tau}$

At knee frequency, voltage attenuation is

$$|H(\omega)| = \underline{\underline{1/\sqrt{2}}}$$

At knee frequency, voltage attenuation in dB

$$20 \log \frac{V_{out}}{V_{in}} = 20 \log |H(\omega)| = \underline{\underline{-3 \text{ dB}}}$$

At knee frequency, power attenuation in dB

$$10 \log \frac{V_{out}^2}{V_{in}^2} = 10 \log |H(\omega)|^2 = \underline{\underline{-3 \text{ dB}}}$$

$\Rightarrow$  We see: Power attenuation in dB = Voltage attenuation in dB

(8)

Above knee frequency

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \approx \frac{1}{\sqrt{\omega^2 R^2 C^2}} = \frac{1}{\omega RC}$$

Inspection of eqn. reveals  $|H(\omega)| \propto 1/\omega$

$\Rightarrow$  Attenuation = -6 dB/octave

= -20 dB/decade

Let us plot what we derived  $\Rightarrow$  Bode plot

