



Electric circuit elements

Resistor  $Z_R = R$

$$\text{Power} = P = IV = I^2 R = \frac{V^2}{R}$$


Notation:  $R = R_1 \parallel R_2 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$

Capacitor  $Z_C = \frac{1}{j\omega C}$

$$\text{Charge } Q = CV \Rightarrow \dot{Q} = I = C\dot{V}$$

$$\text{Energy stored: } E = \frac{1}{2} CV^2$$

\Rightarrow Capacitor resists voltage changes. Why?

Inductor  $Z_L = j\omega L$

$$\text{Magnetic flux } \Phi_m = LI \quad \dot{\Phi}_m = V_{\text{ind}} = L\dot{I}$$


$$\text{Energy stored: } E = \frac{1}{2} LI^2$$

\Rightarrow Inductor resists current changes. Why?


Sources (voltage and current)

②


Ideal voltage
source

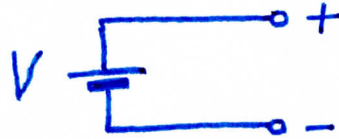


Real voltage
source

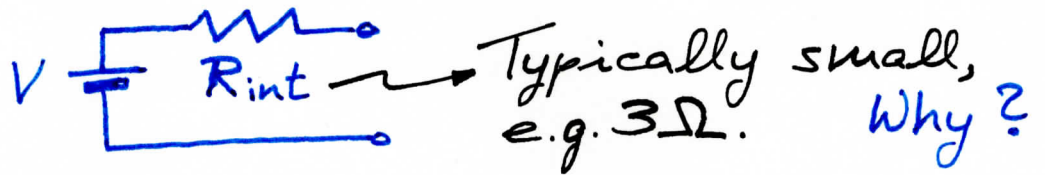

Ideal current
source

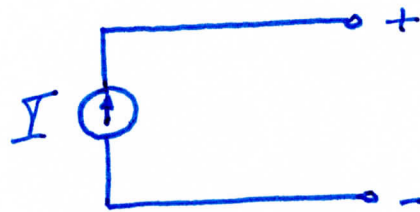

Real current
source

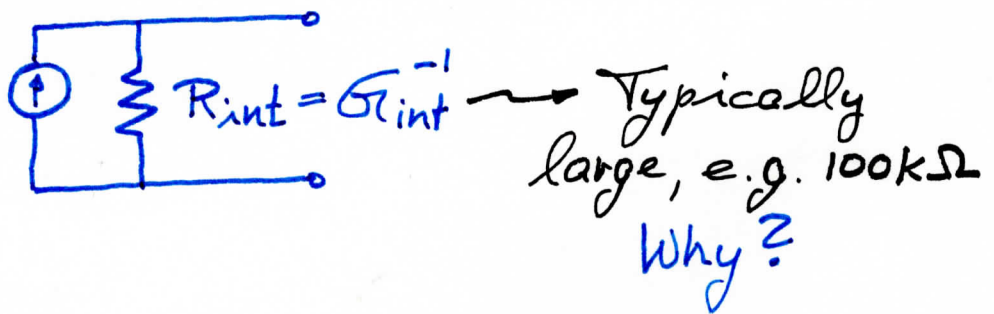

Resistance of ideal voltage source

$$V \parallel \text{I} \quad R = \frac{dV}{dI} = \frac{\Delta V}{\Delta I} = \frac{0}{\Delta I} = 0$$


Question: Why is $\Delta V = 0$?

Resistance of ideal current source

$$I \parallel \text{V} \quad R = \frac{dV}{dI} = \frac{\Delta V}{\Delta I} = \frac{\Delta V}{0} = \infty$$

Question: Why is $\Delta I = 0$?

LC circuit

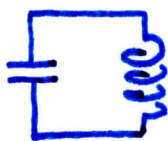


$$\omega_{\text{Resonance}} = 2\pi f_{\text{Resonance}} = \frac{1}{\sqrt{LC}}$$

Mechanical analog: ① Pendulum

② Spring and mass

LCR circuit

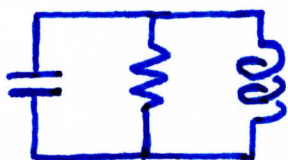

$$\omega_{\text{Resonance}} \approx \frac{1}{\sqrt{LC}}$$

Strong damping $\Rightarrow R = ?$

Weak damping $\Rightarrow R = ?$