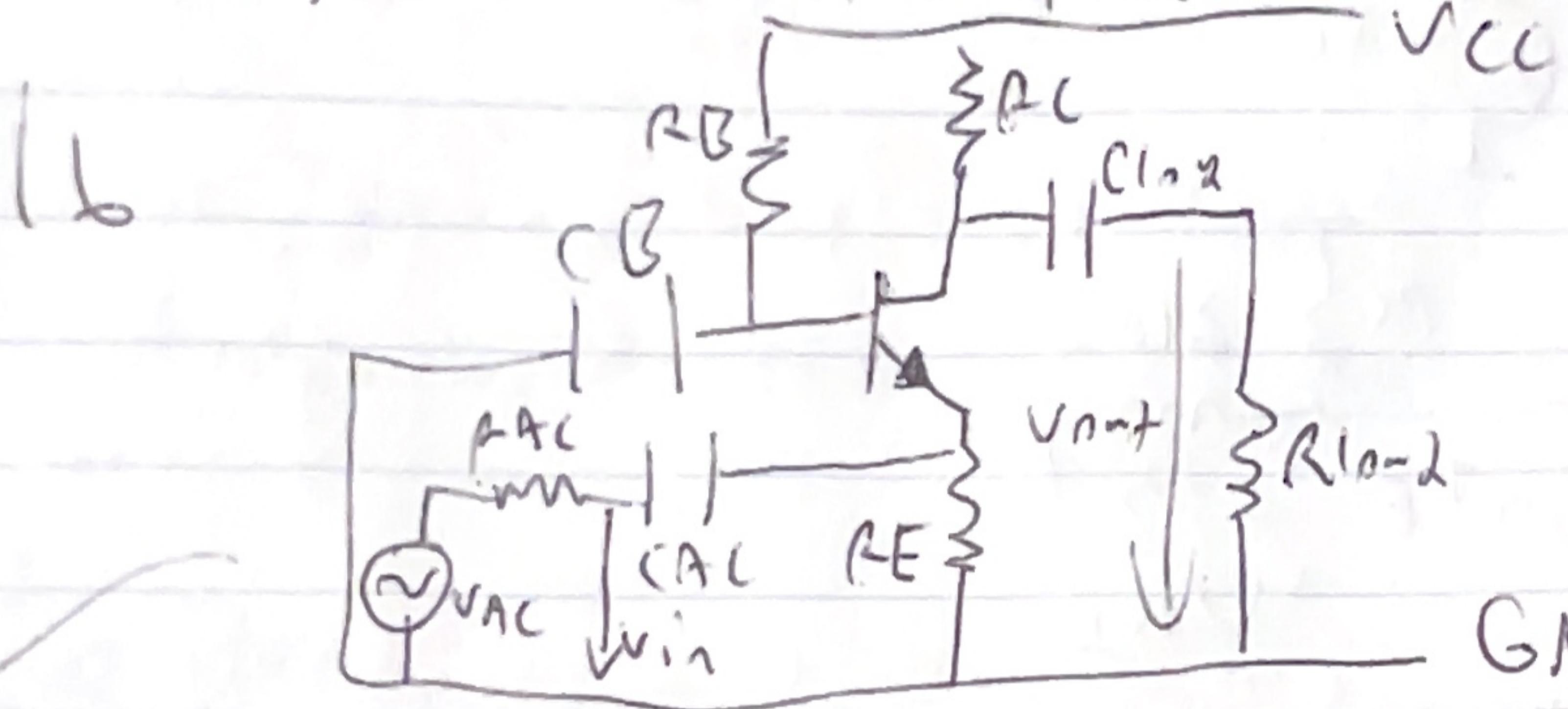


$$V_{CC} = 12V \quad \alpha = 0.99 \quad R_{AC} = 1k \quad R_{1o-2} = 100\Omega$$




$$\text{In } \beta, \text{ betn. } \beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = 99$$



In both  $V_{in}$  and  $V_{out}$  are grounded, and GND connects with base side of the transistor (through a DC blocking capacitor). Since base is grounded (right) through emitter, and output is through collector, this circuit is in common-base form.


$$(2) \quad R_C = R_E = 500\Omega \quad V_{AC} = 3V \quad I_E, I_C, I_B, \alpha_B = ?$$
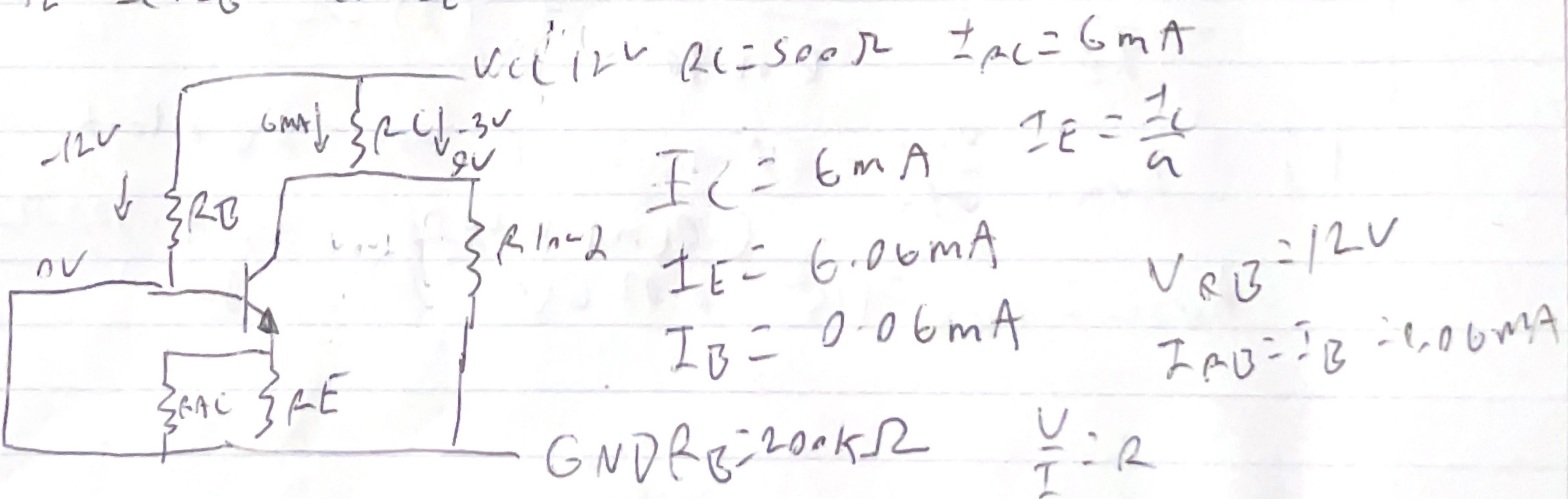
$$I_E = I_C + I_B \quad I_C = \alpha I_E$$




$$I_E R_E = \frac{V_T + V_{BE}}{I_E} = 26mV \Rightarrow 6.06mA \cdot 4.29\Omega$$

1.f

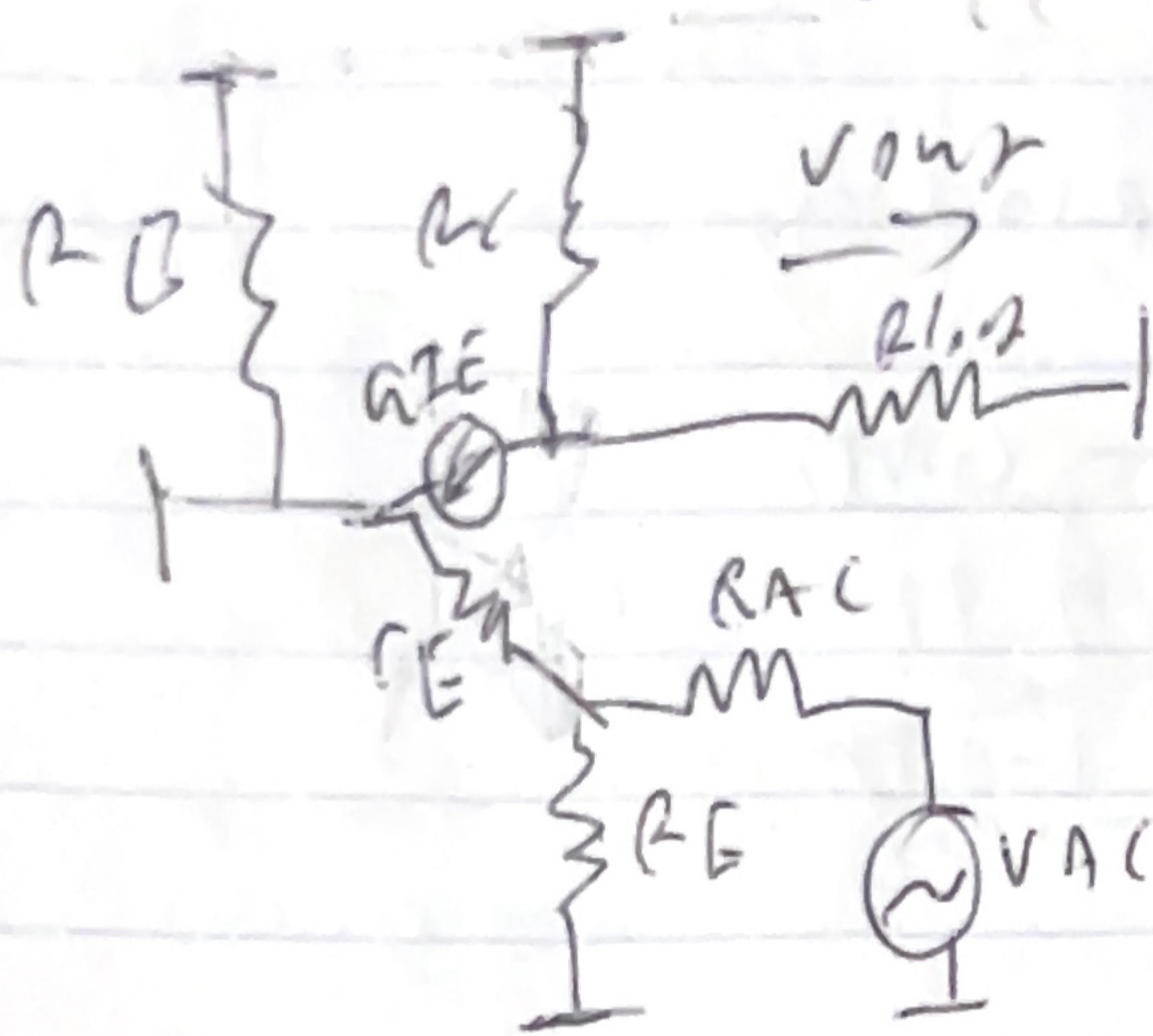

1.g

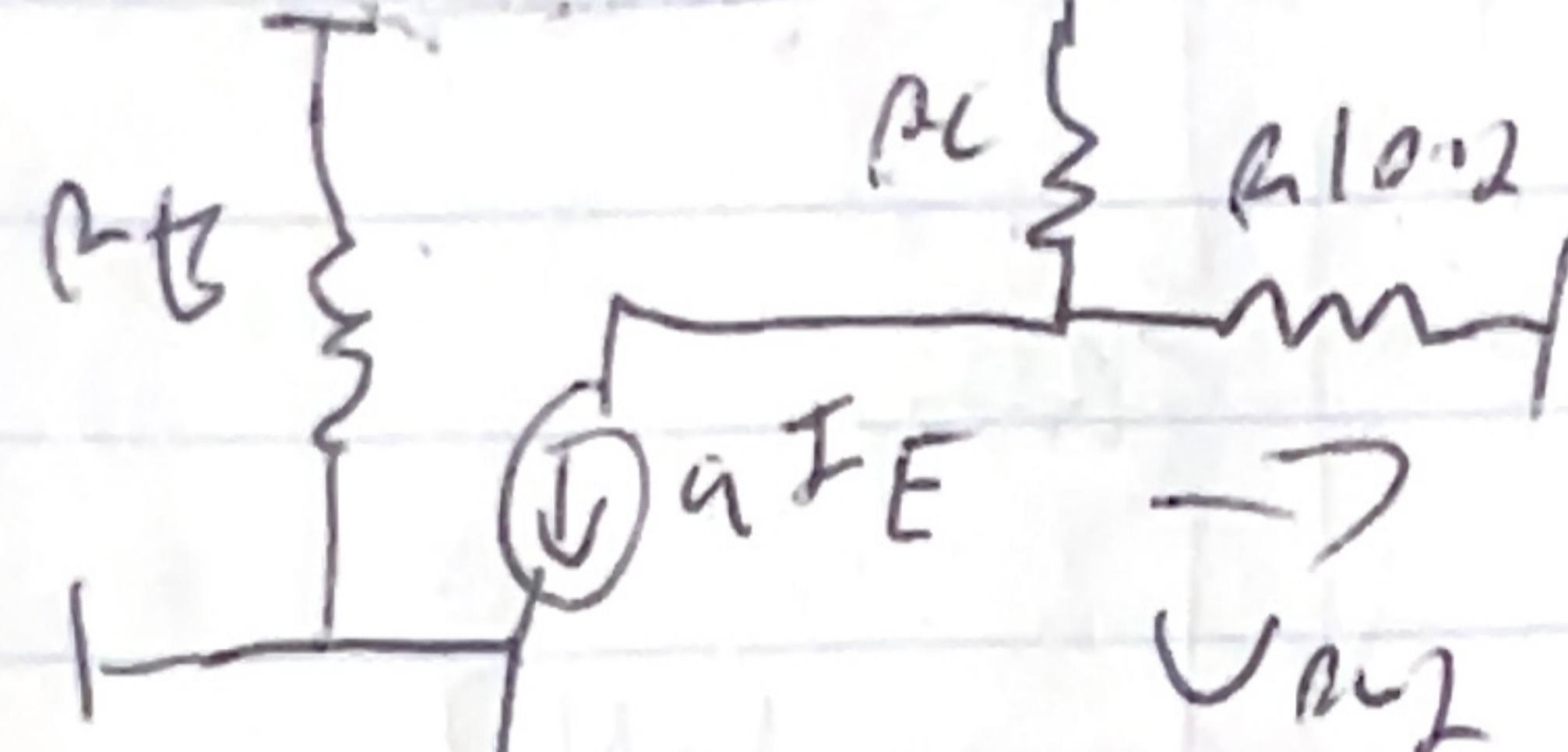

$$1.h \quad Z_{in} = R_E = 4.29\Omega, \text{ Relatively low.}$$

$$1.i \quad Z_{out} = \frac{V_{out2}}{I_E} = \frac{V_{out2}}{\alpha_{IE}} = \frac{V_{out2}}{I_E} = \frac{V_{load}}{I_E} = \frac{I_{load} R_{load}}{I_E}$$

$$\frac{I_C R_{load}}{I_E} = \frac{6 \cdot 10^{-3} \cdot 800}{6.06 \cdot 10^{-3}} = 495 \Omega$$

$$1.j \quad A_{voc} = \frac{V_{out2}}{V_{in}} \quad V_{in} = I_E \cdot R_E \quad V_{out2} = I_C R_{load}$$

$$A_{voc} = \frac{3}{0.026} = 115 \quad 6.06mA \cdot 4.29\Omega \quad 6mA \cdot 500\Omega$$

$$I_C = \alpha I_E$$

$$1K A_{ISL} = \frac{I_{out}}{I_{in}} = \frac{I_C}{I_E} = \alpha = 0.99$$

$$II A_{VOL} = \frac{v_{out}}{v_{in}} = \frac{\beta R_{load}}{I_E \cdot R_E} = \frac{I_C \cdot \frac{\beta R_{load}}{\alpha + \beta}}{I_E \cdot \frac{R_E}{\alpha + \beta}}$$

$$\frac{6mA \cdot \frac{500}{500+500} \cdot 500}{6.06mA \cdot \frac{500}{1000}} = 0.495$$


$$Im A_{ISL} = \frac{I_{out}}{I_{in}} = \frac{I_C \cdot \frac{\beta R_{load}}{\alpha + \beta}}{I_E} = \frac{6mA \cdot \frac{500}{500+500}}{6.06mA} = 0.495$$

In It is a high frequency pass filter. The cut off frequency would be  $\frac{1}{2\pi RC}$  where  $R = R_{load}$  and  $C = C_{load}$

$$10^3 \text{ Hz} = \frac{1}{2\pi RC} \cdot 2000\pi = \frac{1}{500C} \quad 1000000\pi = \frac{1}{C}$$

$$C = \frac{1}{1000000\pi} \quad C = 3.183 \cdot 10^{-7} F \quad \text{or} \quad 0.3183 \text{ nF}$$


2.

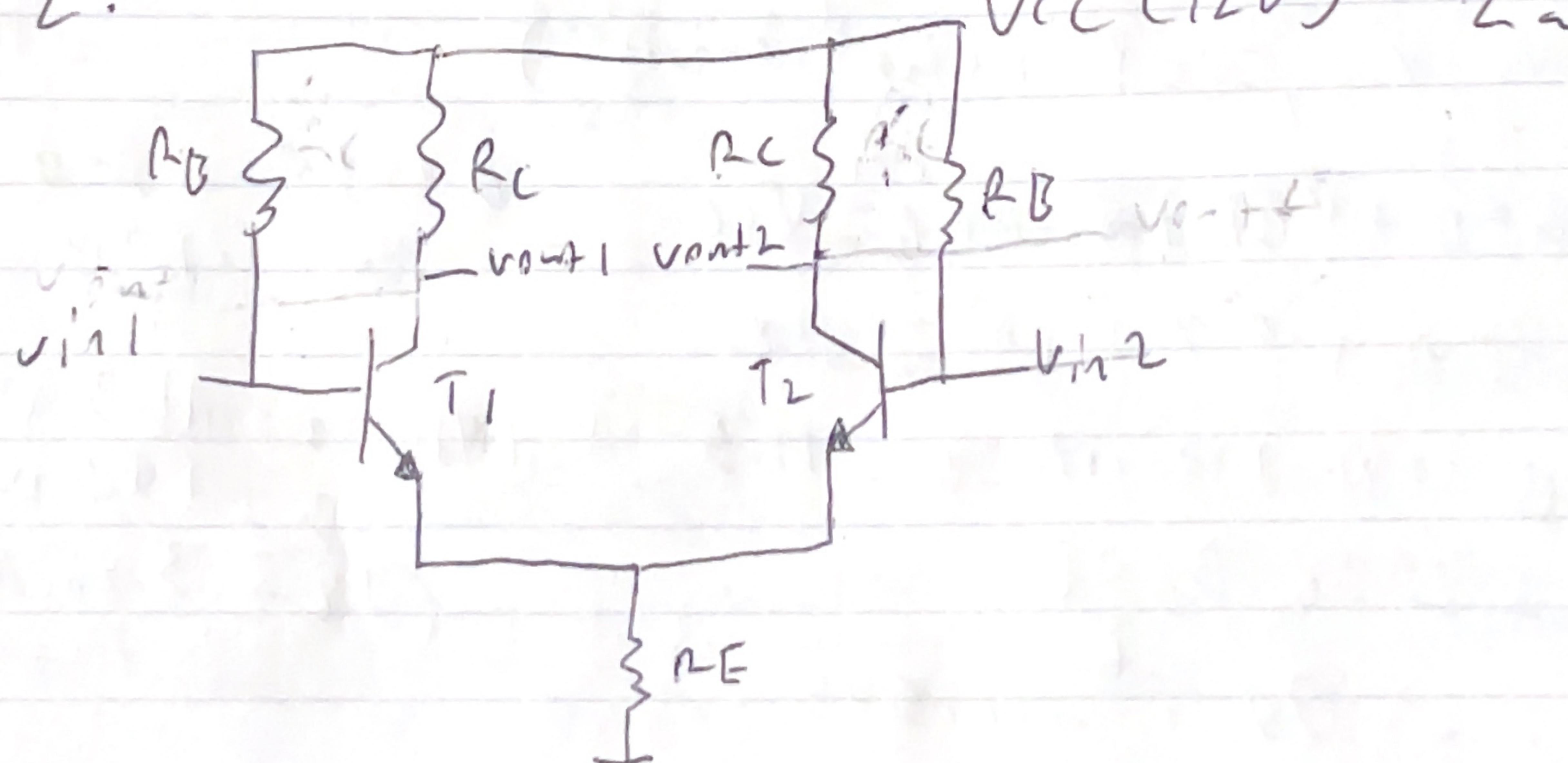

Q point  $\beta = 100$

26  $I_{AE} = 20 \text{ mA}$ ,  $V_{RE} = 1 \text{ V}$ ,  $V_{CE} = 5 \text{ V}$   $R_E, R_C, R_B = ?$

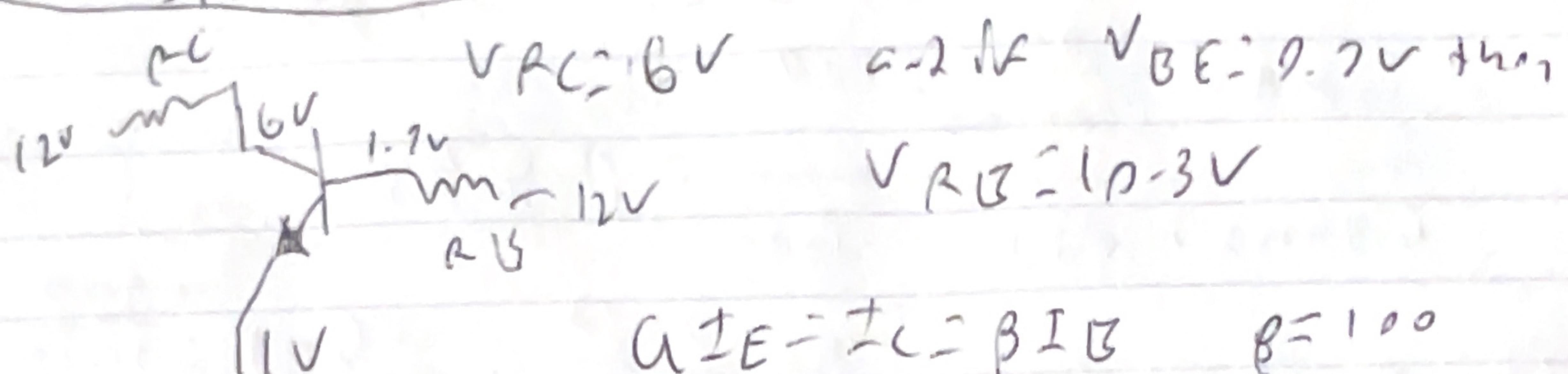$R_E = \frac{V_{RE}}{I_{AE}} = 50 \Omega$ , if  $V_{CC} = 12 \text{ V}$  and  $V_{CE} = 5 \text{ V}$  then



$$\frac{\alpha}{1-\alpha} = \beta \quad \frac{\alpha}{1-\alpha} = 100 \quad \alpha \approx 0.99$$

$$\frac{I_{AE}}{2} = I_E = 10 \text{ mA} \quad I_C = 0.99 \cdot 10 \text{ mA} = 9.9 \text{ mA}$$

$$I_B = \frac{9.9 \text{ mA}}{10^4} = 9.9 \mu\text{A}$$

$$I_C = I_{RE} \quad I_B = I_{AB}$$

$$R_C = \frac{V_{RE}}{I_{RE}} = \frac{5}{9.9 \cdot 10^{-3}} = 506 \text{ ohms}$$

$$R_E = \frac{V_{RE}}{I_{AB}} = \frac{10.3}{9.9 \cdot 10^{-6}} = 104 \text{ kohms}$$

2c  $V_E, V_C, V_{CE}, I_C = ?$  (vihis "removed")

$$I_B R_B + V_{BE} + 2 I_E R_E = V_{CC}$$

$$0.94 + E = 100.1 \text{ V}$$

$$I_E = 10.1 \text{ mA}$$

$$I_B \cdot 10.4 \text{ k} + 0.7 + 100 \cdot E = 12$$

$$I_B \cdot 10.4 \text{ k} + 100 \cdot 10.1 \text{ IB} = 11.3$$

$$V_E = 2 I_B \cdot \beta \cdot R_E$$

$$V_E = 2 \cdot 9.9 \cdot 10^{-6} \cdot 100 \cdot 500$$

$$114 \text{ kT}^{1/2} = 11.3 \text{ V}$$

$$T_B = 192 \text{ mK}$$

$$I_C = 9.9 \text{ mA}$$

$$V_E = 10.1 \text{ V}$$


$$V_C = V_{CC} - \beta I_B R_C$$

$$V_C = -6.7 \text{ V}$$


$$V_{CE} = V_C - V_E = -16.8 \text{ V}$$

~~2c~~ ~~conf~~ My  $V_C$ ,  $V_E$ , and  $V_{CE}$  values are really wrong... I think its because of my resistance values... don't know how to calculate those correctly.

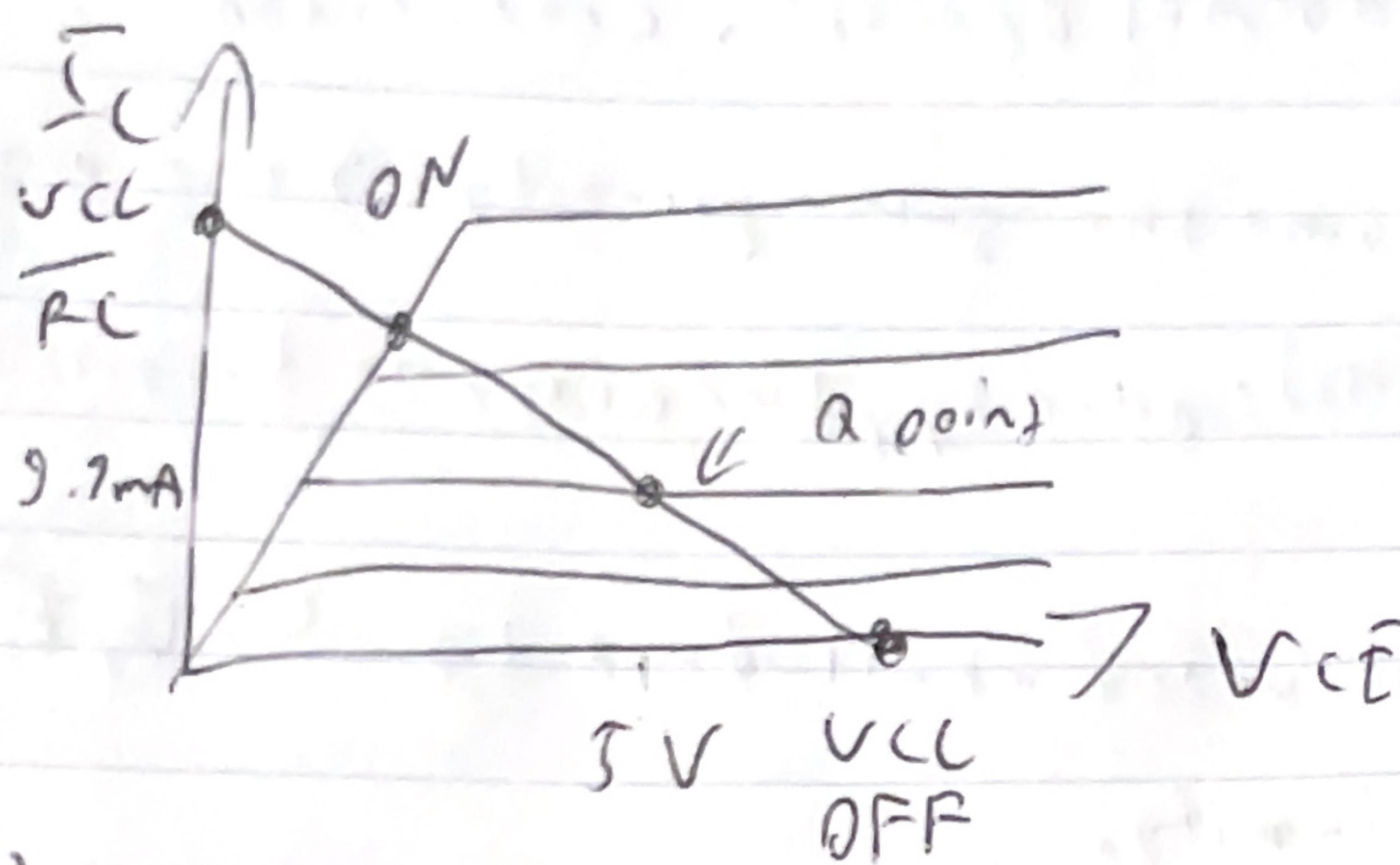Since  $I_{RE}$  is constant (due to symmetry of circuit),  $V_{CE}$  is constant, which makes  $V_E$  constant, or a virtual ground.


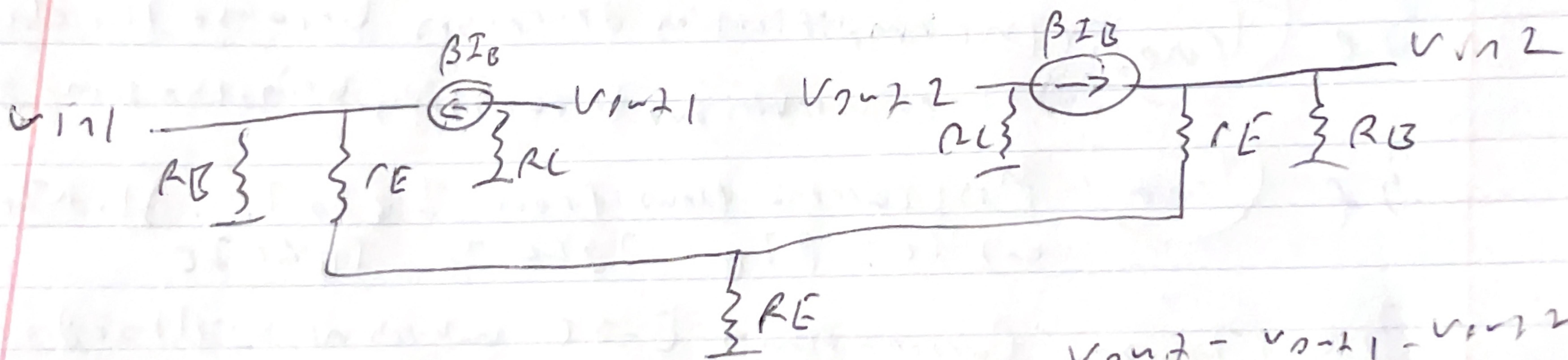
$$2d \quad R_E = \frac{V_T}{I_E} = \frac{26mV}{10mA} = 2.6\Omega$$



$$2e \quad A_{VOL} = ? = \frac{V_{out}}{V_{in}}$$

$$V_{in1} = -V_{in2} \quad V_{out} = V_{out1} - V_{out2} = -20,$$

$$A_{VOL} = \frac{V_{out1} - V_{out2}}{2V_{in1}} = \frac{\beta I_B R_C - \beta I_B R_C}{2 \cdot 2 I_E R_E} = -20,$$

$$A_{VOL} = \frac{2\beta I_B R_C}{4 I_E R_E} \rightarrow \frac{\beta I_B R_C}{2 I_E R_E} \rightarrow \beta I_B \approx I_E$$

$$\frac{R_C}{2 I_E} = A_{VOL}$$

$$2f \quad A_{VAC} = \frac{R_C}{2r_E} = \frac{6\text{ k}\Omega}{2 \cdot 2.6} = \underline{116.5}$$

$$2g \quad A_{VC} \cdot A_{VOC} = 116.5 \cdot 116.5 = \underline{13572}$$

3a True.  $\alpha I_E = I_C$ .  $\alpha$  is always less than 1, so  $I_C$  is always less than  $I_E$ , in normal operation conditions.

3b True. Base will become the same polarity as the emitter, and collector will be opposite polarity, turning the transistor into a type of diode.

3c False It will not work at all due to C, B, E all being the same polarity.

3d True C, B, E will all be the same polarity. It will not work.

3e True The amplification decreases because the circuit stops working due to everything being the same polarity.

3f True Most current flows from  $I_C$  to  $I_E$ . Also  $\alpha I_E = I_C$  and  $I_C = \beta I_B$   $I_B \ll I_C$   $I_B \ll I_G$

3g True Current flows E-C which has voltage drop is positive C-E so since B-C is backwards, or reverse bias.