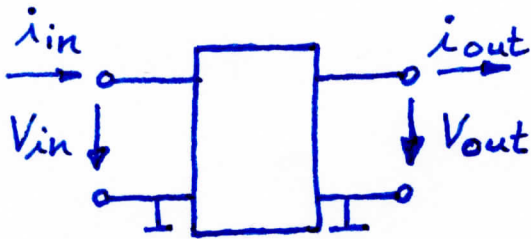


ITE - Homework 6

①

Problem 1 BJT Common-E, -B, and -C circuit Basic version of circuit

(a) Definition of small-signal quantities




$$Z_{in} = \frac{V_{in}}{i_{in}}$$

$$Z_{out} = \frac{V_{out}}{i_{out}}$$


$$A_{voc} = \frac{V_{out}}{V_{in}} \Big|_{oc \text{ output}}$$

$$A_{isc} = \frac{i_{out}}{i_{in}} \Big|_{sc \text{ output}}$$

(b) Common - E circuit

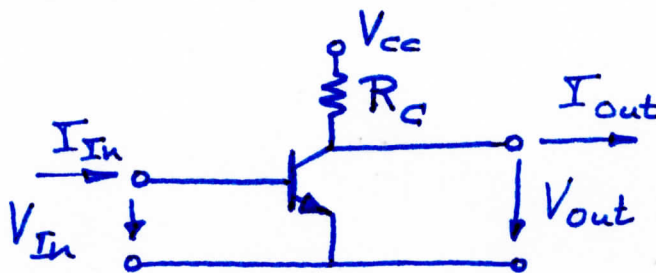

Small-signal equivalent circuit

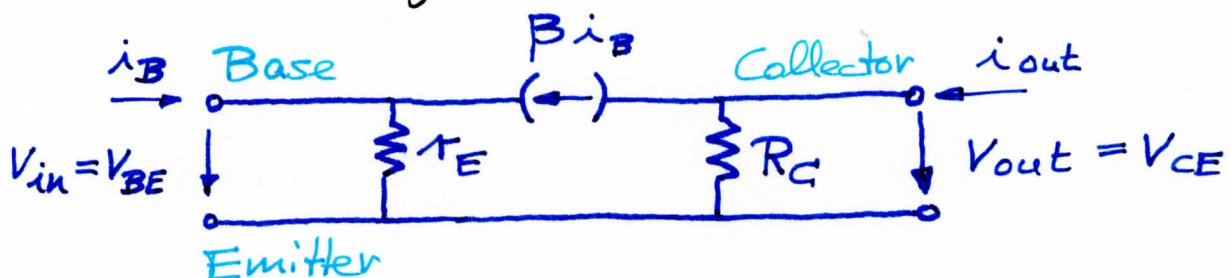

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{i_B r_E + \beta i_B r_E}{i_B} = r_E + \beta r_E = r_E (\beta + 1) \approx \underline{\underline{r_E \beta}}$$


$$Z_{out} = \frac{V_{out}}{i_{out}} = \frac{R_c i_{out}}{i_{out}} = \underline{\underline{R_c}}$$

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{\beta i_B R_c}{i_B \tau_E + \beta i_B \tau_E} = \frac{\beta R_c}{\tau_E (\beta + 1)} \approx \underline{\underline{\frac{R_c}{\tau_E}}}$$


A_{voc} has a large value since τ_E is small.

$$A_{isc} = \frac{i_{out}}{i_{in}} = \frac{\beta i_B}{i_B} = \underline{\underline{\beta}}$$

(c) Common - B circuit

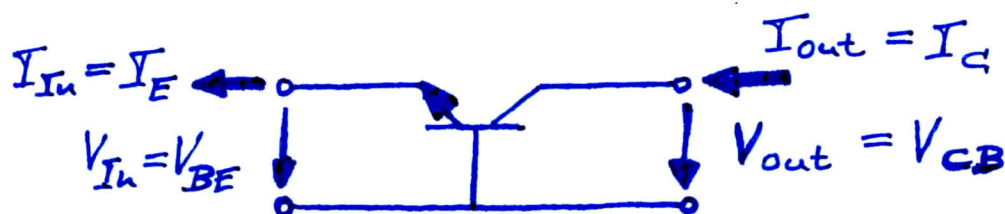

Small-signal equivalent circuit

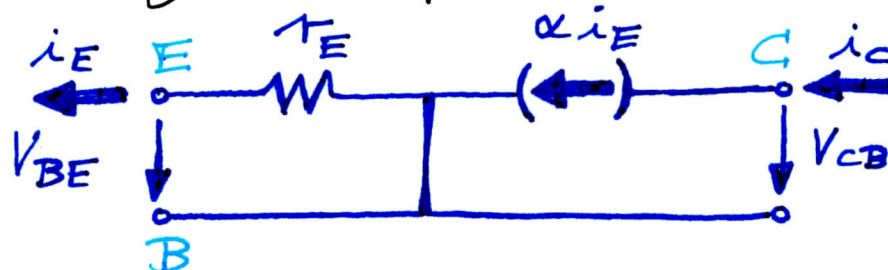

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{\tau_E i_E}{i_E} = \tau_E \quad (\text{small value})$$

$$Z_{out} = \frac{V_{out}}{i_{out}} = \frac{V_{out}}{\alpha i_E} = \infty$$

any value


\Rightarrow Current source has ∞ resistance

$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{\infty}{i_E \tau_E} = \infty$$


For OC at output, V_{out} increases to ∞ .

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{\alpha i_E}{i_E} = \underline{\underline{\alpha \approx 1}}$$

(d) Common - E circuit

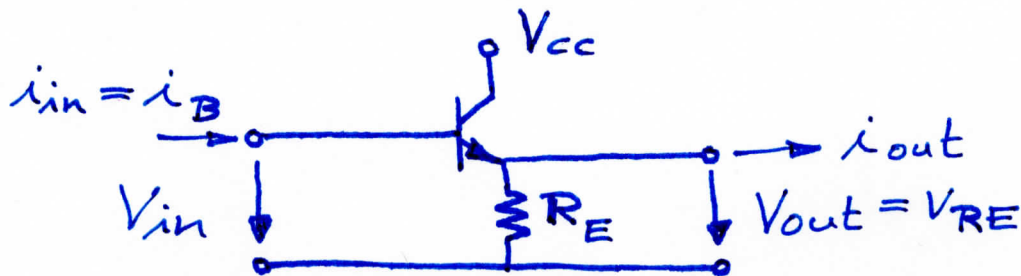

Small-signal equivalent circuit

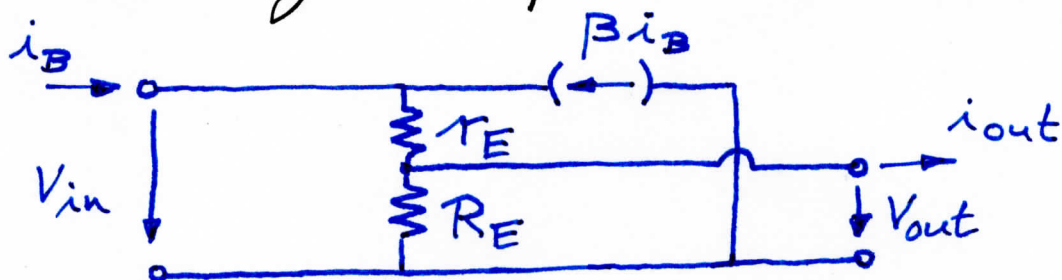

$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{i_B (r_E + R_E) + \beta i_B (r_E + R_E)}{i_B}$$

$$= (\beta + 1) (r_E + R_E) \approx \underline{\underline{\beta (r_E + R_E)}}$$

$$\approx \underline{\underline{\beta R_E}} \quad (\text{highest value of the three circuits})$$

$$Z_{out} = \frac{V_{out}}{i_{out}} = \frac{i_{out} R_E}{i_{out}} = \underline{\underline{R_E}}$$


$$A_{voc} = \frac{V_{out}}{V_{in}} = \frac{(i_B + \beta i_B) R_E}{(i_B + \beta i_B) (r_E + R_E)} = \frac{R_E}{\underset{\substack{\uparrow \text{small}}}{r_E + R_E}} \approx \frac{R_E}{R_E} \approx \underline{\underline{1}}$$

$$A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{(\beta + 1) i_B}{i_B} = \beta + 1 \approx \underline{\underline{\beta}}$$


- (e) Common-B amplifier has lowest input impedance (r_E). Generally not desirable (may overload source)
- (f) Common-E and common-C circuits have low output impedance. This is desirable (load will not overload circuit)
- (g) The common-C-circuit has lowest A_{voc} ($A_{voc} \approx 1$)
- (h) The common-B circuit has lowest A_{isc} ($A_{isc} \approx 1$)
- (i) Common-C \Rightarrow Impedance transformation (i.e. changing a high-impedance source to a low-impedance source)
- Common-E \Rightarrow Amplifier (i.e. amplifying a signal)
- Common-B \Rightarrow If we wish to convert a V-source to an I-source, the common-B circuit will accomplish this.

Problem 2 "T" and " π " equivalent circuit of BJT

(a) "T" equivalent circuit

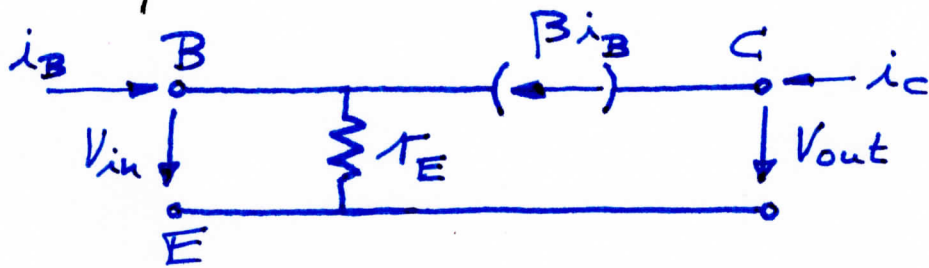

" π " - equivalent circuit

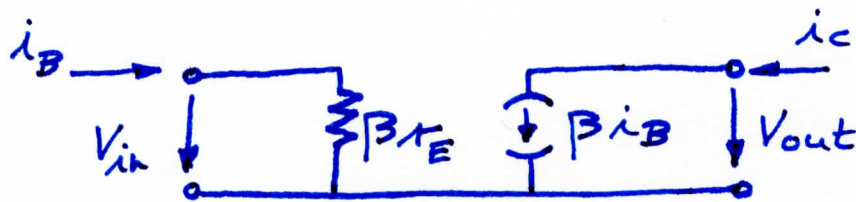

Three conditions

$$Z_{in} = \frac{V_{in}}{i_{in}} \text{ must be the same}$$

$$Z_{out} = \frac{V_{out}}{i_{out}} \text{ must be the same}$$

$$A_{Isc} = \frac{i_{out}}{i_{in}} \text{ must be the same}$$

$$(b) \text{ T: } Z_{in} = \frac{V_{in}}{i_{in}} = \frac{(i_{in} + \beta i_{in}) r_E}{i_{in}} = (1 + \beta) r_E \approx \beta r_E$$

$$\pi: Z_{in} = \frac{V_{in}}{i_{in}} = \beta r_E$$

\Rightarrow Same result

$$T: Z_{out} = \frac{V_{out}}{i_{out}} = \infty$$

$$\pi: Z_{out} = \frac{V_{out}}{i_{out}} = \infty$$

\Rightarrow Same result

$$T: A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{\beta i_B}{i_B} = \beta$$

$$\pi: A_{ISC} = \frac{i_{out}}{i_{in}} = \frac{\beta i_B}{i_B} = \beta$$

\Rightarrow Same result

\Rightarrow T and π circuits are equivalent

(c) T circuit (LHS) advantage:

The circuit is closer to the real physical device.

π circuit (RHS) advantage:

The circuit decouples the input side from the output side thereby facilitating our thinking and our analysis.

Problem 3 True / false questions

- (a) True $V_{BE,DC}$ must be $0.7V$ for the BJT to operate normally.
 $V_{BE,AC}$ must be $\ll 0.7V$ to allow for a linear circuit model.
- (b) True The BJT has 2 diodes: BE diode and CB diode.
- (c) False $A_{voc} \approx 1$ for common-C circuit.
 $\hookrightarrow = \text{low}$
- (d) False Common-B configuration is rarely used due to low Z_{in} and low A_{ISC} .