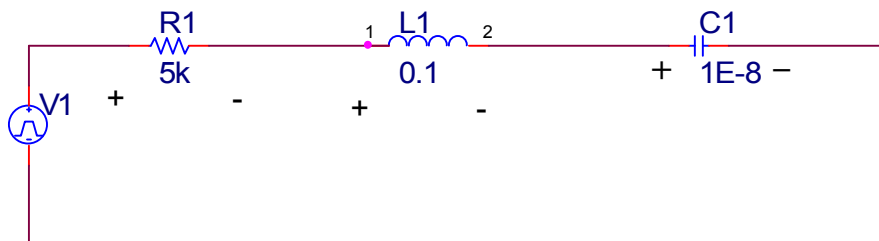


1) Initial Values, Final Values



At $t = 0^-$, the voltage across the capacitor is 5V (polarity shown), the current through the inductor is 2mA to the 'right' and the source is 10V. At $t = 0^+$, the voltage source becomes 5V and doesn't change for $t > 0$.

a. Determine the voltage across each component for $t = 0^-$. Determine the current through each component for $t = 0^-$.


V 10V 2mA
R 10V 2mA
L -5V 2mA
C 5V 2mA

b. Determine the voltage across each component for $t = 0^+$. Determine the current across each component for $t = 0^+$.

V 5V 2mA
R 10V 2mA
L -10V 2mA
C 5V 2mA

c. Determine the voltage across each component for t goes to ∞ . Determine the current across each component for t goes to ∞ .

V 5V 0mA
R 0V 0mA
L 0V 0mA
C 5V 0mA

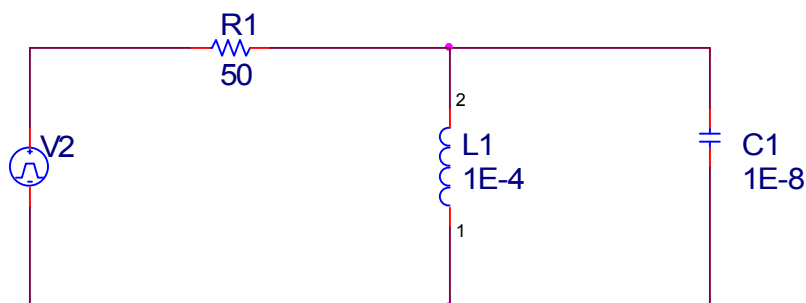

At $t = 0^-$, the voltage across the capacitor is 8V, the current through the inductor is 10mA 'downward' and the source is 10V. At $t = 0^+$, the voltage source becomes 3V and doesn't change for $t > 0$.

V 10V 40mA
R 2V 40mA
L 8V 10mA
C 8V 30mA

d. Determine the voltage across each component for $t = 0^-$. Determine the current through each component for $t = 0^-$. Determine the source voltage at $t = 0^-$.

V 3V -100mA
R -5V -100mA
L 8V 10mA
C 8V -110mA

e. Determine the voltage across each component for $t = 0^+$. Determine the current across each component the $t = 0^+$.

f. Determine the voltage across each componenet for t goes to ∞ . Determine the current across each component for t goes to ∞ .

V 3V 60mA
R 3V 60mA
L 0V 60mA
C 0V 0mA

2) Circuits and Differential Equations

$$IR + IC + IC = 0$$


$$(V_a - V_s)/R + \int (V_a/L) dt + C \cdot dV_a/dt = 0$$

$$V_a/R + \int (V_a/L) dt + C \cdot dV_a/dt = V_s/R$$

$$C \cdot dV_a/dt + V_a/R + \int (V_a/L) dt = V_s/R$$

$$C \cdot d^2 V_a/dt^2 + 1/R \cdot dV_a/dt + V_a/L = 1/R \cdot dV_s/dt$$
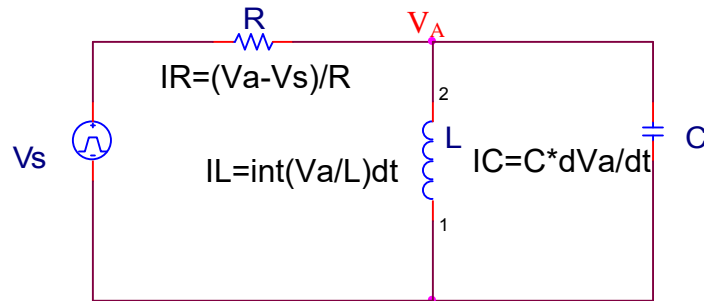
$$d^2 V_a/dt^2 + 1/RC \cdot dV_a/dt + V_a/LC = 1/RC \cdot dV_s/dt$$



a. In the above the circuit, find the differential equation for the voltage across the capacitor C, $V_C(t)$. The source is an arbitrary source.


$$d^2 V_a/dt^2 + 1/RC \cdot dV_a/dt + V_a/LC = 1/RC \cdot dV_s/dt$$

b. For the differential equation, determine the expression for the attenuation constant α , and the resonant frequency, ω_0 .

$$\alpha = 1/(2RC)$$

$$\omega_0 = 1/\sqrt{LC}$$

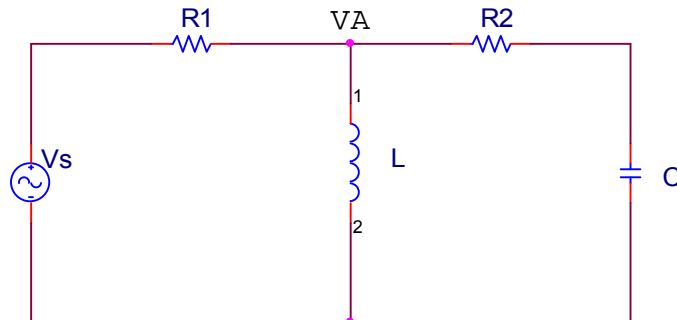c. In the circuit below, find a differential equation for the voltage across C, $V_C(t)$. The source is an arbitrary source.




d. For the differential equation, determine symbolic expressions for the attenuation constant, α , and the resonant frequency, ω_0 , in terms of R_1 , R_2 , L and C .

3) RLC Series Circuits

$$LCdV_c/dt + CR_{th}V_c + \int(V_c)dt = \int(V_{th})$$

$$LCd^2V_c/dt^2 + CR_{th}dV_c/dt + V_c = V_{th}$$
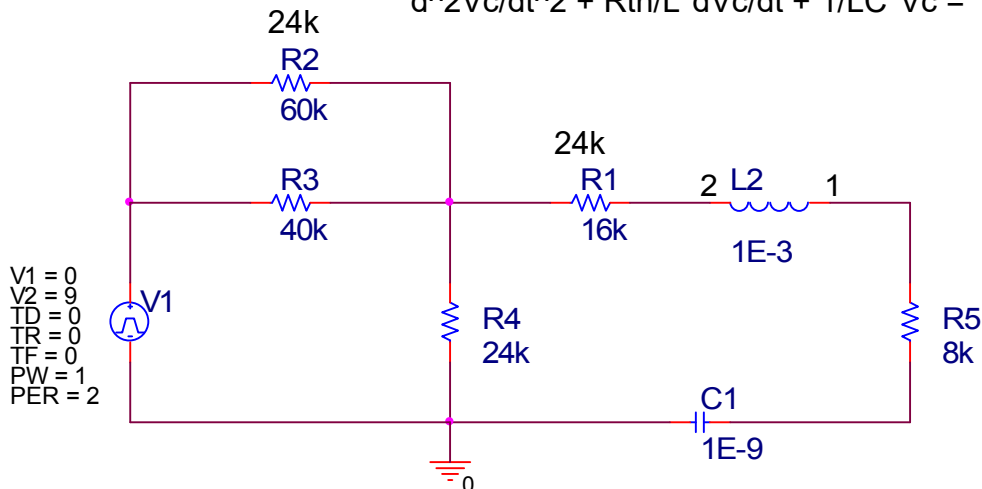
$$d^2V_c/dt^2 + R_{th}/L*dV_c/dt + 1/LC*V_c = 1/LC*V_{th}$$




In the above circuit, the initial conditions are zero and the source can be considered a step function, $9u(t)$.

- Determine the simplified circuit schematic. (Hint: Thevenin equivalent with **inductor and capacitor** as a load...and yes, two components can be a load!). $V_{TH}=4.5$, $I_{TH}=0.125mA$, $R_{TH}=36k$, Load: L and C
- What is the initial ($t = 0+$) current through the capacitor? What is the initial ($t = 0+$) voltage through the capacitor? $I=0$, $V=0$
- What is the DC steady state current through the capacitor as t approaches ∞ ?
 $I=0$
- What is the differential equation defining the current through the capacitor?
 $d^2V_c/dt^2 + R_{th}/L*dV_c/dt + 1/LC*V_c = 1/LC*V_{th}$
- Based on the differential equation, determine the s-polynomial for the circuit.
 $s^2 + R_{th}/L*s + 1/LC = 0$ $s^2 + 36*10^6*s + 10^{12}$
- Determine the roots of the polynomial
 $-2.7799*10^4$, $-3.5972201*10^7$
- Is the system underdamped, overdamped or critically damped?
overdamped
- Determine the general expression for the current through the capacitor (You do not need to determine the coefficients).

$$A1e^{-2.7799*10^4 t} + A2e^{-3.5972201*10^7 t} + A3$$

Problem 4) RLC series circuits

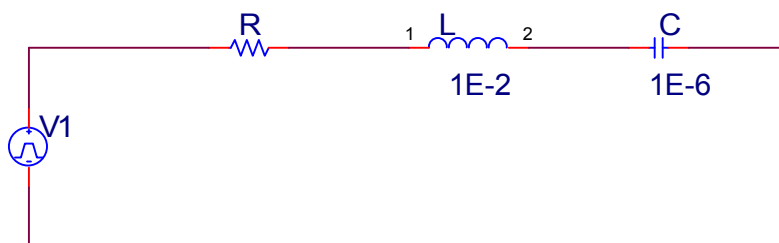

In the above circuit, the source voltage is 5V for $t < 0$ and 10 V for $t > 0$

a. What is the initial ($t=0^+$) voltage across the inductor? What is the initial ($t=0^+$) current through the inductor?

5V, 0A

b. What is the DC steady state current through the inductor at t approaches ∞ .

0A

c. Symbolically (no values, just R, L, C etc.), what is the differential equation defining the voltage across the inductor? $V_L + V_R + V_C = V_S$, $I_L = I_C = I_R = I_S$ $\frac{d}{dt}(I_L) + \frac{d}{dt}(I_L) R/L + 1/LC * I_L = 1/L * \frac{d}{dt}(V_S)$
 $L dI_L/dt + I_L R + 1/C \int (I_L) = V_S$

d. For $R = 4k\Omega$, determine the voltage across the inductor as a function of time for $t > 0$. (Hint: Use differential equation for current through the inductor. Then use the differential relationship between inductor current and inductor voltage.) $a = R/2L = 2E5$, $w = 1/\sqrt{LC} = 1E4$, $a > w$, overd

$I_L = y$, $y'' + y' 4E5 + 1E8 * y = 1E2 * V_S'$ $a_1 = -250$, $a_2 = -4E5$, $y(t) = A_1 e^{250t} + A_2 e^{4E5t}$

e. For $R = 200\Omega$, determine the voltage across the inductor as a function of time for $t > 0$.

f. For $R = 50\Omega$, determine the voltage across the inductor as a function of time for $t > 0$.

d) $y(0) = A_1 e^0 + A_2 e^0 = 0$ Amps, $A_1 + A_2 = 0$, $A_1 = -A_2$ $1599A_2 = 2$, $A_2 = 2/1599 \approx 1.25E-3$, $A_1 \approx -1.25E-3$

$d/dt(I_L) * L = V_L$, $d/dt(I_L) = V_L/L = 5E2$ $y'(0) = 250A_1 e^0 + 4E5A_2 e^0 = 500$, $250A_1 + 4E5A_2 = 500$, $A_1 + 1600A_2 = 2$

$I_L(t) = -1.25E-3 * e^{250t} + 1.25E-3 * e^{4E5t}$, V

$V_L(t) = -1.25E-3 * 250E-2 * e^{250t} + 1.25E-3 * 4E5E-2 * e^{4E5t} = -3.125E-3 * e^{250t} + 5 * e^{4E5t}$

$V_L(t) = -3.125E-3 * e^{250t} + 5 * e^{4E5t}$

e) $a = R/2L = 1E4$, $w = 1/\sqrt{LC} = 1E4$, $a = w$, critD $a_1 = a_2 = 1E4$ $I_L(t) = A_1 e^{-1E4t} + A_2 t e^{-1E4t}$

$I_L(0) = 0 = A_1$, $A_1 = 0$, $I_L(t) = A_2 t e^{-1E4t}$, $I_L'(t) = A_2 e^{-1E4t} - 1E4 A_2 t e^{-1E4t}$, $I_L'(0) = A_2 = 5E2$, $A_2 = 500$

$I_L(t) = 500 t e^{-1E4t}$, $V_L(t) = 5 * e^{-1E4t} - 5E4 * t e^{-1E4t}$

f) $a = R/2L = 2.5E3$, $w = 1E4$, $a < w$, underD, $B = 9682.5$, $I_L(t) = e^{-2.5E3t} [A_1 \cos(9682t) + A_2 \sin(9682t)]$

$I_L(0) = 0 = A_1$, $A_1 = 0$, $I_L(t) = e^{-2.5E3t} [A_2 \sin(9682t)]$,


$I_L'(t) = [-2.5E3 e^{-2.5E3t} A_2 \sin(9682t)] + [e^{-2.5E3t} 9682 A_2 \cos(9682t)]$

$I_L'(0) = 9682 A_2 = 5E2$, $A_2 = .0516$, $I_L(t) = e^{-2.5E3t} [0.0516 \sin(9682t)]$

$V_L(t) = [.01 * -2.5E3 e^{-2.5E3t} 0.0516 \sin(9682t)] + [.01 * e^{-2.5E3t} 0.0516 * 9682 \sin(9682t)]$

$V_L(t) = [-1.29 e^{-2.5E3t} \sin(9682t)] + [5 e^{-2.5E3t} \sin(9682t)]$

4) RLC series design problem

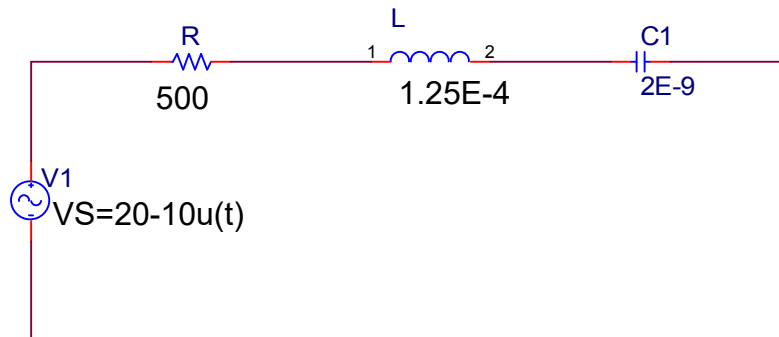


The above circuit has a capacitor voltage defined as

$$V_C(t) = 2E7t \cdot \exp(-2E6t) + 10 \cdot \exp(-2E6t) + 10$$

Determine the resistance, inductance, and source expression (the source is a step function of some kind).

critically damped: $V_C(0)=20$, $V_C(\infty)=10$, $V_S=20-10u(t)$
 $a=w=1/\sqrt{LC}=R/2L=2E6$, $5E-7=\sqrt{LC}$, $2.5E-13=LC$, $L=1.25E-4$
 $R/2L=2E6$, $R=4E6 \cdot 1.25E-4=500$

5) RLC Parallel Circuits

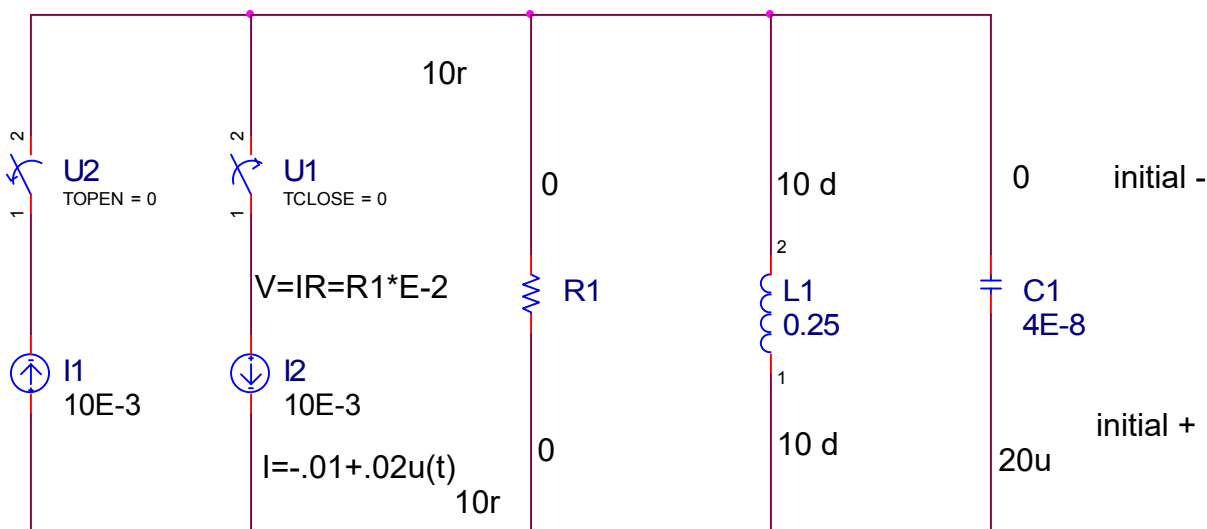

At $t = 0$, $U1$ closes and $U2$ opens.

a. What is the initial ($t=0+$) current through the capacitor? What is the initial ($t=0+$) voltage across the capacitor?
.02A, 0V

b. What is the DC steady state current through the capacitor as t goes to infinity?
0A

c. Find the current through the **CAPACITOR** as a function of time for $R = 12.5k$. (*Hint: Find the voltage across the capacitor equation first then use the current-voltage relationship of a capacitor to get the current! The reason why is because we know the initial conditions for a capacitor voltage not for capacitor current which is necessary to solve the problem*)

$$a=1E3, w=1E4, a < w, \text{ underD}, B=9950, VC(t)=[e^{-1E3t}A1\cos(9950t)]+[e^{-1E3t}A2\sin(9950t)]$$

d. Find the current through the **CAPACITOR** as a function of time for $R = 0.25k$.

$$\begin{aligned} \text{c) } VC(0)=0=A1, A1=0, VC(t)&=e^{-1E3t}A2\sin(9950t), \\ IC(t)&=C \cdot d/dt(VC(t))=[-1E3 \cdot 4E-8 \cdot e^{-1E3t}A2\sin(9950t)]+[9950 \cdot 4E-8 \cdot e^{-1E3t}A2\cos(9950t)] \\ IC(t)&=[-4E-5 \cdot e^{-1E3t}A2\sin(9950t)]+[3.97E-4 \cdot e^{-1E3t}A2\cos(9950t)] \\ IC(0)&=0.02=3.97E-4 \cdot A2, A2=50.25, VC(t)=50.25 \cdot e^{-1E3t} \cdot \sin(9950t), \\ IC(t)&=4E-8 \cdot 50.25 \cdot [[-1E3 \cdot e^{-1E3t} \cdot \sin(9950t)]+[9950 \cdot e^{-1E3t} \cdot \cos(9950t)]] \\ IC(t)&=[-2.01E-3 \cdot e^{-1E3t} \cdot \sin(9950t)]+[2E-2 \cdot e^{-1E3t} \cdot \cos(9950t)] \end{aligned}$$

$$\begin{aligned} \text{d) } a=5E4, w=1E4, a > w, \text{ overD}, a1=-1010, a2=-98990, VC(t)&=A1e^{1010t}+A2e^{98990t} \\ VC(0)=0=A1+A2, A1=-A2, IC(t)&=4E-8[1010A1e^{1010t}+98990A2e^{98990t}] \\ IC(t)&=4.04E-5A1e^{1010t}+3.95E-3A2e^{98990t} \\ IC(0)&=2E-2=-4.04E-5A2+3.95E-3A2=3.92E-3A2, 3.92E-3A2=2E-2, A2=5.103, A1=-5.103 \\ VC(t)&=-5.103 \cdot e^{1010t}+5.103 \cdot e^{98990t} \\ IC(t)&=-2.06E-4 \cdot e^{1010t}+2.02E-2 \cdot e^{98990t} \end{aligned}$$