

Exam-02 – BJTs and BJT circuits

1. This question concerns Class-D amplifiers.
 - (a) Consider a Class-D amplifier that serves as an audio amplifier. Assume that the input of the Class-D amplifier is a sine wave (originating from an audio signal). Sketch the audio input signal into the audio amplifier. Then sketch the associated output signal of the Class-D amplifier (the output signal is received by a loudspeaker).
 - (b) Assume that a Class-D amplifier is used to drive the electric motor of an electric car. Sketch the output signal of the Class-D amplifier (received by the motor) when the electrical power is 10% of its maximum. Then sketch the output signal for 90% of its maximum.
 - (c) What is a marked advantage of the Class-D amplifier? Explain your answer.

2. Consider a two-stage transistor amplifier with the 1st stage being a common-emitter npn BJT circuit, and the 2nd stage being a common-collector npn BJT circuit. The two stages are separated by a DC blocking capacitor. Each stage has a base voltage divider circuit consisting of two resistors (R_{B1} and R_{B2} for the 1st stage, and R_{B3} and R_{B4} for the 2nd stage). The BJTs have a $\beta = 100$. The power supply voltage $V_{CC} = 10$ V DC.
 - (a) Sketch the circuit diagram.
 - (b) Sketch the small-signal AC equivalent circuit diagram.
 - (c) Calculate the output impedance of the 2nd stage.
 - (d) Choose the circuit components of the 2nd stage to yield an output impedance of $100\ \Omega$ and choose the emitter current of the transistor so that the DC operating point is in the middle of the load line. Give the value of voltage V_{CE} (numerical value) and the emitter current (I_E) (numerical value).
 - (e) Determine the base voltage (V_B) and base current (I_B) of the 2nd stage.
 - (f) How should the current through the base voltage divider compare with the base current of the 2nd stage? Choose the current through the base voltage divider. Determine the associated resistances R_{B3} and R_{B4} (numerical values).
 - (g) Sketch the circuit diagram of the 2nd stage of the amplifier and give all resistance values.
 - (h) Sketch the small-signal equivalent circuit of the 1st stage of the transistor amplifier. Derive the voltage amplification (A_{VOC}) of the 1st stage.
 - (i) Assume that the collector resistance is $200\ \Omega$. Choose the emitter current of the transistor such that the voltage amplification ($|A_{VOC}|$) of the 1st stage has a value of 20.
 - (j) Determine the base voltage (V_B) and base current (I_B) of the 1st stage.
 - (k) How should the current through the base voltage divider compare with the base current of the 1st stage? Choose the current through the base voltage divider. Determine the associated resistances R_{B1} and R_{B2} .

3. Are the following statements True or False? Justify your answer.
 - (a) An ideal transistor amplifier has an infinite input impedance and a common-emitter BJT amplifier comes close to the ideal.
 - (b) A DC blocking capacitor may also be referred to as a low-frequency pass filter.