

1) Equivalent circuits



- a. For $I = 8\angle 45^\circ \text{mA}$ in phasor form with a 1.59kHz frequency, determine the voltage V_1 in the time domain form.

$$\omega_1 := 2 \cdot \pi \cdot 1.59 \cdot 10^3 = 9.99 \times 10^3$$

$$L_1 := 25 \cdot 10^{-3} \cdot \text{H}$$

$$Z_{EQ} = Z_{R1} + Z_{L1} = R + j\omega_1 \cdot L_1$$

$$\omega_1 \cdot L_1 = 249.757 \text{ H}$$

$$R_1 := 6 \text{ k}\Omega \quad Z_{L1} := (10j \cdot 10^3 L_1) = 250i \text{ H}$$

$$Z_{EQ} = 6000 + 250j \quad \text{in polar form the next part is easier.}$$

$$\sqrt{6000^2 + (250)^2} = 6.005 \times 10^3$$

$$\text{atan}\left(\frac{250}{6000}\right) = 2.386 \cdot \text{deg}$$

$$Z_{EQ} = 6005 \angle 2.386^\circ$$


$$V_1 = I \cdot Z_{EQ} = (0.008 \angle 45^\circ) \cdot (6005 \angle 2^\circ) = 48.04 \angle 47^\circ$$

$$6005 \cdot 0.008 = 48.04$$

$$\omega_1 = 9.99 \times 10^3$$

$$V_1 = 48.04 \cdot \cos(9.99 \times 10^3 t + 47^\circ)$$

2) First order circuits

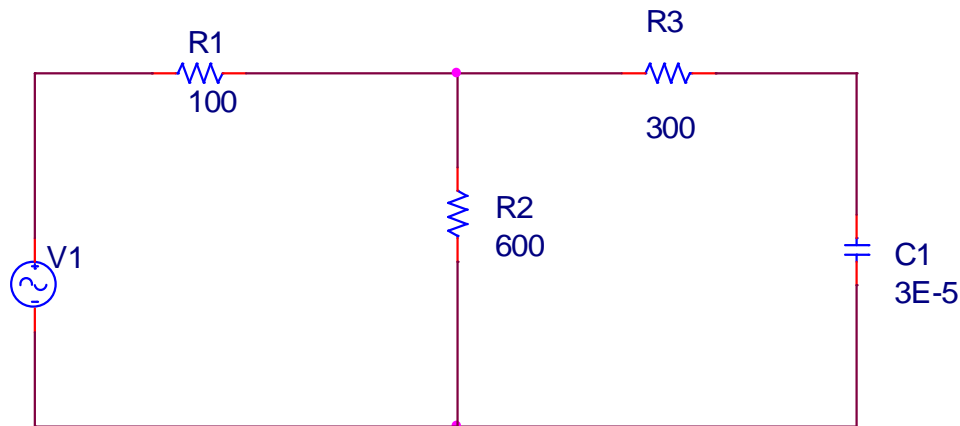

The source is a 15V sinusoidal signal with a frequency of 31.83Hz and has zero phase.

$$Z_1 := 100\Omega \quad Z_2 := 600\Omega \quad Z_3 := 300\Omega \quad C_{1a} := 3 \cdot 10^{-5} \quad \omega_2 := 2 \cdot \pi \cdot 31.83\text{Hz}$$

$$V_{1a} := 15\text{V} \quad \frac{-i}{C_{1a} \cdot \omega_2} = -166.672i \text{ s} \quad \omega_2 = 199.994 \frac{1}{\text{s}}$$

$$Z_{C1a} := -166.7i\Omega$$

a. Determine the phasor expression for the voltage source.

$$V_1 = 15\angle 0^\circ$$

b. Determine the equivalent impedance seen by the source.

$$\frac{(Z_{C1a} + Z_3) \cdot Z_2}{Z_{C1a} + Z_3 + Z_2} + Z_1 = (313.268 - 71.631i) \Omega$$

*Either rectangular or
phasor/polar form is
fine.*

$$\sqrt{(313)^2 + (-71.6)^2} = 321.085$$

$$\text{atan}\left(\frac{-71.6}{313}\right) = -12.885 \cdot \text{deg}$$

$$Z_{EQ2\text{phasor}} := 321 \angle -12.9\text{deg}$$

c. Determine the phasor expression for the current through the source.

$$I_s = \frac{V_1}{Z_{EQ2\text{phasor}}} = \frac{15\angle 0^\circ}{321\angle -13^\circ} = 47\angle 13^\circ \text{ mA} \quad \frac{15}{321} = 0.047$$

d. Determine the phasor expression for the voltage across C1.

Using a current divider, we can obtain the current through C1.

$$I_{C1a} = \frac{Z_2}{Z_2 + Z_3 + Z_{C1a}} \cdot (47\angle 13^\circ \text{ mA}) \quad \frac{Z_2}{Z_2 + Z_3 + Z_{C1a}} = 0.645 + 0.119i$$

$$\sqrt{0.645^2 + 0.119^2} = 0.656$$

$$\text{atan}\left(\frac{0.119}{0.645}\right) = 10.453^\circ$$

$$(0.047\angle 13^\circ) \cdot (0.656\angle 10.45^\circ)$$

$$0.047 \cdot 0.656 = 0.031$$

$$I_{C1a} = 31\angle 23.45^\circ \text{ mA}$$

$$13 + 10.45 = 23.45$$

$$V_{C1a} = Z_{C1a} \cdot I_{C1a} = 166\angle -90^\circ \Omega \cdot (0.031\angle 23.45^\circ) \text{ A} = 5.146\angle -66.55^\circ \text{ V}$$

$$166 \cdot 0.031 = 5.146$$

$$-90 + 23.45 = -66.55$$

e. Determine the time domain expression for the voltage across C1.

$$V_{C1a} = 5.146 \cdot \cos(200t - 66.55^\circ)$$

f. Determine the transfer function, $H(s) = V_{C1}(s) / V_s(s)$, for the above RC circuit.

Find the Thevinin equivalent

$$V_{TH} := \frac{Z_2}{Z_1 + Z_2} \cdot V_{1a} = 12.857 \text{ V}$$

$$R_{TH} := \frac{Z_1 \cdot Z_2}{Z_1 + Z_2} + Z_3$$

$$R_{TH} = 385.714 \Omega$$

$$V_{C1a} = \frac{\frac{1}{sC_{1a}}}{385.7 + \frac{1}{sC_{1a}}} \cdot V_{TH}$$

because we need V_s substitute in V_{th} equation

$$V_{C1a} = \frac{\frac{1}{sC_{1a}}}{385.7 + \frac{1}{sC_{1a}}} \cdot \left(\frac{Z_2}{Z_1 + Z_2} \cdot V_s \right) \qquad \frac{Z_2}{Z_1 + Z_2} = 0.857$$

$$H(s) = \frac{V_{C1}}{V_s} = \frac{-166.7j}{385.7 - 166.7j} \cdot 12.857$$

g. Verify your solution to part d. using the transfer function (remember $s = j\omega$ in AC steady state).

$$H(j200) = \frac{-166.7j}{385.7 - 166.7j} \cdot 12.857$$

for $\omega = 200 \text{ rad/s}$


$$\frac{-166.7j}{385.7 - 166.7j} \cdot 12.857 = 2.024 - 4.682j$$

$$\sqrt{2.024^2 + (-4.682)^2} = 5.101$$

$$\text{atan}\left(\frac{-4.682}{2.024}\right) = -66.621 \cdot \text{deg}$$

$$H_{j200} = 5.1 < -66 \text{deg}$$

3) Phasors- RLC

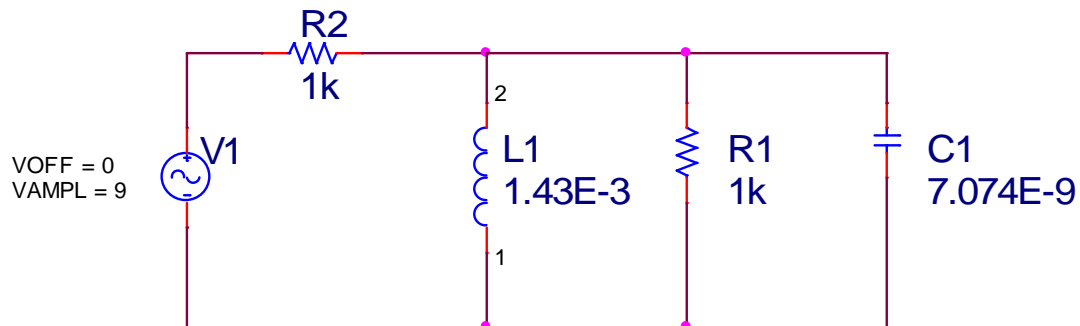

a. Using phasor analysis, determine the voltage across the capacitor when the source is 50kHz.

Find the admittance, the invert to get inductance. Use this in your analysis.

$$Y_{EQ} = \frac{1}{R_1} + \frac{1}{s \cdot L_1} + s \cdot C_1$$

$$\omega_3 := 2 \cdot \pi \cdot 50 \times 10^3$$

$$\omega_3 = 3.142 \times 10^5$$

$$Y_{EQ} = \frac{1}{R_1} + \frac{1}{j\omega L_1} + j\omega C_1$$

$$Y_{EQ} := \left[\frac{1}{1000} + \frac{-j}{(\omega_3) \cdot (1.43 \cdot 10)^{-3}} + (\omega_3) \cdot 7.07j \cdot 10^{-9} \right] \quad \begin{aligned} (\omega_3 \cdot 1.433 \cdot 10^{-3})^{-1} &= 2.221 \times 10^{-3} \\ (\omega_3) \cdot 7.07j \cdot 10^{-9} &= 2.221i \times 10^{-3} \end{aligned}$$

$$Y_{EQ} = 0.001 - 0.0022j + 0.0022j \quad \text{they cancelled}$$

$$Y_{EQ} = 0.001$$

$$Z_{EQ} = 1000$$

$$V_C = \frac{Z_{EQ}}{Z_{EQ} + R_2} \cdot V_1 = \frac{1000}{1000 + 1000} \cdot (9 \angle 0^\circ)$$

$$V_C = 4.5 \angle 0^\circ$$

b. Using phasor analysis, determine the voltage across the capacitor when the source is 50 Hz.
(reminder: -90degrees is -j) **Partial answer check: ZRLC = 0.45j**

$$\omega_{3b} := 2 \cdot \pi \cdot 50$$

$$Y_{EQ} = \frac{1}{1000} + \frac{-j}{(314) \cdot 1.43 \cdot 10^{-3}} + j \cdot (314) \cdot 7.07 \cdot 10^{-9}$$

$$\omega_{3b} = 314.159$$

$$Y_{EQ} = 0.001 - 2.22j + 0.0000022j$$

$$Y_{EQ} = 0.001 - 2.22j \quad \sqrt{0.001^2 + (-2.22)^2} = 2.22$$

$$Y_{EQ} = 2.22 \angle -90^\circ \quad \text{atan}\left(\frac{-2.22}{0.001}\right) = -89.974 \cdot \text{deg}$$

$$Y_{EQ} = -2.22j$$

$$Z_{EQ} = 0.45j \quad \text{Answer check}$$

$$V_C = \frac{Z_{EQ}}{Z_{EQ} + R_1} \cdot V_1 = \frac{0.45j}{0.45j + 1000} \cdot (9 \angle 0^\circ) \quad \text{Very close to 0}$$

At relatively low frequencies, the inductor looks like a short circuit.

c. Using phasor analysis, determine the voltage across the capacitor when the source is 50MHz
(50E6Hz).(reminder: 90degrees is j)

$$\omega_{3c} := 2 \cdot \pi \cdot 50 \cdot 10^6$$

$$Y_{EQ} = \frac{1}{1000} + \frac{-j}{(3.14 \cdot 10^8) \cdot 1.43 \cdot 10^{-3}} + j \cdot (3.14 \cdot 10^8) \cdot 7.07 \cdot 10^{-9}$$

$$\omega_{3c} = 3.142 \times 10^8$$

$$Y_{EQ} = 0.001 - 0.00000022j + 2.22j$$

$$Y_{EQ} = 0.001 + 2.22j \quad \sqrt{0.001^2 + (2.22)^2} = 2.22$$

$$Y_{EQ} = 2.22 \angle 90^\circ \quad \text{atan}\left(\frac{2.22}{0.001}\right) = 89.974 \cdot \text{deg}$$

$$Y_{EQ} = 2.22j$$

$$Z_{EQ} = -0.45j \quad \text{Answer check}$$


$$V_C = \frac{Z_{EQ}}{Z_{EQ} + R_1} \cdot V_1 = \frac{-0.45j}{-0.45j + 1000} \cdot (9 \angle 0^\circ) \quad \text{Very close to 0}$$

At relatively high frequencies, the capacitor looks like a short circuit.

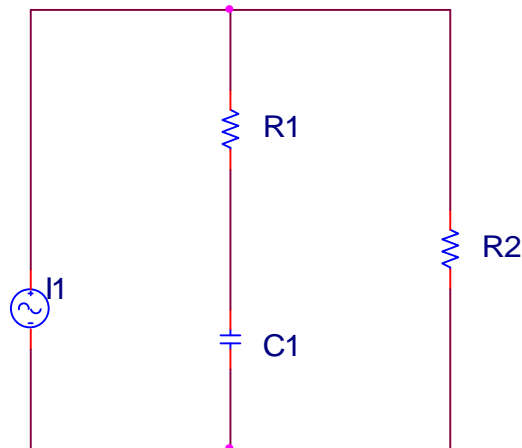4) Transfer functions

Determine the transfer functions in the following circuit. Determine the behavior of the transfer function as

$\omega \rightarrow 0$ and $\omega \rightarrow \infty$



- a. Voltage across C1 relative to the source voltage $H(s) = \frac{V_{C1}(s)}{I_1(s)}$
Using the current divider formula (then ohms law)

$$V_{C1} = \frac{1}{sC} \cdot \left(\frac{R_2}{R_2 + R_1 + \frac{1}{sC}} \cdot I_1 \right)$$


$$H(s) = \frac{V_{C1}}{I_1} = \frac{R_2}{s(R_2 + R_1) \cdot C + 1} = \frac{\frac{R_2}{[(R_1 + R_2) \cdot C]}}{s + \frac{1}{(R_1 + R_2)C}}$$

- b. Determine the magnitude of the transfer function as frequency approaches zero, $|H(s \rightarrow 0)|$

$$H(s \rightarrow 0) = \frac{\frac{R_2}{[(R_1 + R_2) \cdot C]}}{s + \frac{1}{(R_1 + R_2)C}} = \frac{\frac{R_2}{[(R_1 + R_2) \cdot C]}}{\frac{1}{(R_1 + R_2)C}} = R_2$$

- c. Determine the magnitude of the transfer function as frequency approaches infinity, $|H(s \rightarrow \infty)|$
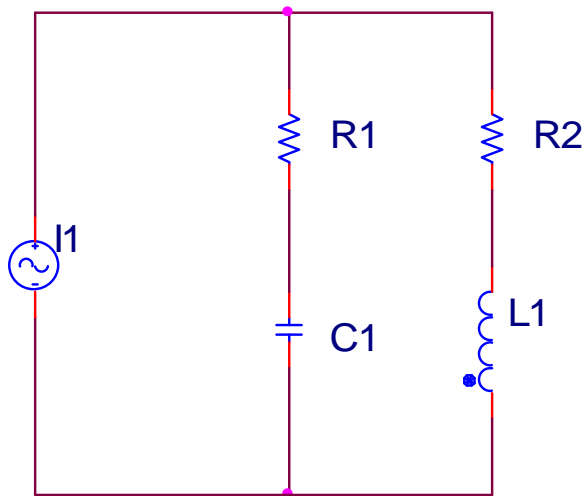
$$H(s \rightarrow \infty) = \frac{\frac{R_2}{[(R_1 + R_2) \cdot C]}}{s + \frac{1}{(R_1 + R_2)C}} = \frac{\frac{R_2}{[(R_1 + R_2) \cdot C]}}{s} = 0$$



d. Voltage across L_1 relative to the source current $H(s) = \frac{V_{L1}(s)}{I_1(s)}$

This is a current divider

$$H(s) = \frac{V_L(s)}{I_1(s)} = \frac{R_1 + \frac{1}{sC_1}}{R_1 + \frac{1}{sC_1} + R_2 + sL_1} sL_1 = \frac{s^2 R_1 C_1 L_1 + sL_1}{s^2 L_1 C_1 + sC_1(R_1 + R_2) + 1}$$

e. Determine the magnitude of the transfer function as frequency approaches zero, $|H(s \rightarrow 0)|$

$$H(s \rightarrow 0) \approx \frac{s^2 R_1 C_1 L_1 + sL_1}{s^2 L_1 C_1 + sC_1(R_1 + R_2) + 1} = sL_1 \rightarrow 0$$

As frequency goes to zero, an inductor becomes a short circuit and the voltage across the inductor goes to zero.

f. Determine the magnitude of the transfer function as frequency approaches infinity, $|H(s \rightarrow \infty)|$

$$H(s \rightarrow \infty) \approx \frac{s^2 R_1 C_1 L_1}{s^2 L_1 C_1} = R_1$$

As frequency goes to infinity, an inductor becomes an open circuit and the current goes through R_1 , with the associated voltage drop.