
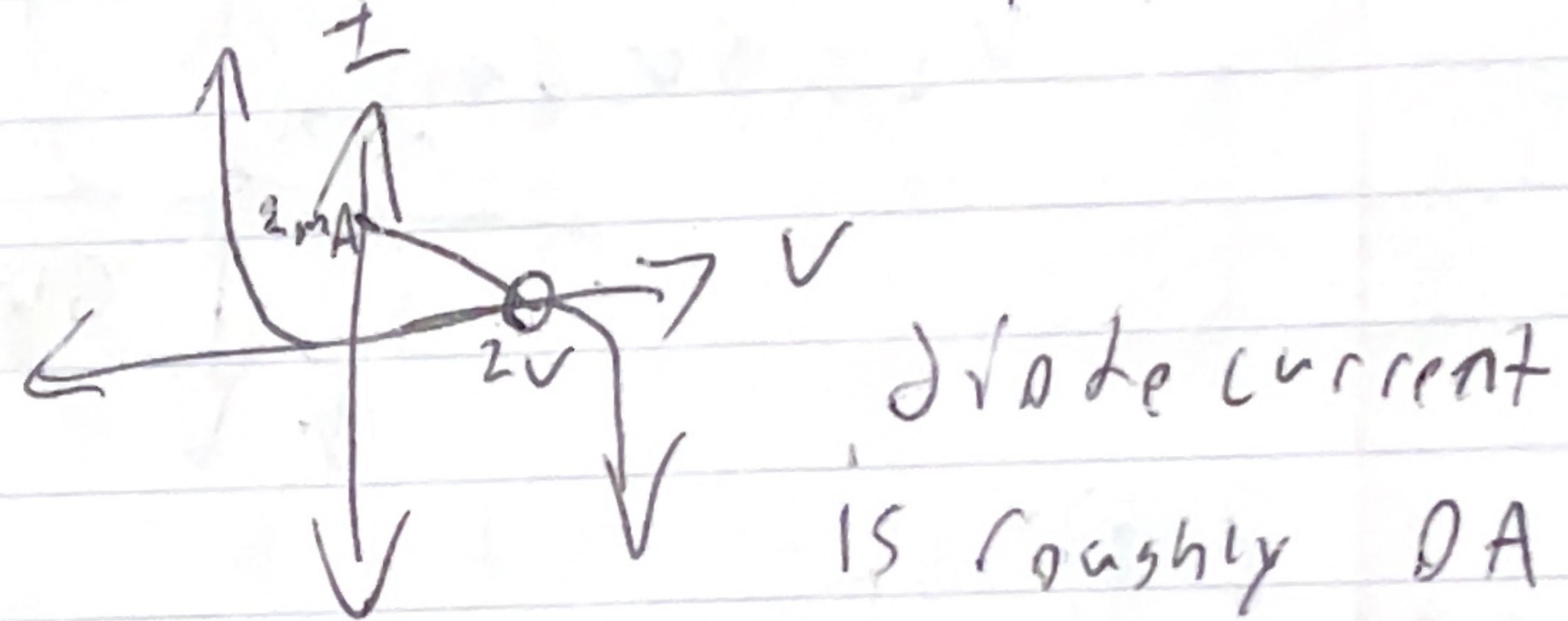


With 2V power source, current through diode is very high (lets all current through). Probably increase of  $10^6$  or  $10^9$ .

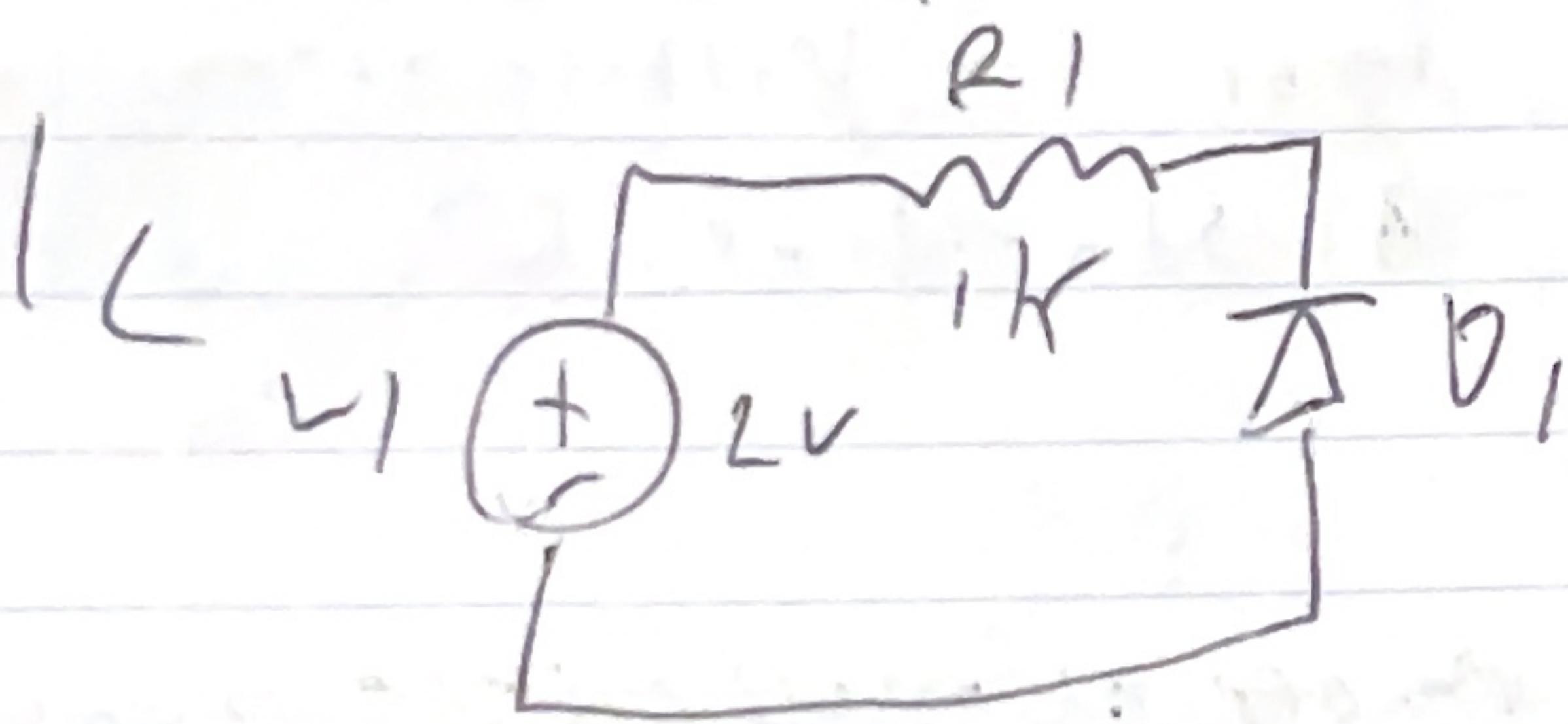(b)  $I = I_0 (e^{V/V_T})$   $I_0 = 10^{-9}$   $V_T = 26mV$

 $I = 10^{-9} (e^{2/0.026}) \rightarrow 2.55 \cdot 10^{-4} A$


Answers agree, both are very large numbers  
so they agree




1.2 voltage is flipped, so equation becomes

$I = 10^{-9} (e^{-2/0.026}) = 3.92 \cdot 10^{-4} A$

Numbers agree!

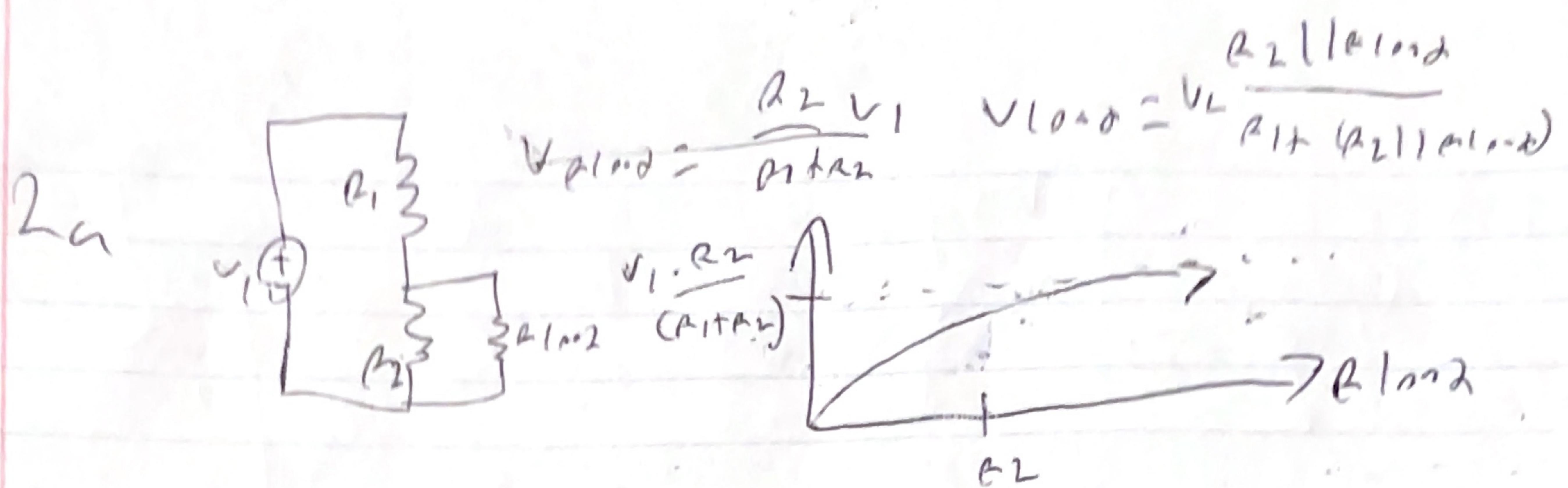

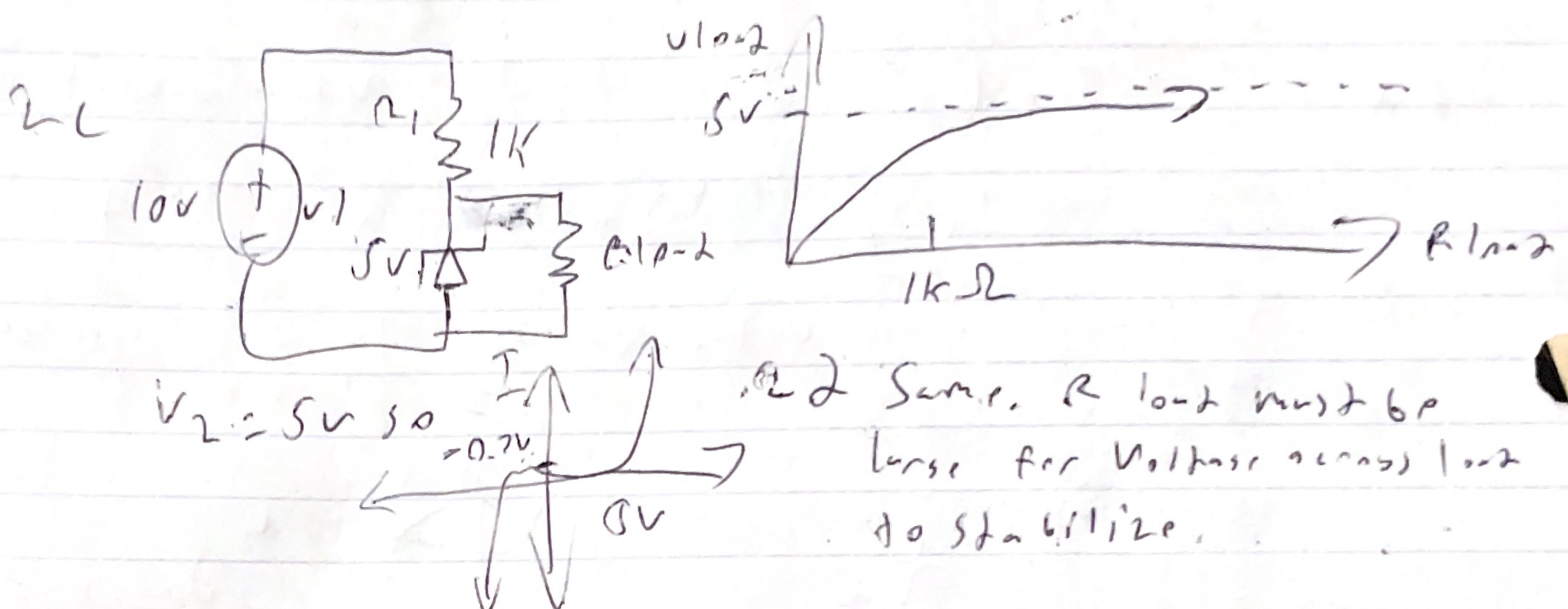26. Load must be much greater than other resistances  
otherwise current will go through load instead of circuit.




20. First circuit has a more adjustable core since  
switching  $R_1$  will result in load change's more.  
But second circuit, thanks to zero d.f.o.e., has  
a much more adjustable voltage stabilization, as it is  
equal to  $V_2$ .

~~$V_{source} = V_{mid} + V_2$~~

3a The Zener diode is there to smooth the voltage out.

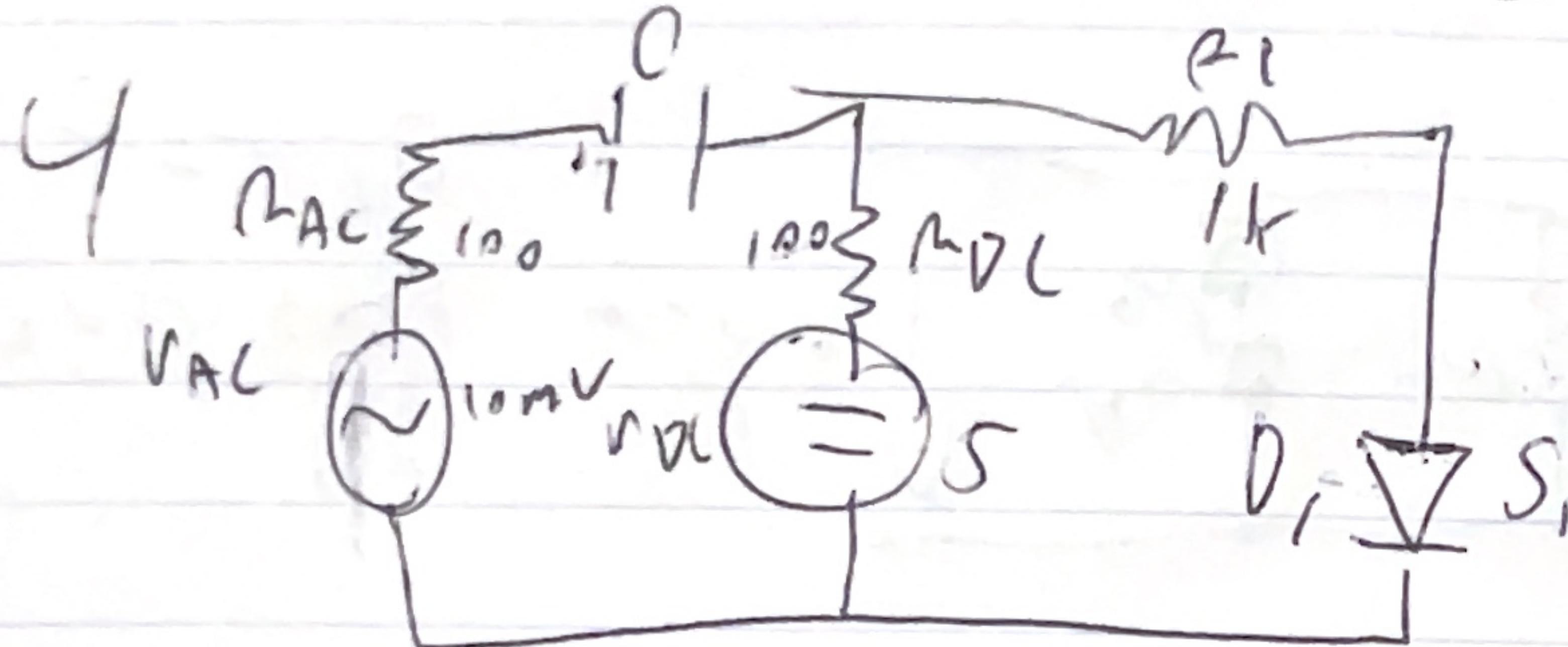3b A large part of the AC voltage is clipped off if  $V_A$  of  $V_{source}$  is  $> V_2$ .




4a  $V_{DC}$  sees  $1100\ \Omega$  resistance.  $R_{DC}$  and  $R_2$  in series since C shorts through  $\rightarrow 0\ \text{DC}$

$$I = \frac{V_{DC} - V_{diode}}{R} = \frac{4.3}{1100} = 3.9\ \text{mA} = I_{DC}$$

$$4b R_2 = \frac{V}{I_{DC}} = \frac{26\ \text{mV}}{3.9\ \text{mA}} = 6.66\ \Omega$$

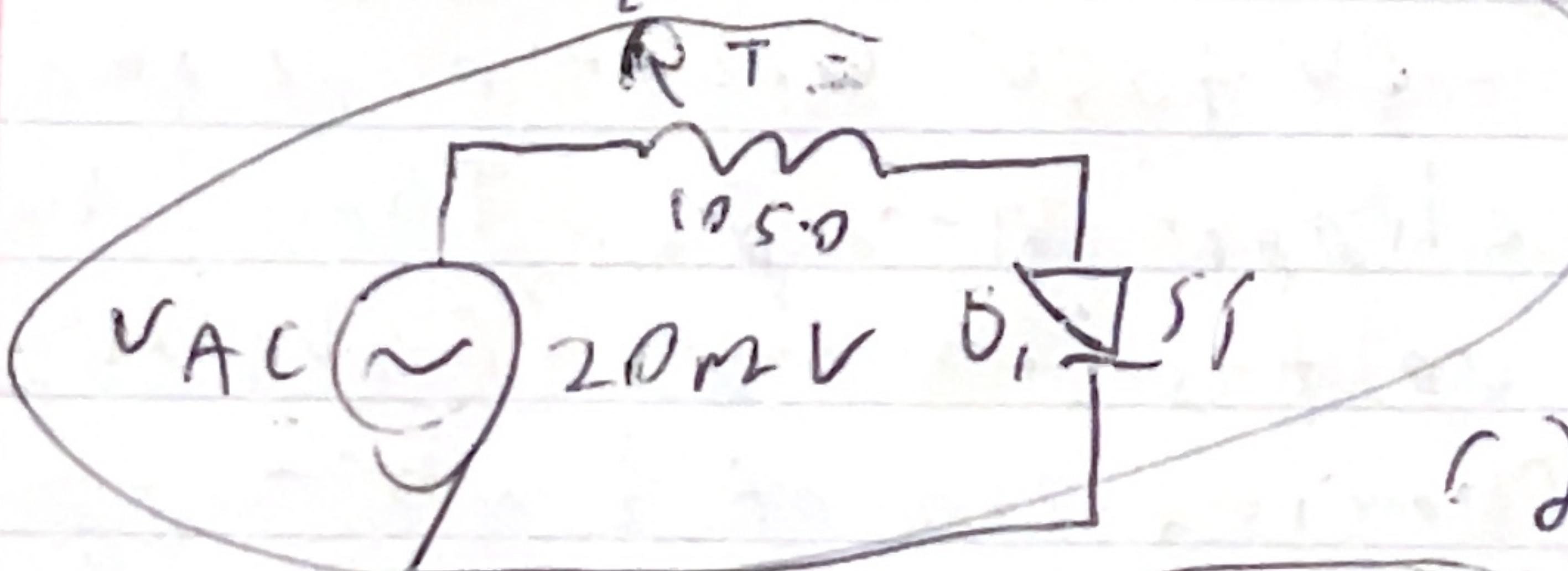Draw AC  $\leftrightarrow$  shorting DC so it can be shorted too with equivalent sources.  $R_{ACDC}$  becomes  $50\ \Omega$  and  $V_{AC} \rightarrow 20\ \text{mV}$




$$4c V_{AC}^{D_{1,2}} = \frac{R_2}{R+R_2} V_{AC}$$

$$R_2 = 6.66\ \Omega, R = 1050\ \Omega, V_{AC} = 0.02\ \text{V}$$

$$V_{AC}^{D_{1,2}} = 0.13\ \text{mV}$$

$$V = \pm 1\ \text{V}, V = 0.13\ \text{mV}, R = 6.66\ \Omega, I = 0.0195\ \text{mA}$$

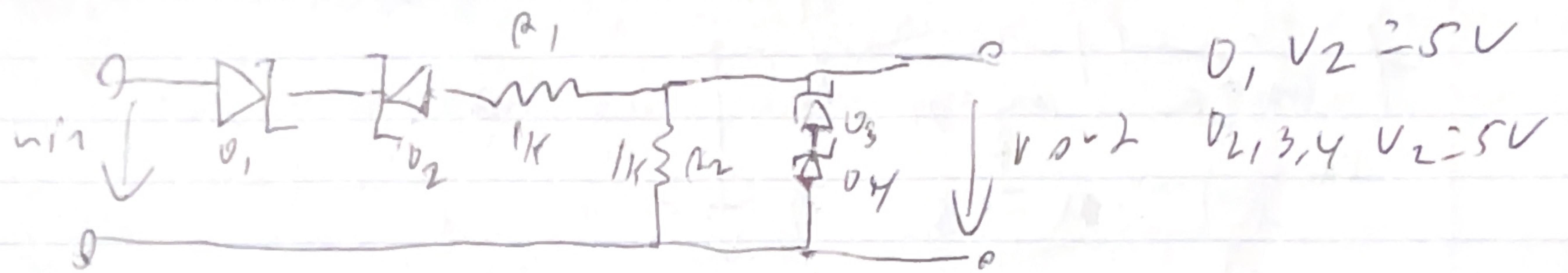
5a Diode threshold voltage is the voltage at which the diode has enough energy to "turn on". There are silicon zener diodes so the value for the circuit is  $-0.7V$ . Zener voltage is the voltage where reverse breakdown happens, which is  $5V$ . Let's current through. In the circuit it is  $5V$ .



$D_1$  and  $D_2$  make a reverse clipper.

$R_1$  and  $R_2$  make a  $\frac{1}{2}$  voltage divider.

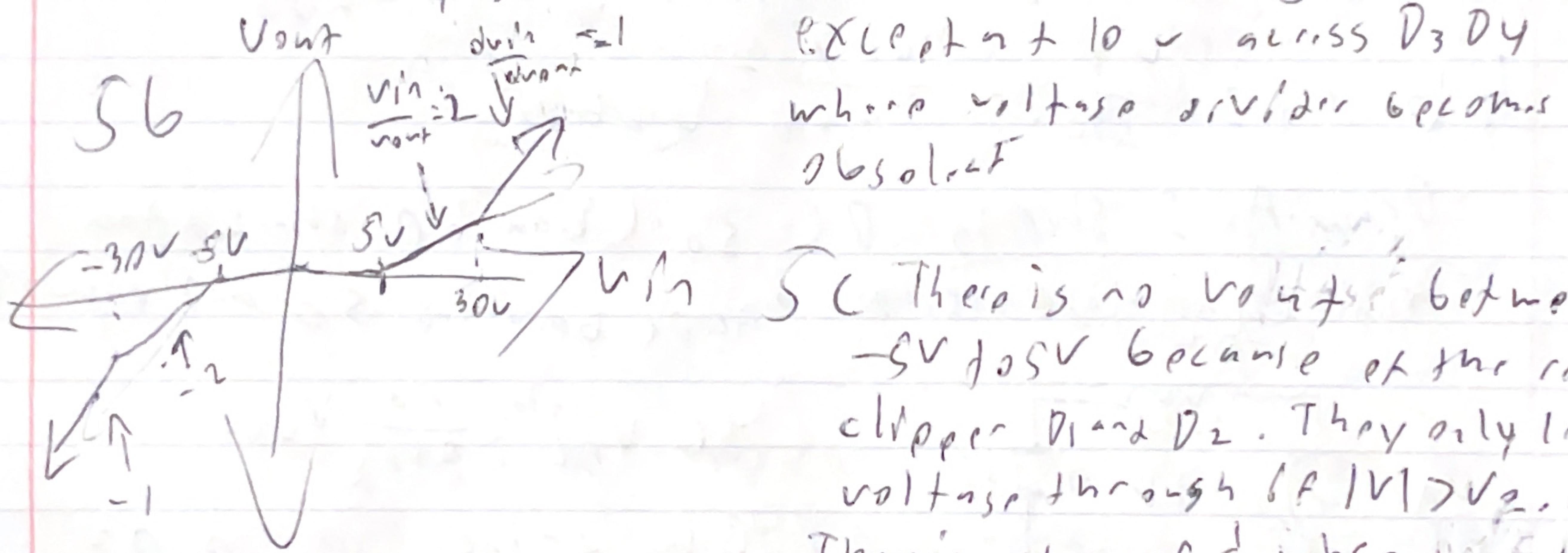$D_3$  and  $D_4$  smooth (no real effect on DC)



With SC There is no voltage between  $-5V$  and  $5V$  because of the reverse clipper  $D_1$  and  $D_2$ . They only let voltage through if  $|V| > 5V$ .

There is a slope of  $\frac{1}{2}$  when  $|V| > 5V$  ( $|V| > 5V$  and  $|V| < 10V$ ) and a slope of 1 when  $|V| > 10V$ . This is because

$D_1$  and  $D_2$  still have 10V,  $R_1$  and  $R_2$  halve the voltage, and it takes 10V going across  $D_3 D_4$  for voltage to go through.

$$\frac{1}{2}(x-10) = 10 \times 2 = 30$$

$$50 \Rightarrow (x-50) \rightarrow \frac{1}{2}x - \frac{5}{2}V \text{ and } \frac{5}{2}mA$$

$$\text{So } x = 17.5 \Rightarrow (12.5V \text{ and } 12.5mA)$$