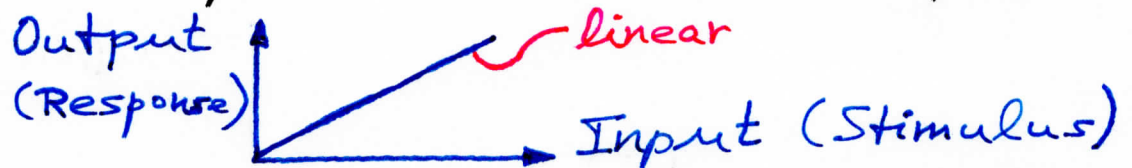


# Superposition principle

⇒ Superposition principle applies to linear systems

What is a linear system?

- \* Output  $\propto$  Input (Response  $\propto$  Stimulus or Effect  $\propto$  Cause)
- \* Output depends linearly on input
- \* Double input  $\Rightarrow$  Double output




**Superposition principle:** In a linear system having multiple sources (V or I sources) the total effect of the sources is the sum of the effects of each source.

Recall:  $\begin{array}{c} + \\ \text{---} | \text{---} \\ - \end{array}$  Ideal V source  $\Rightarrow R=0$   
 $\begin{array}{c} \text{---} ( \text{---} ) \text{---} \\ \text{---} \end{array}$  Ideal I source  $\Rightarrow R=\infty$

Q: Is a resistor a linear system?

Q: Is a diode a linear system?

# 1<sup>ST</sup> example

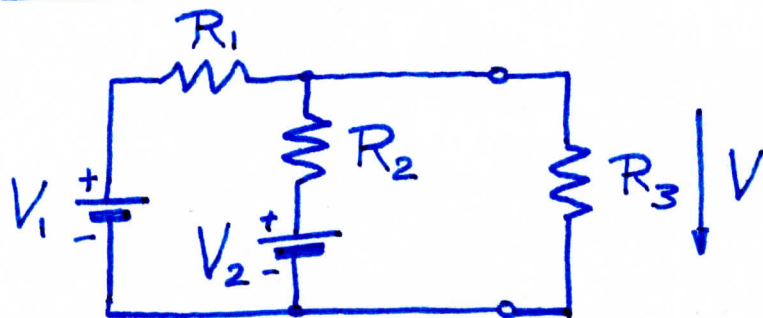

## Effect of $V_1$

Ohm:  $I_{R1} = V_1 / (R_1 + (R_2 \parallel R_3))$

$$\Rightarrow V = V_1 - I_{R1} R_1$$

$$= V_1 - \frac{V_1}{R_1 + (R_2 \parallel R_3)} R_1$$

## Effect of $V_2$

Ohm:  $I_{R2} = V_2 / (R_2 + (R_1 \parallel R_3))$


$$\Rightarrow V = V_2 - I_{R2} R_2$$

$$= V_2 - \frac{V_2}{R_2 + (R_1 \parallel R_3)} R_2$$

## Superposition

$$V = V_1 - \frac{V_1 R_1}{R_1 + (R_2 \parallel R_3)} + V_2 - \frac{V_2 R_2}{R_2 + (R_1 \parallel R_3)}$$

↪ Superposition

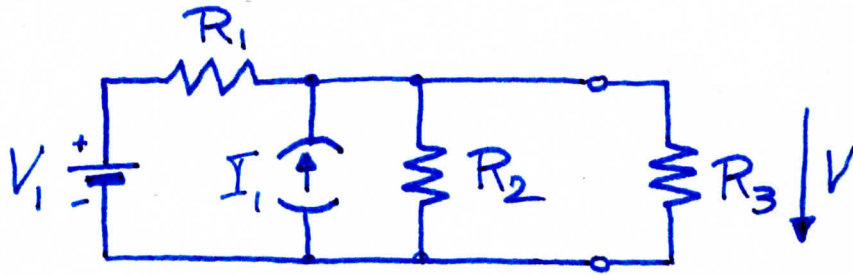2<sup>ND</sup> exampleEffect of  $V_1$ 

$$\text{Ohm } I_{R1} = \frac{V_1}{R_1 + (R_2 \parallel R_3)}$$

$$\Rightarrow V = V_1 - I_{R1} R_1$$

$$= V_1 - \frac{V_1}{R_1 + (R_2 \parallel R_3)} R_1$$

Effect of  $I_1$ 


$$V = V_{R3} = I_1 (R_1 \parallel R_2 \parallel R_3)$$

Superposition

$$V = V_1 - \frac{V_1 R_1}{R_1 + (R_2 \parallel R_3)} + I_1 (R_1 \parallel R_2 \parallel R_3)$$

↪ Superposition

### 3<sup>RD</sup> example

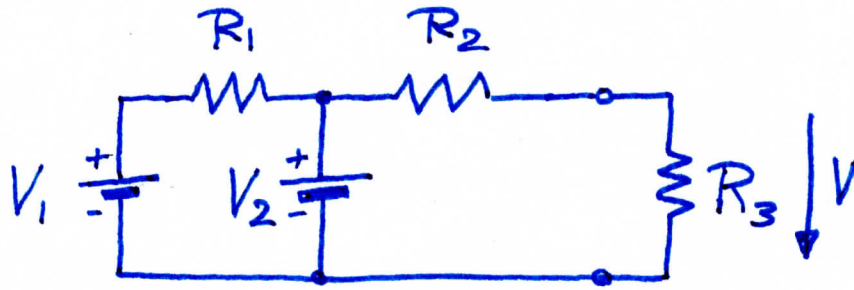

Consider the superposition principle.

Will  $V_1$  have any effect on  $V$ ?

Does  $V$  depend on  $V_1$ ?

Answers: No. Why?

#### Effect of $V_1$

$$V = 0$$

#### Effect of $V_2$

$$V = V_2 \frac{R_3}{R_2 + R_3} \quad (\text{voltage divider})$$


#### Superposition

$$V = 0 + V_2 \frac{R_3}{R_2 + R_3} = V_2 \frac{R_3}{R_2 + R_3}$$

└─ Superposition


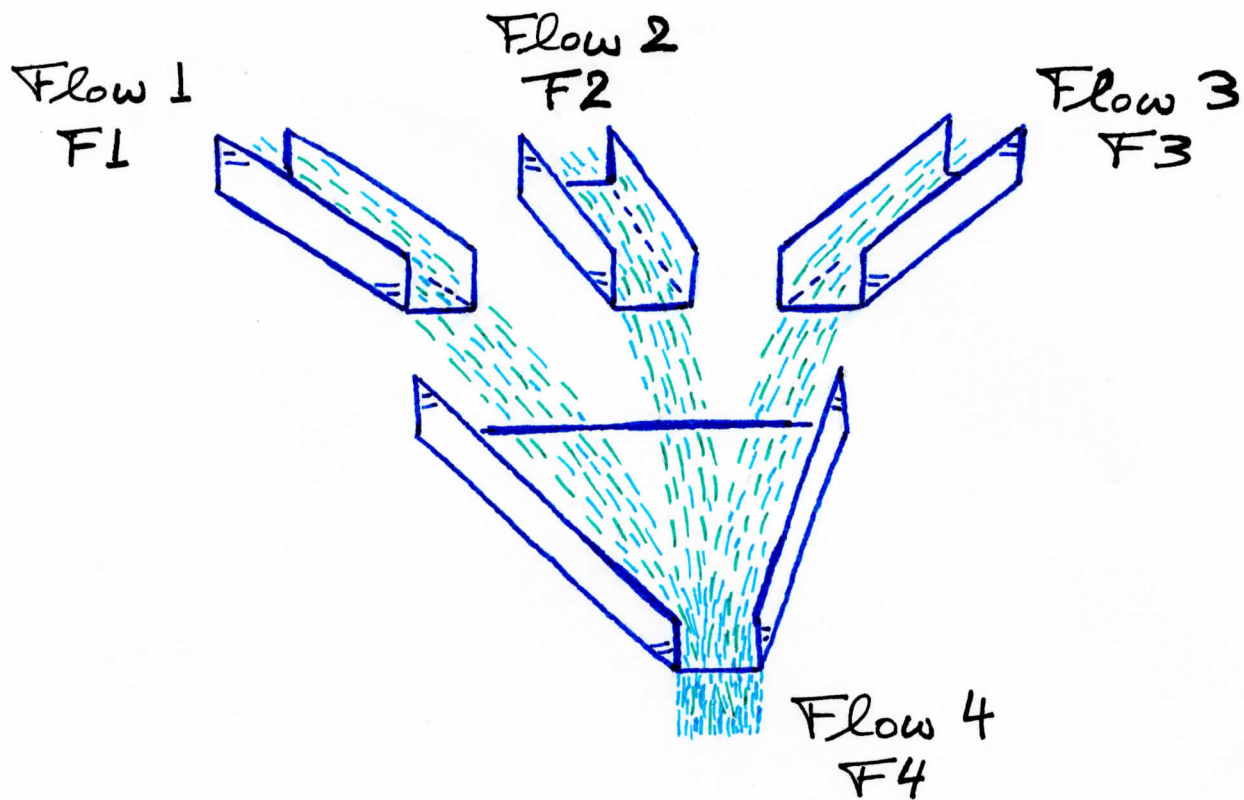
## Superposition principle $\Rightarrow$ Mechanical analog ⑤



Linear system:  $F_4 = F_1 + F_2 + F_3$

Effect =  $\Sigma$  Causes

Q: Starting with the above-shown linear mechanical system, how can we modify the system to make it a non-linear mechanical system?


$\Rightarrow$  Name two modifications!

Q: Can you give other examples of mechanical or electrical or acoustic or optical systems?

Q: Is our ear an acoustic system?

Q: Are most systems linear or non-linear systems?

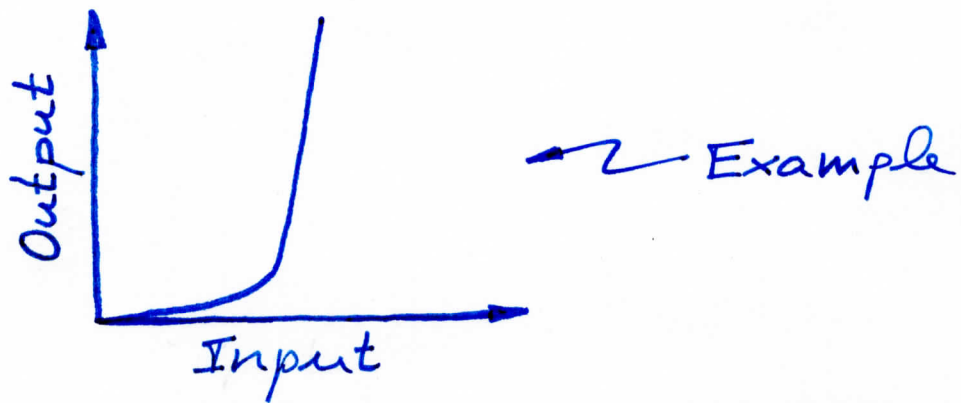Input-output characteristic of non-linear system:



Note: All systems can be linearized in a small range of operating conditions.

