
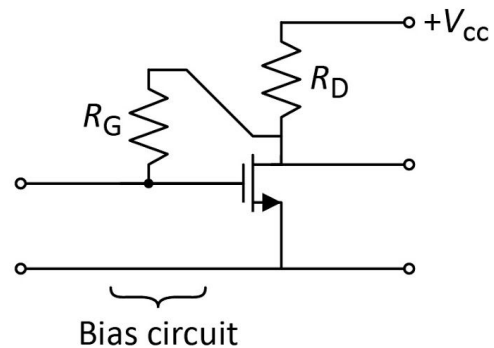


Homework 09

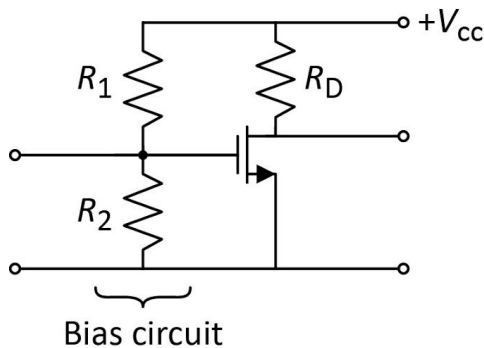1. **FET:** This problem concerns properties of FETs.
 - (a) Draw the I_D versus V_{DS} family of output curves of an FET (I_D on vertical axis or ordinate and V_{DS} on horizontal axis or abscissa). Indicate three significant regions in the drawing and name these regions.
 - (b) Draw the I_D versus V_{GS} curve of an FET. Indicate two significant regions in the drawing and name these regions.
 - (c) What is the relationship between source current and drain current of an FET?
 - (d) What occurs when the gate voltage reaches the threshold voltage?
2. **FET:** This problem also concerns properties of FETs.
 - (a) What is the value of any DC gate current?
 - (b) The input power of a transistor may be defined as **input voltage \times input current**. Given this definition, what is the input power of an FET? When comparing BJTs with FETs, which one of the two consumes a higher input power?
 - (c) Why is low input power (or zero input power) an advantage?
 - (d) Point out some similarities between BJTs and FETs.
 - (e) Point out some differences between BJTs and FETs.
3. **FET bias circuits:** Consider the bias circuits below. The power supply voltage is $V_{CC} = +10\text{ V}$.



- (a) Draw the LHS (left hand side) circuit diagram. What kind of circuit is it? Assume $V_{th} = 2\text{ V}$, $k = 5\text{ mA/V}^2$, and $I_D = 4\text{ mA}$. Determine the numerical values of R_1 and R_2 , assuming that R_1 carries a current of $10\text{ }\mu\text{A}$.
 - (b) Determine the numerical value of R_D so that the Q-point is in approximately the middle of the load line.
 - (c) Draw the RHS (right hand side) circuit. What kind of circuit is it? Assume $V_{th} = 2\text{ V}$, $k = 5\text{ mA/V}^2$, and $I_D = 4\text{ mA}$. Determine the numerical values of R_D and R_G .
 - (d) Name an advantage of the LHS bias circuit.
 - (e) Name an advantage of the RHS bias circuit.
4. **True / false questions:** Are the following statements true or false? Explain your answer with one or two sentences.
 - (a) Because the gate current is zero, the input power of an FET is zero.
 - (b) Although an FET device does not consume any input power, an FET circuit (e.g. an FET amplifier circuit) may still consume an input power.
 - (c) In a BJT, the emitter current is slightly larger than the collector current. Similarly, in an FET, the source current is slightly larger than the drain current.