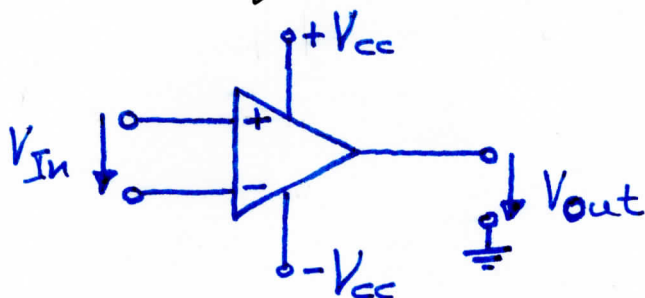


Differential amplifier

Supply voltage $+V_{cc}$ and $-V_{cc}$


⊕ Non-inverting input

⊖ Inverting input



* $V_{In} = \text{positive} \Rightarrow V_{out} = \text{positive}$

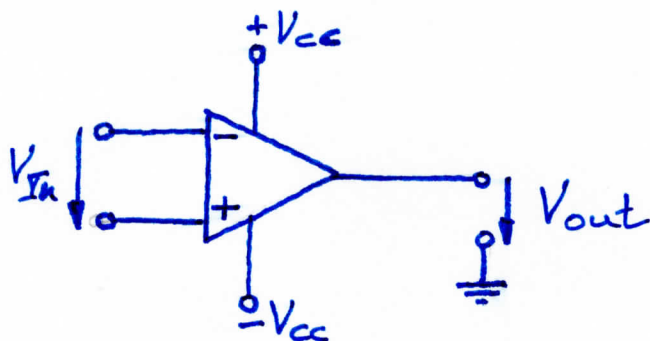
* Output V-range:
 $V_{cc} \geq V_{out} \geq -V_{cc}$



* $V_{In} = \text{positive} \Rightarrow V_{out} = \text{negative}$


* Output V-range:
 $V_{cc} \geq V_{out} \geq -V_{cc}$

Alternative voltage supply: $+V_{cc}$ & **GND**

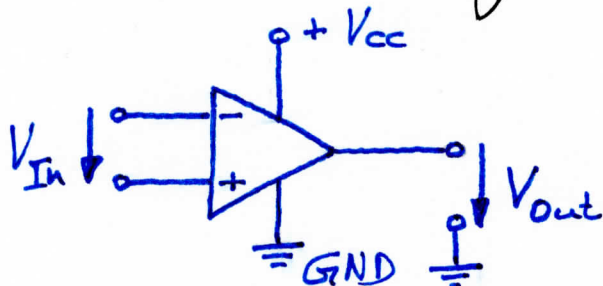

* Output V-range:
 $V_{cc} \geq V_{out} \geq 0$

The ideal differential amplifier

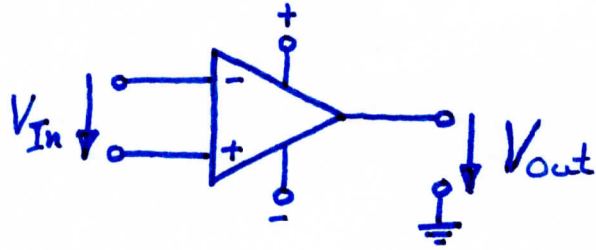

Differential amplifier is a voltage-to-voltage amplifier.

Ideal properties

* Input impedance = $Z_{In} = \frac{V_{In}}{I_{In}} = \infty$

* Amplification = $A = \frac{V_{out}}{V_{In}} = \infty$

* Output impedance = $Z_{out} = \frac{dV_{out}}{dI_{out}} = 0$

Consequences of ideal properties

$\Rightarrow V_{In} = 0$

Why?

If V_{out} = finite, and $A = \infty$ then $V_{In} = \frac{V_{out}}{\infty} = 0$

$\Rightarrow I_{In} = 0$



Why?

$Z_{In} = \infty$



\Rightarrow If \oplus connected to GND, then \ominus may be called "virtual GND"

Why? $V_{In} = 0$

Non-inverting differential amplifier

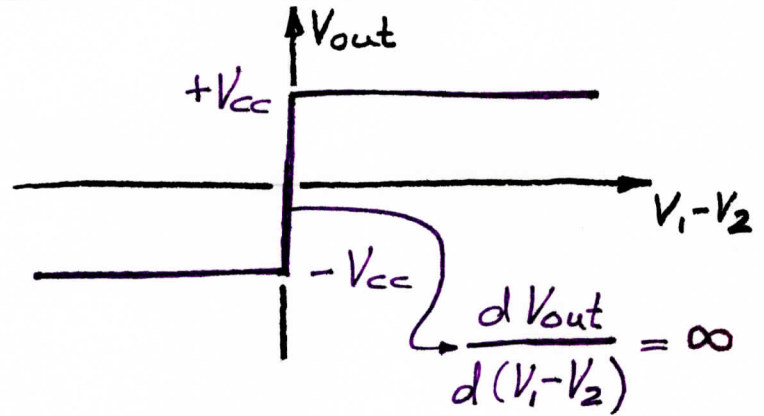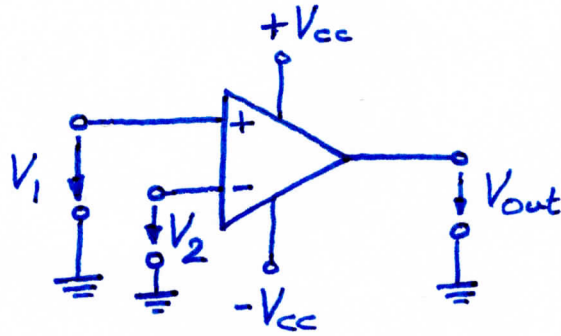

Inverting differential amplifier

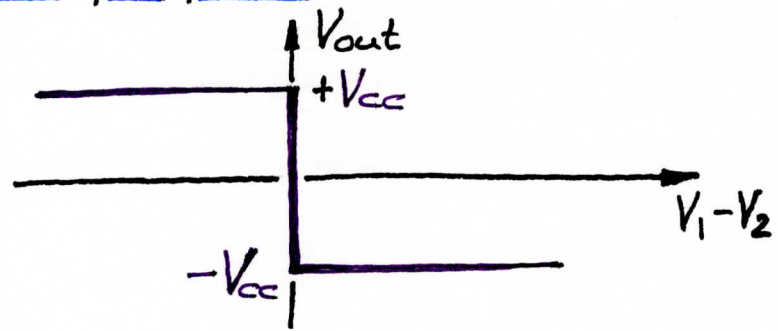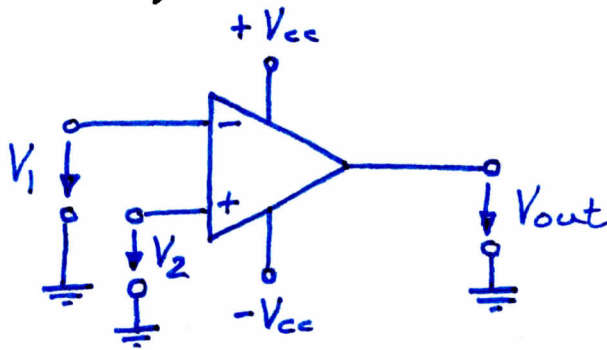

Alternative power supply : +Vcc & GND

