
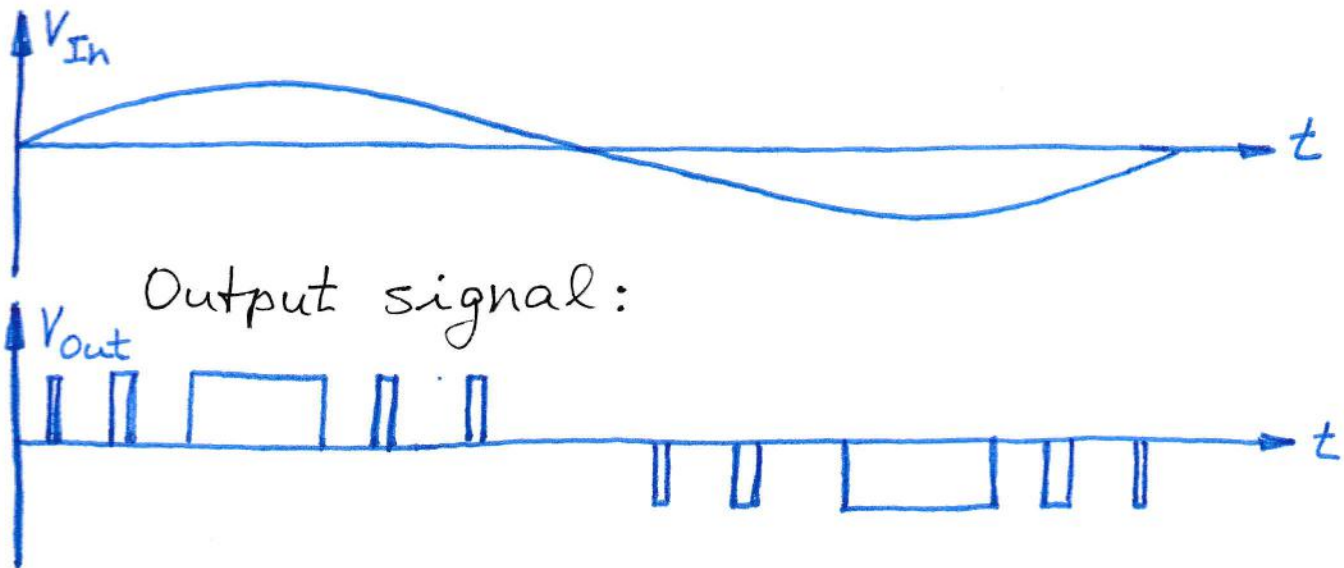


Problem 1 Class-D amplifier


(a) Input signal:

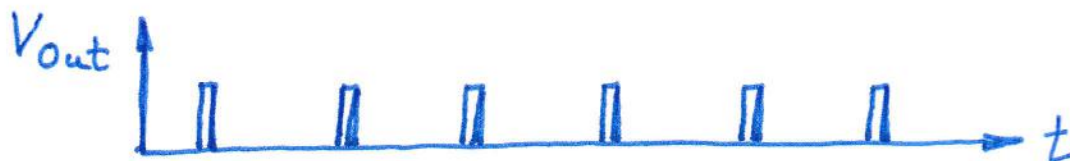

(b) Electric motor driven at 10% of power



Electric motor driven at 90% of power

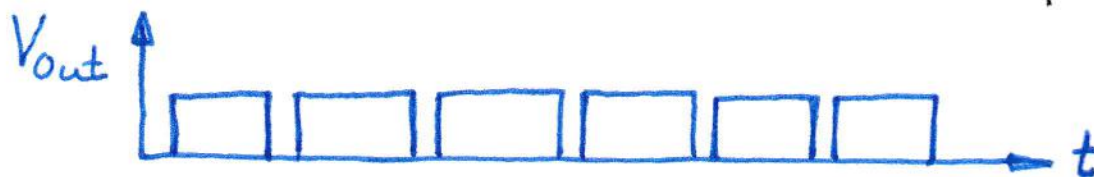


(c) A Class-D amplifier is an ON/OFF amplifier. $R_{ON} = 0\Omega$ $R_{OFF} = \infty\Omega$
The amplifier does not consume any power. This is a marked advantage.


Problem 2 Two-stage transistor amplifier

(2)

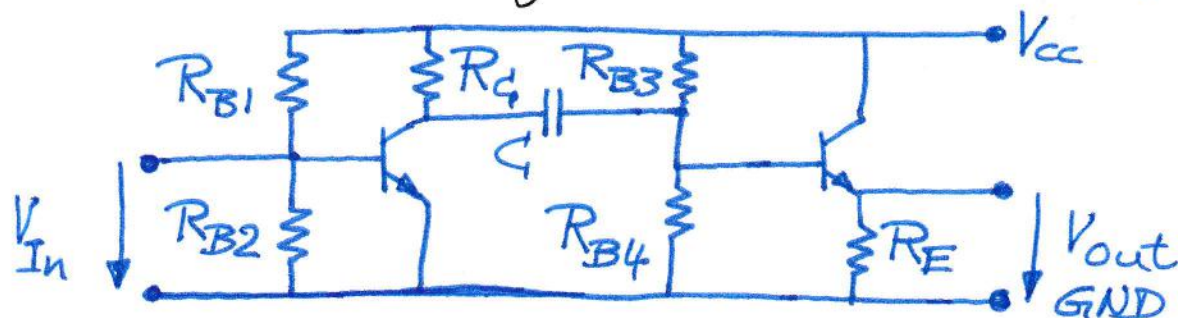(a) Circuit diagram ($V_{CC} = 10V$ $\beta = 100$)



(b) Small-signal AC circuit diagram

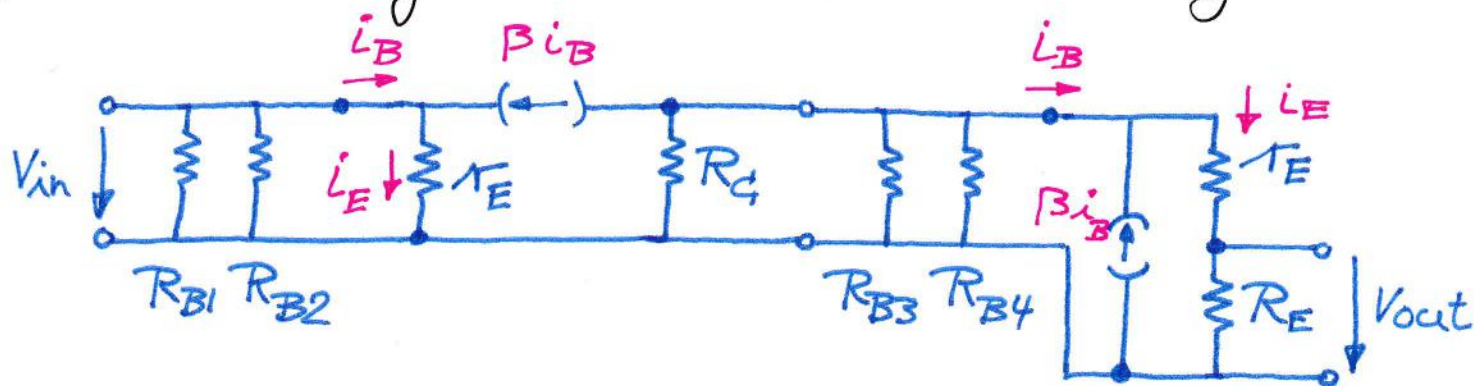

(c) Output impedance of 2nd stage

$$R_{out} = R_E \parallel (\tau_E + \underbrace{(R_{B3} \parallel R_{B4})}_{\gg R_E}) \approx \underline{\underline{R_E}}$$

(d) I choose: $R_E = 100\Omega$

If the DC operating point is in the middle of the load line, then $V_{CE} = 5V$.

$$\Rightarrow V_{RE} = 5V \quad \underline{\underline{I_{RE}}} = \frac{V_{RE}}{R_E} = \frac{5V}{100\Omega} = \underline{\underline{50mA}}$$

(3)

$$\Rightarrow \underline{I_E} = I_{RE} = \underline{50 \text{ mA}}$$

(e) Base voltage = $\underline{V_B} = V_{RE} + 0.7V = 5V + 0.7V = \underline{5.7V}$

Base current: $I_C = \beta I_B$

$$i_c = \beta i_B \quad i_E = i_c + i_B = \beta i_B + i_B = (\beta + 1) i_B$$

$$\Rightarrow \underline{I_B} = \frac{I_E}{\beta + 1} = \frac{50 \text{ mA}}{101} \approx \underline{0.5 \text{ mA}}$$

(f) Current through base voltage divider should be much greater than the base current. I choose a current of 5mA.
(5mA \gg 0.5mA)


$$\Rightarrow \underline{R_{B3} + R_{B4}} = \frac{V_{CC}}{5 \text{ mA}} = \frac{10V}{5 \text{ mA}} = \underline{2 \text{ k}\Omega}$$

Voltage divider $\frac{R_{B4}}{R_{B3} + R_{B4}} \times 10V = 5.7V (=V_B)$


$$\Rightarrow \underline{R_{B4}} = \frac{5.7V}{10V} \times 2 \text{ k}\Omega = \underline{1.14 \text{ k}\Omega}$$

$$\Rightarrow \underline{R_{B3}} = 2 \text{ k}\Omega - R_{B4} = 2 \text{ k}\Omega - 1.14 \text{ k}\Omega = \underline{0.86 \text{ k}\Omega}$$

(g)

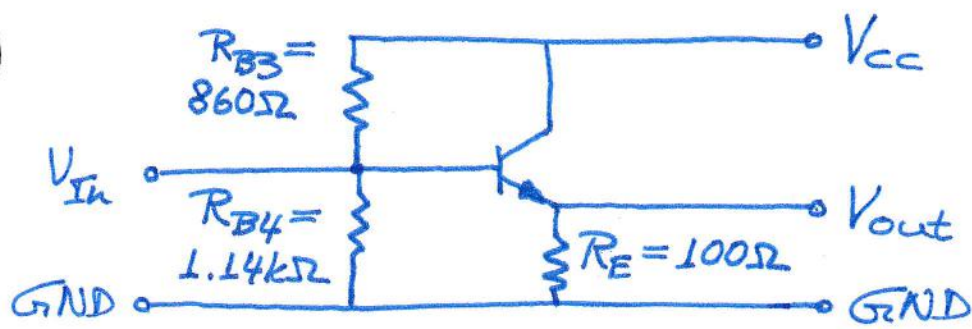

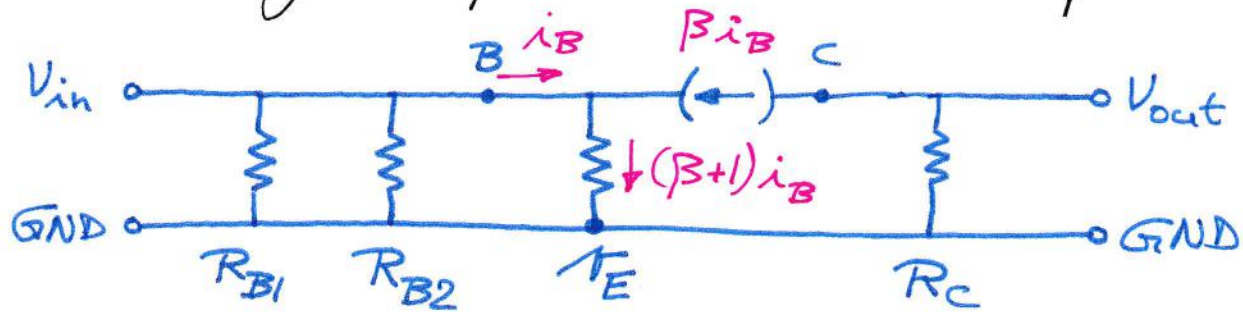(h) Small-signal equivalent circuit of 1st stage:



Voltage amplification

$$V_{out} = -\beta i_B R_C$$

$$V_{in} \approx (i_B + \beta i_B) R_E$$

$$\Rightarrow \underline{A_{voc}} = \frac{V_{out}}{V_{in}} \approx \underline{R_C / R_E}$$

(i)

$$R_C = 200\Omega \quad A_{voc} = 20$$

$$\Rightarrow R_E = \frac{R_C}{A_{voc}} = \frac{200\Omega}{20} = \underline{10\Omega}$$

$$\Rightarrow \text{Recall: } R_E = \frac{V_t}{I_E} = \frac{26mV}{I_E}$$

$$\Rightarrow \underline{I_E} = \frac{V_t}{R_E} = \frac{26mV}{10\Omega} = \underline{2.6mA}$$

(j) Base voltage = $V_B = V_{BE} = \underline{0.7V}$

Base current = $\underline{I_B} = \frac{I_E}{\beta+1} = \frac{2.6mA}{101} \approx \underline{26\mu A}$

(k) Current through base voltage divider should be much greater than I_B

I choose $\underline{I_{RB}} = 10 \times I_B = 10 \times 26\mu A = \underline{260\mu A}$

$\underline{R_{B1} + R_{B2}} = \frac{V_{CC}}{I_{RB}} = \frac{10V}{260\mu A} = \underline{38.5k\Omega}$

Voltage divider eqn.:

$\frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} = 0.7V (= V_B)$

$\Rightarrow \underline{R_{B2}} = \frac{0.7V}{V_{CC}} (R_{B1} + R_{B2}) = \frac{0.7V}{10V} 38.5k\Omega = \underline{2.7k\Omega}$

$\Rightarrow \underline{R_{B1}} = (R_{B1} + R_{B2}) - R_{B2} = 38.5k\Omega - 2.7k\Omega$
 $= \underline{35.8k\Omega}$

Problem 3

(a) False.

A BJT common-emitter amplifier has a relatively low input impedance (not close to ∞).

(b) False.

A DC blocking capacitor constitutes a high-frequency pass filter.