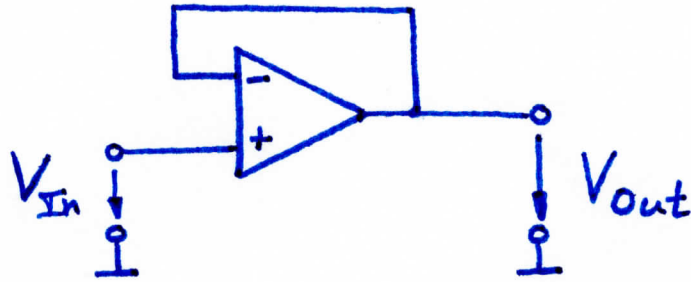


(1)

Slew rate of Op Amp

The response of an Op Amp is not instantaneous. Consider the circuit:



Analysis: $V_+ = V_- \Rightarrow V_{out} = V_{in}$


\Rightarrow Voltage follower

Q: What is a voltage follower useful for? \Rightarrow Impedance transformation

Consider the following input:



Output:

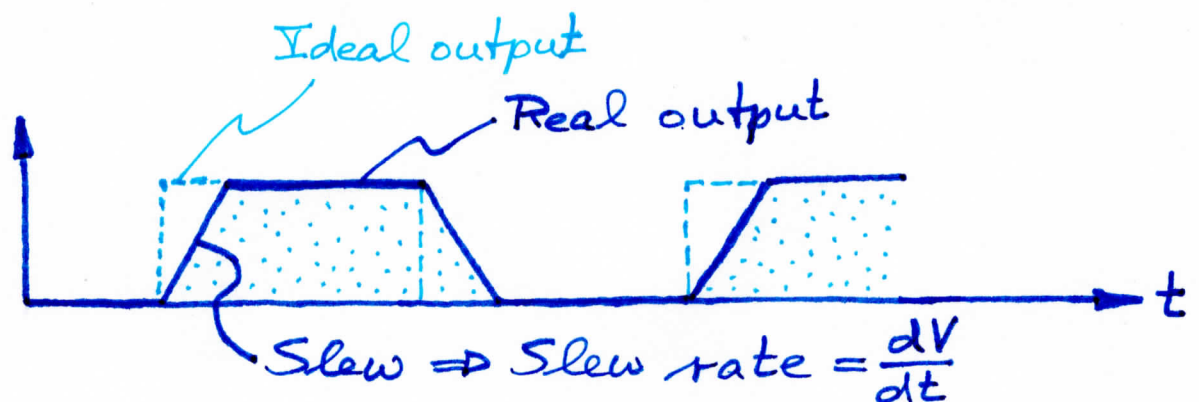

Slew rate = $\frac{dV_{out}}{dt} \Rightarrow$ Fastest $\frac{dV_{out}}{dt}$ (2)
the Op Amp is capable of. Example:

$$\text{Slew rate} = 1 \text{ V}/\mu\text{s}$$

Q: Ideal slew rate? $\Rightarrow SR = \infty$
 \rightarrow Slew Rate


Q: What is cause of finite slew rate?

\Rightarrow Parasitic capacitances inside Op Amp.

$$\text{Recall } Q = CV \Rightarrow \underbrace{I = \frac{dQ}{dt}}_{\text{Charging current}} = C \underbrace{\frac{dV}{dt}}_{SR}$$

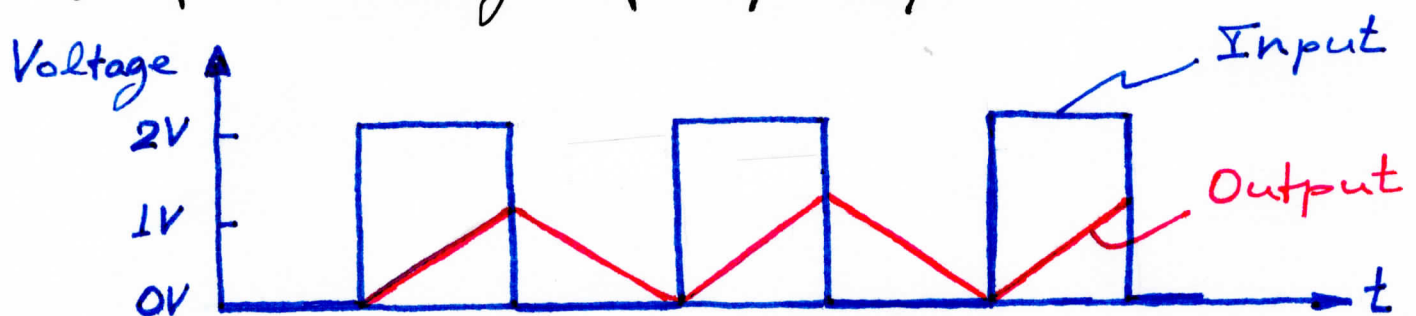Example

Consider Op Amp voltage follower with $SR = 1 \text{ V}/\mu\text{s}$ being subjected to a square wave input with $V_0 = 2 \text{ V}$ and $T = 2 \mu\text{s}$. Construct output voltage of Op Amp




\Rightarrow Distortion $\Rightarrow SR$ must be sufficiently high to not distort the signal

Example

Consider sinusoidal input of Op Amp

$$V_{in} = V_o \sin \omega t$$

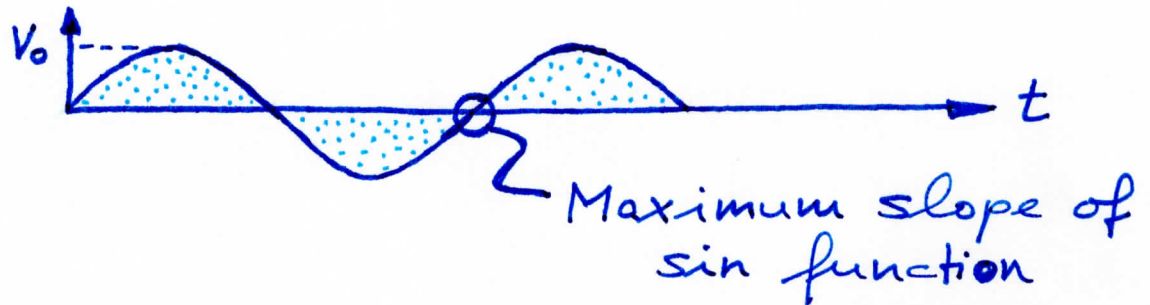

Q: What is maximum slope?

$$\frac{dV_{in}}{dt} = V_o \cos(\omega t) \omega$$

$$\left. \frac{dV_{in}}{dt} \right|_{t=0} = \omega V_o = 2\pi f V_o$$

To faithfully reproduce the sin function

$$SR \geq 2\pi f V_o$$

↳ Slew rate

Q: What happens if SR is too slow?

⇒ Distortion

