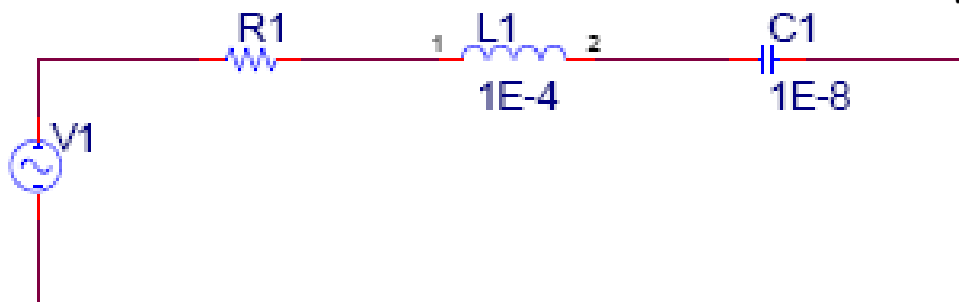


NAMES _____

Laplace!
put in
s-domain
current
use
PFE

1)



e. For $R1 = 200 \, \Omega$ determine the voltage across the capacitor as a function of time for $t > 0$. Note may have to use $F(1)$ instead of $F(0)$.

Note: Non-zero initial condition!

$V1 = 10V \, t < 0$
 $8V \, t > 0$